



**The Abdus Salam  
International Centre for Theoretical Physics**



**1977-3**

**First ICTP Regional Microelectronics Workshop and Training on  
VHDL for Hardware Synthesis and FPGA Design in Asia-Pacific**


*16 June - 11 July, 2008*

**The CMOS inverter.**

Paulo Moreira  
*PH ESE ME Division  
CERN  
CH-1211 Geneva 23  
SWITZERLAND*

 
# Outline

- Introduction
- Transistors
- The CMOS inverter
  - DC operation
  - Dynamic operation
    - Propagation delay
    - Power consumption
  - Layout
- Technology
- Scaling
- Gates
- Sequential circuits
- Storage elements
- Phase-Locked Loops
- Example




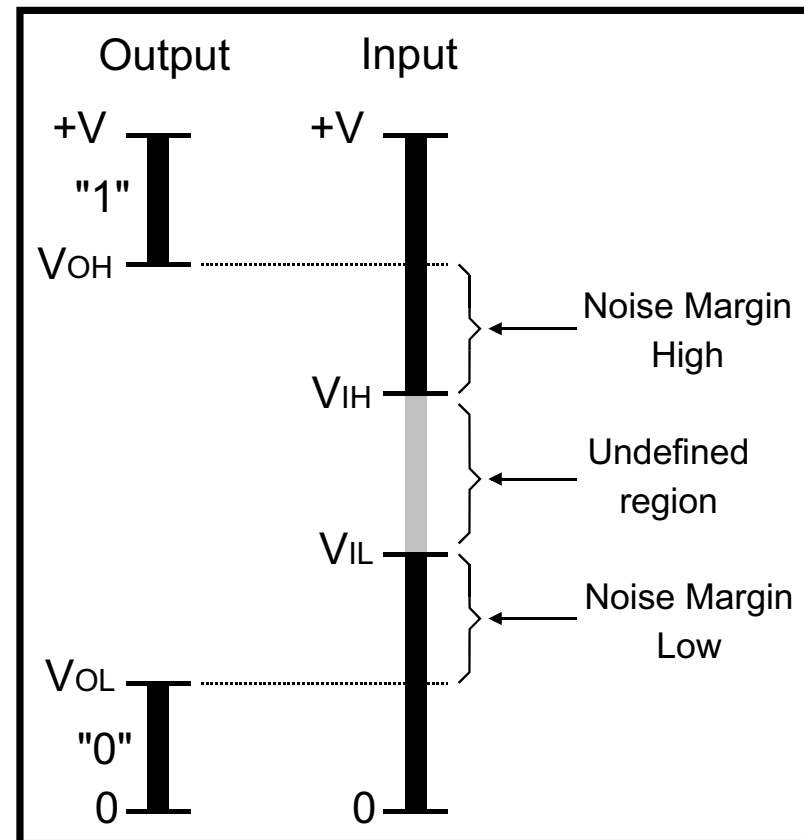
# CMOS logic: "0" and "1"

- Logic circuits process Boolean variables
- Logic values are associated with voltage levels:
  - $V_{IN} > V_{IH} \Rightarrow "1"$
  - $V_{IN} < V_{IL} \Rightarrow "0"$
- Noise margin:
  - $NM_H = V_{OH} - V_{IH}$
  - $NM_L = V_{IL} - V_{OL}$





# The MOST - a simple switch

**p-switch**

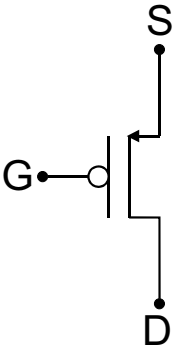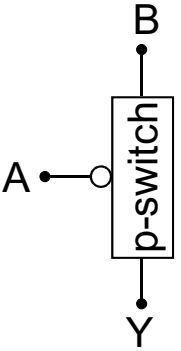
A	B	Y
0	0	bad 0 (source follower)
0	1	<b>good 1</b>
1	0	? (high Z)
1	1	? (high Z)

**n-switch**

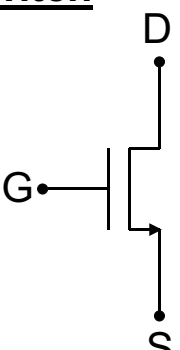
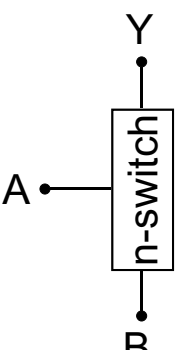



A	B	Y
0	0	? (high Z)
0	1	? (high Z)
1	0	<b>good 0</b>
1	1	bad 1 (source follower)

# The CMOS inverter

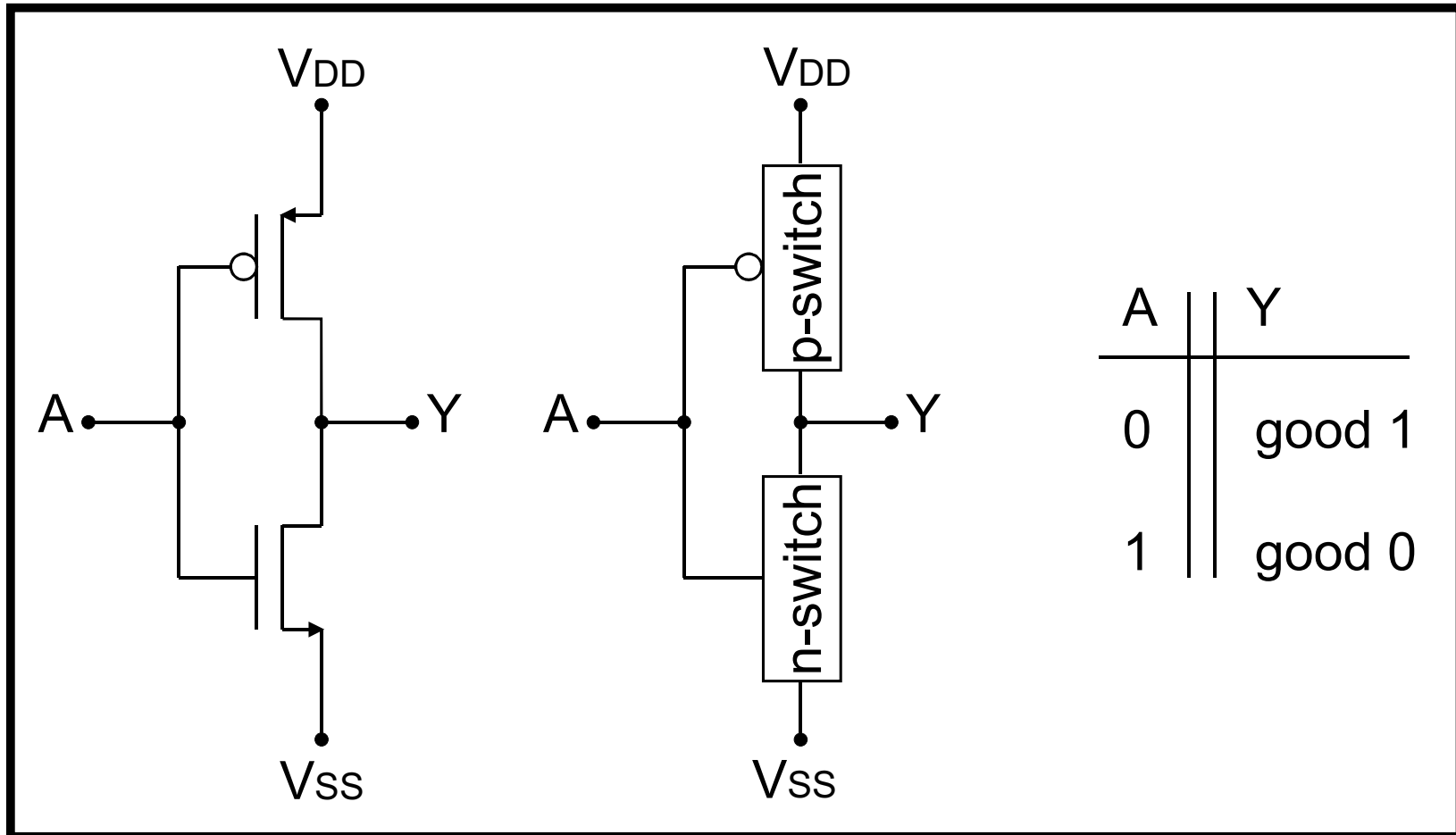

# DC operation

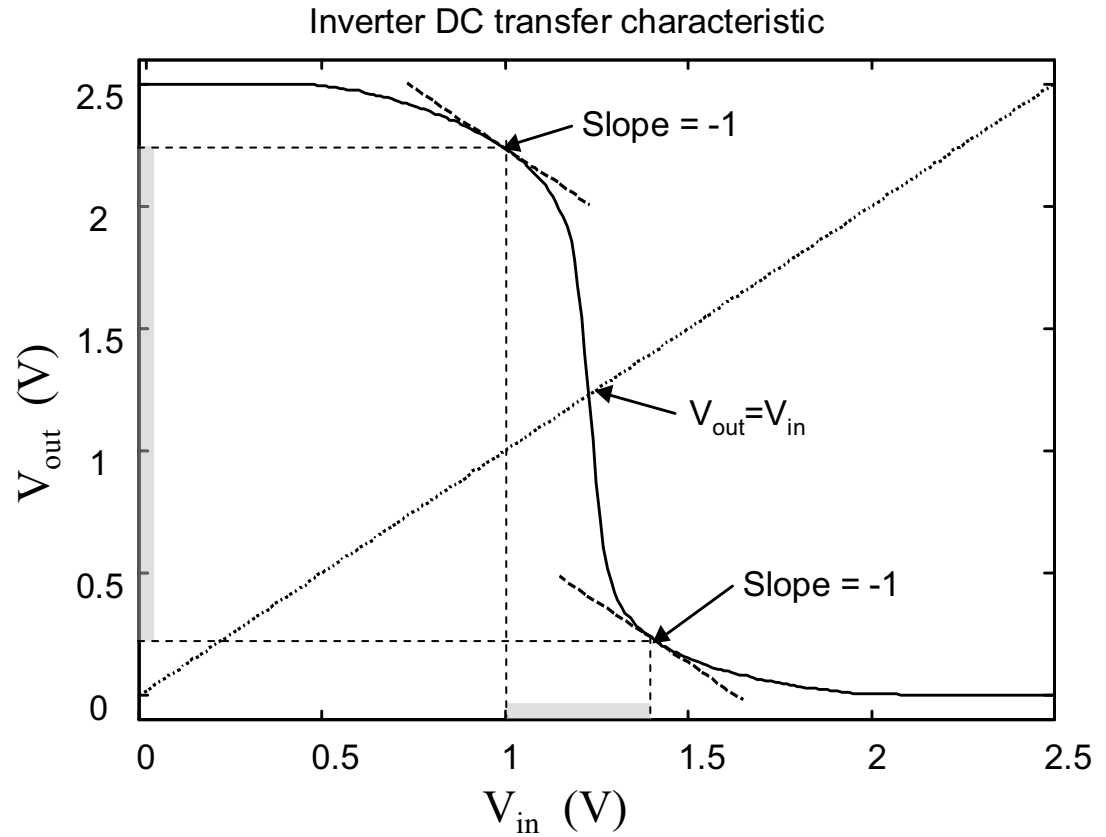 


# DC operation

---

Regions of operation (balanced inverter):

$V_{in}$	n-MOS	p-MOS	$V_{out}$
0	cut-off	linear	$V_{dd}$
$V_{TN} < V_{in} < V_{dd}/2$	saturation	linear	$\sim V_{dd}$
$V_{dd}/2$	saturation	saturation	$V_{dd}/2$
$V_{dd} -  V_{TP}  > V_{in} > V_{dd}/2$	linear	saturation	$\sim 0$
$V_{dd}$	linear	cut-off	0

# Dynamic operation

 



# Dynamic operation

---

- Propagation delay
  - Main origin: load capacitance

$$t_{pLH} = \frac{C_L \cdot L_p \cdot V_{dd}}{\mu_p \cdot C_{ox} \cdot W_p \cdot (V_{dd} - |V_{TP}|)^2} \approx \frac{C_L}{k_p \cdot V_{dd}}$$

$$t_{pHL} = \frac{C_L \cdot L_n \cdot V_{dd}}{\mu_n \cdot C_{ox} \cdot W_n \cdot (V_{dd} - |V_{TN}|)^2} \approx \frac{C_L}{k_n \cdot V_{dd}}$$

$$t_p \approx \frac{1}{2} (t_{pLH} + t_{pHL}) = \frac{C_L}{2 \cdot V_{dd}} \left( \frac{1}{k_n} + \frac{1}{k_p} \right)$$

- To reduce the delay:
  - Reduce  $C_L$
  - Increase  $k_n$  and  $k_p$ . That is, increase  $W/L$


# Dynamic operation

---

- CMOS power budget:
  - Dynamic power consumption:
    - Charging and discharging of capacitors
  - Short circuit currents:
    - Short circuit path between power rails during switching
  - Leakage
    - Leaking diodes and transistors
 
# Dynamic operation

- The dynamic power dissipation is a function of:
  - Frequency
  - Capacitive loading
  - Voltage swing
- To reduce dynamic power dissipation
  - Reduce:  $C_L$
  - Reduce:  $f$
  - Reduce:  $V_{dd} \Leftarrow$  The most effective action



# Layout

