



*The Abdus Salam  
International Centre for Theoretical Physics*



**2177-17**

**ICTP Latin-American Basic Course on FPGA Design for Scientific  
Instrumentation**

*15 - 31 March 2010*

**Digital arithmetic III  
(basic arithmetic operations)**

BAZARGAN SABET Pirouz  
*LIP6, University Pierre et Marie Curie  
Paris  
France*

# Outline

- ❑ Digital CMOS design
- ❑ Arithmetic operators
- ❑ Sequential functions

# Outline

## Digital CMOS design

## Arithmetic operators

 Adders

 Comparators


 Shifters

 Multipliers

# Adders
 
## Adding two natural numbers

Let consider two natural numbers  $a$  and  $b$   
coded on 8 bits using Natural Binary Code




# Adders
 
## Adding two natural numbers

At each stage, I need to sum 3 single bit numbers  $a_i$   $b_i$   $c_i$

The carry out of the stage  $i$  is the input carry of the next stage



$s_i$  and  $c_{i+1}$  are Boolean functions of  $a_i$   $b_i$   $c_i$

# Adders

Adding two natural numbers

	00	01	11	10	$a_i \ b_i$
0	0	1	0	1	
1	1	0	1	0	

$c_i$

$s_i$

$$s_i = a_i \oplus b_i \oplus c_i$$

	00	01	11	10	$a_i \ b_i$
0	0	0	1	0	
1	0	1	1	1	

$c_i$

$c_{i+1}$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$



# Adders

Adding two natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$
  
$$c_{i+1} = a_i \cdot (b_i + c_i) + b_i \cdot c_i$$





# Adders

Adding two natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$
  
$$c_{i+1} = a_i \cdot b_i + (a_i + b_i) \cdot c_i$$





# Adders


## Adding two natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$

$$c_{i+1} = a_i \cdot b_i + (a_i + b_i) \cdot c_i$$

 
$$c_{i+1} = a_i \cdot b_i + (a_i \oplus b_i) \cdot c_i$$



# Adders

 
## Adding two natural numbers

The circuit generating  $s_i$  and  $c_{i+1}$  is called a Full Adder (FA)




# Adders

Adding two natural numbers

 


## Adders

# Adding two natural numbers

 

# Adders

Adding two natural numbers

 

# Adders

Adding two natural numbers

Sequential Adder

Area  $\propto n$

Delay  $\propto n$  cycles

Timing should be improved




# Adders
 
## Adding two natural numbers

At each stage, I need to sum 3 single bit numbers  $a_i$   $b_i$   $c_i$

The carry out of the stage  $i$  is the input carry of the next stage




# Adders

Adding two natural numbers

Ripple Carry Adder (RCA)

Area  $\propto n$

Delay  $\propto n$

 


Timing should be improved



# Adders

Adding two natural numbers

Acceleration technics

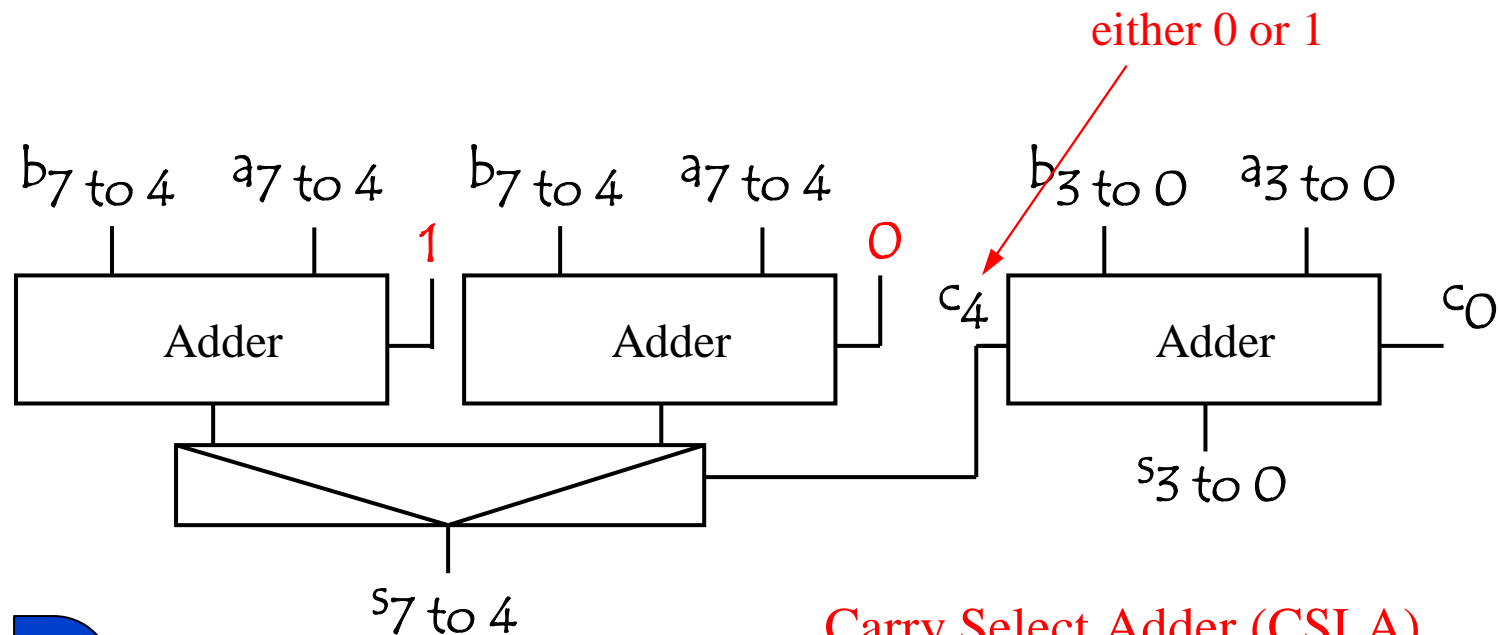


Carry Select Adder (CSLA)

# Adders

## Adding two natural numbers Carry Select Adder (CSLA)


$$\text{Area} \propto n^{\log(3)} = n^{1.585}$$

$$\text{Delay} \propto \log(n)$$

 

# Adders
 
## Adding two natural numbers Acceleration technics



00	01	11	10	$a_i b_i$
absorption	propagation	generation	propagation	

# Adders

Adding two natural numbers  
Acceleration technics

	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$a_i b_i$

$c_i$

$c_{i+1}$

$$G_i = a_i b_i$$

$$P_i = a_i \oplus b_i$$

$$c_{i+1} = G_i + P_i c_i$$


$$s_i = P_i \oplus c_i$$

00	01	11	10
absorption	propagation	generation	propagation

$a_i b_i$
 
# Adders

Adding two natural numbers  
Acceleration technics



$$G_i = a_i b_i$$

$$P_i = a_i \oplus b_i$$


$$c_{i+1} = G_i + P_i c_i$$

$$s_i = P_i \oplus c_i$$

00	01	11	10	$a_i b_i$
absorption	propagation	generation	propagation	

 
# Adders

Adding two natural numbers  
Acceleration technics


 
# Adders

Adding two natural numbers  
Acceleration technics




$$G_{i+1} = a_{i+1} b_{i+1} \quad G_i = a_i b_i$$

$$P_{i+1} = a_{i+1} \oplus b_{i+1} \quad P_i = a_i \oplus b_i$$

$$G_{i+1,i} = G_{i+1} + G_i \cdot P_{i+1}$$


$$P_{i+1,i} = P_i \cdot P_{i+1}$$

# Adders

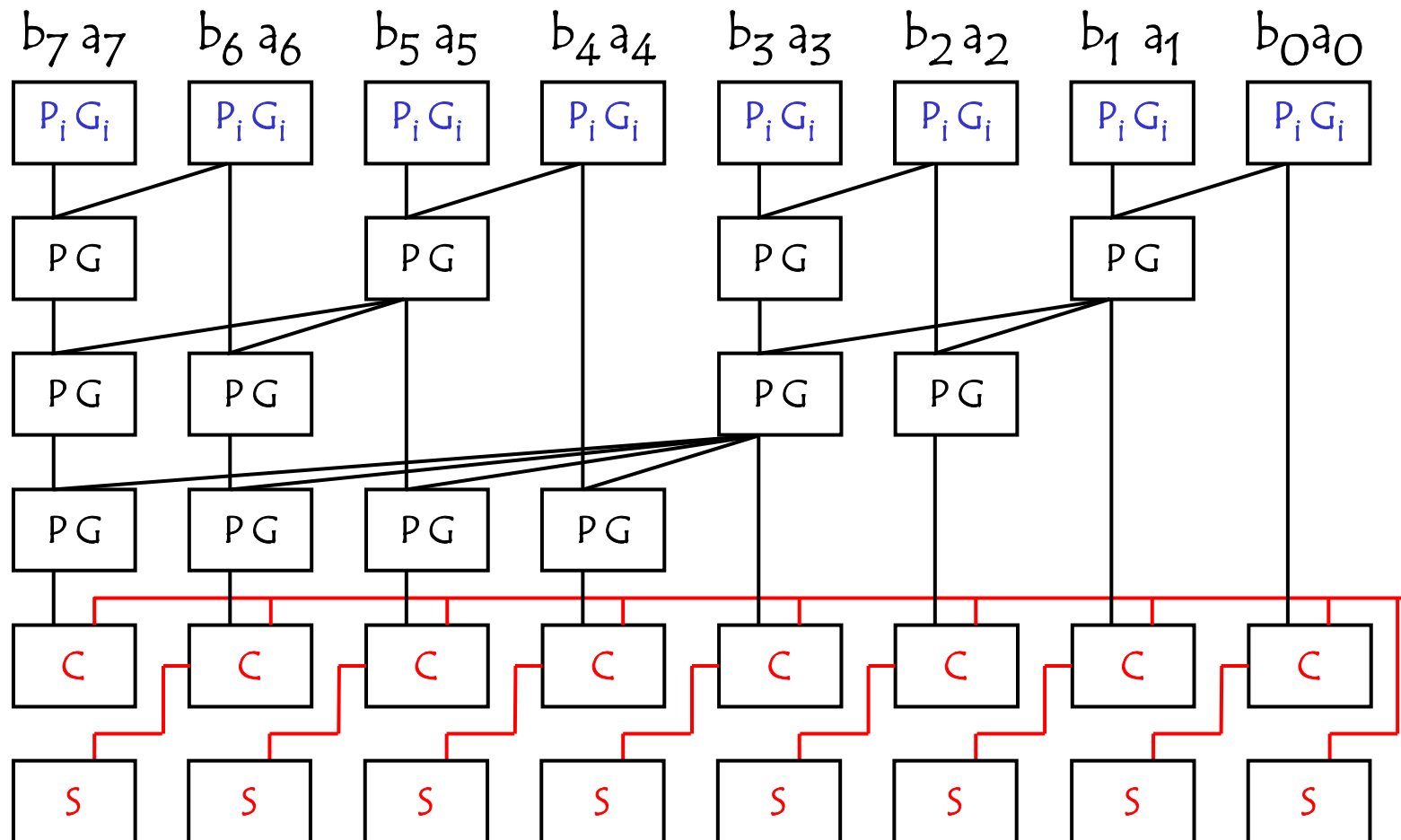




# Adders

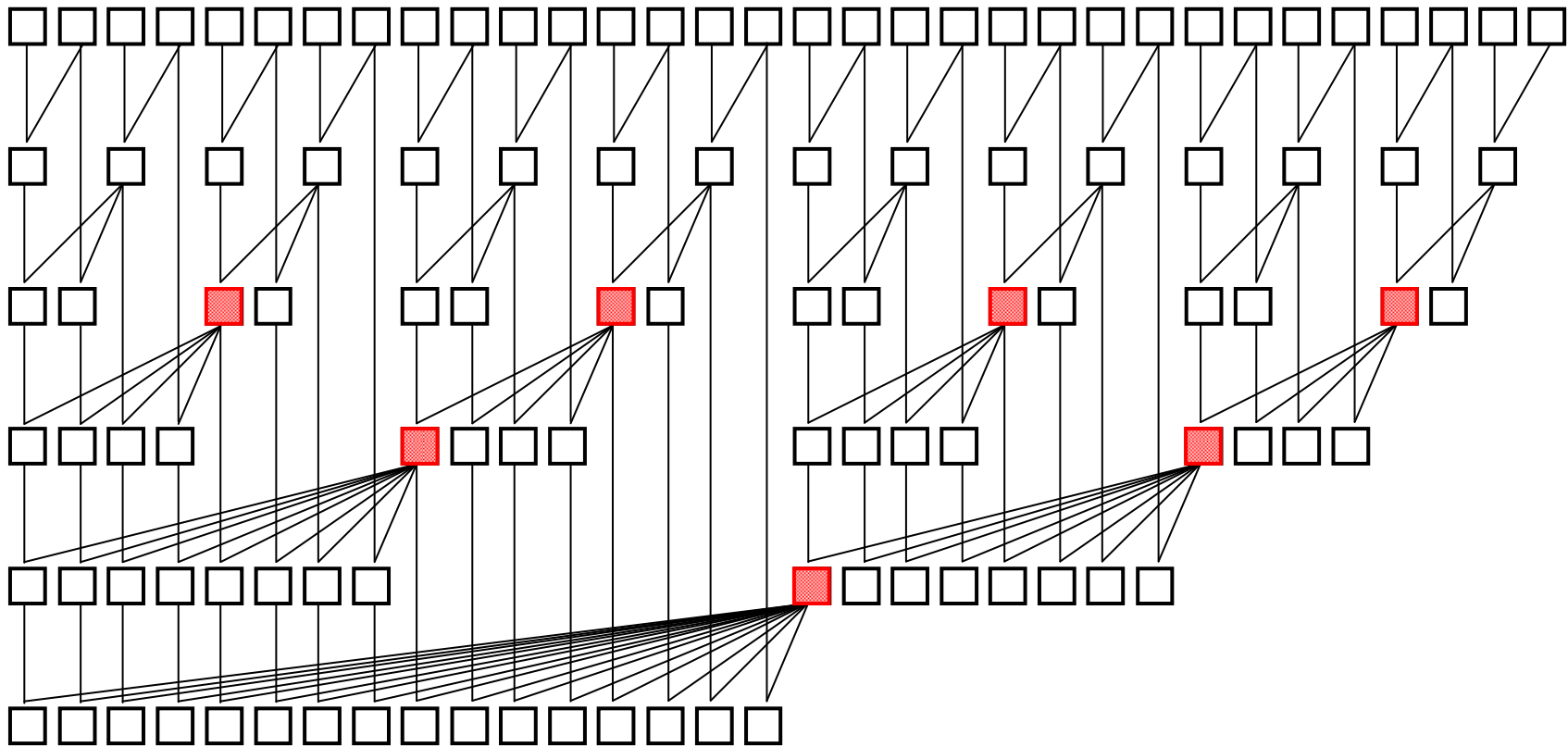

# Adders

 

# Adders

## Adding two natural numbers (summary)

	Area	Delay
Ripple Carry (RCA)	$n$	$n$
Carry Select (CSLA)	$n \log(3)$	$\log(n)$
Carry Lookahead (CLA)	$n \log(n)$	$\log(n)$
Magic Adder	$n$	$C_{ste}$




More improvements ?

# Adders

Adding two natural numbers

Ripple Carry Adder (RCA)

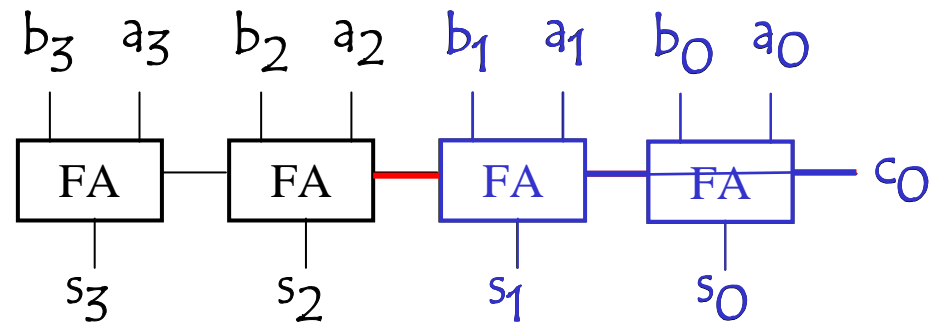


# Adders

Adding two natural numbers

Ripple Carry Adder (RCA)

pipelining

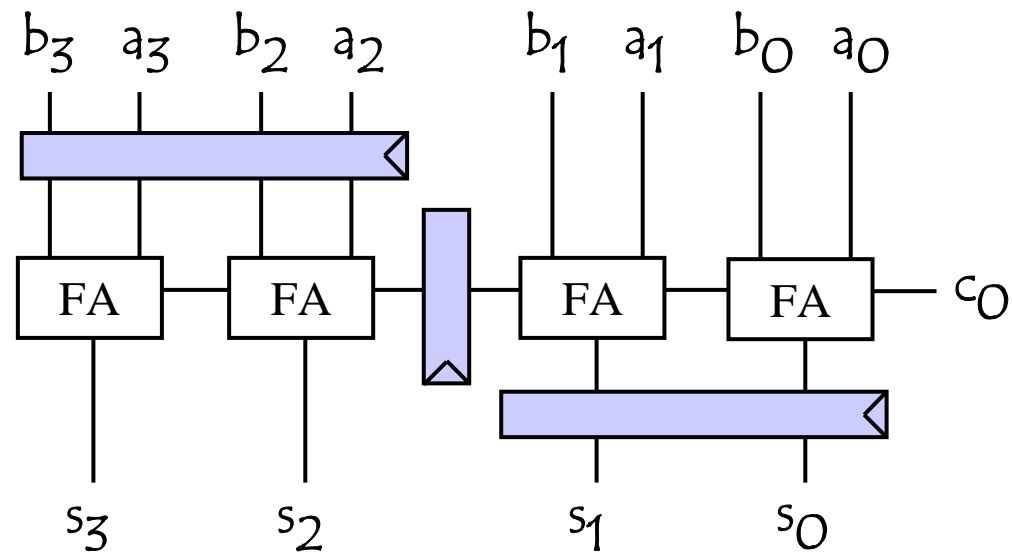


# Adders

Adding two natural numbers


Ripple Carry Adder (RCA)

pipelining

 

# Adders

Adding two natural numbers

 

# Adders

## Adding two natural numbers (summary)

	Area	Delay
Ripple Carry (RCA)	$n$	$n$
Carry Select (CSLA)	$n \log(3)$	$\log(n)$
Carry Lookahead (CLA)	$n \log(n)$	$\log(n)$
Pipeline Adder	$n^2$	Cste (1 cycle)
Magic Adder	$n$	Cste




When there is no door to escape break the wall



# Adders

Adding **three** natural numbers

 

**delay**


# Adders

Adding **three** natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$

 the expressions are symmetrical in regard of  $a$ ,  $b$  and  $c$




**A full adder creates 2  
numbers from 3**

# Adders


Adding **three** natural numbers

Carry Save Adder (CSA)

 

# Adders

Adding **three** natural numbers

 

Delay = cste  
Area  $\propto n$

# Adders

Adding two natural numbers

Change the representation of numbers

Given a natural number  $a$  :  $a$  is coded using  $2n$  bits

$$a = a_0 + a_1 \quad \text{Redundant Binary Code}$$

**Example** : the number 5 can be coded on 4 bits as

$$0000 + 0101$$

$$0001 + 0100$$

$$0010 + 0011$$



# Adders

Adding two natural numbers

Changing the representation of numbers

$$a = a_0 + a_1$$

$$b = b_0 + b_1$$

Adding  $a$  and  $b$  in Redundant Binary Code is finding  $c$

$$c = c_0 + c_1 \text{ such as}$$


$$c_0 + c_1 = a_0 + a_1 + b_0 + b_1$$

Adding 4 numbers to generate 2



# Adders

Adding two natural numbers

 

Delay = cste

Area  $\propto n$