



**The Abdus Salam  
International Centre for Theoretical Physics**



**2177-9**

**ICTP Latin-American Basic Course on FPGA Design for Scientific  
Instrumentation**

*15 - 31 March 2010*


**Phase-Locked Loops**

MOREIRA Paulo Rodrigues S.

*CERN  
Geneva  
Switzerland*

 
# Outline

- Introduction
- Transistors
- The CMOS inverter
- Technology
- Scaling
- Gates
- Sequential circuits
- Storage elements
- **Phase-Locked Loops**
  - PLL overview
  - Building blocks:
  - PLL analysis:
  - PLL simulation with Verilog
- Example




Complete set of slides and notes on DLLs and PLLs can be found in:  
<http://paulo.moreira.free.fr/microelectronics/padova/padova.htm>

# Why Phase-Locked Loops?

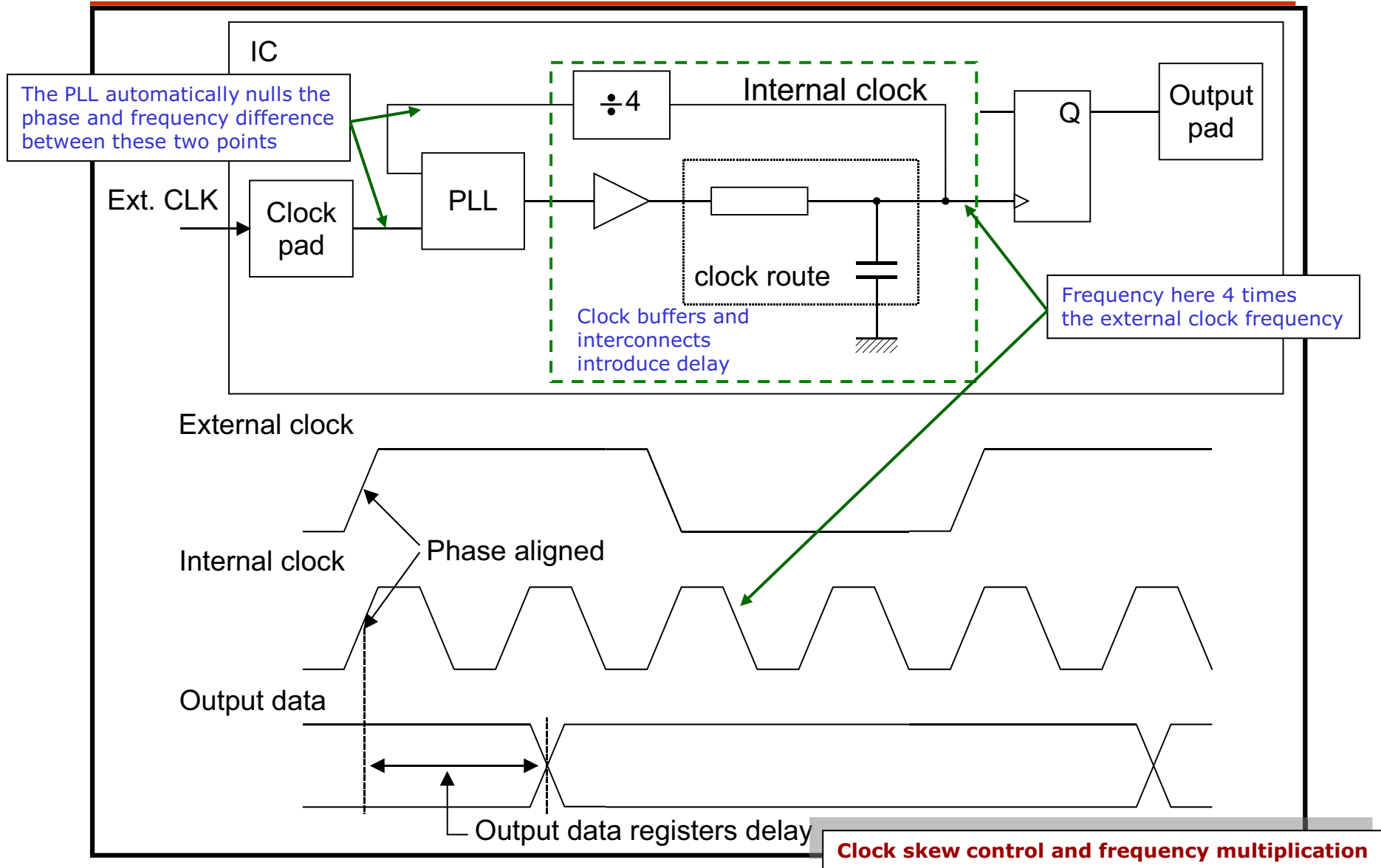

# PLL Block Diagram

 

- **Phase-Locked Loop functional blocks**

- **Phase Detector (PD):**

- Compares the phase of the reference signal to the VCO phase
- Depending on the type, produces an error signal:
  - Proportional to the phase difference between the input and output phases;
  - Gives just an indication on the sign of the phase error (bang-bang detector).
- Phase detectors can be also frequency sensitive; in this case they are called Phase-Frequency Detectors (PFD).


- **Loop filter (LF):**

- Eliminates the high frequency components of the error signal
- Introduces a loop-stabilizing zero
- It can be implemented as:
  - An RC low-pass filter
  - An active low-pass filter
  - A charge-pump a resistor and a capacitor

- **Voltage Controlled Oscillator (VCO):**

- As the name indicates is an oscillator whose frequency is controlled by a voltage:  $f_{\text{out}} = F(V_{\text{control}})$
- Sometimes the control quantity can be a current. In this case we have a Current Controlled Oscillator (CCO)
- We will assume that the higher the voltage (or the current) the higher the frequency

# PLL Basic Operation

 

# Starved Inverter VCO

## The VCO is an oscillator

- The oscillation frequency depends on the control voltage
- It is usually modeled as:

$$f(t) = K_{vco} \cdot V_{cnt}(t) + f_0$$


$$\Phi(t) = \int_0^t f(t) dt + \Phi_0$$

$$\Phi(s) = K_{vco} \cdot \frac{1}{s} \cdot V_{cnt}(s)$$


## Practical advice:

- An odd-number of inverters is mandatory;
- Always buffer the output signal;
- Ensure a minimum oscillation frequency;
- Preferably use a minimum of 3 inverters.


The VCO behaves as a phase integrator

 

# VCO Transfer function

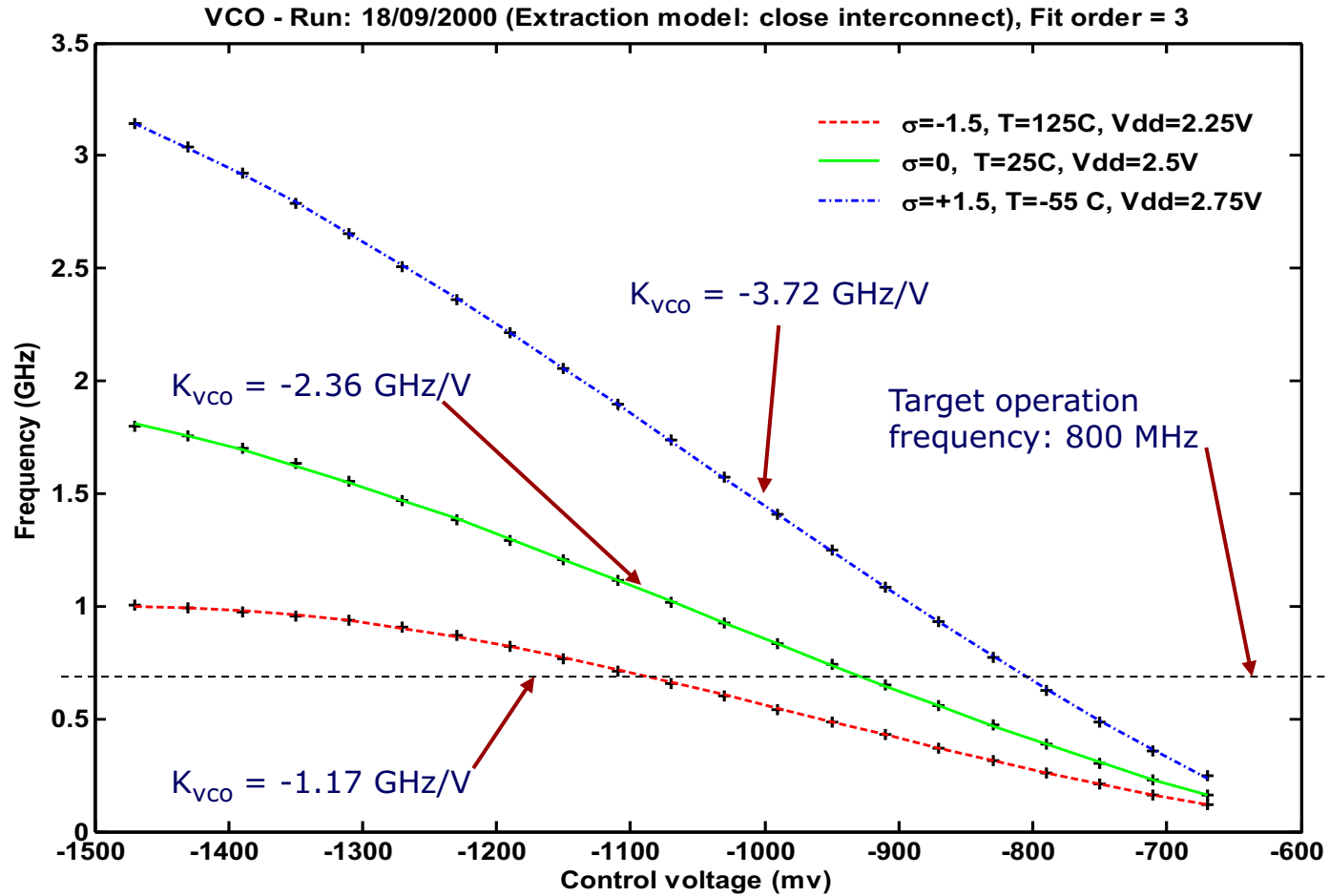


# Phase Frequency Detector


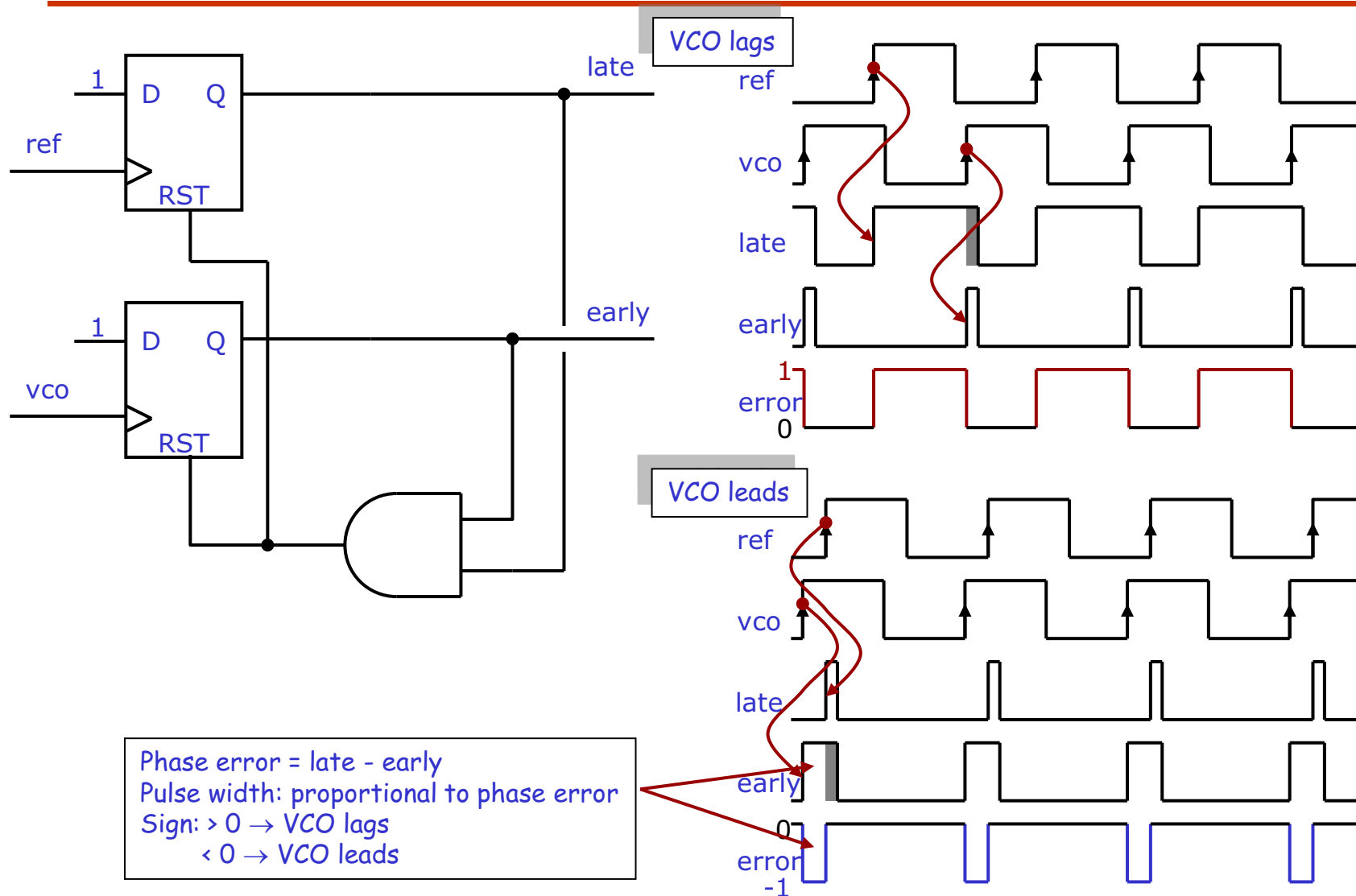




# PFD: Frequency sensitivity

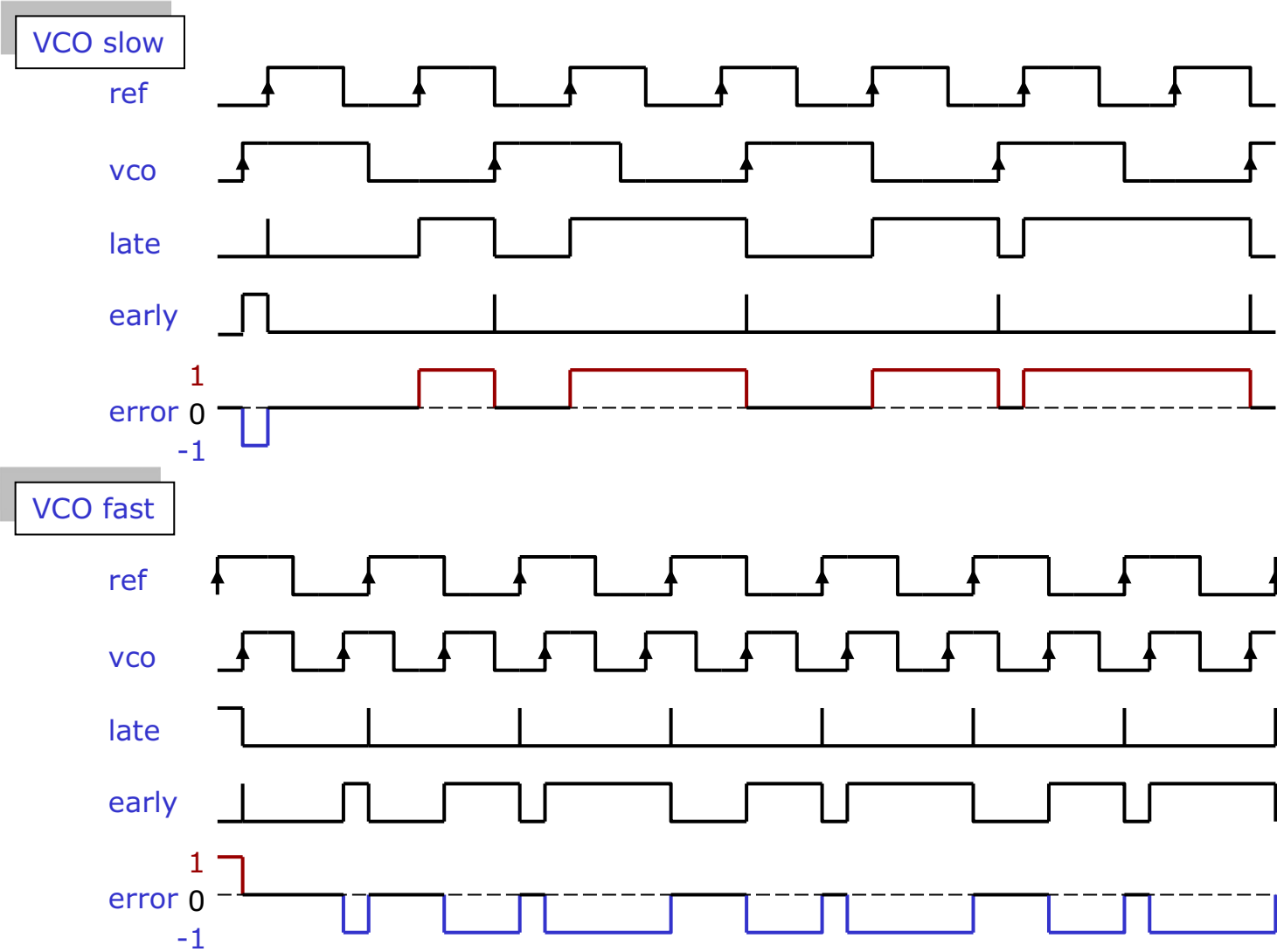


# PFD Characteristics

 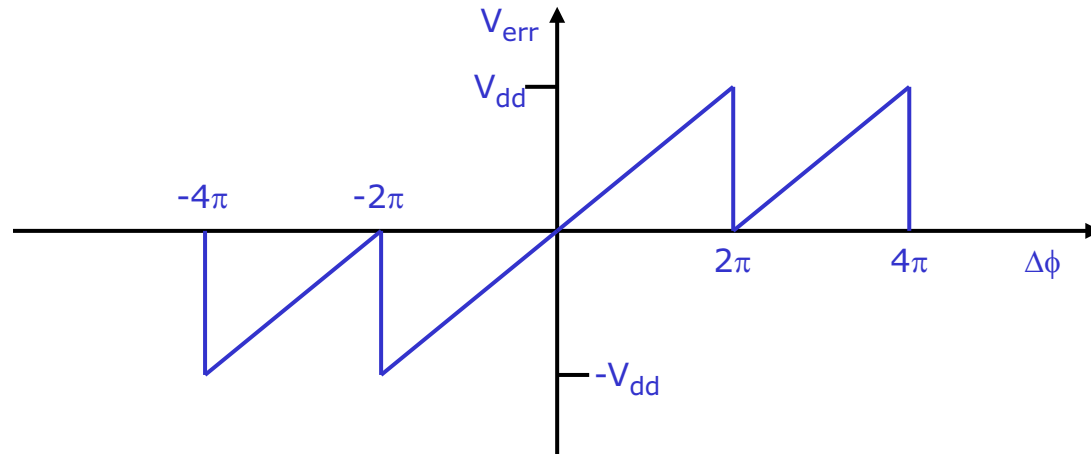

# Active Filter: Charge-Pump + RC network

$$\phi_{err,n}(t) = \frac{\phi_{err}}{2\pi} \propto \text{late}(t) - \text{early}(t)$$

$$\phi_{err,n}(t) \in [-1, 1]$$

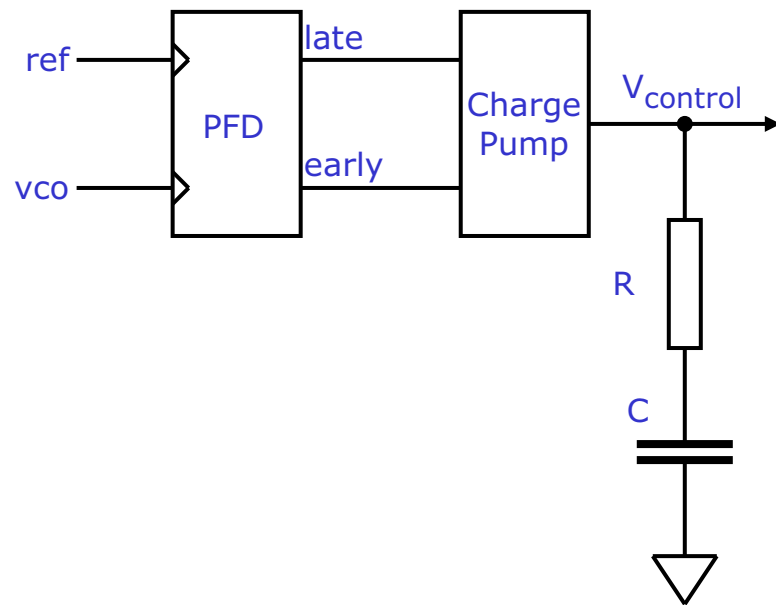

$$V_{control}(t) = V_{res}(t) + V_{cap}(t)$$

$$V_{control}(t) = I_{cp} \cdot \left[ R \cdot \phi_{err,n}(t) + \frac{1}{C} \int_0^t \phi_{err,n}(t) dt \right] + V_0$$

Integral term controlled by 'C'

Proportional term controlled by 'R'

Current magnitude  $I_{cp}$  affects both

Zero at:  $f_z = \frac{1}{2\pi \cdot R \cdot C}$


Infinite gain at DC

$$H_{LF}(s) = I_{cp} \cdot \frac{1 + s \cdot R \cdot C}{s \cdot C}$$


Independent

Pole at the origin

# Charge Pump Implementation

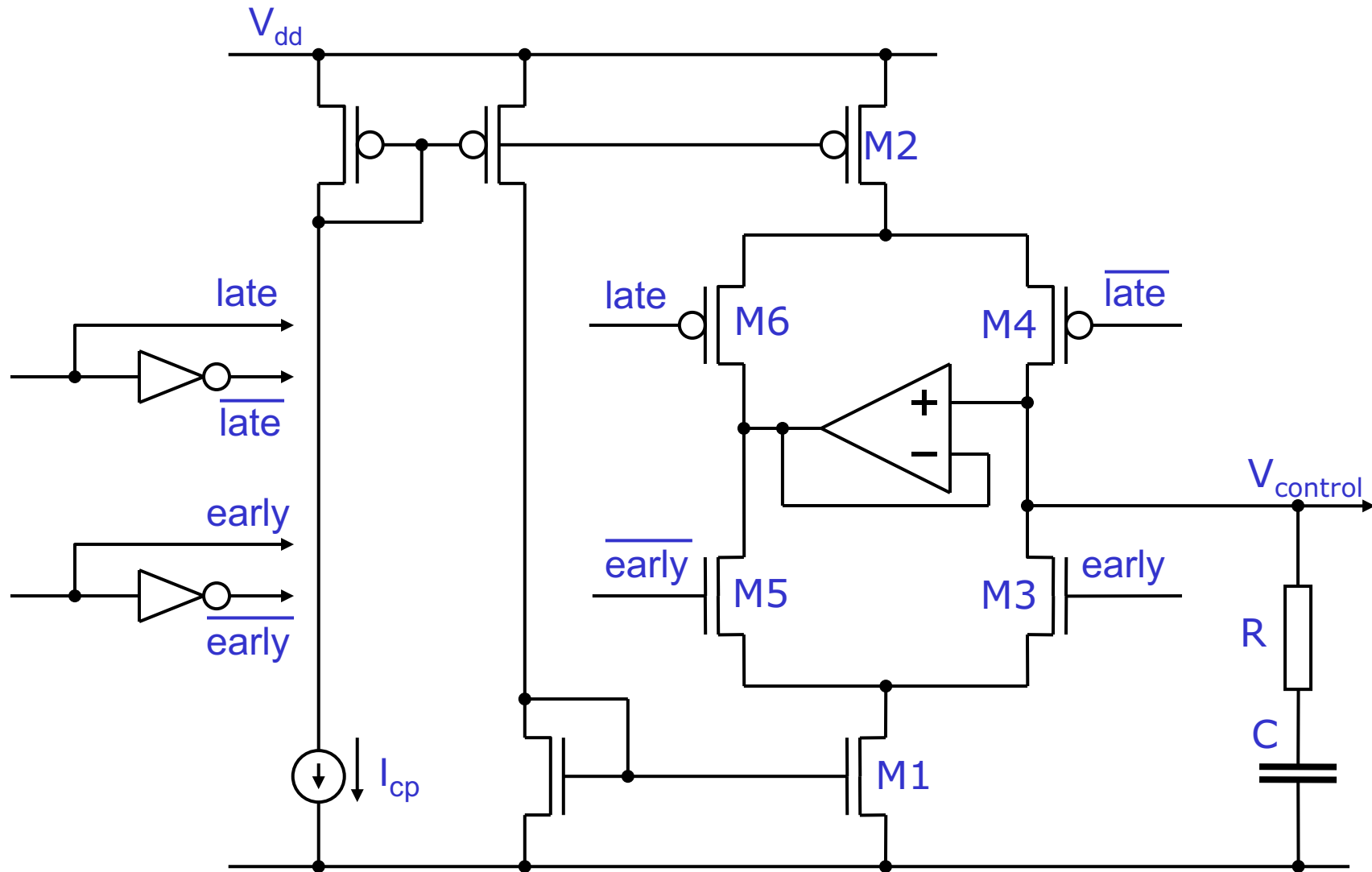

# Charge Pump Operation

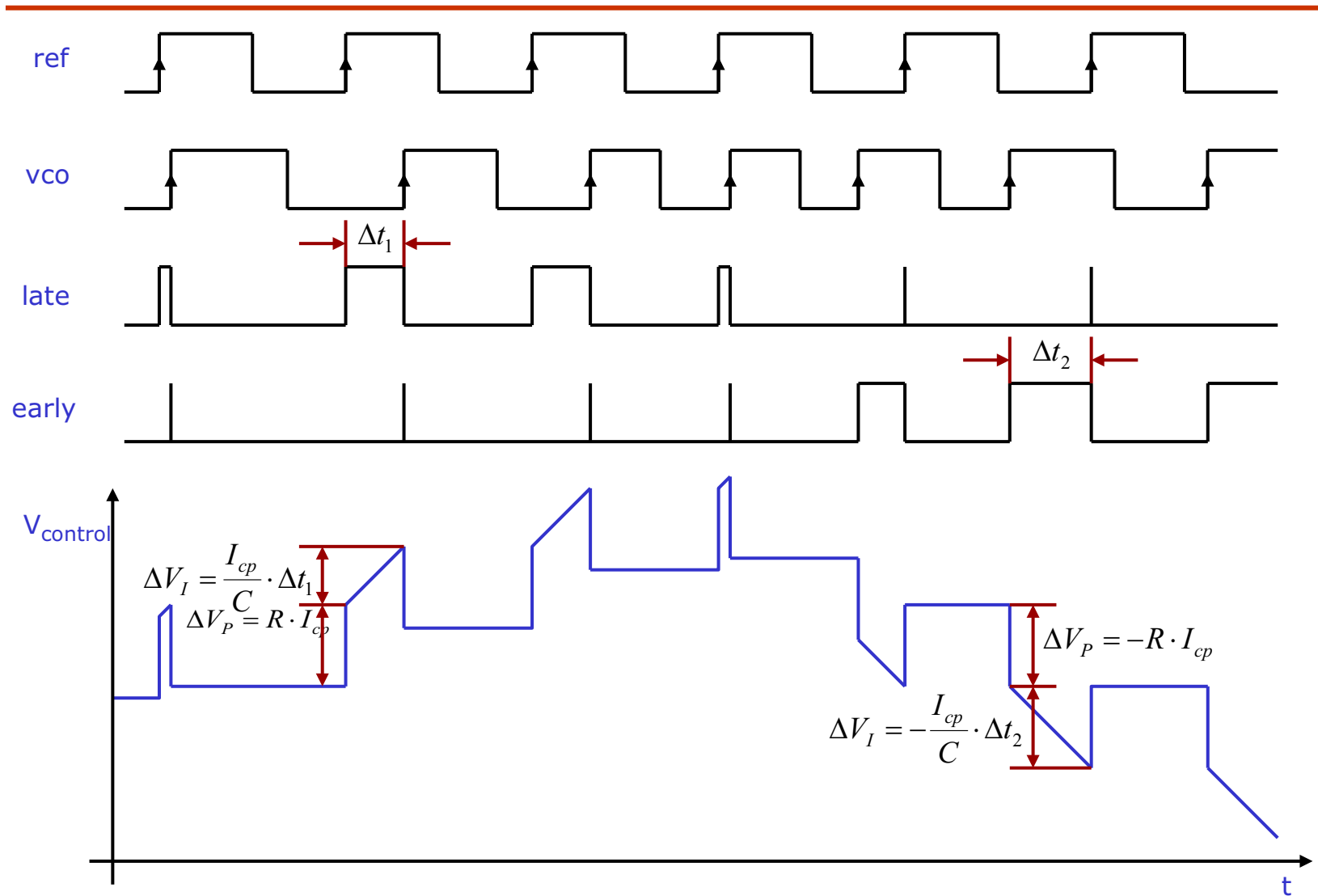

# Charge-Pump PLL with PFD

Assume the PLL is locked  $\omega_{in} = \omega_{out}$

Phase error

$$\phi_{err}(s) = \phi_{in}(s) - \phi_{out}(s) \quad [1]$$

'ON' time for either 'Late' or 'Early'


Average current in one cycle

Lumped contributions of:

- Phase-Frequency Detector
- Charge-Pump
- Filter impedance

$$t_{on} = \frac{|\phi_{err}|}{\omega_{in}} \rightarrow Q = I_{cp} \frac{\phi_{err}}{\omega_{in}} \rightarrow i_d = I_{cp} \frac{\phi_{err}}{2\pi} \rightarrow V_{cnt}(s) = I_{cp} \cdot \frac{\phi_{err}(s)}{2\pi} \cdot Z(s) \quad [2]$$

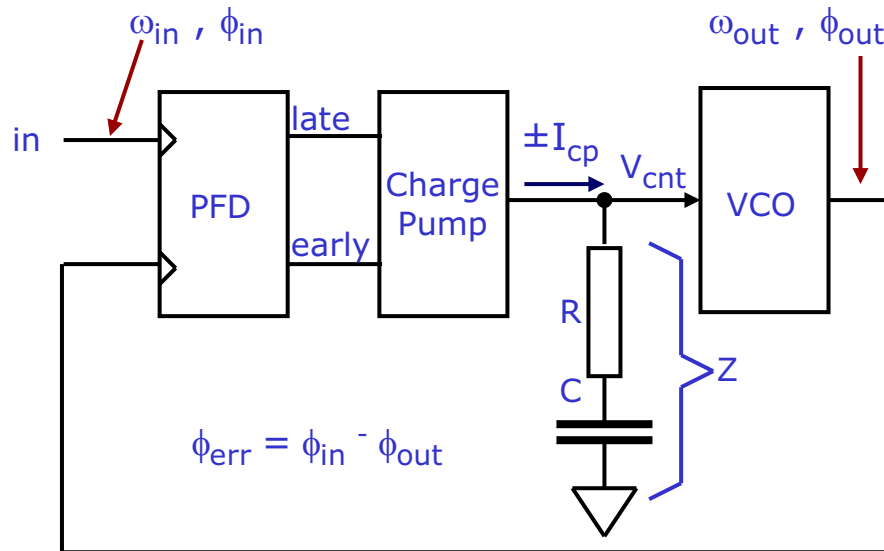
The charge delivered in one cycle is proportional to the phase error  $\phi_{err}$



VCO phase

$$\phi_{out}(s) = \frac{K_{vco}}{s} \cdot V_{cnt}(s) \quad [3]$$

$K_{vco}$  in rad/(s.V)

 

$$\frac{\phi_{out}(s)}{\phi_{in}(s)} = H(s) = \frac{K_{vco} \cdot I_{cp} \cdot Z(s)}{2\pi \cdot s + K_{vco} \cdot I_{cp} \cdot Z(s)} \quad [4]$$

# A Second Order System

$$Z(s) = R + \frac{1}{s \cdot C} \quad [5]$$

$$[4] \left. \vphantom{\begin{matrix} [4] \\ [5] \end{matrix}} \right\} \longrightarrow H(s) = \frac{I_{cp} \cdot (1 + R \cdot C \cdot s) \cdot K_{vco}}{2\pi \cdot C \cdot s^2 + I_{cp} \cdot (1 + R \cdot C \cdot s) \cdot K_{vco}} \quad [6]$$

[6] can be put in the form:

A zero appears in the transfer function:  
It is used to compensate the PLL response

The loop is second order

$$H(s) = \frac{(1 + \tau_z \cdot s)}{\frac{1}{\omega_n^2} \cdot s^2 + \frac{2 \cdot \xi}{\omega_n} \cdot s + 1} \quad [7]$$

$$\tau_z = R \cdot C$$

$$\omega_n = \sqrt{\frac{I_{cp} \cdot K_{vco}}{2\pi \cdot C}}$$

$$\xi = \frac{R \cdot C}{2} \cdot \omega_n$$

$$K = 2 \cdot \xi \cdot \omega_n = \frac{R \cdot I_{cp} \cdot K_{vco}}{2\pi}$$

Compensating zero time constant

Natural frequency

Damping factor


Loop gain

Any two of these parameters define the linearized, time-averaged behavior of the PLL
 
# PLL Stability


Open-loop transfer function:

$$H_O(s) = \frac{I_{cp}}{2\pi} \cdot \frac{1 + s \cdot \tau_z}{s \cdot C} \cdot \frac{K_{vco}}{s}$$




For acceptable phase margin  
Place the zero  $1/\tau_z$  well below  $\omega_n$

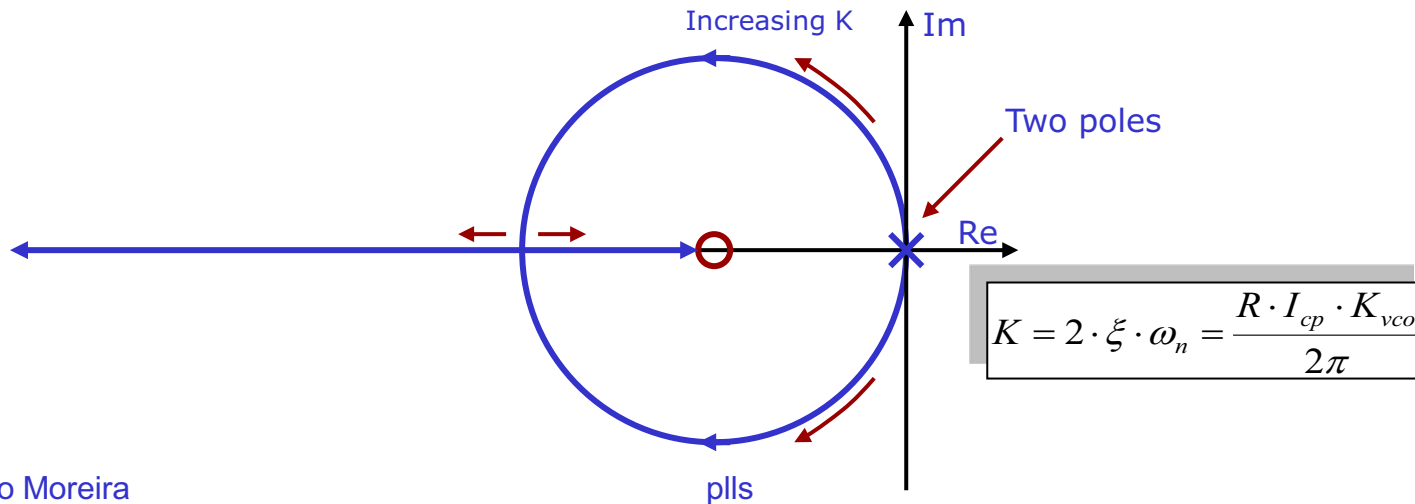( $\omega_n$  cross over frequency of  $H_O(s)$  if no zero was present)





# Jitter Peaking

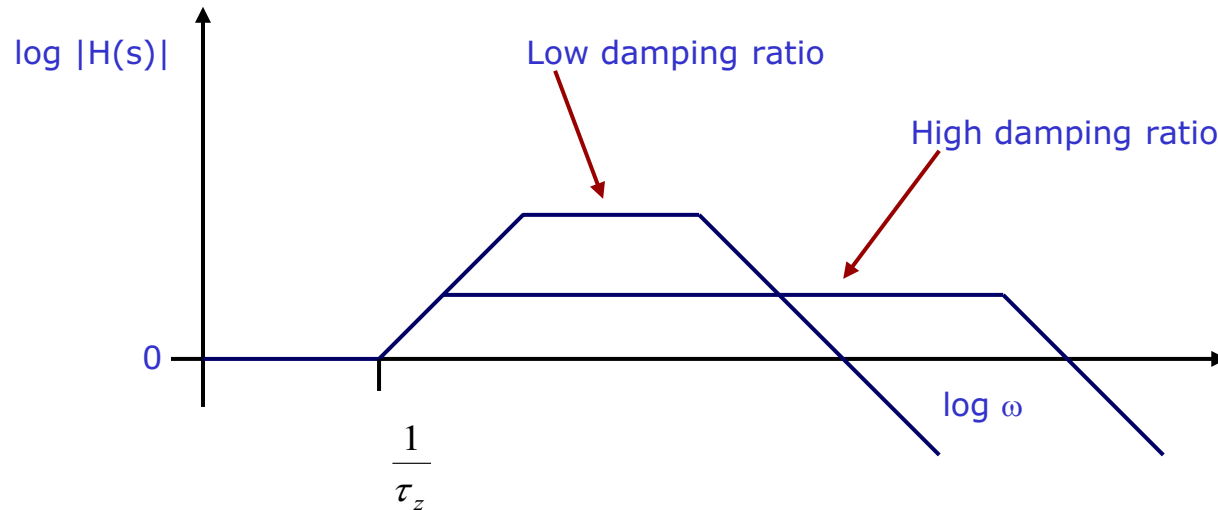

$$|H(s)| = \left| \frac{(1 + \tau_z \cdot s)}{\frac{1}{\omega_n^2} \cdot s^2 + \frac{2 \cdot \xi}{\omega_n} \cdot s + 1} \right|$$

For large damping ratios the zero frequency is below the closed-loop poles

Over a given band of frequencies,  $H(s)$  will exceed unity. Jitter frequencies within this band will be amplified


To minimize jitter peaking keep the first closed-loop pole next to the zero by using high loop gains

# PLL Modeling with Verilog

Verilog → Hardware description language for digital circuits

Used for:

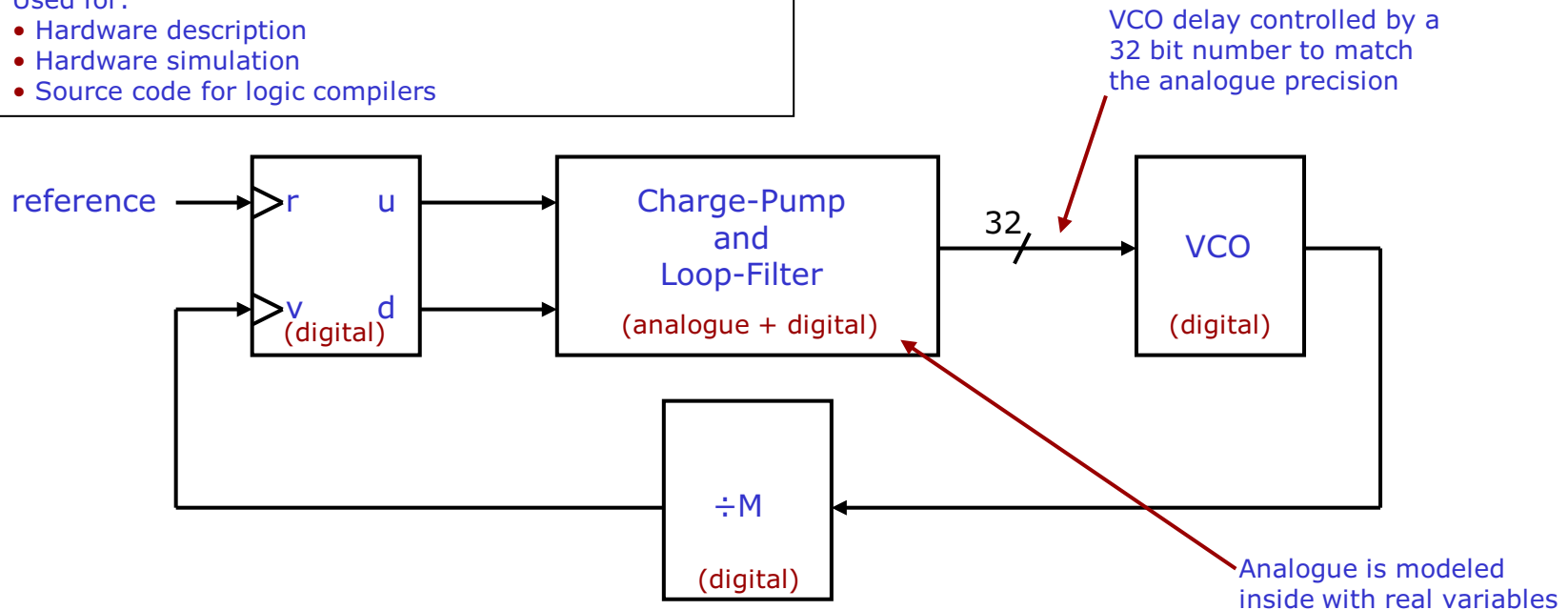- Hardware description
- Hardware simulation
- Source code for logic compilers



Algorithm:

- Slice the time in very thin intervals (much smaller than  $T_{VCO}$ )
- Make the time advance in these time increments
- At every time increment do:
  - Update the phase detector outputs
  - Calculate the new filter voltage according to the phase detector state
  - Update the VCO frequency as function of the filter voltage

# Phase Detector and VCO

## Phase Frequency Detector

```
`timescale 1 fs / 1 fs
module ThreeStatePD (down, up, r, v);
output
    down,      // Early signal
    up;        // Late signal
input
    r,         // Reference input
    v;        // VCO input
wire
    r, v, reset;
reg
    up, down;
initial
    begin
        up = 0;
        down = 0;
    end
always @ (posedge r)
    up <= #1 1'b1;
always @ (posedge v)
    down <= #1 1'b1;
always @ (posedge reset)
    begin
        up <= #1 1'b0;
        down <= #1 1'b0;
    end
assign #1
    reset = up & down;
endmodule
```

## VCO

```
`timescale 1 fs / 1 fs
module VCO( delay_control, vco_output);
input[31:0]  delay_control;
output vco_output;
reg reset;

initial begin
    reset=1;
    #100000;
    reset=0;
end

delay_element10
    delay1( .in(~vco_output & ~reset), .delay_control(delay_control),
            .out(tap1)),
    delay2( .in(tap1), .delay_control(delay_control), .out(tap2)),
    delay3( .in(tap2), .delay_control(delay_control), .out(tap3)),
    delay4( .in(tap3), .delay_control(delay_control), .out(vco_output));
endmodule

// ----- //
`timescale 1 fs / 1 fs
module delay_element10( in, delay_control, out);
input
    in;
input[31:0]  delay_control;
output
    out;
reg
    out;
initial
    out = 1'b0;


always @(in)
    begin
        out <= #( delay_control/8 ) in; // delay =
            delay_control/(2*number_of_delay_cells);
    end
endmodule
```

Delay control: 32 bit number

Ring oscillator with delay control

Cell delay is controlled here

# Loop Filter Simulation: R-C filter

 

Notice that the time increments don't need to be constant (they have to be small). In that case, replace in the equation  $\Delta t$  by:  $\Delta t_n = t_n - t_{n-1}$

$$\frac{T_{VCO}}{100} \leq \Delta t \leq \frac{T_{VCO}}{10}$$

Typically

Paulo Moreira

- Simulation step:  $t_n = t_{n-1} + \Delta t$
- The current  $I(t)$ 
  - It is "imposed" on the circuit (it is the independent variable)
  - It is controlled by the phase-detector output
- For accuracy the time advances in small increments  $\Delta t$ :
  - Capacitor voltages change very little during a simulation step
  - The time integral of a function in the interval  $t_{n-1}$  to  $t_n$  can be approximated by:

$$\int_{t_{n-1}}^{t_n} f(t) dt = f(t_{n-1}) \cdot \Delta t \quad [1]$$

- For the simple R-C filter:

$$V_{cap}(t_n) = V_{cap}(t_{n-1}) + \frac{1}{C} \int_{t_{n-1}}^{t_n} I(t) dt \quad [2]$$

$$V_{control}(t_n) = R \cdot I(t_n) + V_{cap}(t_n) \quad [3]$$

- Simulation equations:

$$V_{cap}(t_n) \cong V_{cap}(t_{n-1}) + \frac{1}{C} \cdot I(t_{n-1}) \cdot \Delta t \quad [4]$$

$$V_{control}(t_n) = R \cdot I(t_n) + V_{cap}(t_n) \quad [5]$$

# Charge Pump & Loop Filter

Charge-Pump (includes the loop filter)

```
`timescale 1 fs / 1 fs
module ChargePump(up, down, delay_control);
.
.
.
`define DeltaVProportional (`Icp * `Rfilt)/1.0E-3 // PLL proportional term (in mV)
`define DeltaVIntegral (`Tref * `Icp / `Cfilt)/1.0E-3 // PLL integral term (in mV)
.
.
.
real ← dv_capacitor, // Differential capacitor voltage (in mV)
        control_voltage, // Integral plus proportional control voltage (in mV)
        frequency, // VCO frequency (in GHz)
        period, // VCO period (in ns)
        integral_term, // loop control integral term (in mV)
        direct_term; // loop control proportional term (in mV)

initial
begin
.
.
.
        integral_term = `DeltaVIntegral/`IntegrationPoints;
        direct_term = `DeltaVProportional;
        integral_evaluation_time = 25000000/`IntegrationPoints;
end
.
.
.
```

Variables used in 'analogue' computations declared as real

# Charge Pump

Main loop, runs at regular time intervals

always

begin

if ( ~reset )

begin

// The integral and proportional terms are expressed as voltages

if (up)

// Up refers to frequency not voltage

begin

if ( `InitialFilterVoltage + dv\_capacitor > `MinimumFilterVoltage)

dv\_capacitor = dv\_capacitor - integral\_term;

end

if (down)

// Up refers to frequency not voltage

begin

if ( `InitialFilterVoltage + dv\_capacitor < `MaximumFilterVoltage)

dv\_capacitor = dv\_capacitor + integral\_term;

end

end

Calculate capacitor voltage increment

Update the capacitor voltage

if ((~up & ~down) | (up & down))

control\_voltage = `InitialFilterVoltage + dv\_capacitor;

else if (up)

control\_voltage = `InitialFilterVoltage + (dv\_capacitor - direct\_term);

else if (down)

control\_voltage = `InitialFilterVoltage + (dv\_capacitor + direct\_term);

frequency = `C0 + control\_voltage\*(`C1 + control\_voltage\*(`C2 + control\_voltage\*`C3));

period = 1.0/frequency;

DelayControl = period\*1e6; // first convert the real into an integer

#(integral\_evaluation\_time);

Update the VCO period

end

assign

/\* The variable "delay\_control" represents the ring oscillator period in fs \*/

#1 delay\_control = DelayControl + vco\_phase\_noise;


Add VCO phase noise

endmodule

Time step control

pll5

# Simulation Example

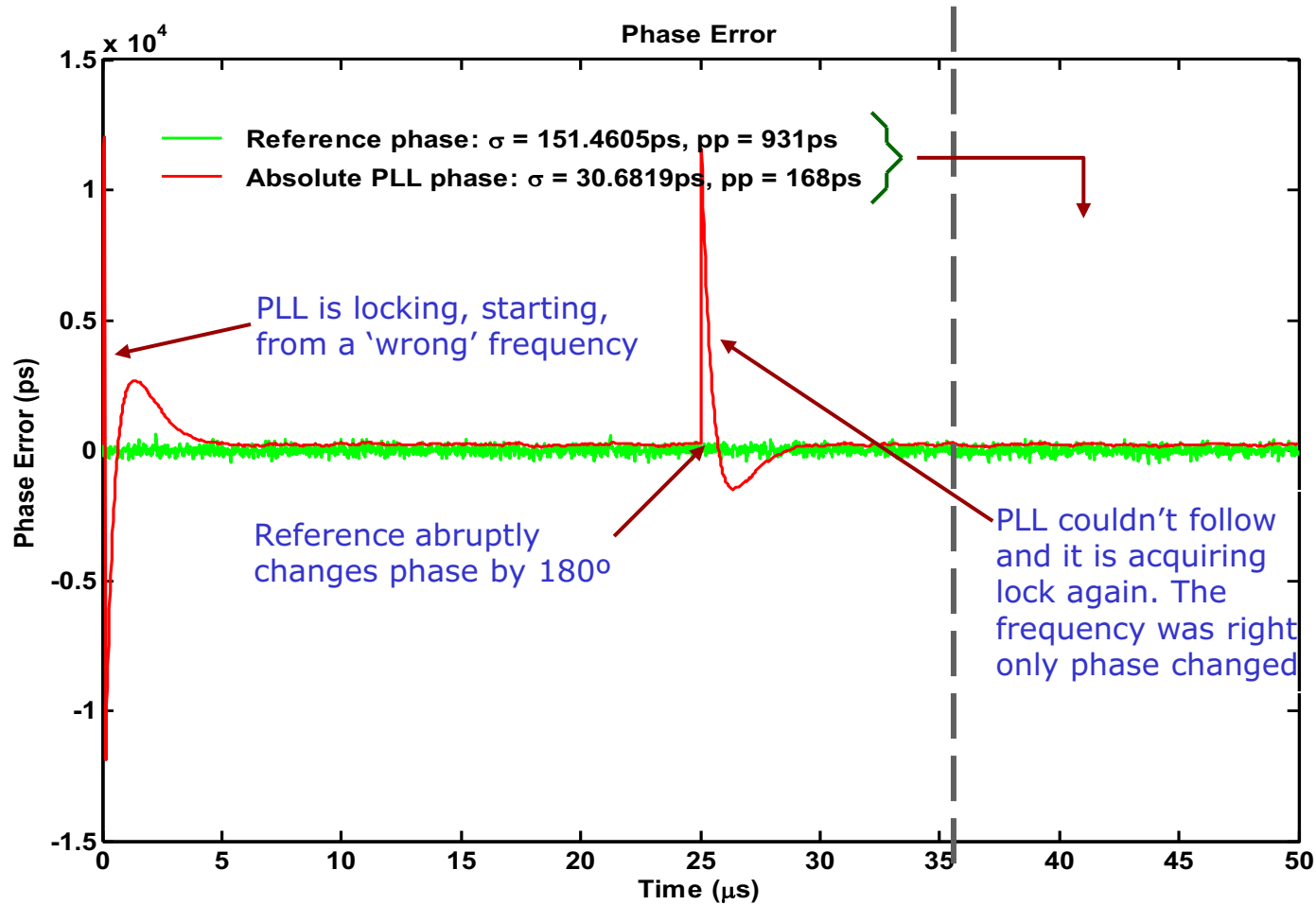

# Loop Filter Simulation: (R-C)||C filter

- The filter equations are:

$$V_1(t_n) = V_1(t_{n-1}) + \frac{1}{C_1} \int_{t_{n-1}}^{t_n} I_1(t) dt \quad [1]$$


$$V_2(t_n) = V_2(t_{n-1}) + \frac{1}{C_2} \int_{t_{n-1}}^{t_n} I_2(t) dt \quad [2]$$

$$I_1(t) = \frac{V_2(t) - V_1(t)}{R} \quad [3]$$

$$I_2(t) = I(t) - I_1(t) \quad [4]$$

$$[1] \ \& \ [3] \ \longrightarrow \ V_1(t_n) = V_1(t_{n-1}) + \frac{1}{C_1} \int_{t_{n-1}}^{t_n} \left[ \frac{V_2(t) - V_1(t)}{R} \right] dt \quad [5]$$
 
$$[2], [3] \ \& \ [4] \ \longrightarrow \ V_2(t_n) = V_2(t_{n-1}) + \frac{1}{C_2} \int_{t_{n-1}}^{t_n} \left[ I(t) - \frac{V_2(t) - V_1(t)}{R} \right] dt \quad [6]$$





# Loop Filter Simulation: (R-C)||C filter

$$I_1(t_{n-1}) = \frac{V_2(t_{n-1}) - V_1(t_{n-1})}{R}$$

[7]


- Using the same approximations as before:

$$V_1(t_n) = V_1(t_{n-1}) + \frac{I_1(t_{n-1}) \cdot \Delta t}{C_1}$$

[8]

$$V_2(t_n) = V_2(t_{n-1}) + \frac{[I(t_{n-1}) - I_1(t_{n-1})] \cdot \Delta t}{C_2}$$

[9]




 


$$\frac{T_{VCO}}{100} \leq \Delta t \leq \frac{T_{VCO}}{10}$$

Time increment guideline:

- Simulation speed  $\Delta T = T_{VCO}/10$
- Simulation accuracy  $\Delta T = T_{VCO}/100$

# SPICE versus Model

    

$\Delta T = t_{cp}/3$

$\Delta T = t_{cp}/10$

