



**The Abdus Salam
International Centre for Theoretical Physics**



2177-6

**ICTP Latin-American Basic Course on FPGA Design for Scientific
Instrumentation**

15 - 31 March 2010


Gates

MOREIRA Paulo Rodrigues S.


*CERN
Geneva
Switzerland*

Outline

- Introduction
- Transistors
- The CMOS inverter
- Technology
- Scaling
- **Gates**
 - The NAND gate
 - "Reading" CMOS gates
 - Designing CMOS gates
- Sequential circuits
- Storage elements
- Phase-Locked Loops
- Example

 


NAND 2-inputs

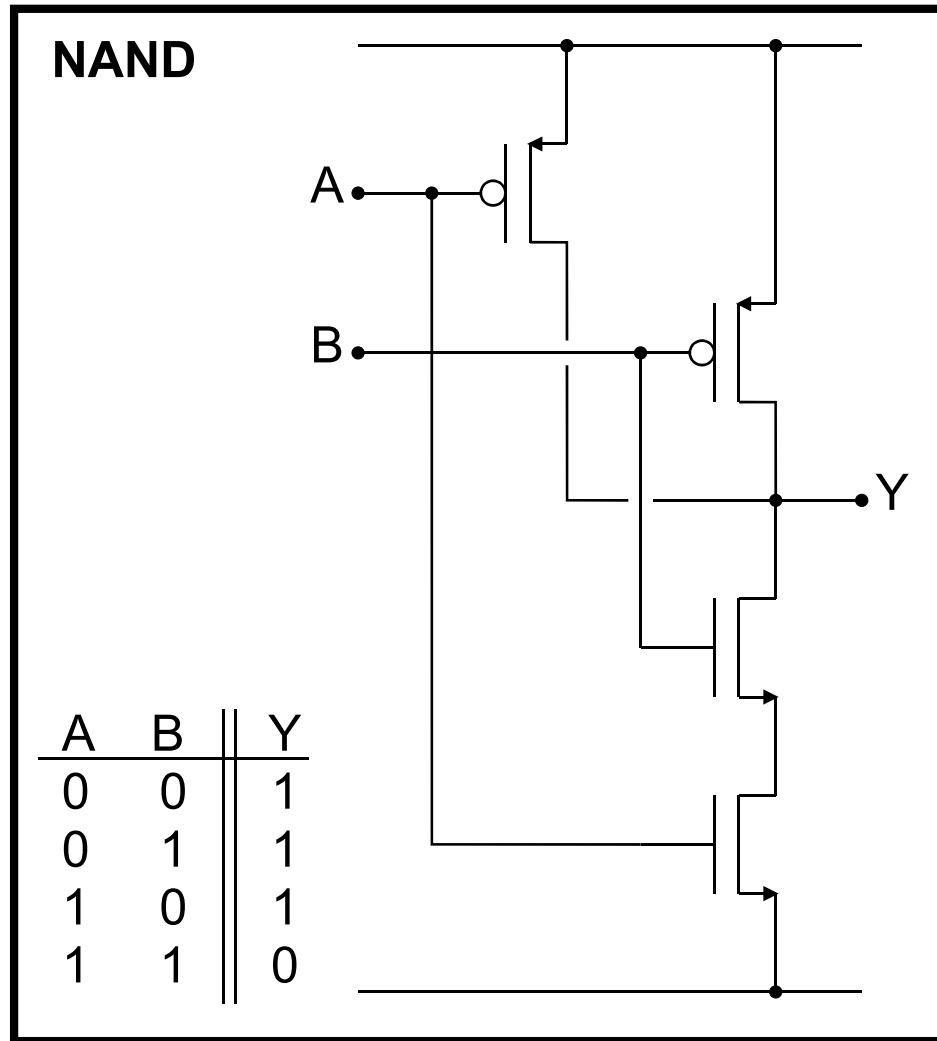


"Gates are
inverters in
disguise!"


NAND 3-inputs

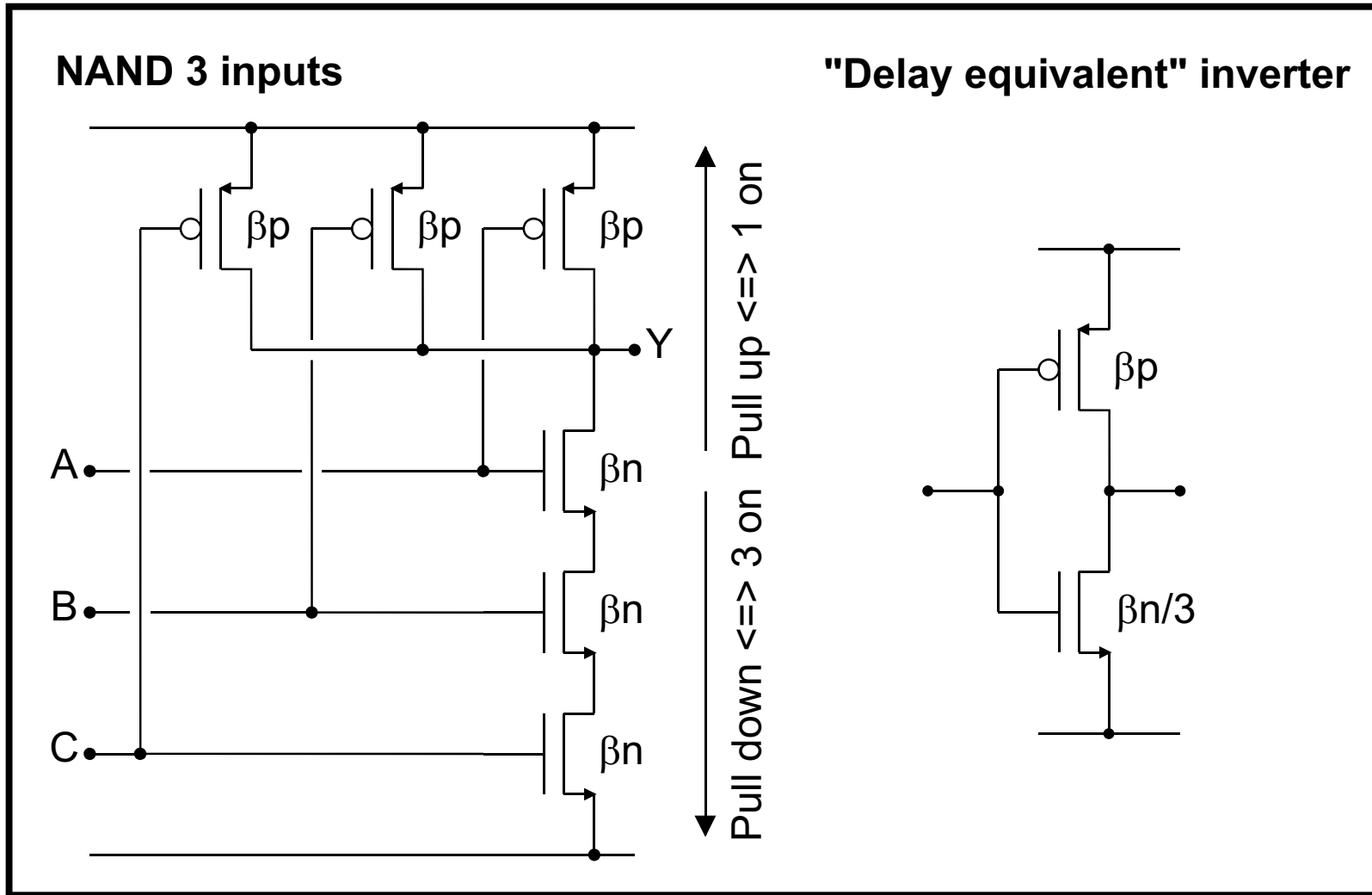


NAND 3-inputs

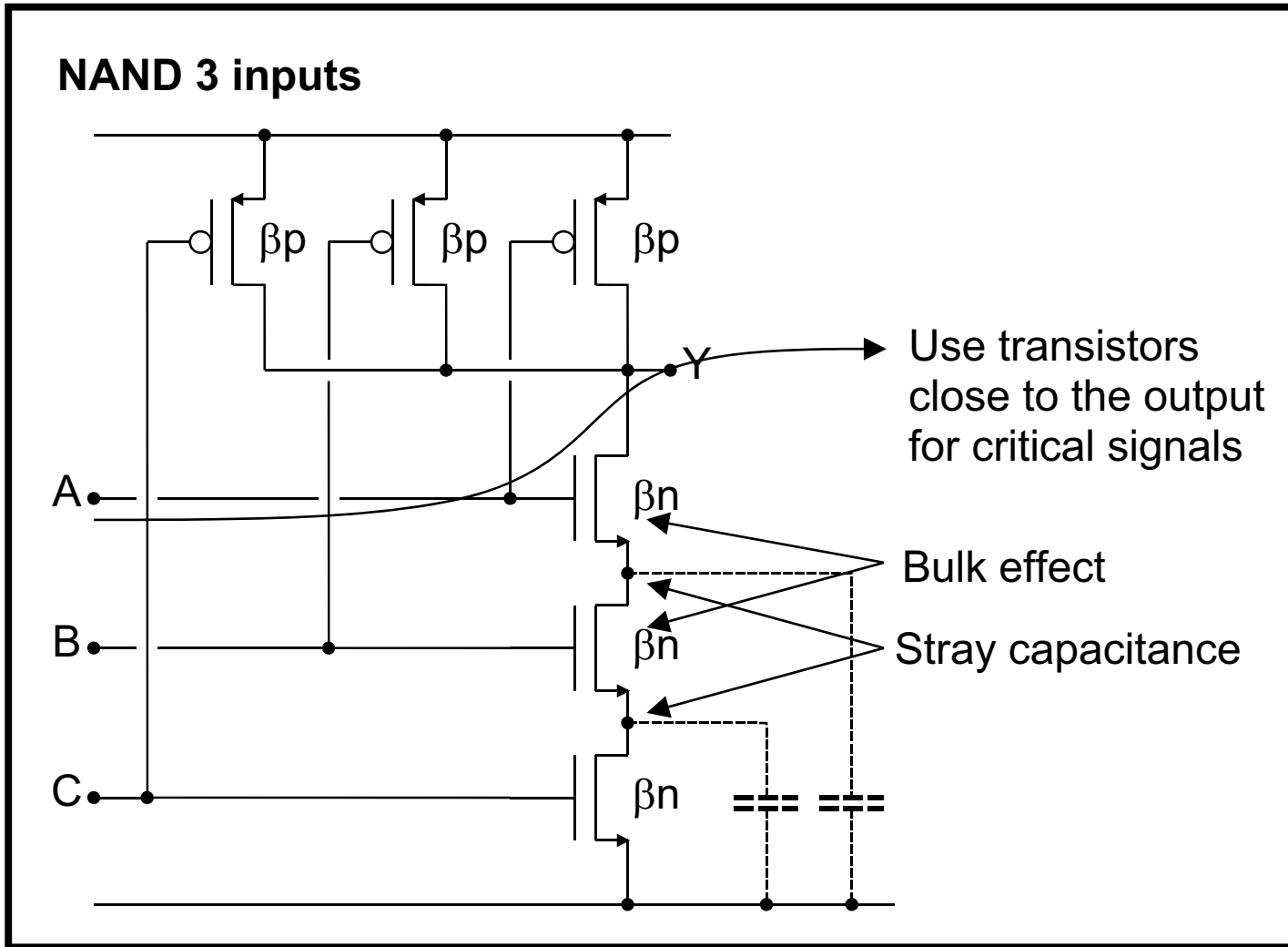


NAND 3-inputs

 


NAND 3-inputs

 

"Reading" CMOS gates

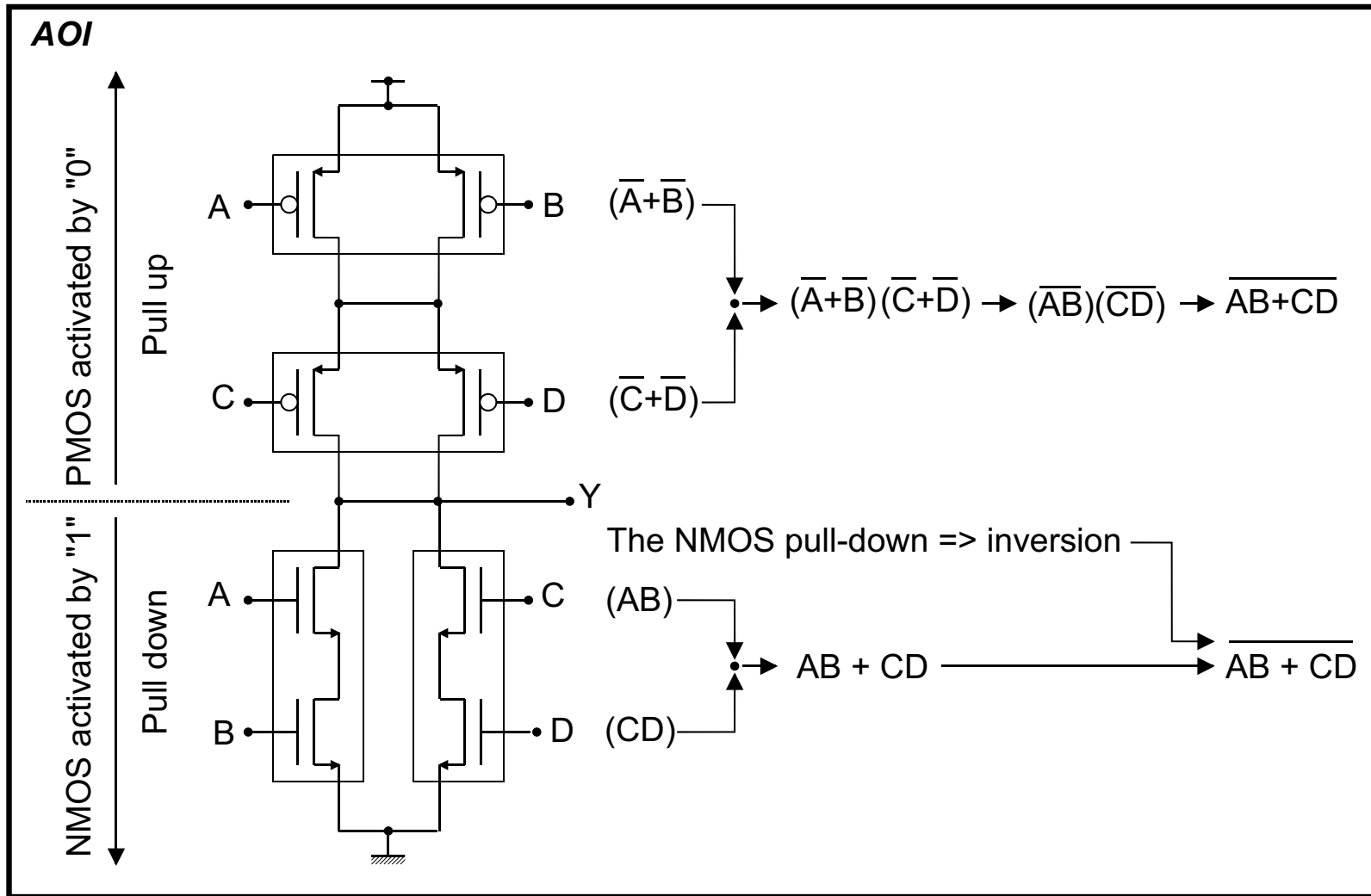

Designing CMOS gates

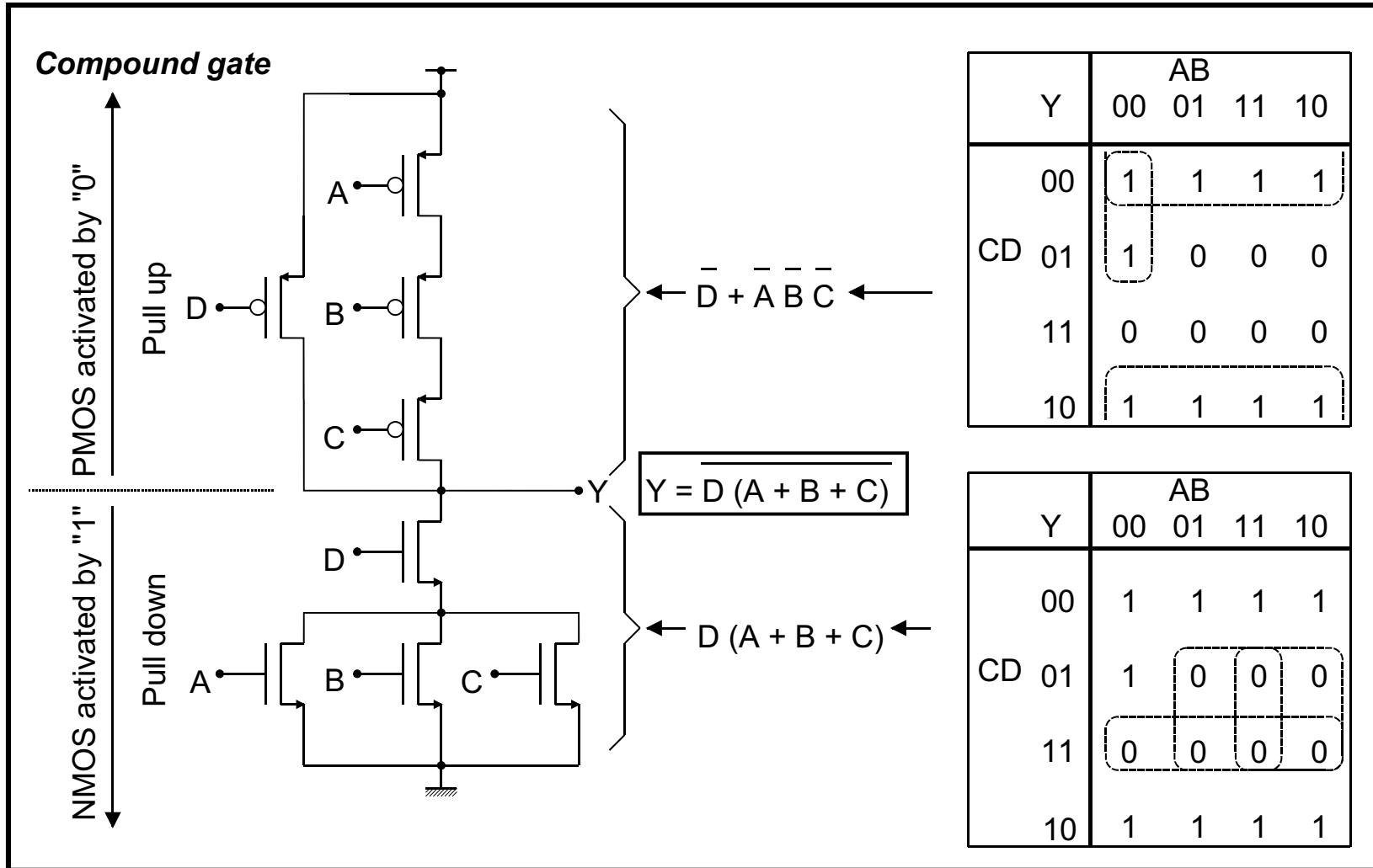

Complex CMOS gates

- Can a compound gate be arbitrarily complex?

- NO, propagation delay is a strong function of fan-in:

$$t_p = a_0 \cdot FO + a_1 \cdot FI + a_2 \cdot (FI)^2$$

- FO \Rightarrow Fan-out, number of loads connected to the gate:

- 2 gate capacitances per FO + interconnect

- FI \Rightarrow Fan-in, Number of inputs in the gate:

- Quadratic dependency on FI due to "RC" signal path across the channels:

- The resistance increases with the number of transistors in series
- Each drain and source diffusion adds additional parasitic capacitance

- Avoid large FI gates (Typically $FI \leq 4$)