

2499-22

**International Training Workshop on FPGA Design for Scientific
Instrumentation and Computing**

11 - 22 November 2013

Serial Communicaton with FPGA

Thulasiraman NANDHA KUMAR
*Department of Electrical & Electronic Engineering, Faculty of
Engineering, Jalan Broga, 43500 Semenyih, Selangor
Malaysia*



Serial communication with FPGA

Dr.T .Nandha Kumar

Senior Member IEEE, Fellow HEA(UK), C.Eng.(UK)

(nandhakumaar.t@nottingham.edu.my)

Associate Professor

The University of Nottingham



Malaysia

Objective


- Design & Implementation RS232 Transceiver on FPGA

- Verification
 - Simulation
 - Hardware


RS232 Transceiver

  

Serial port in Nexys2

 

RS232 Specification

 

Baud Rate	T
110	9.09 ms
300	3.33 ms
1200	833 us
2400	417 us
4800	208 us
9600	104 us
19200	52 us
115200	8.6 us

The parity bit is disabled. Therefore the efficient data rate be $(115200 \cdot (8/10)) / 8$ bits/sec that is equal to 11520 bits/sec.



Receiver Design (Rxd)

```
entity Rs232Rxd is
    port( Reset, Clock16x, Rxd: in std_logic;
          DataOut1: out std_logic_vector (7 downto 0));
end Rs232Rxd;
```

Rxd- Clock 16x

```
process (SystemClock)
begin

if SystemClock'event and SystemClock = '1' then
  if Reset = '1' then
    iCount9 <= (others=>'0');
  elsif
    iCount9 = "101000101" then -- the divider is 325, or "101000101"
    iCount9 <= (others=>'0');
  else iCount9 <= iCount9 + '1';
  end if;
end if;

end process;


iClock16x <= iCount9(8);
```

153846Hz, which is equal to $50\text{MHz}/325$
 $16 * \text{baudrate} = 153600\text{Hz}$


Rxd -START Bit Detection

```
process (Clock16x)
begin
if rising_edge(Clock16x) then
if Reset = '1' or iReset = '1' then
iRxd1 <= '1';
iRxd2 <= '1';
iClock1xEnable <= '0';
iClockDiv <= (others=>'0');
else
iRxd1 <= Rxd;
iRxd2 <= iRxd1;
end if;
if iRxd1 = '0' and iRxd2 = '1' then
iClock1xEnable <= '1';
end if;
if iClock1xEnable = '1' then
iClockDiv <= iClockDiv + '1';
end if;
end if;
end process;

iClock1x <= iClockDiv(3);
```

 

Detection of
falling edge

 

Generation of
9600Hz clock



Rxd - Synchronous state machine

```
process (iClock1xEnable, iClock1x)
begin

if iClock1xEnable = '0' then
    iNoBitsReceived <= (others=>'0');
    presState <= stIdle;
elseif rising_edge(iClock1x) then
    iNoBitsReceived <= iNoBitsReceived + '1';
    presState <= nextState;
end if;

if rising_edge(iClock1x) then
    if iEnableDataOut = '1' then
        iDataOut1 <= iShiftRegister;
    else
        iShiftRegister <= Rxd & iShiftRegister(7 downto 1);
    end if;
end if;


end process;

DataOut1 <= iDataOut1;
```


```

process (presState, iClockIxEnable, iNoBitsReceived)
begin
iReset <= '0';
iEnableDataOut <= '0';
case presState is
when stIdle =>
if iClockIxEnable = '1' then
nextState <= stData;
else
nextState <= stIdle;
end if;
when stData =>
if iNoBitsReceived = "1001" then
iEnableDataOut <= '1';
nextState <= stStop;
else
iEnableDataOut <= '0';
nextState <= stData;
end if;
when stStop =>
nextState <= stRxdCompleted;
when stRxdCompleted =>
iReset <= '1';
nextState <= stIdle;
end case;
end process;

```

 

Rxd - Simulation


 




Transmitter

- Read the data in parallel
 - Use slide switches
 - Start signal
- Transmit in Serial

7 Segment Display

  

An un-illuminated seven-segment display, and nine illumination patterns corresponding to decimal digits

7 Segment LED -HDL Design

```
entity decoder is
  Port(      Q : in std_logic_vector(3 downto 0);
        Seg : out std_logic_vector(6 downto 0));
end decoder;
```

```
architecture Behavioral of decoder is
```

```
begin
```

```
  Seg <="0000001" when q = "0000" else
    "1001111" when q = "0001" else
    "0010010" when q = "0010" else
    "0000110" when q = "0011" else
    "1001100" when q = "0100" else
    "0100100" when q = "0101" else
    "0100000" when q = "0110" else
    "0001111" when q = "0111" else
    "0000000" when q = "1000" else
    "0000100" when q = "1001" else
    "0001000" when q = "1010" else
    "1100000" when q = "1011" else
    "0110001" when q = "1100" else
    "1000010" when q = "1101" else
    "0110000" when q = "1110" else
    "0111000" when q = "1111" else
    "1111111";
```

```
end Behavioral;
```

-- Segment encoding

```


  a
  ---
  f |   | b
    --- <- g
  e |   | c
    ---
  d


```

LED seg order

a, b, c, d, e, f, g
seg6, seg5, seg4, seg3, seg2, seg1, seg0

7 segment LED – Nexys2

 


 


```
-- Generate the scan clock 50MHz/2**16 (763Hz)
process(Clock)
begin
if Clock'event and Clock='1' then
    iCount16 <= iCount16 + '1';
end if;
end process;
--Send four digits to four 7-segment display using scan mode
with iCount16 (15 downto 14) select
    iDigitOut <=    Digit0 when "00", -- Connect Digit0 to the 7-segment display
                   Digit1 when "01", -- Connect Digit1 to the 7-segment display
                   Digit2 when "10", -- Connect Digit2 to the 7-segment display
                   Digit3 when "11", -- Connect Digit3 to the 7-segment display
                   Digit0 when others;

with iCount16 (15 downto 14) select
    An <= "1110" when "00", -- with AN0 low only
          "1101" when "01", -- with AN1 low only
          "1011" when "10", -- with AN2 low only
          "0111" when "11", -- with AN3 low only
          "1110" when others;
```

RS 232 Top Level

 

RTL View – RS232

 

ASCII - Hex

ASCII (HEX)	SYMBOL	ASCII (HEX)	SYMBOL	ASCII (HEX)	SYMBOL	ASCII (HEX)	SYMBOL
00	NUL	20	(SPACE)	40	@	60	`
01	SOH	21	!	41	A	61	a
02	STX	22	"	42	B	62	b
03	ETX	23	#	43	C	63	c
04	EOT	24	\$	44	D	64	d
05	ENQ	25	%	45	E	65	e
06	ACK	26	&	46	F	66	f
07	BEL	27	'	47	G	67	g
08	BS	28	(48	H	68	h
09	TAB	29)	49	I	69	i
0A	LF	2A	*	4A	J	6A	j
0B	VT	2B	+	4B	K	6B	k
0C	FF	2C	,	4C	L	6C	l
0D	CR	2D	-	4D	M	6D	m
0E	SO	2E	.	4E	N	6E	n
0F	SI	2F	/	4F	O	6F	o
10	DLE	30	0	50	P	70	p
11	DC1	31	1	51	Q	71	q
12	DC2	32	2	52	R	72	r
13	DC3	33	3	53	S	73	s
14	DC4	34	4	54	T	74	t
15	NAK	35	5	55	U	75	u
16	SYN	36	6	56	V	76	v
17	ETB	37	7	57	W	77	w
18	CAN	38	8	58	X	78	x
19	EM	39	9	59	Y	79	y
1A	SUB	3A	:	5A	Z	7A	z
1B	ESC	3B	;	5B	[7B	{
1C	FS	3C	<	5C	\	7C	
1D	GS	3D	=	5D]	7D	}
1E	RS	3E	>	5E	^	7E	~
1F	US	3F	?	5F	_	7F	



THANK YOU
