



The Abdus Salam
International Centre
for Theoretical Physics



Secretaría
Nacional de
Ciencia y
Tecnología



INTERNATIONAL UNION OF
PURE AND APPLIED PHYSICS



USAC
TRICENTENARIA
Universidad de San Carlos de Guatemala

1st Mesoamerican Workshop on
Reconfigurable X-ray
Scientific Instrumentation for
Cultural Heritage

Hardware Description Language (HDL) for Reconfigurable Instrumentation

Cristian Sisterna

Senior Associate, ICTP-MLAB




Universidad Nacional San Juan- Argentina



Hardware Description Languages

What are them ?

 

Used to **describe** structure, behavior, and timing of digital hardware

Specialized computer languages for describing electronic circuits


They are fundamental to modern digital design, especially for **creating** ASICs and **configuring** FPGAs.

Allow designers to work at a higher level of abstraction than schematic capture

HDL

VHDL
Verilog
SystemVerilog
Chisel
MyHDL

Hardware Description Languages

 

- Developed under the U.S. DoD's VHSIC program.
- Strongly typed
- More verbose and formal (resembles Ada)


- Started as a proprietary language.
- Weakly typed.
- Syntax similar to C programming language

Superset of Verilog.
Adds OOP, improved data types, assertions, interfaces.
Powerful for system-level verification.

C++ libraries for system-level modeling.
Often used for Transaction-Level Modeling (TLM).


Python based HDL

Why HDLs are keys in Digital Design?

 


Abstraction

 Design complex circuits without low-level details




Verification

 Simulate and test designs before fabrication (cost-saving)




Reusability

 Create modular and reusable IP (Intellectual Property) blocks.



Synthesis

 Automatically transform HDL into ASIC/FPGA's hardware components




Scalability

Enable design of very large and complex systems

Introduction to VHDL

Hardware

Language

 

Very High Speed IC

Description


Introduction to VHDL

- ✓ High level of abstraction

```
if(reset='1') then
    count <= 0;
elsif(rising_edge(clk)) then
    count <= count+1;
end if;
```

- ✓ Easy to debug
- ✓ Parameterized designs
- ✓ Re-use
- ✓ IP Cores (free) available

VHDL Synthesis & Simulation

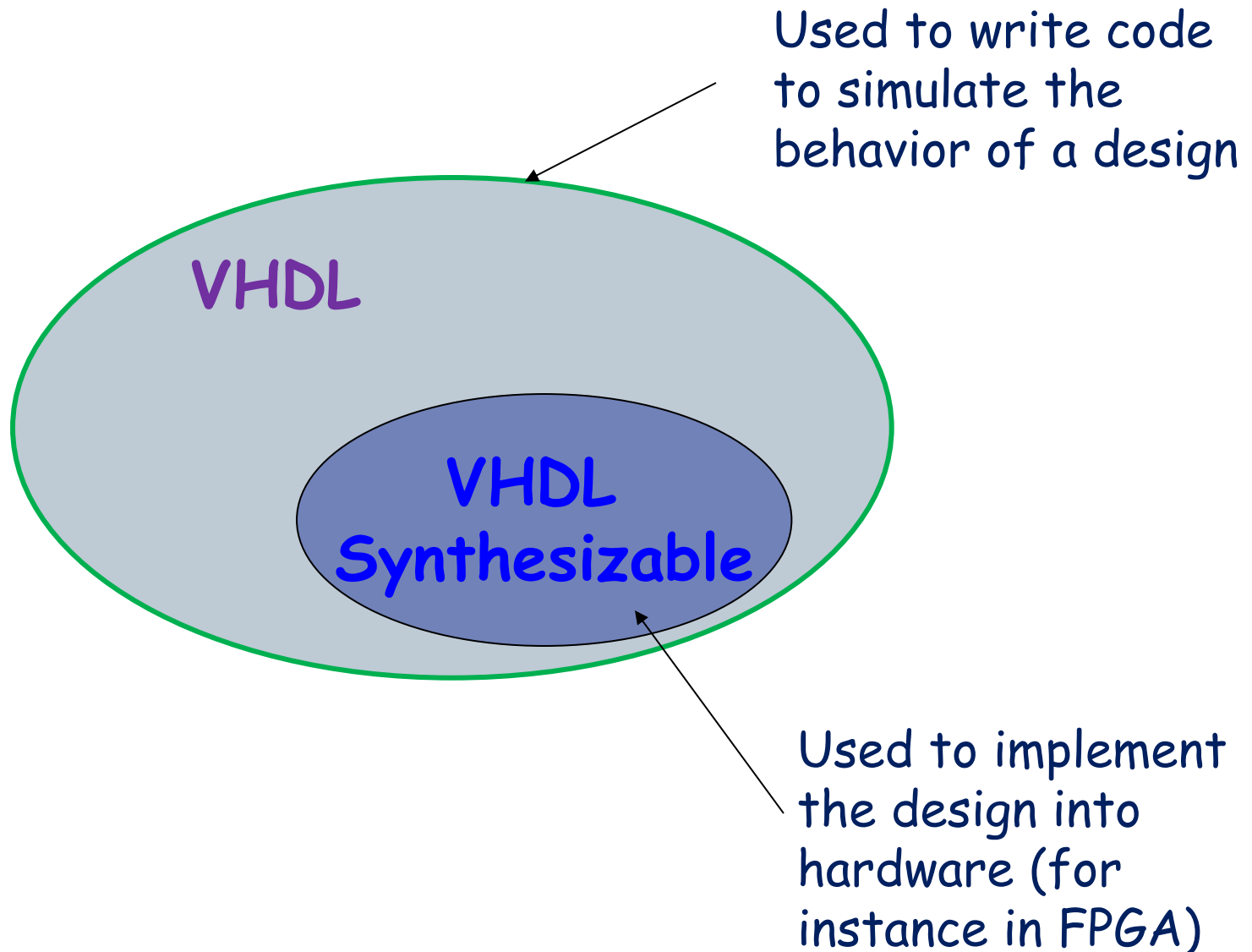

Synthesis versus Simulation

It's important to understand that VHDL is both, a *Synthesis* language and a *Simulation* language.


Synthesis

- Small subset of the language is '*synthesizable*', meaning that it can be translated into logic gates, flip-flops, and other 'hardware' components.
- Every line of VHDL code must have a direct translation into hardware.


Another subset of the language include many features for '*simulation*' or '*verification*', features that have **NO** meaning in hardware.

Simulation

VHDL -> Hardware Description

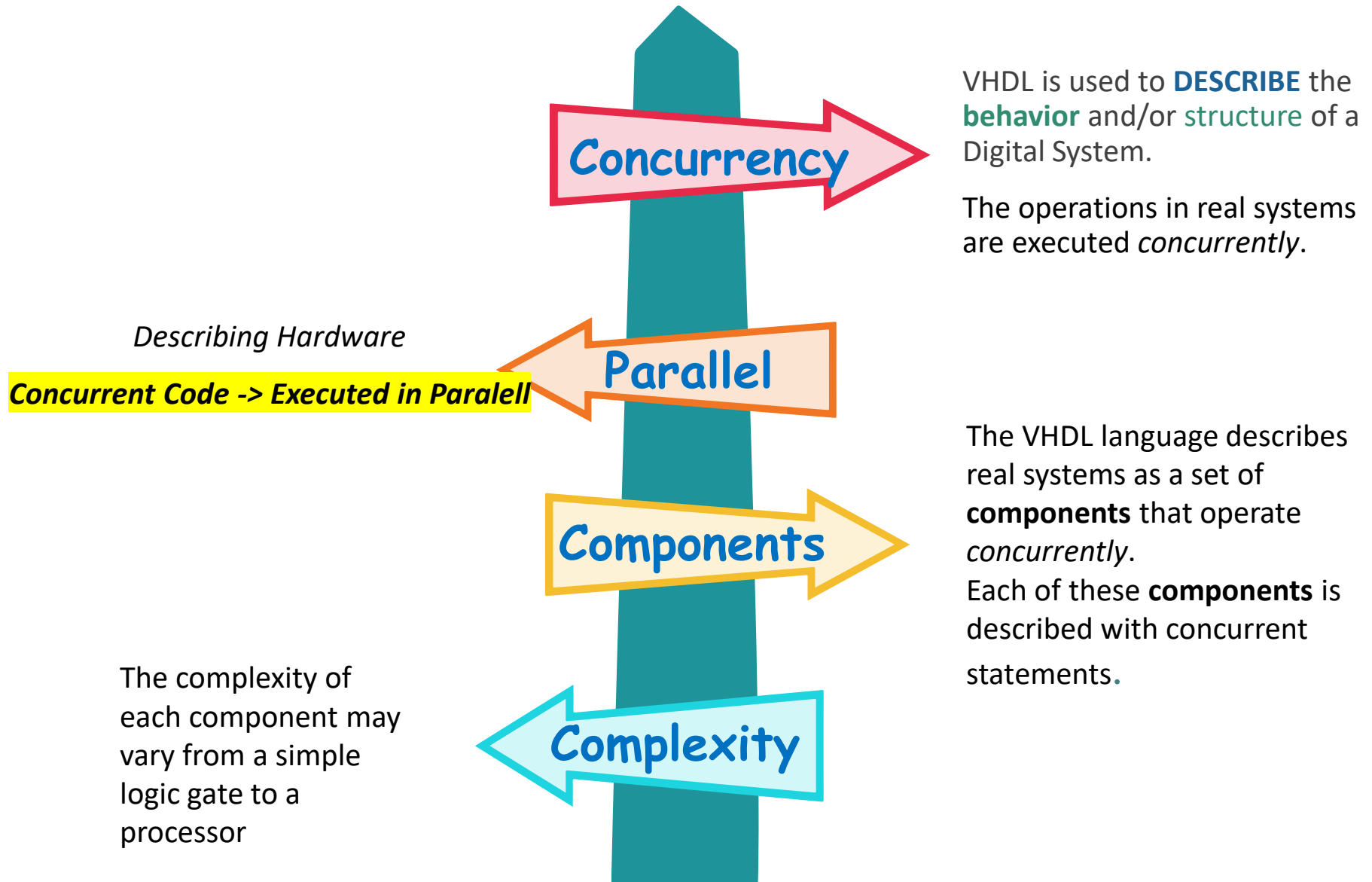


VHDL 'Description' Examples

 

```
if (sel = '1') then
    z <= y;
else
    z <= x;
end if;
```

```
z <= y when sel = '1' else x;
```

VHDL - General Component Structure

 

Libraries and **packages** provides the incorporation of external functions, data types and components to the component to be described

The **entity** defines the I/O ports as well as the name of the component.

Some times a constant(s) is defined (generic) to write parameterized VHDL code



The **architecture** it's where the hardware **behavior** and/or **structure** is described.

It can have from a couple of lines to thousands lines of VHDL code.

ALL CONCURRENTs !


VHDL - General Component Structure

mux2x1.vhd

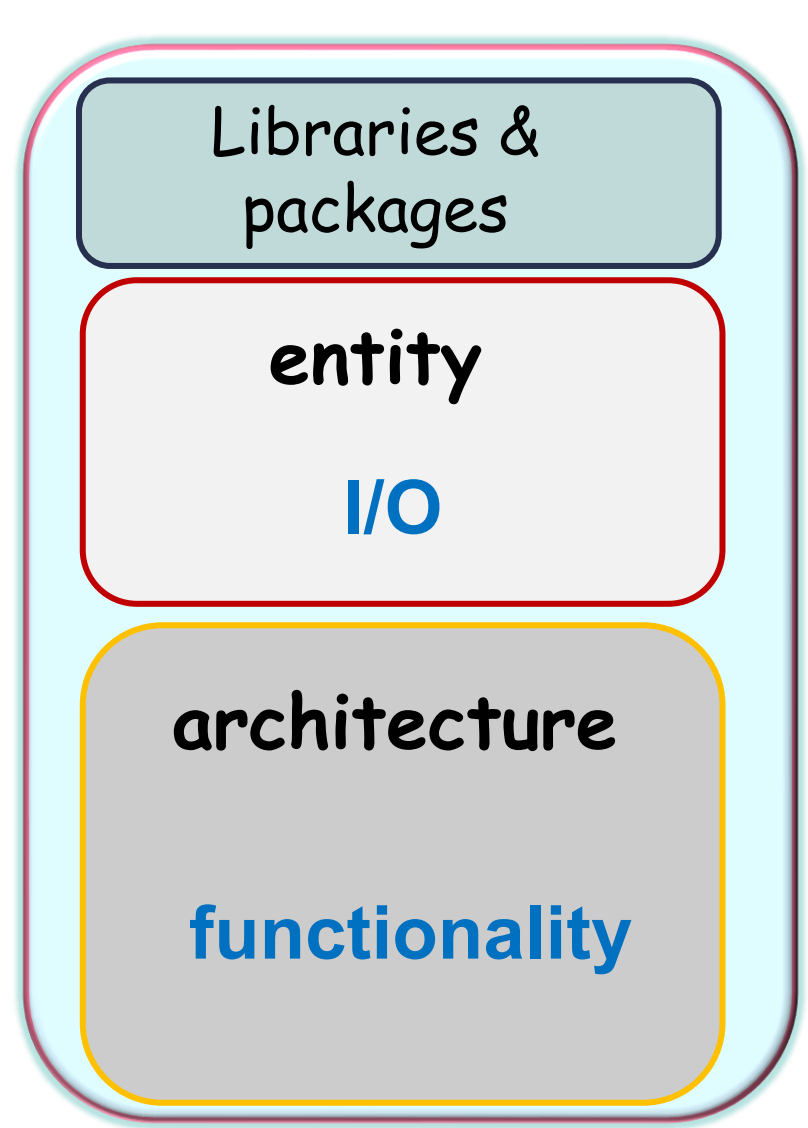 


VHDL - General Component Structure

mux2x1.vhd

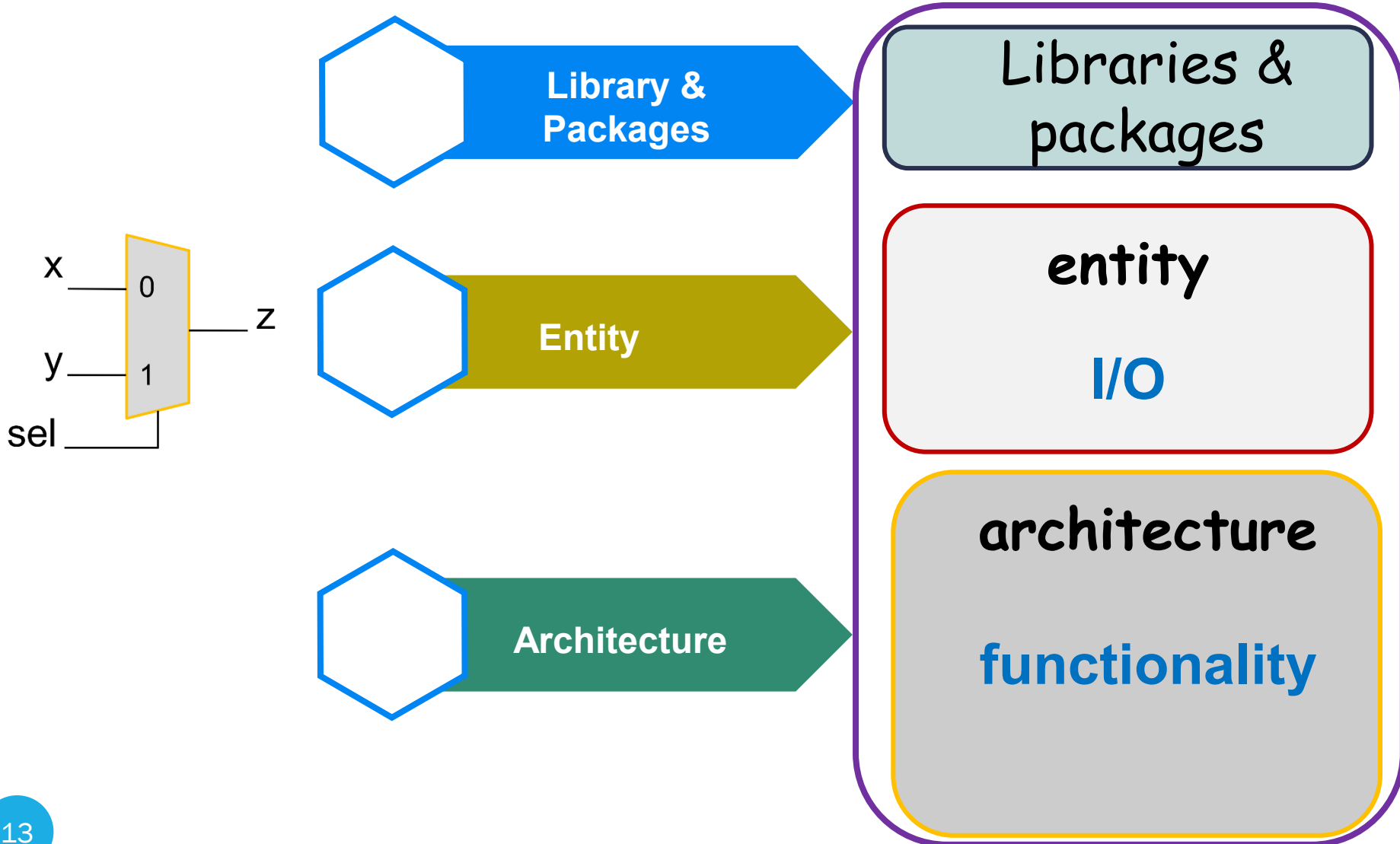


VHDL - General Component Structure

 


Library &
Packages
 
```
library ieee;  
use ieee.std_logic_1164.all;
```



Entity
 
```
entity mux2x1 is  
port (  
    x, y, sel: in std_logic;  
    z         : out std_logic);  
end mux2x1;
```



Architecture

```
architecture test of mux2x1 is  
begin  
    process (x, y, sel)  
    begin  
        if (sel = '1') then  
            z <= y;  
        else  
            z <= x;  
        end if;  
    end process;  
end test;
```

VHDL - General Component Structure

Library & Packages


```
library ieee;  
use ieee.std_logic_1164.all;
```

Entity

```
entity mux2x1 is  
port(  
    x, y, sel: in std_logic;  
    z       : out std_logic);  
end mux2x1;
```

Architecture
 
```
architecture test of mux2x1 is  
begin  
    z <= y when sel='1' else x;  
end test;
```




Test Bench

VHDL Code - Is it really Works?

A **test bench** is a crucial part of the hardware design and verification process.

It's a separate VHDL entity that is used to **simulate and verify the functionality of a VHDL design** (known as the "Device Under Test" or "DUT") by providing it with input stimuli and observing its outputs

Purposes of a test bench


 


Stimuli Generation

It applies a sequence of input values (stimuli) to the DUT's input ports. These stimuli are designed to stimulate all the different operational modes and corner cases of the DUT.

It observes the DUT's output ports and compares them against expected values.

Output Monitoring

  

Verification

It determines whether the DUT behaves as intended:


Assertions: Checking if certain conditions are met during simulation.

Expected Value Comparison: Directly comparing actual outputs with pre-calculated expected outputs.


Self-checking Test Benches: More advanced test benches that automatically report pass/fail status.

When the DUT doesn't behave as expected, the test bench provides a controlled environment to isolate and debug issues.

Debugging

 


Test Bench - Verification

 



Test Bench

Simulator

 


VHDL - Simulation / Verification

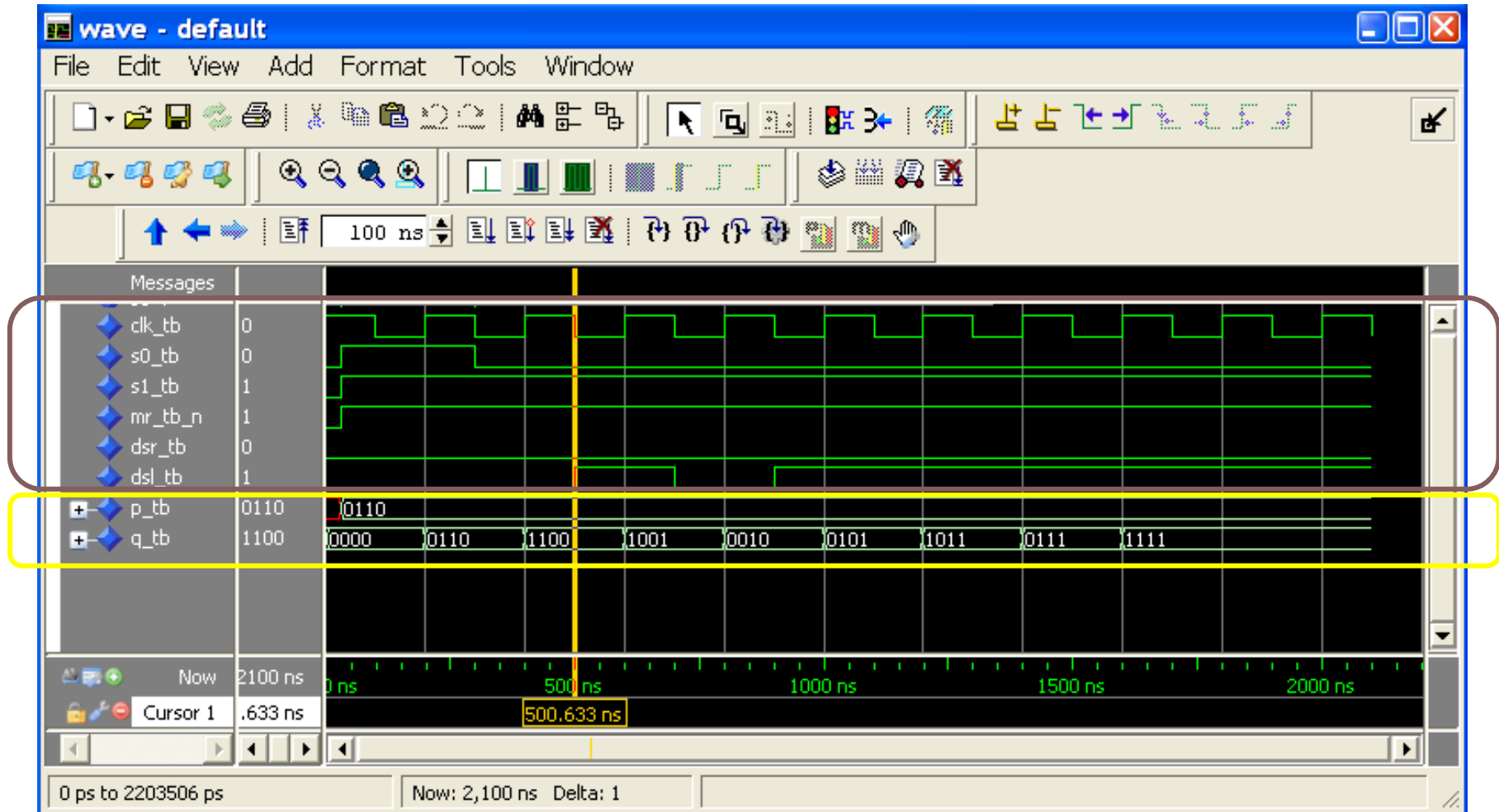

 

VHDL-FPGA Design Flow

VHDL - FPGA Design Flow

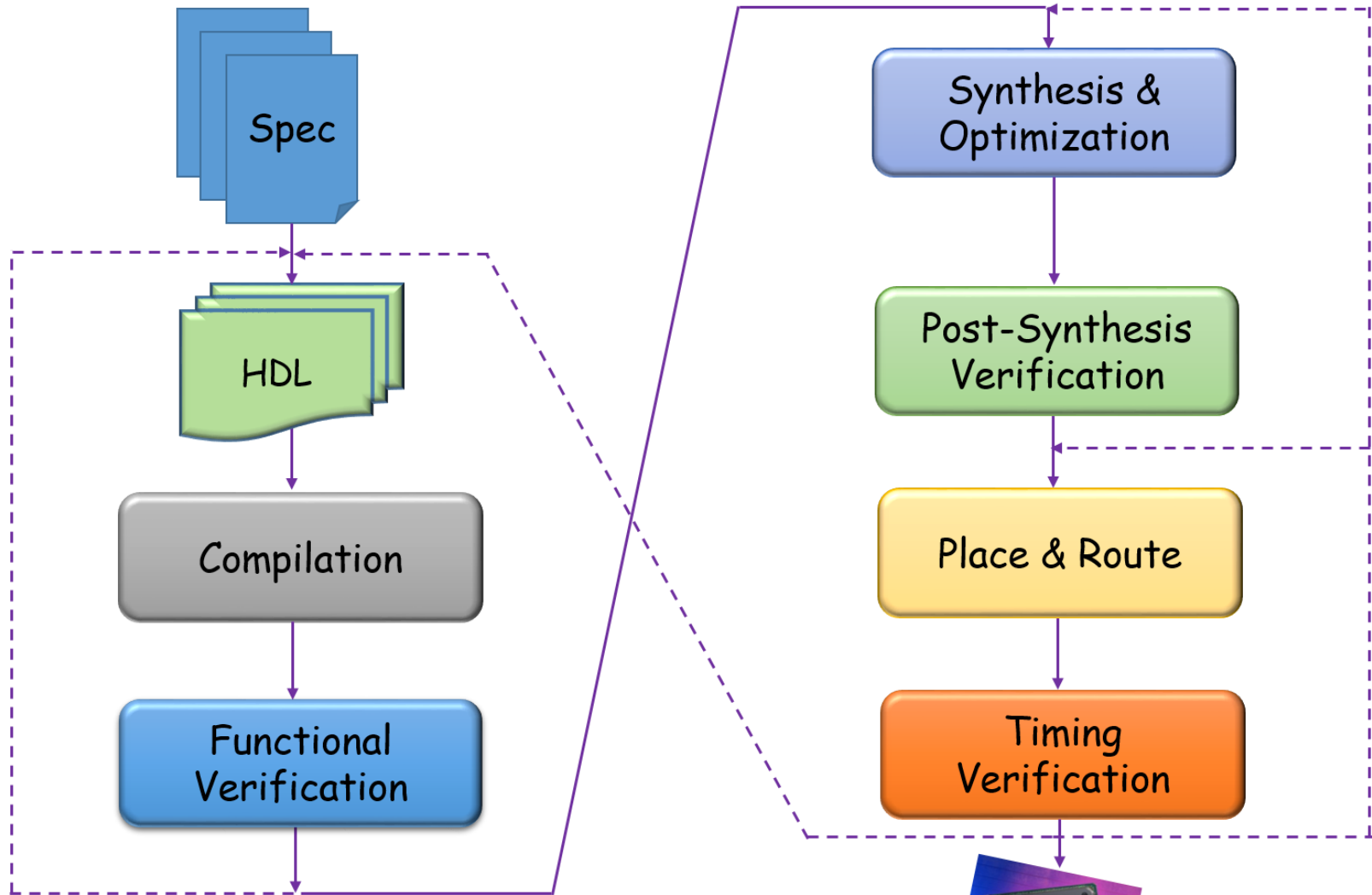

FGPA - Hardware Design Flow

VHDL Code

```
process (clk,rst)
  if (rst = '1') then
    dbus <= (others => '0');
  elsif( rising_edge(clk)) then
    dbus <= data;
  endif;
end process;
```

Timing & Placement Constraints


```
Net "CLK" LOC=V10 | IOSTANDARD=LVC MOS33;
Net "CLK" TNM_NET = sys_clk_pin;
TIMESPEC TS_sys_clk_pin = PERIOD sys_clk_pin 100000 kHz;
Net "CS" LOC = T12 | IOSTANDARD = LVC MOS33;
```


FPGA Library of Components

Virtex, Spartan,
Arria, Artix, Zynq

Synthesis Attributes
 
```
attribute syn_encoding of my_fsm: type is
  "one-hot";
```



 


VHDL Simple Example

Simple Example - VHDL

Design a BCD up-down counter. The count should be displayed in a 7-segment display.

 The system has a high frequency clock and system reset as inputs.



Libraries & Packages

```
-- Library Declarations
```

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

```
-- Synopsys non-standard packages  
-- use ieee.std_logic_arith.all;  
-- use ieee.std_logic_signed.all;  
-- use ieee.std_logic_unsigned.all;
```

```
library ieee;  
use ieee.std_logic_1164.all;
```

Must be present to use *std_logic* type. That is, for ALL synthesisable designs.

```
use ieee.numeric_std.all;
```


Must be present to add arithmetic functions for *signed* and *unsigned* types.

Note: do not do arithmetic operations with *std_logic*/*std_logic_vector*

```
-- Synopsys non-standard packages  
-- use ieee.std_logic_arith.all;  
-- use ieee.std_logic_signed.all;  
-- use ieee.std_logic_unsigned.all;
```

DO NOT USE these packages. They do not belong to the VHDL IEEE standard.

Signal/Port Declarations in the Entity

 


```
-- -----  
-- Entity Declaration  
-- -----  
  
entity top is  
  port (  
    -- system signals  
    high_freq_clock : in  std_logic;  
    sys_reset       : in  std_logic;  
    -- control signals  
    up_down         : in  std_logic;  
    dsply1_anodo    : out std_logic;  
    -- output signals  
    seven_segm_dsply : out std_logic_vector(6 downto 0));  
end entity top;
```

use only
in/out modes


use only
std_logic/std_logic_vector
types

use only **inout** mode in
the higher lever top-
module

Architecture (top)

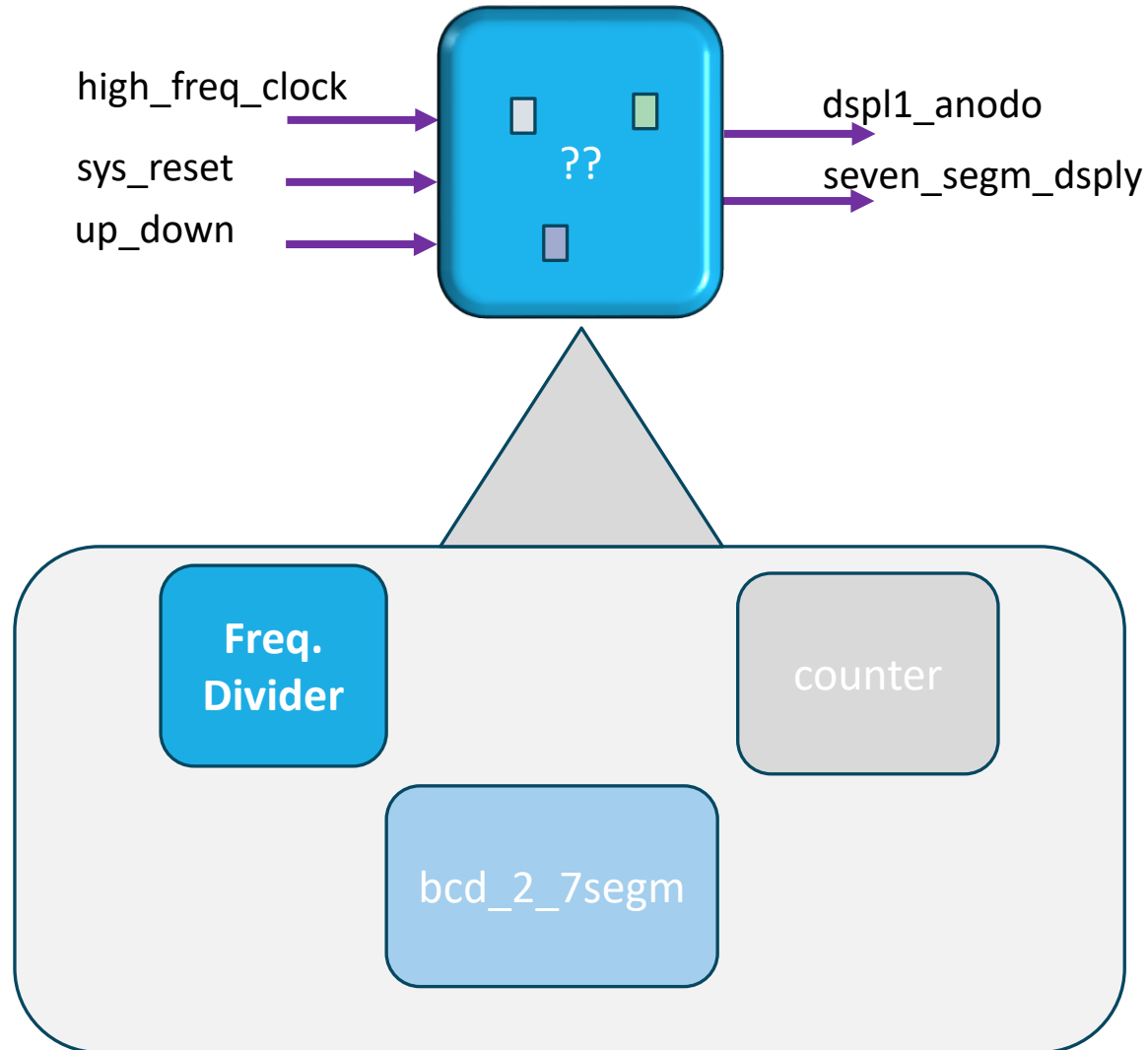

Counter entity/arch.

 

```
-- Entity Declaration
entity cont_4bits is
  port (
    -- Clocks, resets, Config & Miscellaneous Ports
    low_freq_clock_en: in  std_logic;
    sys_clock         : in  std_logic;
    reset             : in  std_logic;
    -- Control Ports
    up_down           : in  std_logic;
    -- Counter Output Ports
    count             : out std_logic_vector (3 downto 0)
  );
end cont_4bits;
```

```
-- architecture
architecture behavioral of cont_4bits is
  -- signal declarations
  signal i_count: unsigned(3 downto 0);

  -- Architecture Body
begin
  -- 4 bits counter
  cnt_pr: process(sys_clock, reset)
  begin
    if(reset = '1') then
      i_count <= (others => '0');
    elsif rising_edge(sys_clock) then
      if (low_freq_clock_en = '1') then
        if(up_down = '1') then
          i_count <= i_count + 1;
        else
          i_count <= i_count - 1;
        end if;
      end if;
    end if;
  end process cnt_pr;

  count <= std_logic_vector(i_count);
end behavioral;
```

Counter Architecture

Declarative part

Descriptive part
(concurrent)

Sequential
statements
(inside a
process)

Concurrent
statement

```
-- architecture
-----
architecture behavioral of cont_4bits is
  -----
  -- signal declarations
  -----
  signal i_count: unsigned(3 downto 0);
  -----

  -- Architecture Body
  -----
begin
  -----
  -- 4 bits counter
  -----


  cnt_pr: process(sys_clock, reset)
  begin
    if(reset = '1') then
      i_count <= (others => '0');
    elsif rising_edge(sys_clock) then
      if (low_freq_clock_en = '1') then
        if(up_down = '1') then
          i_count <= i_count + 1;
        else
          i_count <= i_count - 1;
        end if;
      end if;
    end if;
  end process cnt_pr;
  -----

  count <= std_logic_vector(i_count);
  -----
end behavioral;
```


Understanding Concurrency

```
architecture example of entity_ex is
-- architecture declarative part

begin
-- architecture descriptive part
    signal assignment concurrent statement;
    signal assignment concurrent statement;
    process concurrent statement;
    begin
        signal assignment sequential statement;
        signal assignment sequential statement;
    end process;
    signal assignment concurrent statement;
    process concurrent statement;
    begin
        signal assignment sequential statement;
        signal assignment sequential statement;
    end process;
end example;
```

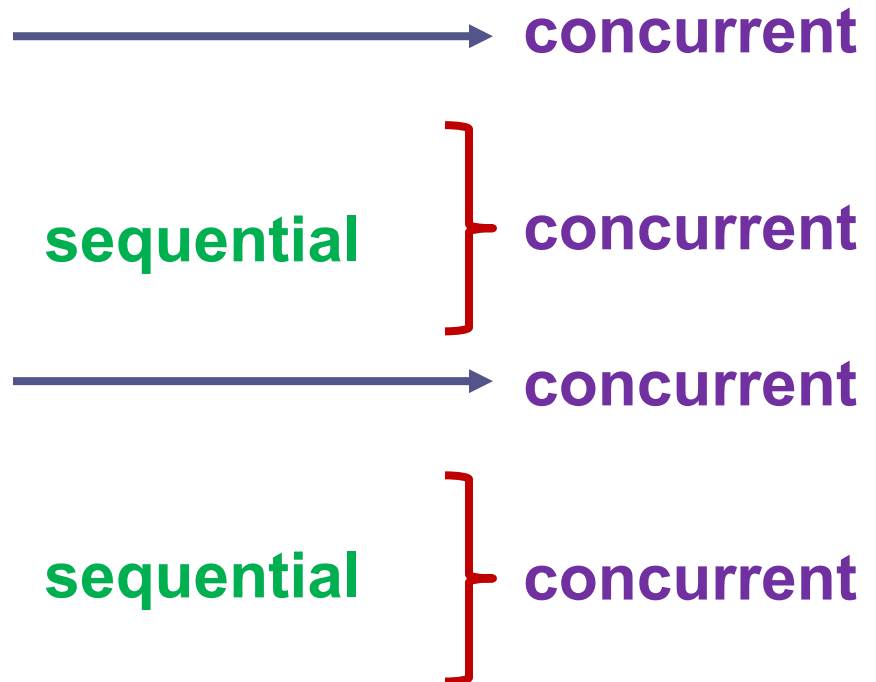

Architecture (top)

 


```

-- architecture
--
architecture structural of top is
--
-- internal signal declarations
--
signal count_i : std_logic_vector(3 downto 0);
signal low_freq_clock_en_i : std_logic;
--
-- architecture body
--
begin
--
-- component instantiations
--
-- bdc-7seg decoder
bcd_7seg_1: entity work.bcd_7seg
port map (
    bcd_in    => count_i,
    segs_out  => seven_seg_dsply,
    enable    => '1',
    dot_out   => open);

-- divisor de frecuencia (50MHz-> ~ 1 seg)
freq_div_1: entity work.freq_div
port map (
    sys_rst      => sys_reset,
    sys_clock_50 => high_freq_clock,
    low_freq_clock_en => low_freq_clock_en_i);


-- contador de 4 bits con reloj de baja frecuencia
cont_4bits_1: entity work.cont_4bits
port map (
    low_freq_clock_en => low_freq_clock_en_i,
    sys_clock         => high_freq_clock,
    reset              => sys_reset,
    up_down            => up_down,
    count              => count_i);

```

 VHDL Types, Objects & Classes

VHDL Data Types

 

Signal Assignment - strongly typed

```
count      <= count + 1;  
carry_out <= (a and b) or (a and c) or (b and c);  
Z          <= y;
```

Left Hand Side (LHS)
Target Signal

Right Hand Side (RHS)
Source Signal(s)

LHS Signal Data Type **==** **RHS Signal Data Type**

```
signal bandera: integer;  
signal flag, enable : std_logic;  
.  
.  
.  
.  
bandera <= flag;      -- ?  
enable  <= flag;      -- ?
```

VHDL Object

An **object** holds a value of some specified **type** and can be one of the three **classes**:
signal, variable, constant

Declaration Syntax:

```
object_class <identifier> : type[ := initial_value];
```

Class

signal
variable
constant

Object

identifier

Type

boolean
std_logic/std_ulogic
std_(u)logic_vector
unsigned
signed
integer

std_logic Type

```
PACKAGE std_logic_1164 IS
-----
-- logic state system  (unresolved)
-----

TYPE std_ulogic IS ( 'U',  -- Uninitialized
                      'X',  -- Forcing  Unknown
                      '0',  -- Forcing  0
                      '1',  -- Forcing  1
                      'Z',  -- High Impedance
                      'W',  -- Weak      Unknown
                      'L',  -- Weak      0
                      'H',  -- Weak      1
                      '-'   -- Wild card
                      );

SUBTYPE std_logic IS resolved std_ulogic;
```

Type Conversion - Casting

VHDL does allow restricted type of CASTING, that is converting values between related types

```
datatype <= type(data_object);
```

```
signal max_rem: unsigned (7 downto 0);  
signal more_t: std_logic_vector( 7 downto 0);  
  
max_rem <= more_t;  
  
max_rem <= unsigned(more_t);
```


unsigned and ***std_logic_vector*** are both vectors of the same element type, therefore it's possible a direct conversion by ***casting***. When there is not type relationship a conversion ***function*** is used.

Type Conversion - Functions


VHDL does have some built-in functions to convert some different data types (not all the types allow conversions)

```
datatype <= to_type(data_object);
```
 
```
signal internal_counter: integer range 0 to 15;  
signal count: std_logic_vector( 3 downto 0);  
  
count <= internal_count;  
  
CoUnT <= std_logic_vector(to_unsigned(internal_count,4));
```



Type Conversion - Cast / Function

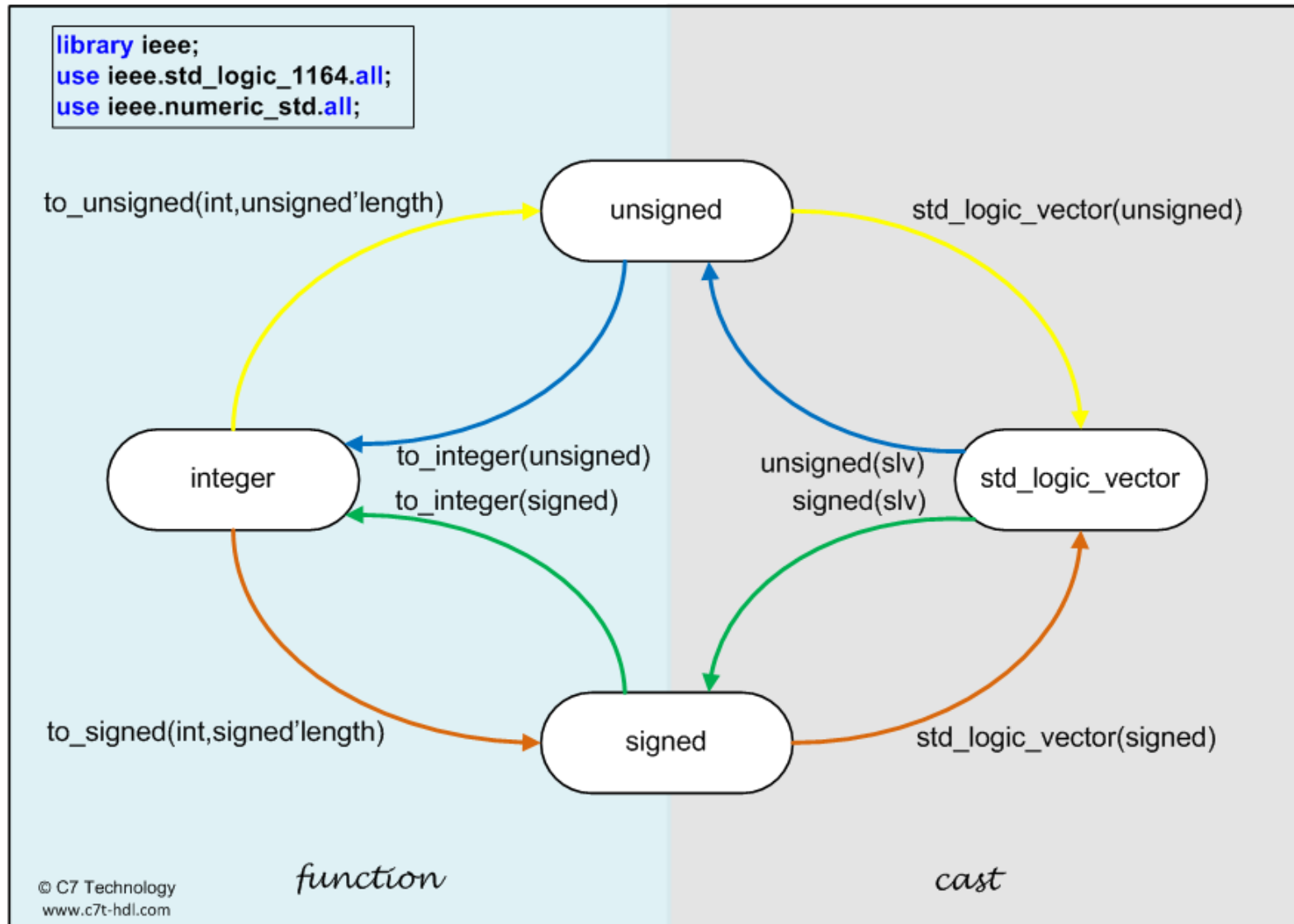


VHDL Operators

Operator	Description	Data type of a	Data type of b	Data type of result
$a ** b$	exponentiation	integer		
abs a	absolute value	integer		
not a	negation	boolean, bit, bit_vector		
$a * b$, a / b , $a \bmod b$, $a \text{ rem } b$	multiplication, division, modulo, remainder	integer		
$+a$, $-a$	identity, negation	integer		integer
$a + b$, $a - b$ $a \& b$	addition, subtraction, concatenation	integer		
		1D array, element		
$a \ll b$, $a \gg b$, $a \lll b$, $a \ggg b$, $a \text{ rol } b$, $a \text{ ror } b$	shift-left (right) logical, shift-left (right) arithmetic, rotate left (right)	bit_vector	integer	bit_vector
$a = b$, $a \neq b$, $a < b$, $a \leq b$, $a > b$, $a \geq b$		any	same as a	boolean
		scalar or 1D array	same as a	boolean
$a \text{ and } b$, $a \text{ or } b$, $a \text{ xor } b$, $a \text{ nand } b$, $a \text{ nor } b$, $a \text{ xnor } b$		boolean, bit, bit_vector	same as a	same as a

VHDL Attributes

 - ☑ It's a way of **extracting** information from a type, from the values of a type
- ☑ It's also a way to allow to **assign additional** information to objects in your design description (such as data related to synthesis)



Array Attributes

- ✓ Array attributes are used to obtain information on the size, range and indexing of an array
- ✓ It's good practice to use attributes to refer to the size or range of an array. So, if the size of the array is change, the VHDL statement using attributes will automatically adjust to the change

Array Attributes – Range Related	
A'range	Returns the range value of a constrained array
A'reverse_range	Returns the reverse value of a constrained array

Array Attributes

Use of the attributes *range* and *reverse_range*

```
variable w_bus: std_logic_vector(7 downto 0);
```

```
then:
```

```
    w_bus' range      -- will return:    7 downto 0
```

```
while:
```

```
    w_bus' reverse_range -- will return:    0 to 7
```

User-defined/Synthesis Attributes

VHDL provides designers/vendors with a way of adding additional information to the system to be synthesized

- + Synthesis tools use this features to add timing, placement, pin assignment, hints for resource locations, type of encoding for state machines and several others physical design information
- + The bad side of synthesis attributes is that the VHDL code becomes synthesis tools/FPGA dependant, NO TRANSPORTABLE

User-defined/Synthesis Attributes

Syntax

```
attribute attr_name: type;
```

```
attribute attr_name of data_object: ObjectType is AttributeValue;
```

Example

```
attribute syn_preserve: boolean;
```

```
attribute syn_preserve of ff_data: signal is true;
```

```
type my_fsm_state is (reset, load, count, hold);
```


```
attribute syn_encoding: string;
```

```
attribute syn_encoding of my_fsm_state: type is "gray";
```

User-defined/Synthesis Attributes

 Example:

```
type ram_type is array (63 downto 0) of  
                                std_logic_vector (15 downto 0);  
signal ram: ram_type;  
attribute syn_ramstyle: string;  
attribute syn_ramstyle of ram: signal is "block_ram";
```



VHDL Statements

Selective Signal Assignment Statement

Syntax

```
with <selection_signal> select  
    target_signal <= <expression> when <value1_ss>,  
        <expression> when <value2_ss>,  
        ...  
        <expression> when <last_value_ss>,  
        <expression> when others;
```

A selective signal assignment describes logic based on mutually exclusive combinations of values of the selection signal

Selective Signal Assignment Statement

Example: Truth Table

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	-
1	1	1	-

"|" means OR only when used in "with" or "case"

'-' means don't care


```
library ieee;
use ieee.std_logic_1164.all;

entity TRUTH_TABLE is
    port(A, B, C: in std_logic;
         Y: out std_logic);
end TRUTH_TABLE;

architecture BEHAVE of TRUTH_TABLE is
    signal S1: std_logic_vector(2 downto 0);
begin
    S1 <= A & B & C; -- concatenate A, B, C
    with S1 select
end BEHAVE;
```


Selective Signal Assignment Statement

*Synthesis
Result*

 

RTL View

FPGA Technology
View

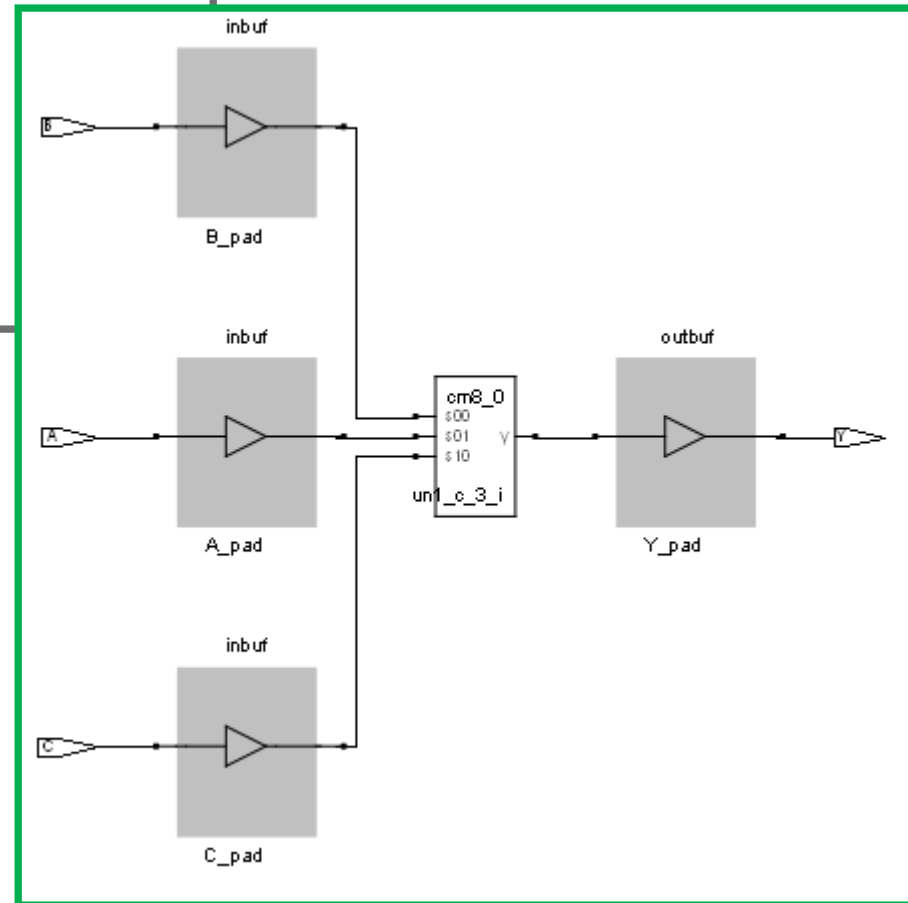

Conditional Signal Assignment

Syntax

```
target_signal <=
    <expression> when <boolean_condition> else
    <expression> when <boolean_condition> else
    . . . .
    <expression> when <boolean_condition> [else
        <expression>];
```

A conditional signal assignment describes logic based on unrelated *boolean_conditions*, the *first condition that is true* the value of expression is assigned to the *target_signal*

Conditional Signal Assignment

Main usage

```
dbus <= data    when enable = '1' else 'Z';
```

```
dbus <= data when enable = '1' else (others=>'Z');
```


Conditional Signal Assignment

Example

```
library ieee;
use ieee.std_logic_1164.all;


entity my_tri is
  generic(bus_ancho: integer := 4);
  port(
    data:   in std_logic_vector(bus_ancho-1 downto 0);
    enable: in std_logic;
    dbus :  out std_logic_vector(bus_ancho-1 downto 0)
  );
end my_tri;

 architecture behave of my_tri is
begin
  y <= a when en = '1' else (others => 'z') ;
end behave;
```



process Statement

A process is a concurrent statement, but it is the primary mode of introducing sequential statements

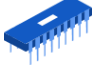
 A process, with all the sequential statements, is a *simple concurrent statement*.

 Multiple *processes* can be executed in parallel

 From the traditional programming view, a *process* is an *infinite loop*


Process Statement

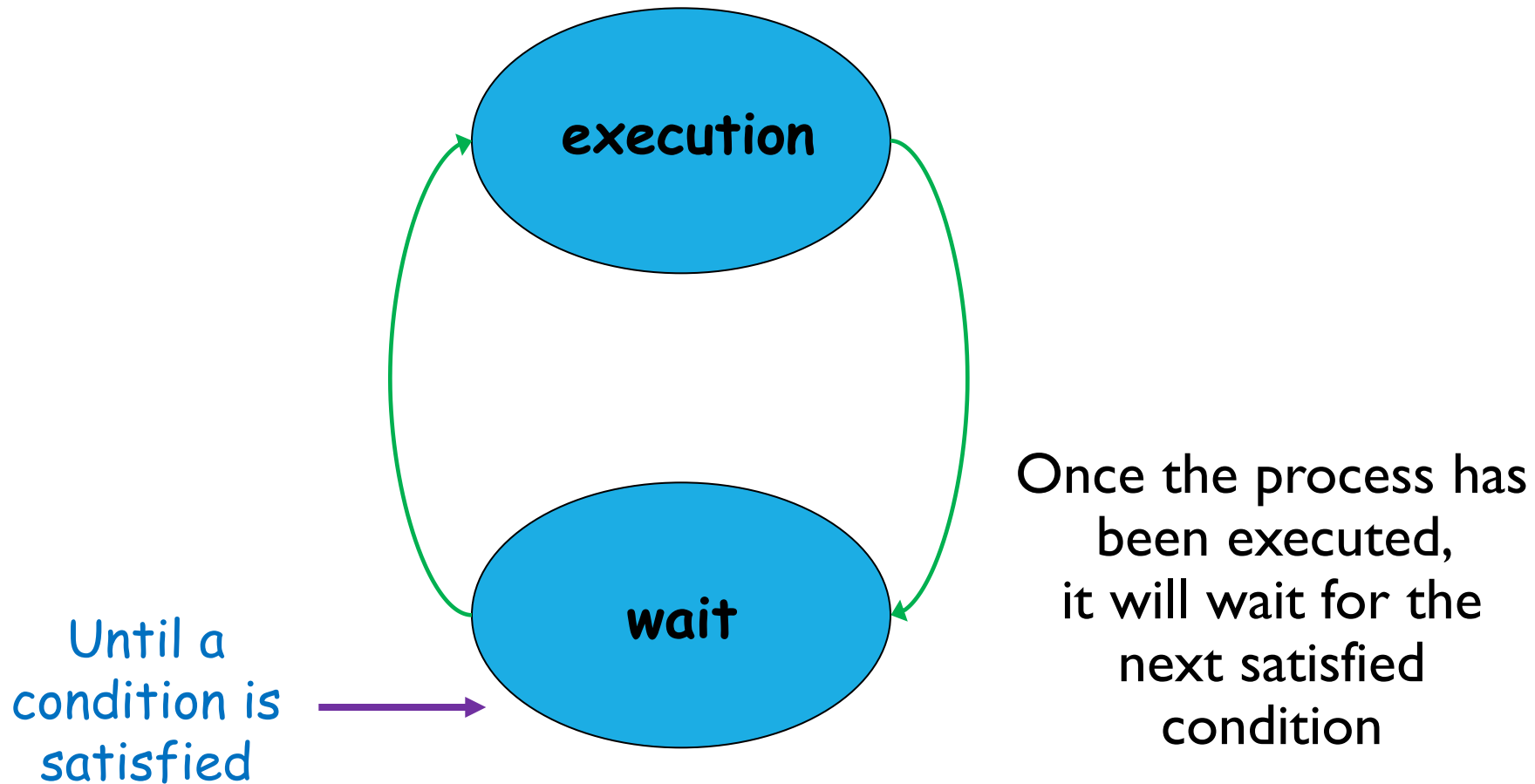A process has two states: *execution* and *wait*



process Statement Syntax

```
[process_label:] process [(sensitivity_list)] [is]  
[process_data_object_declarations]  
begin  
    variable_assignment_statement  
    signal_assignment_statement  
    wait_statement  
    if_statement  
    case_statement  
    loop_statement  
    null_statement  
    exit_statement  
    next_statement  
    assertion_statement  
    report_statement  
    procedure_call_statement  
    [wait on sensitivity_list]  
end process [process_label];
```

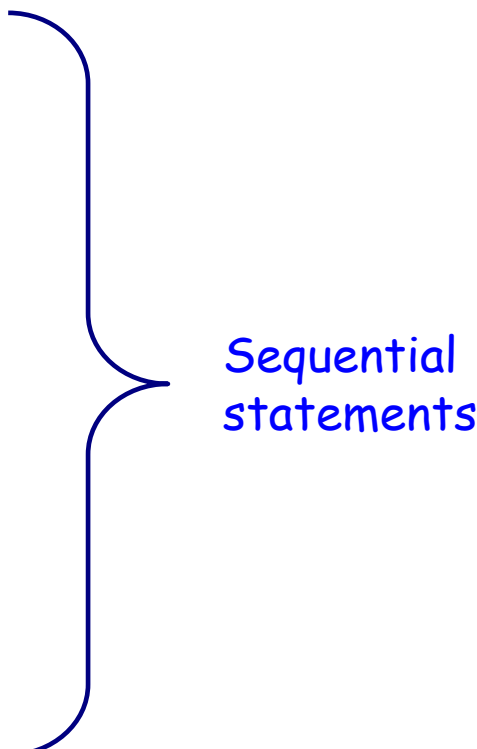

Sequential
statements

Parts of the process statement

sensitivity_list

- List of all the signals that are able *to trigger the process*
- Simulation tools monitor events on these signals
- Any event on any signal in the sensitivity list will cause to execute the process at least once

■ *declarations*

- Declarative part. Types, functions, procedures and variables can be declared in this part
- Each declaration is local to the process

✚ *sequential_statements*

- ✚ All the sequential statements that will be executed each time that the process is activated

Signal Behaviour in a process

While a process is running ALL the SIGNALS in the system remain unchanged -> Signals are in effect **CONSTANTS** during process execution, EVEN after a signal assignment, the signal will NOT take a new value

SIGNALS are updated at the end of a process


Signals are a mean of communication between processes -> VHDL can be seen as a network of processes intercommunicating via signals

Variable Behavior in a process

While a process is running ALL the Variables in the system are updates **IMMEDIATELY** by a variable assignment statement

process - Combinational/Sequential

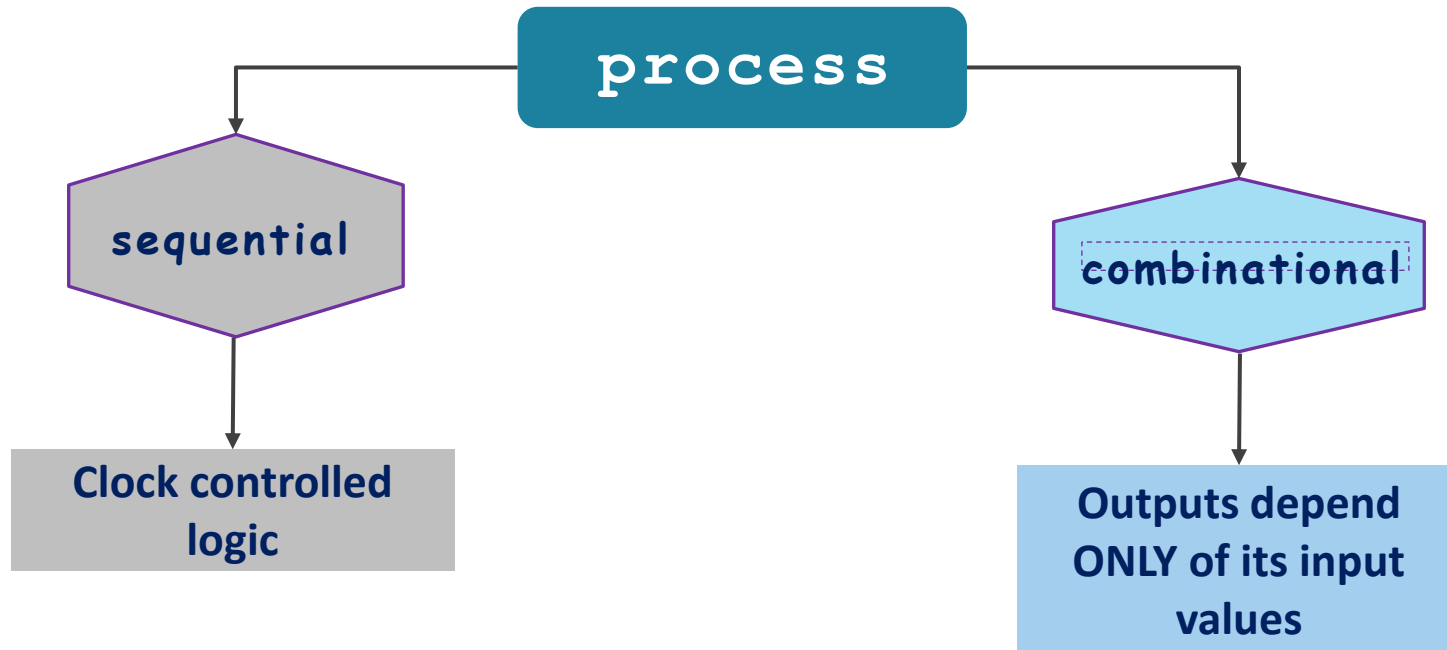When using processes, a key distinction is made between those that model sequential logic (controlled by a clock) and those that model combinational logic.



process - Combinational/Sequential



A clock-controlled process, also known as a **sequential process**, describes logic whose outputs change only at specific edges of a clock signal (e.g., rising edge or falling edge). This type of process is used to model sequential elements like flip-flops, registers, counters, and state machines, which have memory and store state.

Key Characteristics:

- It is **ONLY** sensitive to the **clock signal** and often a **reset signal**.
- It typically contains an IF statement that checks for a clock edge (e.g., `rising_edge(clk)` or `falling_edge(clk)`).
- Signal assignments inside the clock edge condition are implemented as some storage element (e.g., flip-flop, memory).

process - Combinational/Sequential



A **combinational process** describes logic whose outputs depend *only* on the current values of its inputs. There is no memory or state involved; if the inputs change, the outputs change (after a propagation delay).

Key Characteristics:

- Its sensitivity list must include **all input signals** that affect the process's outputs. If an input changes, the process must re-evaluate to produce the correct output.
- It **does not** contain clock edge detection (`rising_edge` or `falling_edge`).
- Signal assignments are typically **concurrent updates**, as outputs are directly derived from inputs.
- There should be **no unassigned** signals in all possible execution paths within the process; **otherwise, the VHDL synthesizer will infer latches, which is generally undesirable for combinational logic**. All outputs must be assigned a value for every possible combination of inputs.

Sequential *process* example

```
library ieee;
use ieee.std_logic_1164.all;

entity D_FF is
    port (
        clk    : in  std_logic;
        reset  : in  std_logic; -- Asynchronous reset input
        D      : in  std_logic; -- Data input
        Q      : out std_logic  -- Data output
    );
end entity D_FF;

architecture Behavioral of D_FF is
begin
    -- This process models the behavior of a D-Flip-Flop.
    -- It is a clock-controlled (sequential) process because its state
    -- (the value of Q) only changes on the rising edge of the clock (clk)
    -- or asynchronously when reset is high.
    process (clk, reset) -- Sensitivity list: Process re-evaluates if clk or reset
    begin
        -- Asynchronous reset: If reset is '1', Q is immediately set to '0'.
        -- This takes precedence over the clock edge.
        if reset = '1' then
            Q <= '0';
        -- Synchronous operation: If reset is '0', check for a rising clock edge.
        elsif rising_edge(clk) then
            -- On the rising edge of the clock, the value of D is sampled and
            -- assigned to Q. This assignment happens after a delta delay.
            Q <= D;
        end if;
    end process;
end architecture Behavioral;
```

Description:

- The **process (clk, reset)** line defines the sensitivity list. This means the process will execute whenever there's an event (a change in value) on either the clk or reset signal.
- The **if reset = '1'** condition handles the asynchronous reset. If reset is active (high), Q is immediately set to '0'. This happens independently of the clock.
- The **elsif rising_edge(clk)** condition means that if the reset is not active, the statements within this block will only execute when the clk signal transitions from '0' to '1'.
- Q <= D;** inside the **rising_edge** block indicates that the output Q will take on the value of the input D at that specific clock edge. This correctly describes the memory element of a D-flip-flop.

Combinational *process* example

```
library ieee;
use ieee.std_logic_1164.all;


entity MUX_2_to_1 is
    port (
        A      : in  std_logic; -- First data input
        B      : in  std_logic; -- Second data input
        Sel    : in  std_logic; -- Select signal (0 for A, 1 for B)
        Y      : out std_logic  -- Output
    );
end entity MUX_2_to_1;

architecture Behavioral of MUX_2_to_1 is
begin
    -- This process models the behavior of a 2-to-1 Multiplexer.
    -- It is a combinational process because its output (Y) depends solely
    -- on the current values of its inputs (A, B, Sel).
    process (A, B, Sel) -- Sensitivity list: Includes ALL inputs that determine Y
    begin
        -- If Sel is '0', output Y takes the value of A.
        if Sel = '0' then
            Y <= A;
        -- If Sel is '1', output Y takes the value of B.
        else -- Sel = '1'
            Y <= B;
        end if;
    end process;
end architecture Behavioral;
```

Description

- The **process** (A, B, Sel) line defines the sensitivity list. The process will execute whenever there's an event on A, B, or Sel. This ensures that Y is always updated whenever any of its inputs change.
- There are no clock edge or reset conditions; the logic simply evaluates based on current inputs.
- The **if Sel = '0'** and **else** branches ensure that the output Y is **always** assigned a value, regardless of the **Sel** input. This is critical to avoid inferring a latch.

if Statement - 3 to 8 Decoder

 

```
entity if_decoder_example is
  port (
    a: in  std_logic_vector(2 downto 0);
    z: out std_logic_vector(7 downto 0);
  end entity;

architecture rtl of if_decoder_example is
begin
  if_dec_ex: process (a)
  begin
    if (a = "000") then
      z <= "00000001";
    elsif (a = "001") then
      z <= "00000010";
      . . .
    else
      z <= (others => '0');
    end if;
  end process if_dec_ex;
end rtl;
```

if Statement

Most common mistakes for describing combinatorial logic

```
entity example3 is
    port ( a, b, c: in  std_logic;
           z, y: out std_logic);
end example3;

architecture beh of example3 is
begin
    process (a, b)
    begin
        if c='1' then
            z <= a;

        else
            y <= b;

        end if;
    end process;
end beh;
```

case Statement

```
[case label:] case <selector_expression> is
  when <choice_1> =>
    <sequential_statements> -- branch #1
  when <choice_2> =>
    <sequential_statements> -- branch #2
    . . .
  [when <choice_n to/downto choice_m > =>
    <sequential_statements>] -- branch #n
    . . . .
  [when <choice_x | choice_y | . . .> =>
    <sequential_statements>] -- branch #...
  [when others =>
    <sequential_statements>] -- last branch
end case [case_label];
```

case Statement

```
entity mux4 is
  port ( sel          : in std_ulogic_vector(1 downto 0);
        d0, d1, d2, d3 : in std_ulogic;
        z             : out std_ulogic );
end entity mux4;

architecture demo of mux4 is
begin
  out_select : process (sel, d0, d1, d2, d3) is
  begin
    case sel is
      when "00" =>
        z <= d0;
      when "01" =>
        z <= d1;
      when "10" =>
        z <= d2;
      when others =>
        z <= d3;
    end case;
  end process out_select;
end architecture demo;
```

case Statement with *if* Statement

```
mux_mem_bus :process
  (cont_out, I_P0, I_P1, I_A0, I_A1, Q_P0, Q_P1, Q_A0, Q_A1)
begin
  mux_out <= I_P0;
  case (cont_out) is
    when "00" =>
      if (iq_bus = '0') then
        mux_out <= I_P0; -- I_A0;
      else
        mux_out <= Q_P0; -- Q_A0;
      end if;
    when "01" =>
      if (iq_bus = '0') then
        mux_out <= I_A0; -- I_P0;
      else
        mux_out <= Q_A0; -- Q_P0;
      end if;
    . . . . .
```

for loop-end loop Statement


```
[loop_label]: for <identifier> in discrete_range loop  
    <sequential_statements>  
end loop [loop_label];
```

<identifier>

- The identifier is called loop parameter, and for each iteration of the loop, it takes on successive values of the discrete range, starting from the left element
- It is not necessary to declare the identifier
- By default the type is integer
- Only exists when the loop is executing

for-loop Statement
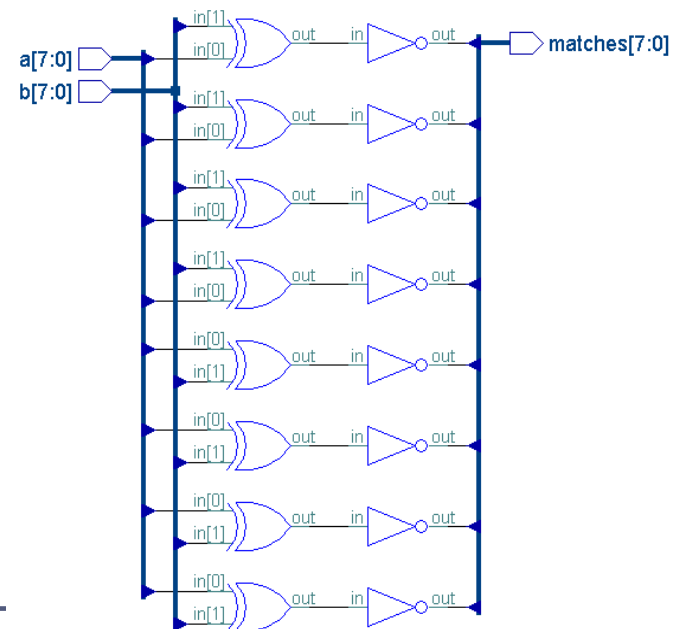
```
entity match_bit is
    port ( a, b      : in  std_logic_vector(7 downto 0);
          matches: out std_logic_vector(7 downto 0));
end entity;
architecture behavioral of match_bit is
begin
    process (a, b)
    begin
        for i in a'range loop
            matches(i) <= not (a(i) xor b(i));
        end loop;
    end process;
end behavioral;
```



for-loop Statement

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity count_??? is
    port (vec: in std_logic_vector(15 downto 0);
          count: out std_logic_vector(3 downto 0))
end count_ones;

architecture behavior of count_???? is
begin
    cnt_ones_proc: process (vec)
        variable result: unsigned(3 downto 0);
    begin
        result := (others => '0');
        for i in vec'range loop
            if vec(i) = '1' then
                result := result + 1;
            end if;
        end loop;

        count <= std_logic_vector(result);
    end process cnt_ones_proc;
end behavior;
```

The Role of Componentes in VHDL

Hierarchy in VHDL



Divide & Conquer



Each subcomponent can be designed and completely tested



Create library of components (technology independent if possible)



Third-party available components



Code for reuse

Component Instantiation

Component instantiation is a concurrent statement that is used to connect a component I/Os to the internal signals or to the I/Os of the higher level component

```
component_label: entity work.component_name  
    [generic map (generic_association_list)]  
    port map (port_association_list);
```

- `component_label` it labels the instance by giving a name to the instanced
- `generic_association_list` assign new values to the default generic values (given in the entity declaration)
- `port_association_list` associate the signals in the top entity/architecture with the ports of the component. There are two ways of specifying the port map:

 *Positional Association / Name Association*

Association By Name

In named association, an association list is of the form

(formal1=>actual1, formal2=>actual2, ... formaln=>actualn);

Component I/O Port

Connected to

Internal Signal or Entity
I/O Port

```
-- component declaration
component NAND2
    port (a, b: in std_logic;
          z: out std_logic);
end component;


-- component instantiation
U1: entity work.NAND2 port map (a=>S1, z=>S3, b=>S2);
-- S1 associated with a, S2 with b and S3 with z
```


Component Instantiation Example

```
library ieee;
use ieee.std_logic_1164.all;

entity glue_logic is
    port (A, CK, MR, DIN: in std_logic;
          RDY, CTRLA      : out std_logic);
end glue_logic ;


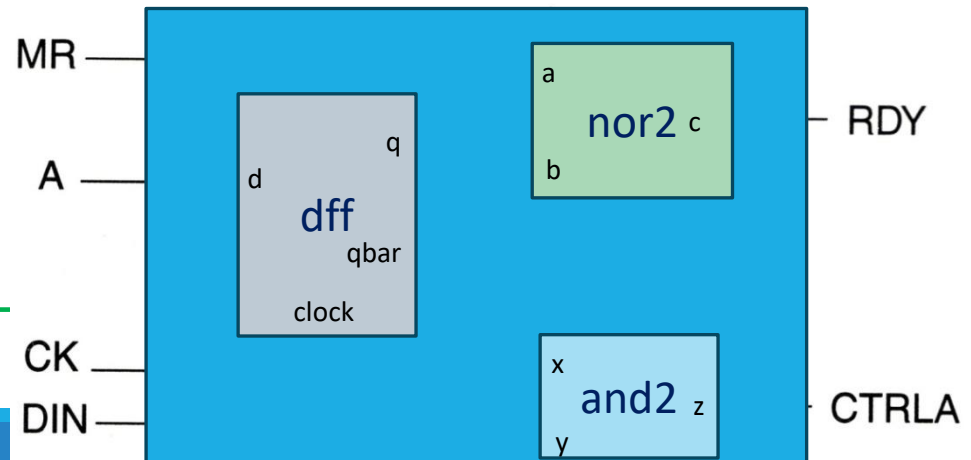
architecture STRUCT of glue_logic is
    signal S1, S2: std_logic;
begin
    D1: entity work.DFF port map (D=>A, CLOCK=>CK, Q=>S1, QBAR=>S2);
    A1: entity work.AND2 port map (X=>S2, Y=>DIN, Z=>CTRLA);
    N1: entity work.NOR2 port map
        (a =>S1,
         b =>MR,
         c =>RDY);
end STRUCT;
```



 

VHDL for Sequential Logic Design


D Flip-Flop - VHDL

  

```
entity ff_d_example is
    port(
        d      : in  std_logic;
        clk    : in  std_logic;
        q      : out std_logic);
end entity;
```


```
architecture rtl of ff_d_example is
begin
    ff_d: process (clk)
    begin
        if (rising_edge(clk)) then
            q <= d;
        end if;
    end process ff_d;
end rtl;
```

D-ff with asynchronous reset

 



```
entity ff_example is
    port(
        d, clk, rst_n: in std_logic;
        q: out std_logic);
end entity;
architecture rtl of ff_example is
begin
    ff_d_rst: process (clk, rst_n)
        -- Empty process body
    end process ff_d_rst;
end rtl;
```


D-ff with synchronous reset

 

```
entity ff_d_srst is
    port(
        d, clk, rst: in std_logic;
        q: out std_logic);
end entity;
architecture rtl of ff_d_srst is
begin
    ff_d_srst: process (clk)
begin
    -- Empty process body
end process ff_d_srst;
end rtl;
```


D-ff with async. reset and enable

  

```
entity ff_d_en_rst is
  port(
    d, clk, en, rst: in std_logic;
    q: out std_logic);
end entity;
```

```
end entity;
architecture rtl of ff_d_en_rst is
begin
  ff_d_en_rst: process (clk, rst)
  begin
    -- Implementation of the D flip-flop logic
  end process ff_d_en_rst;
end rtl;
```

Registers

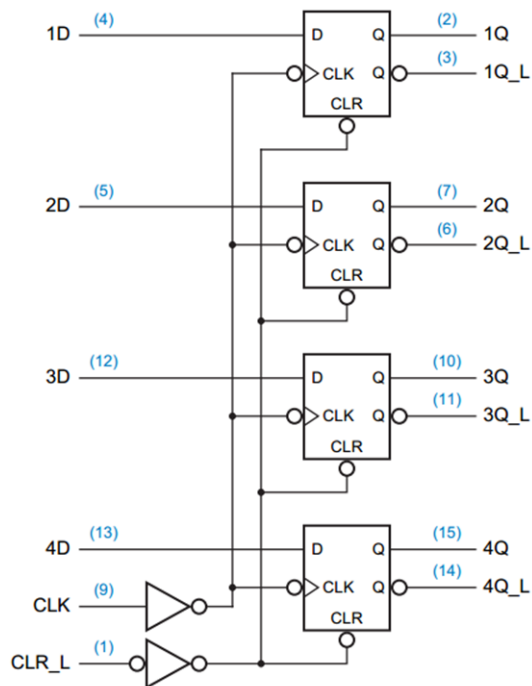

```
entity reg_d_rst is
  generic(width:= 4);
  port(
    d      : in  std_logic_vector(width-1 downto 0);
    clk, clr_l: in  std_logic;
    q      : out std_logic_vector(width-1 downto 0));
end entity;

architecture rtl of reg_d_rst is
begin
  reg_d_arst: process (clk,clr_l)
  begin
    if (clr_l = '1') then
      q <= (others => '0');      -- q <= "0000"
    elsif(rising_edge (clk)) then
      q <= d;
    end if;
  end process reg_d_arst;
end rtl;
```

What is the implementation result??

```
library ieee;
use ieee.std_logic_1164.all;
entity shift_pi_po_x8 is
    port(
        clk, clr    : in  std_logic;
        serial_in   : in  std_logic;
        data_out    : out std_logic_vector(7 downto 0);
    end shift_pi_po_x8;
architecture behav of shift_si_so_x4 is
    signal data_out_temp: std_logic_vector(3 downto 0);
begin
    shift_proc: process(clk, clr)
    begin
        if (clr = '0') then
            data_out_temp <= others(=>'0');
        elsif (rising_edge(clk)) then
            data_out_temp <= serial_in & data_out_temp(3 downto 1);
        end if;
    end process shift_proc;
    data_out <= data_out_temp;
end behave;
```

Shift Register : 74x194

```
architecture behav of shift_74x194 is
    signal temp_q: std_logic_vector(3 downto 0);
    signal ctrl  : std_logic_vector(1 downto 0);
begin
    ctrl <= s0 & s1;
    shift_proc: process(clk, clr_n)
    begin
        if (clr_n = '0') then
            temp_q <= (others => '0');
        elsif (rising_edge(clk)) then
            -- 
        end if;
    end process;
    q <= temp_q;
end behav;
```

Function	Inputs		Next state			
	S1	S0	QA*	QB*	QC*	QD*
Hold	0	0	QA	QB	QC	QD
Shift right	0	1	RIN	QA	QB	QC
Shift left	1	0	QB	QC	QD	LIN
Load	1	1	A	B	C	D

Counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity counter_nbits is
  generic(cnt_w: natural:= 4)
  port (
    -- clock & reset inputs
    clk      : in std_logic;
    rst      : in std_logic;
    -- outputs
    count     : out std_logic_vector(
0));
end counter_nbits;
```

```
architecture rtl of counter_nbits is
  -- signal declarations
  signal count_i: unsigned(cnt_w-1 downto 0);
begin
  count_proc: process(clk, rst)
  begin
    if(rst='0') then
      count_i <= (others => '0');
    elsif(rising_edge(clk)) then
      count_i <= count_i + 1;
    endif;
  end process count_proc;
  count <= std_logic_vector(count_i);
end architecture rtl;
```

Up/Down Counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity counter_ud is
  generic(cnt_w: natural:= 4)
  port (
    -- clock & reset inputs
    clk      : in std_logic;
    rst      : in std_logic;
    -- control input signals
    up_dw    : in std_logic;
    -- outputs
    count     : out std_logic_vector(cnt_w-1 downto 0));
end counter_ud;
```

```
architecture rtl of counter_ud is
  -- signal declarations
  signal count_i: unsigned(cnt_w-1 downto 0);

begin
  count_proc: process(clk, rst)
  begin
    if(rst='0') then
      count_i <= (others => '0');
    elsif(rising_edge(clk)) then
      if(up_dw = '1') then -- up
        count_i <= count_i + 1;
      else -- down
        count_i <= count_i - 1;
      end if;
    end if;
  end process count_proc;

  count <= std_logic_vector(count_i);

end architecture rtl;
```

Up/Down Counter - Integers

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;


entity counter_ud_i is
  generic(cnt_w: natural := 4)
  port (
    -- clock & reset inputs
    clk      : in std_logic;
    rst_n    : in std_logic;
    -- outputs
    count    : out std_logic_vector(cnt_w-1 to 0));
end counter_ud_i;
```

?


```
architecture rtl of counter_ud_i is
begin
  count_proc: process(clk, rst)
    variable count_i: integer range 0 to 255;
  begin
    if(rst_n = '0') then
      count_i := 0;
    elsif(rising_edge(clk)) then
      if(count_i = 255) then
        count_i := 0;
      else
        count_i := count_i + 1;
      end if;
    end if;
  end process count_proc;

  count <= std_logic_vector(to_unsigned(count_i, 8));
end architecture rtl;
```




Asynchronous Inputs

 

Synchronizer

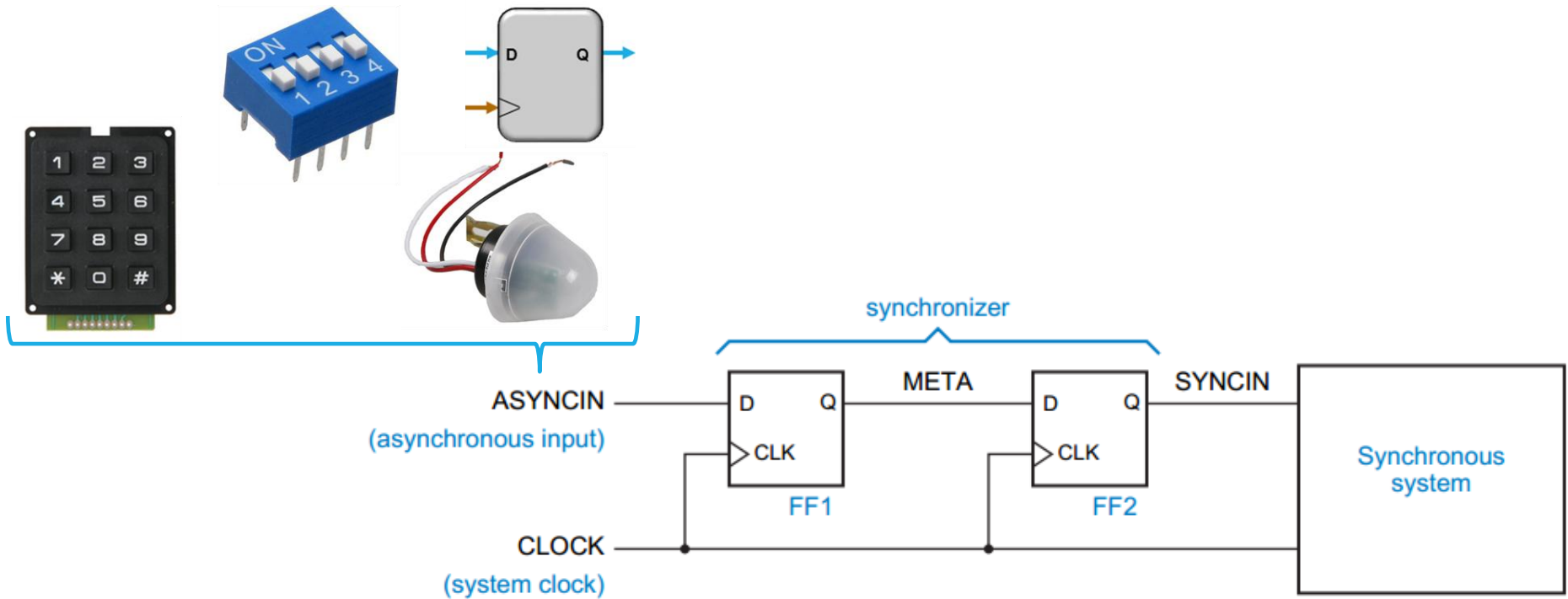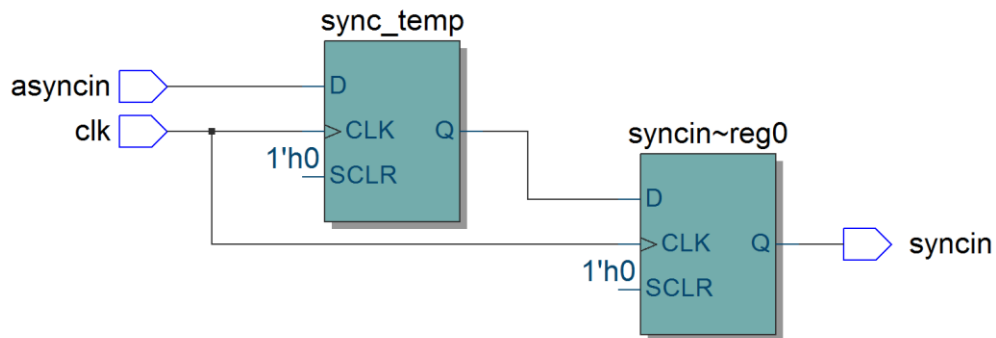 

Synchronizer




```

library ieee;
use ieee.std_logic_1164.all;
entity synchronizer is
    port(
        clk      : in  std_logic;
        asyncin   : in  std_logic;
        syncin    : out std_logic);
end synchronizer;


architecture behave of synchronizer is
    signal sync_temp: std_logic;
begin
    sync_proc: process(clk)
    begin
        if (rising_edge(clk)) then
            sync_temp <= asyncin;
            syncin    <= sync_temp;
        end if;
    end process;
end behave;

```

 


FINITE STATE MACHINES (FSM) DESCRIPTION IN VHDL


State Machine General Scheme 1

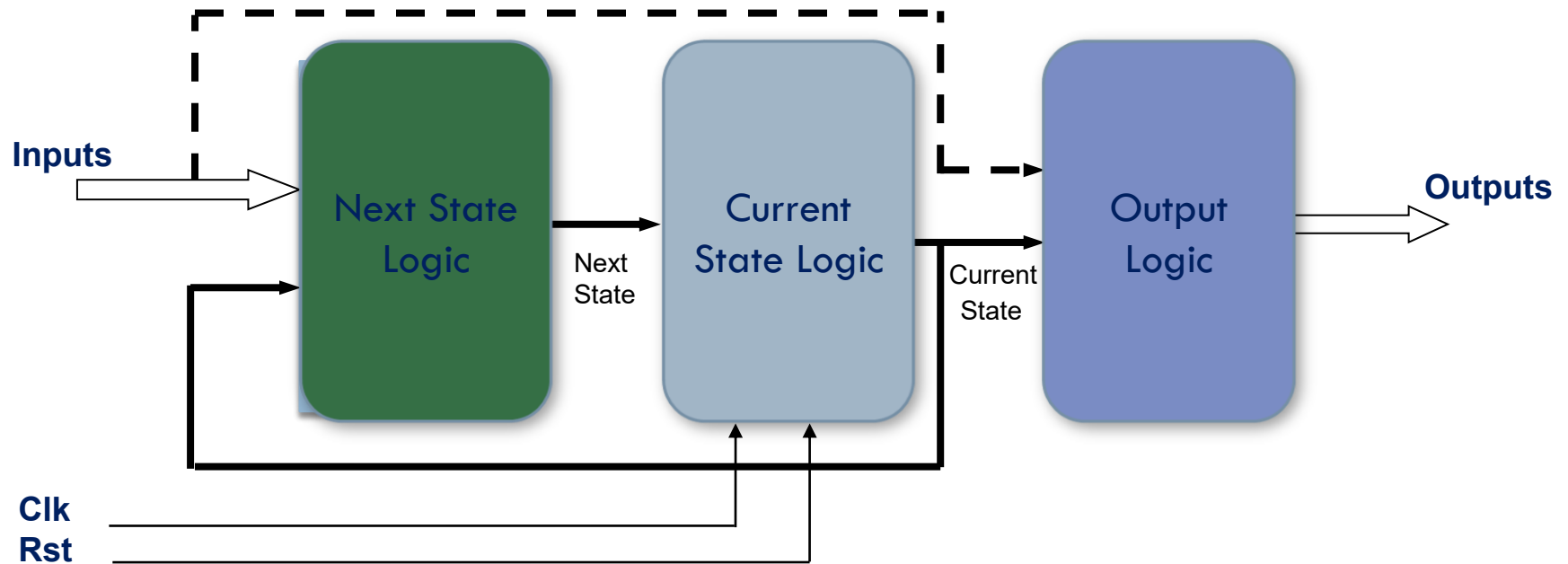

State Machine General Scheme 2

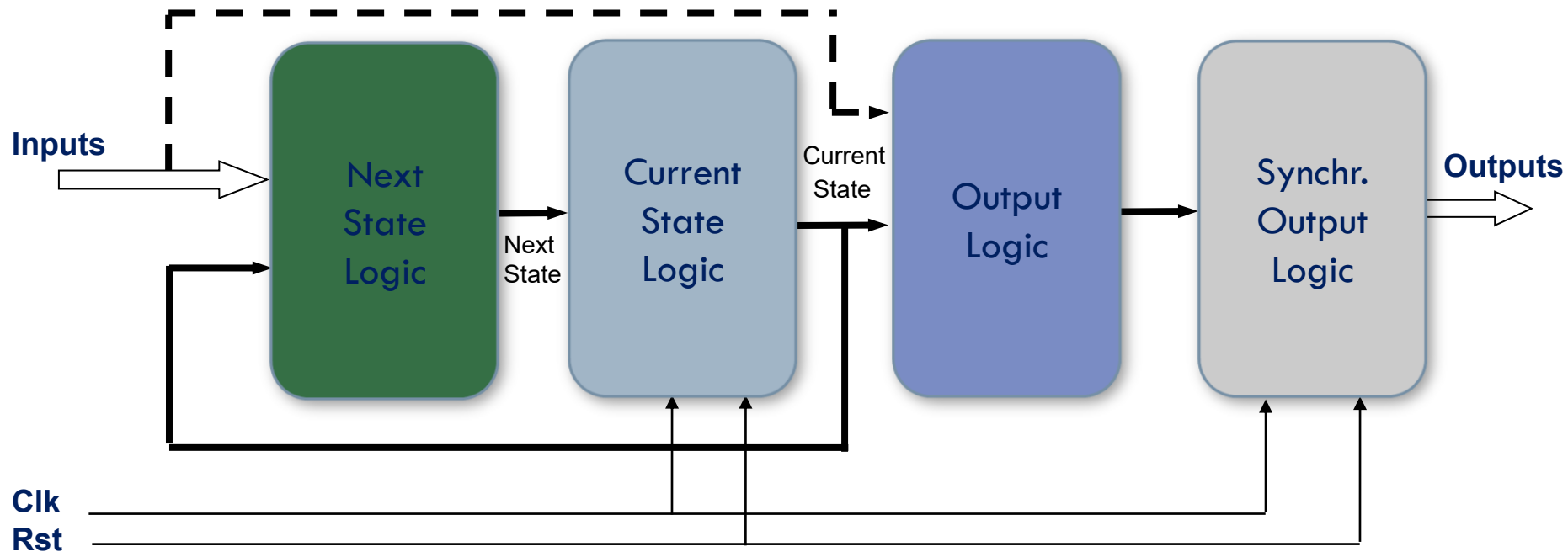

FSM VHDL General Design Flow

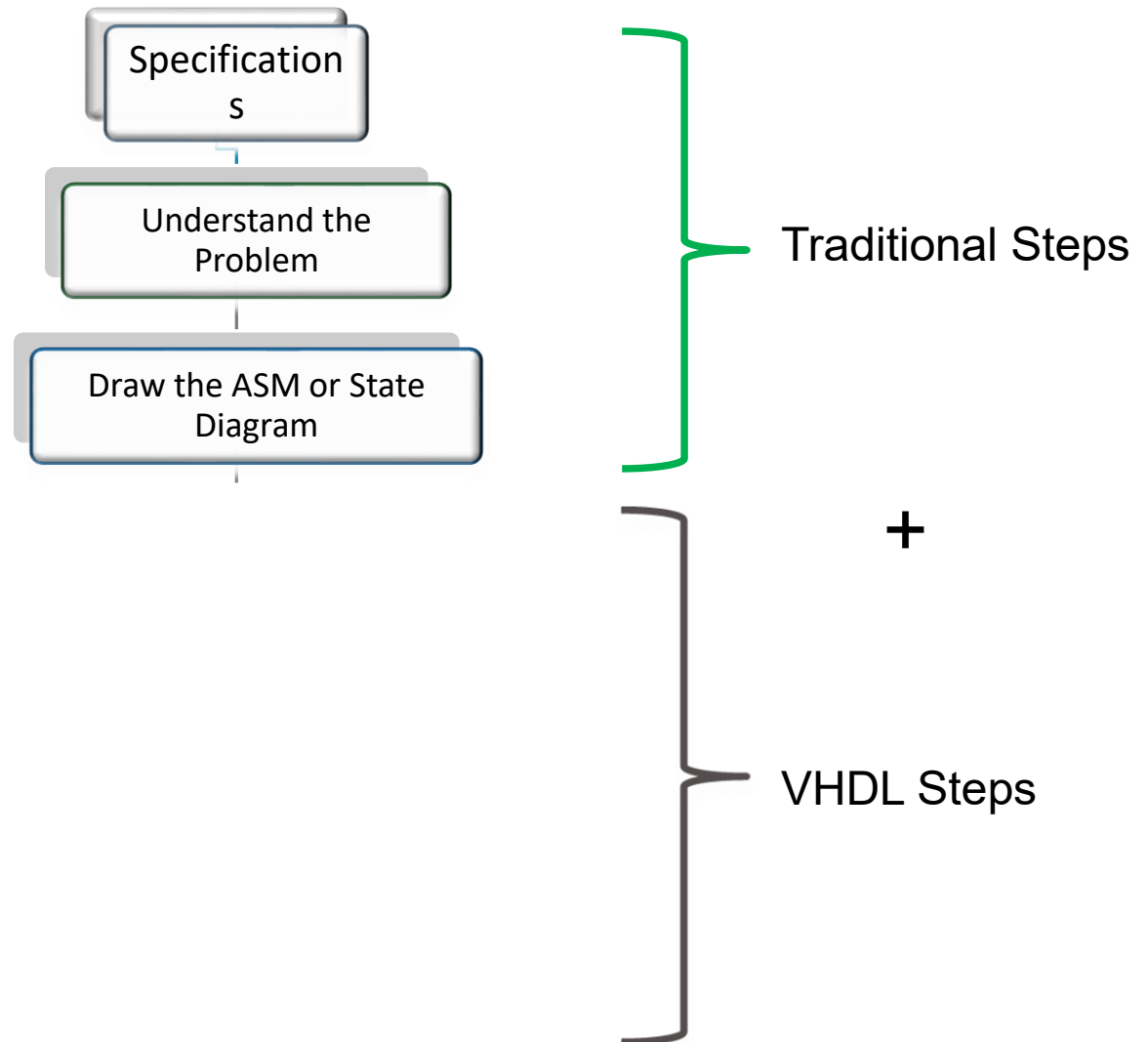

FSM Enumerated Type Declaration

Declare an enumerated data type with values (names) that symbolize the states of the state machine

```
-- declare the states of the state-machine  
-- as enumerated type  
type FSM_States is (IDLE, START, STOP_1BIT, PARITY, SHIFT) ;
```

Symbolic State
Names



Declare the signals for the next state and current state of the state machine as signal of the enumerated data type already defined for the state machine

```
-- declare signals of FSM_States type  
signal current_state, next_state: FSM_States;
```

The only values that current_state and next_state can hold are:
IDLE, START, STOP_1BIT, PARITY, SHIFT



FSM Encoding Techniques

State Assignment

- During synthesis each *symbolic state name* has to be mapped to a *unique binary representation*

```
type FSM_States is (IDLE, START, STOP_1BIT, PARITY, SHIFT);  
signal current_state, next_state: FSM_States;
```

- A good state assignment can *reduce* the circuit *size* and *increase* the *clock rate* (by reducing propagation delays)
- The hardware needed for the implementation of the next state logic and the output logic is *directly related* to the state assignment selected

FSM Encoding Schemes

An FSM with n symbolic states requires at least $\lceil \log_2 n \rceil$ bits to encode all the possible symbolic values

Commonly used state assignment schemes:


- **Binary:** assign states according to a binary sequence
- **Gray:** use the Gray code sequence for assigning states
- **One-hot:** assigns one 'hot' bit for each state
- **Almost one-hot:** similar to one-hot but add the all zeros code (initial state)

FSM Encoding Schemes

	Binary	Gray	One-Hot	Almost One-hot
idle	000	000	00001	0000
start	001	001	00010	0001
stop_1 bit	010	011	00100	0010
parity	011	010	01000	0100
shift	100	110	10000	1000

Encoding Schemes in VHDL

 During *synthesis* each *symbolic state name* has to be mapped to a *unique binary representation*




Results for Different Encoding Schemes

19 states, state machine

	One-hot safe	One-hot	Gray	Gray-Safe	Binary	Johnson
Total combinational functions	556	523	569	566	561	573
Dedicated logic registers	215	215	201	201	201	206
Max. frq.	187.3	175.22	186.39	180.6	197.63	186.22

State Machine VHDL Coding - Example

 Describe in VHDL an FSM that generate a pulse per each rising edge of the input.



FSM VHDL Coding

Comb. Next State

```

nxt_pr: process (state, in_2det)
begin
  case state is
    when wait_inp =>
      if (in_2det='0') then
        next_state <= wait_inp;
      else
        next_state <= edge_det;
      end if;
    when edge_det =>
      if (in_2det='0') then
        next_state <= wait_inp;
      else
        next_state <= wait_fall;
      end if;
    when wait_fall =>
      if (in_2det='0') then
        next_state <= wait_inp;
      else
        next_state <= wait_fall;
      end if;
    when others =>
      next_state <= wait_inp;
    end case;
  end process nxt_pr;
  
```

Seq. Present State


```

cst_pr: process (clk, rst)
begin
  if (rst = '1') then
    state <= wait_inp;
  elsif (rising_edge(clk)) then
    state <= next_state;
  end if;
end process cst_pr;
  
```

Seq. Output

```

 out_pr: process (clk, rst)
begin
  if (rst = '1') then
    pulse <= '0';
  elsif (rising_edge(clk)) then
    case state is
      when wait_inp =>
        pulse <= '0';
      when edge_det =>
        pulse <= '1';
      when wait_fall =>
        pulse <= '0';
      when others =>
        pulse <= '-';
    end case;
  end if;
end process out_pr;
  
```



in_2det

state

pulse

Clk
Rst

State Machine VHDL Coding (complete)

-- VHDL code example for an FSM

library ieee;

use ieee.std_logic_1164.all;

entity fsm_edge_detect **is**

port(

in_2det : **in** std_logic;

clk : **in** std_logic;

rst : **in** std_logic;

pulse : **out** std_logic);

end entity fsm_edge_detect;

architecture beh **of** my_fsm **is**

-- fsm enumerated type declaration

type fsm_states **is** (wait_inp, edge_det, wait_fall);

-- fsm signal declarations

signal next_state, state: fsm_states;

begin

-- current state logic

cst_pr: **process** (clk, rst)

begin

if(rst = '1') **then**

state <= wait_inp;

elsif (rising_edge(clk)) **then**

state <= next_state;

end if;

end process cst_pr;

-- next state logic

nxt_pr: **process** (state, in_2det)

begin

case state **is**

when wait_inp =>

if(in_2det='0') **then**

next_state <= wait_inp;

else

next_state <= edge_det;

end if;

when edge_det =>

if

next_state <= .. ;

....

when others =>

....

end case;

end process nxt_pr;

-- output logic

out_pr: **process** (clk, rst)

begin

if(rst = '1') **then**

pulse <= '0';

elsif (rising_edge(clk)) **then**

case state **is**

when wait_inp => pulse <= '0';

...



when others => pulse <= '-';

end case;

end process out_pr;

end architecture beh;

FSM Simulation

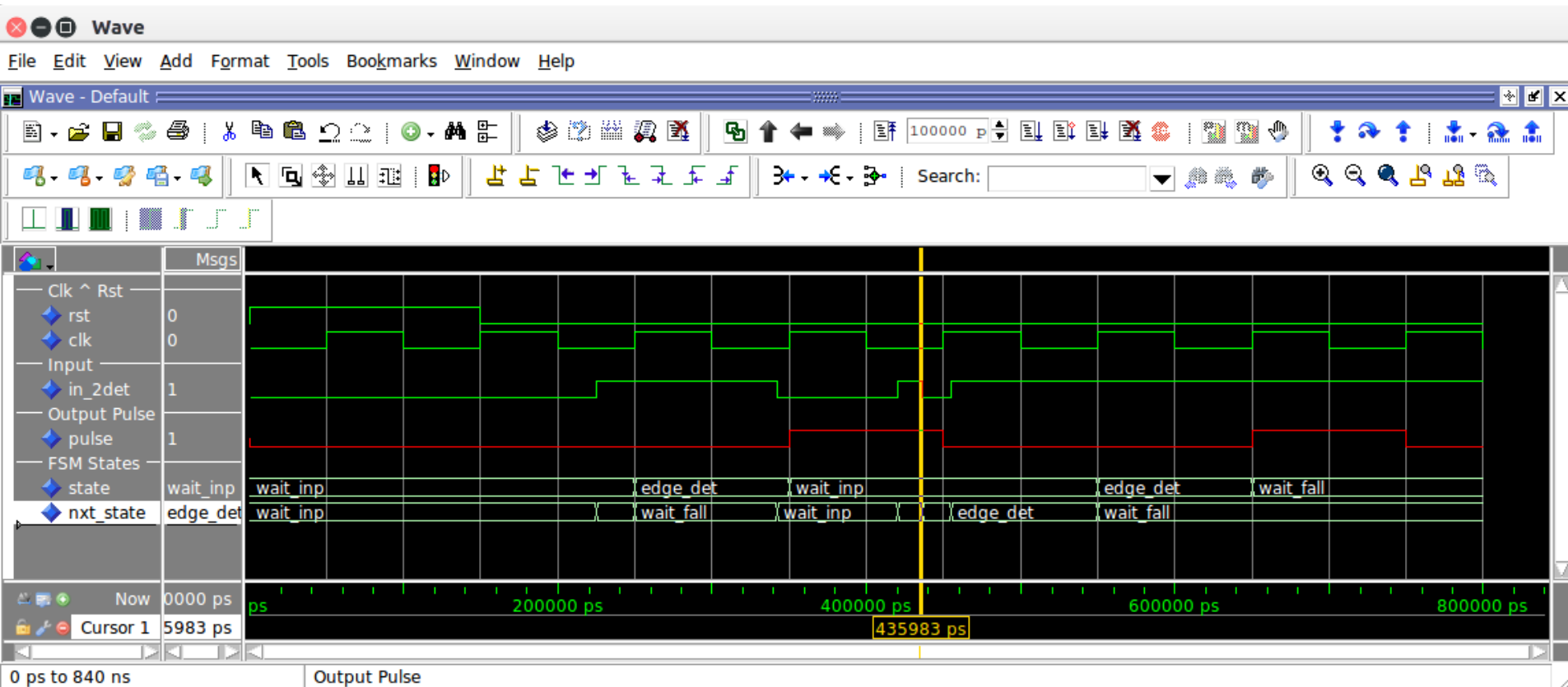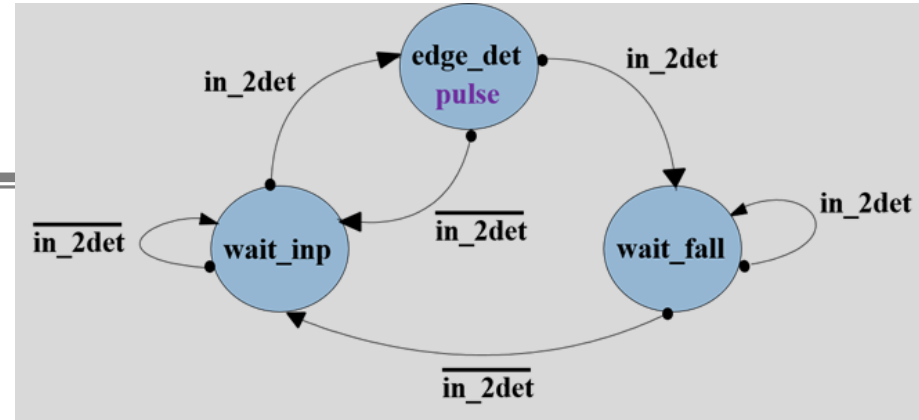

Another Ex.: Memory Controller FSM


Let's try to obtain an state diagram of a hypothetical memory controller FSM that has the following specifications:

The controller is between a processor and a memory chip, interpreting commands from the processor and then generating a control sequence accordingly. The commands, **mem**, **rw** and **burst**, from the processor constitute *the input signals* of the FSM. The **mem** signal is asserted to high when a memory access is required. The **rdwr** signal indicates the type of memory access, and its value can be either '1' or '0', for memory read and memory write respectively. The **burst** signal is for a special mode of a memory read operation. If it is asserted, four consecutive read operations will be performed. The memory chip has two control signals, **oe** (for output enable) and **we** (for write enable), which need to be asserted during the memory read and memory write respectively. The two output signals of the FSM, **oe** and **we**, are connected to the memory chip's control signals. For comparison purpose, let also add an artificial Mealy output signal, **we_mealy**, to the state diagram. Initially, the FSM is in the **idle** state, waiting for the **mem** command from the processor. Once **mem** is asserted, the FSM examines the value of **rdwr** and moves to either the **read1** or the **write** state. The input conditions can be formalized to logic expressions, as shown below:


- **mem'** : represents that *no* memory operation is required ($\text{mem} = '0'$)
- **mem.rdwr**: represents that a memory *read* operation is required ($\text{mem} = \text{rdwr} = '1'$).
- **mem.rdwr'**: represents that a memory *write* operation is required ($\text{mem} = '1'; \text{rdwr} = '0'$)

Based on an example from the "RTL Hardware Design Using VHDL" book, By Pong Chu

Memory Controller FSM

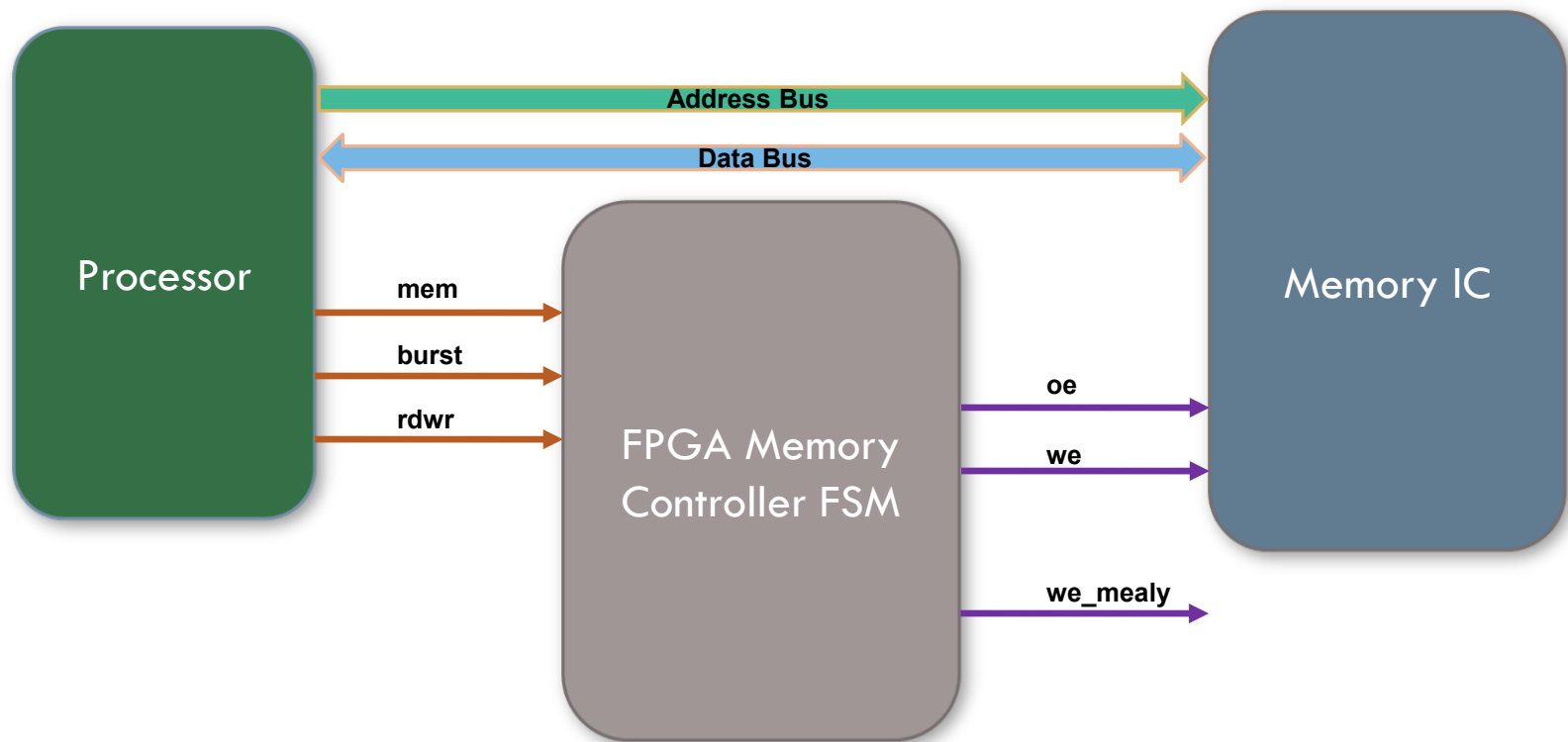

Memory Controller FSM

 

Memory Controller FSM - VHDL Code

```
library ieee ;
use ieee.std_logic_1164.all;

entity mem_ctrl is
port (
    clk, reset      : in  std_logic;
    mem, rdwr, burst: in  std_logic;
    oe, we, we_mealy: out std_logic
);
end mem_ctrl ;

architecture mult_seg_arch of mem_ctrl is
    type fsm_states_type is
        (idle, read1, read2, read3, read4, write);
    signal crrnt_state, next_state: fsm_states_type;
begin
```


Memory Controller FSM - VHDL Code

```
-- current state process
cs_pr: process (clk, reset)
begin
    if(reset = '1') then
        crrnt_state <= idle ;
    elsif(rising_edge(clk)) then
        crrnt_state <= next_state;
    end if;
end process cs_pr;
```

Memory Controller FSM - VHDL Code

□ Next state process (1)

 
```
-- next-state logic
nxp:process (currnt_state, mem, rdwr, burst)
begin
  case currnt_state is
    when idle =>
      if mem = '1' then
        if rdwr = '1' then
          next_state <= read1;
        else
          next_state <= write;
        end if;
      else
        next_state <= idle;
      end if;
    when write =>
      next_state <= idle;
```



Memory Controller FSM - VHDL Code


□ Next state process (2)
 
```
when read1 =>
  if (burst = '1') then
    next_state <= read2;
  else
    next_state <= idle;
  end if;
when read2 =>
  next_state <= read3;
when read3 =>
  next_state <= read4;
when read4 =>
  next_state <= idle;
when others =>
  next_state <= idle;
end case;
end process nxp;
```



Memory Controller FSM - VHDL Code

□ Moore outputs process

 


```

-- Moore output logic
moore_pr: process (currnt_state)
begin
    we <= '0'; -- default value
    oe <= '0'; -- default value
    case currnt_state is
        when idle => null;
        when write =>
            we <= '1';
        when read1 =>
            oe <= '1';
        when read2 =>
            oe <= '1';
        when read3 =>
            oe <= '1';
        when read4 =>
            oe <= '1';
        when others => null;
    end case ;
end process moore_pr;
    
```

Memory Controller FSM - VHDL Code


□ Mealy output process

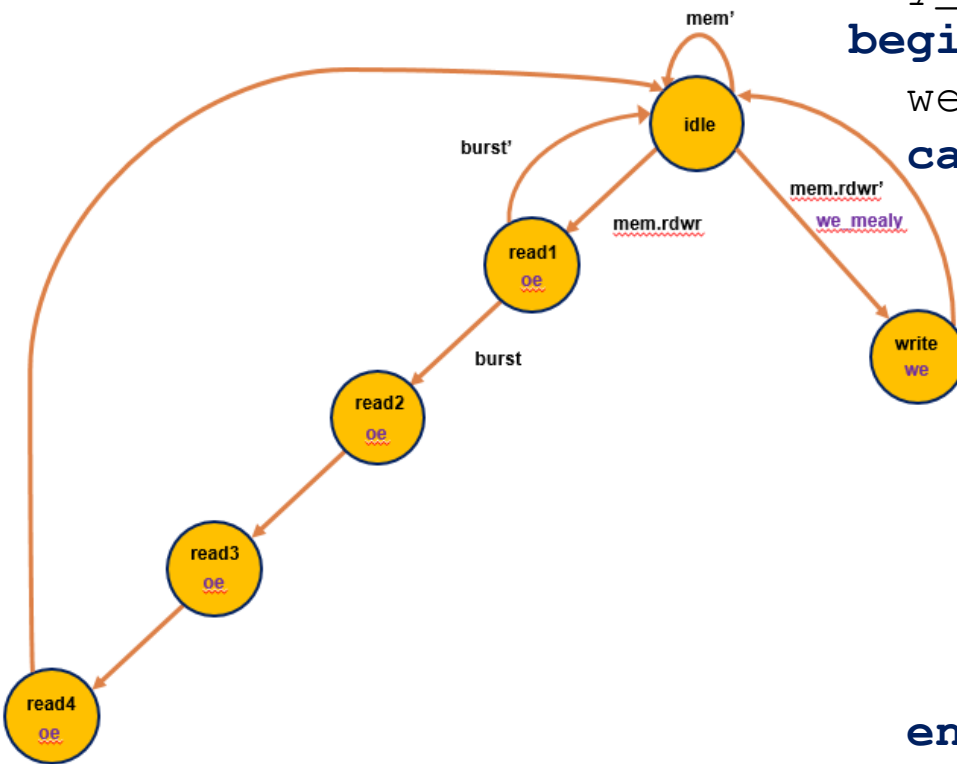


```
-- Mealy output logic
mly_pr: process(crtr_state,mem,rdwr)
begin
    we_me <= '0'; -- default value
    case state_reg is
    when idle =>
        if (mem='1') and (rdwr ='0') then
            we_me <= '1';
        end if;
    when write => null;
    when read1 => null;
    when read2 => null;
    when read3 => null;
    when read4 => null;
    end case;
end process mly_pr;
```

Memory Controller FSM - VHDL Code

□ Mealy output statement

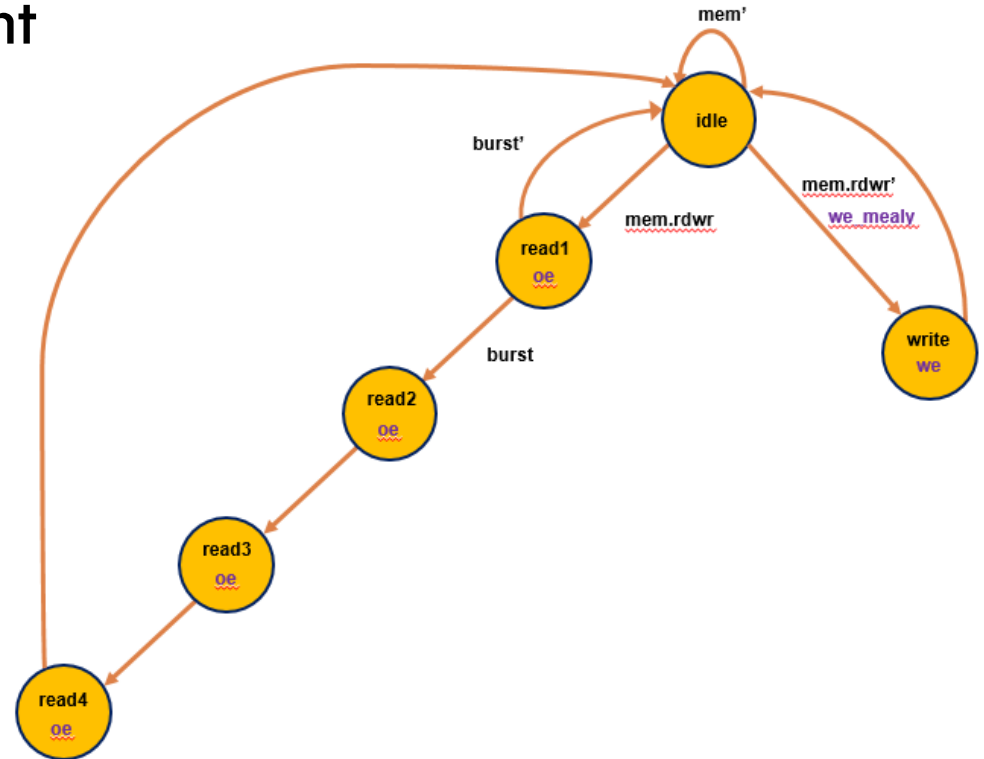

 
```
-- Mealy output logic
we_me <= '1' when ((crrent_state=idle) and (mem='1') and (rdwr='0'))
           else
           '0';
```



VHDL Code to be used in the Labs

Synchronous one-shot-timer

 The purpose of the module **oneShotTimer** is to generate a single output pulse of a predefined duration (**pulse_len**) every time it receives a rising edge on its **trig_in** input.



Synchronous one-shot-timer

```
27  entity oneShotTimer is
28      Generic(
29          DATA_BUS_WIDTH : NATURAL := 16 -- Configurable width for the pulse_len input
30      );
31      Port(
32          clk      : in std_logic;           -- Clock input (for synchronous operations)
33          aresetn   : in std_logic;          -- Asynchronous active-low reset input
34          ce        : in std_logic;          -- Clock Enable (not used in the provided code, but declared)
35          trig_in   : in std_logic;          -- Input trigger signal (rising edge detected)
36          pulse_len : in std_logic_vector(DATA_BUS_WIDTH - 1 downto 0); -- Duration of the output pulse in clock cycles
37          trig_out  : out std_logic          -- Output pulse
38      );
39  end oneShotTimer;
```

- generic(DATA_BUS_WIDTH : NATURAL := 16):**

- generic** is a way to pass constant values into an entity from its instantiation.
- DATA_BUS_WIDTH** defines the bit width of the **pulse_len** input. It defaults to 16 bits, meaning **pulse_len** can specify a pulse length from 0 to 65535 clock cycles.

- Port (...):** Defines the input and output signals of the block:

- clk**: Standard clock input. All internal state changes occur on its rising edge.
- aresetn**: Asynchronous active-low reset. When aresetn is '0', the timer is reset.
- ce**: Clock Enable. *Note: This port is declared but not used yet.*
- trig_in**: The input signal that, upon a rising edge, initiates the one-shot pulse.
- pulse_len**: An input vector that defines the desired duration of the output pulse in terms of clock cycles.
- trig_out**: The output signal that generates a pulse (goes high) for the specified **pulse_len** duration.

Synchronous one-shot-timer

```
41  architecture Behavioral of oneShotTimer is
42
43      -- Internal signal to store the previous state of trig_in for edge detection
44      signal lastTrig_in : std_logic;
45      -- Internal counter to track the pulse duration
46      signal counter : integer range 0 to 2**DATA_BUS_WIDTH - 1;
47
48  begin
```

- **architecture Behavioral of oneShotTimer** is: Defines the behavior or implementation of the **oneShotTimer** entity.
- **signal lastTrig_in : std_logic;**
 - Declares an internal signal named **lastTrig_in**.
 - This signal is crucial for **rising edge detection** of **trig_in**. It will store the value of **trig_in** from the *previous* clock cycle.
- **signal counter : integer range 0 to 2**DATA_BUS_WIDTH - 1;**
 - Declares an internal signal named **counter**.
 - It's declared as an INTEGER with a specified range, from 0 up to the maximum value that can be represented by DATA_BUS_WIDTH bits (e.g., if DATA_BUS_WIDTH is 16, the range is 0 to 65535). This counter tracks the duration of the output pulse.

Synchronous one-shot-timer

```
50  process(clk, aresetn)
51  begin
52      -- Asynchronous Reset
53      if aresetn = '0' then
54          lastTrig_in <= '0'; -- Reset lastTrig_in to '0'
55          counter <= 0;      -- Reset counter to 0 (trig_out will be '0')
56      -- Synchronous operations on rising edge of clock
57      elsif rising_edge(clk) then
58          -- Store current trig_in to lastTrig_in for the next clock cycle's edge detection
59          lastTrig_in <= trig_in; -- This creates a 1-cycle delay for trig_in
```

- **process(clk, aresetn):** This is a **sequential (clock-controlled) process**.
 - It's sensitive to **clk** and **aresetn**. This means the code inside the process will execute whenever **clk** or **aresetn** changes value.
- **if aresetn = '0' then ...:** This handles the **asynchronous reset**. If **aresetn** goes low, both **lastTrig_in** and **counter** are immediately forced to '0'. This initializes the timer to an inactive state.
- **elsif rising_edge(clk) then ...:** This block executes only on the **rising edge of the clock**, *after* checking the reset condition. All the logic inside this **elsif** is **synchronous**.
- **lastTrig_in <= trig_in;** On each rising clock edge, the current value of **trig_in** is stored into **lastTrig_in**. This is the standard way to create a one-clock-cycle delayed version of a signal for edge detection.

Synchronous one-shot-timer

```
60
61      -- Check for a rising edge on trig_in (current trig_in is '1' and lastTrig_in was '0')
62  ✓      if(lastTrig_in = '0' and trig_in = '1') then -- Trigger condition met
63          counter <= 1; -- Start the counter from 1 (the pulse length is counted from 1 to pulse_len)
64      -- If the counter is still running (not zero and less than the target pulse_len)
65  ✓      elsif((counter < to_integer(unsigned(pulse_len))) and (counter /= 0)) then
66          counter <= counter + 1; -- Increment the counter
67      -- If the counter has reached or exceeded pulse_len, or if it's already zero (not active)
68  ✓      else
69          counter <= 0; -- Reset counter to 0, ending the pulse
70      end if;
71
72      end if;
73  end process;
```

- **if(lastTrig_in = '0' and trig_in = '1')** then -- Trigger condition:
 - This is the **rising edge detection** logic. It checks if **trig_in** was '0' in the *previous* clock cycle (**lastTrig_in**) and is '1' in the *current* clock cycle (**trig_in**).
 - If a rising edge is detected, **counter <= 1**; initializes the counter. This makes the **trig_out** go high starting from the next clock cycle (because trig_out is 1 when counter /= 0).
- **elsif((counter < to_integer(unsigned(pulse_len))) and (counter /= 0))** then: The **counting** phase.
 - **to_integer(unsigned(pulse_len))**: Converts the STD_LOGIC_VECTOR **pulse_len** into an INTEGER so it can be compared with **counter**. unsigned() treats the vector as an unsigned number.
 - **counter < ...**: Checks if the counter has not yet reached the desired pulse length.
 - **counter /= 0**: Ensures that the counter is actually active (has been triggered).
- If both conditions are true, **counter <= counter + 1**; increments the counter, continuing the pulse.
- **else counter <= 0**; This is the default case.

Synchronous one-shot-timer

```
74  
75     trig_out <= '1' when counter /= 0 else '0';  
76
```

- This is a **concurrent signal assignment statement**. It is outside the process block, meaning it's continuously evaluated.
- **trig_out <= '1' when counter /= 0 else '0';**
 - The **trig_out** signal will be '1' whenever the counter is *not equal* to 0.
 - Otherwise (when counter is 0), **trig_out** will be '0'.
 - This effectively means that **trig_out** is high for the duration that counter is counting (from 1 up to **pulse_len**), and low when the timer is idle or reset.

Synchronous one-shot-timer

How it Works Together:


1. **Idle State:** counter is 0, **trig_out** is '0'.
2. **Trigger:** A rising edge on **trig_in** is detected.
3. **Start Pulse:** On the next rising **clk** edge after the **trigger**, **counter** is set to 1. **trig_out** immediately becomes '1'.
4. **Pulse Duration:** For subsequent clock cycles, if counter is less than **pulse_len** and not 0, counter increments. **trig_out** remains '1'.
5. **Pulse End:** When counter becomes equal to **pulse_len** (meaning **pulse_len** clock cycles have passed since the trigger), in the *next* clock cycle, the **elsif** condition (**counter < to_integer(unsigned(pulse_len))**) becomes false. The **else** branch executes, resetting **counter** to 0.
6. **Output Low:** As counter becomes 0, **trig_out** immediately reverts to '0', ending the pulse.
7. **Reset:** If **aresetn** goes low at any point, **counter** and **lastTrig_in** are reset to 0, forcing **trig_out** to '0' and stopping any ongoing pulse.

This design creates a reliable, retriggerable one-shot timer with a configurable pulse length, synchronized to the system clock.

Synchronous level-crossing trigger

Its purpose is to detect when an input data value, **dIn**, crosses a specified **threshold** value, specifically looking for either a positive-going (rising) edge crossing or a negative-going (falling) edge crossing, depending on the **edgeSel** input.

 The output, **trigger**, will be set to '1' during one clock cycle whenever a trigger event is detected



Synchronous level-crossing trigger

```
28  entity crossLevelTriggerBlock is
29      Generic(
30          DATA_BUS_WIDTH : NATURAL := 14 -- Configurable width for data and threshold
31      );
32      Port (
33          clk      : in STD_LOGIC;          -- Clock input (for synchronous operations)
34          aresetn  : in STD_LOGIC;          -- Asynchronous active-low reset input
35          dIn      : in STD_LOGIC_VECTOR (DATA_BUS_WIDTH - 1 downto 0); -- Input data
36          threshold : in STD_LOGIC_VECTOR (DATA_BUS_WIDTH - 1 downto 0); -- Threshold value
37          edgeSel  : in STD_LOGIC;          -- Edge selection: '0' for Positive Edge, '1' for Negative Edge
38          trigger  : out STD_LOGIC          -- Output: '1' when a trigger condition is met, '0' otherwise
39      );
40  end crossLevelTriggerBlock;
```

- ✓ **generic(DATA_BUS_WIDTH : NATURAL := 14):**
 - ✓ Generic is a way to pass constant values into an entity from its instantiation.
 - ✓ DATA_BUS_WIDTH is a generic parameter defining the width of the **dIn** and threshold buses. It's set to a default value of 14 bits. This makes the design reusable for different data widths without modifying the core code.
- ✓ **Port (...):** Defines the input and output signals of the block:
 - ✓ **clk**: Standard clock input. All internal state changes will occur on its edge.
 - ✓ **aresetn**: Asynchronous active-low reset. When aresetn is '0', the circuit is reset. *The n suffix typically indicates active-low.*
 - ✓ **dIn**: Input data bus, DATA_BUS_WIDTH bits wide.
 - ✓ **threshold**: Reference value for comparison, DATA_BUS_WIDTH bits wide.
 - ✓ **edgeSel**: A single bit to select the type of trigger: '0' for positive-going edge (crossing threshold from below), '1' for negative-going edge (crossing threshold from above).
 - ✓ **trigger**: A single-bit output that goes '1' when a trigger condition is detected.

Synchronous level-crossing trigger

```
42     architecture Behavioral of crossLevelTriggerBlock is
43         -- declare an internal signal to store the previous value of dIn
44         signal lastVal : std_logic_vector(DATA_BUS_WIDTH - 1 downto 0);
45     begin
```

- **architecture Behavioral of crossLevelTriggerBlock** is:
Defines the behavior or implementation of the **crossLevelTriggerBlock** entity.
- **signal lastVal** : std_logic_vector(DATA_BUS_WIDTH - 1 downto 0);
 - Declares an internal signal named last **lastVal**.
 - **lastVal** is a STD_LOGIC_VECTOR of the same width as **dIn** and **threshold**.
 - This signal is crucial for detecting *edge* crossings: it stores the value of **dIn** from the *previous* clock cycle.

Synchronous level-crossing trigger

```
47  process(clk, aresetn)
48      begin
49          -- Asynchronous Reset
50          if (aresetn = '0') then
51              trigger <= '0'; -- Reset trigger output to '0'
52          -- Synchronous operations on rising edge of clock
53          elsif (rising_edge(clk)) then
54              -- Store current dIn to lastVal for the next clock cycle's comparison
55              lastVal <= dIn;
56              -- Positive slope cross-level trigger
57              if (edgeSel = '0') then
58                  -- Condition for positive edge crossing:
59                  -- Previous value was BELOW threshold AND Current value is AT or ABOVE threshold
60                  if (unsigned(lastVal) < unsigned(threshold) and unsigned(dIn) >= unsigned(threshold)) then
61                      trigger <= '1'; -- Activate trigger
62                  else
63                      trigger <= '0'; -- Deactivate trigger
64                  end if;
65              -- Negative slope cross-level trigger
66              else -- edgeSel = '1'
67                  -- Condition for negative edge crossing:
68                  -- Previous value was ABOVE threshold AND Current value is AT or BELOW threshold
69                  if (unsigned(lastVal) > unsigned(threshold) and unsigned(dIn) <= unsigned(threshold)) then
70                      trigger <= '1'; -- Activate trigger
71                  else
72                      trigger <= '0'; -- Deactivate trigger
73                  end if;
74              end if;
75          end if;
76      end process;
```

Synchronous level-crossing trigger

```
47  process(clk, aresetn)
48      begin
49          -- Asynchronous Reset
50          if (aresetn = '0') then
51              trigger <= '0'; -- Reset trigger output to '0'
52          -- Synchronous operations on rising edge of clock
53          elsif (rising_edge(clk)) then
54              -- Store current dIn to lastVal for the next clock cycle's comparison
55              lastVal <= dIn;
```

- **process(clk, aresetn):** This is a **sequential (clock-controlled) process**.
 - It's sensitive to **clk** and **aresetn**. This means the code inside the process will execute whenever **clk** or **aresetn** changes value (aka, an event on one of those signals).
- **if (aresetn = '0')** then trigger <= '0'; This handles the **asynchronous reset**. If **aresetn** goes low, the output **trigger** is immediately forced to '0', regardless of the clock. This is common for initial circuit states.
- **elsif (rising_edge(clk)) then:** This block executes only on the **rising edge of the clock**, *after* checking the reset condition. All the logic inside this **elsif** is **synchronous**.
- **lastVal <= dIn;**
 - This is a synchronous assignment. On each rising clock edge, the current value of **dIn** is stored into **lastVal**.
 - This means **lastVal** will always hold the value of **dIn** from the *previous* clock cycle, allowing for edge detection.

Synchronous level-crossing trigger

```
56      -- Positive slope cross-level trigger
57      if (edgeSel = '0') then
58          -- Condition for positive edge crossing:
59          -- Previous value was BELOW threshold AND Current value is AT or ABOVE threshold
60          if (unsigned(lastVal) < unsigned(threshold) and unsigned(dIn) >= unsigned(threshold)) then
61              trigger <= '1'; -- Activate trigger
62          else
63              trigger <= '0'; -- Deactivate trigger
64          end if;
```

if (edgeSel = '0') then -- Positive slope cross-level trigger:

- If **edgeSel** is '0', the block is configured to detect a positive-going (rising) edge crossing.
- **if (unsigned(lastVal) < unsigned(threshold) and unsigned(dIn) >= unsigned(threshold))**

then: This is the core detection logic for a positive edge.

- **unsigned():** cast that converts STD_LOGIC_VECTOR signals to UNSIGNED type for *numerical comparison*.
- The condition checks if the *previous* data value (**lastVal**) was strictly **less than** the **threshold**, **AND** the *current* data value (**dIn**) is **greater than or equal to** the **threshold**. This accurately defines a *positive cross-level event*.
- If this condition is met, **trigger** is set to '1'.
- **else trigger <= '0';** Otherwise, **trigger** is '0'. *This ensures **trigger** is only '1' for one clock cycle when the condition is met.*

Synchronous level-crossing trigger

```
65         -- Negative slope cross-level trigger
66     else -- edgeSel = '1'
67         -- Condition for negative edge crossing:
68         -- Previous value was ABOVE threshold AND Current value is AT or BELOW threshold
69         if (unsigned(lastVal) > unsigned(threshold) and unsigned(dIn) <= unsigned(threshold)) then
70             trigger <= '1'; -- Activate trigger
71         else
72             trigger <= '0'; -- Deactivate trigger
73         end if;
74     end if;
75 end if;
76 end process;
```

else -- Negative slope cross-level trigger (**edgeSel = '1'**):

- If **edgeSel** is '1', the block is configured to detect a negative-going (falling) edge crossing.
- if (**unsigned(lastVal) > unsigned(threshold) and unsigned(dIn) <= unsigned(threshold)**)

then: This is the core detection logic for a **negative edge**.

- The condition checks if the *previous* data value (**lastVal**) was strictly **greater than** the **threshold**, AND the *current* data value (**dIn**) is **less than or equal to** the **threshold**.

This defines a negative cross-level event.

- If this condition is met, **trigger** is set to '1'.
- else **trigger <= '0'**:: Otherwise, **trigger** is '0'.

Synchronous level-crossing trigger

In Summary:

This **crossLevelTriggerBlock** VHDL design acts as a programmable level-crossing detector:

1. It stores the previous sample of the input data (**dIn**) in **lastVal** synchronously on each clock edge.
2. On *each clock edge*, it compares the current **dIn** and the previous **lastVal** against a **threshold**.
3. Based on the **edgeSel** input, it determines if a positive-going or negative-going level crossing has occurred.
4. If a crossing is detected, the **trigger** output goes *high for one clock cycle*.
5. It also includes an asynchronous active-low reset to initialize the trigger output to '0'.

This type of module is common in digital signal processing or control systems where events need to be detected based on signal levels crossing certain thresholds