

Outline

■ Digital CMOS design

- Boolean algebra
- Basic digital CMOS gates
- Combinational and sequential circuits
- Coding - Representation of numbers

Basic CMOS Gates


How to implement Boolean functions
in CMOS technology ?

Which functionalities are available





Basic CMOS Gates

N-MOS transistor


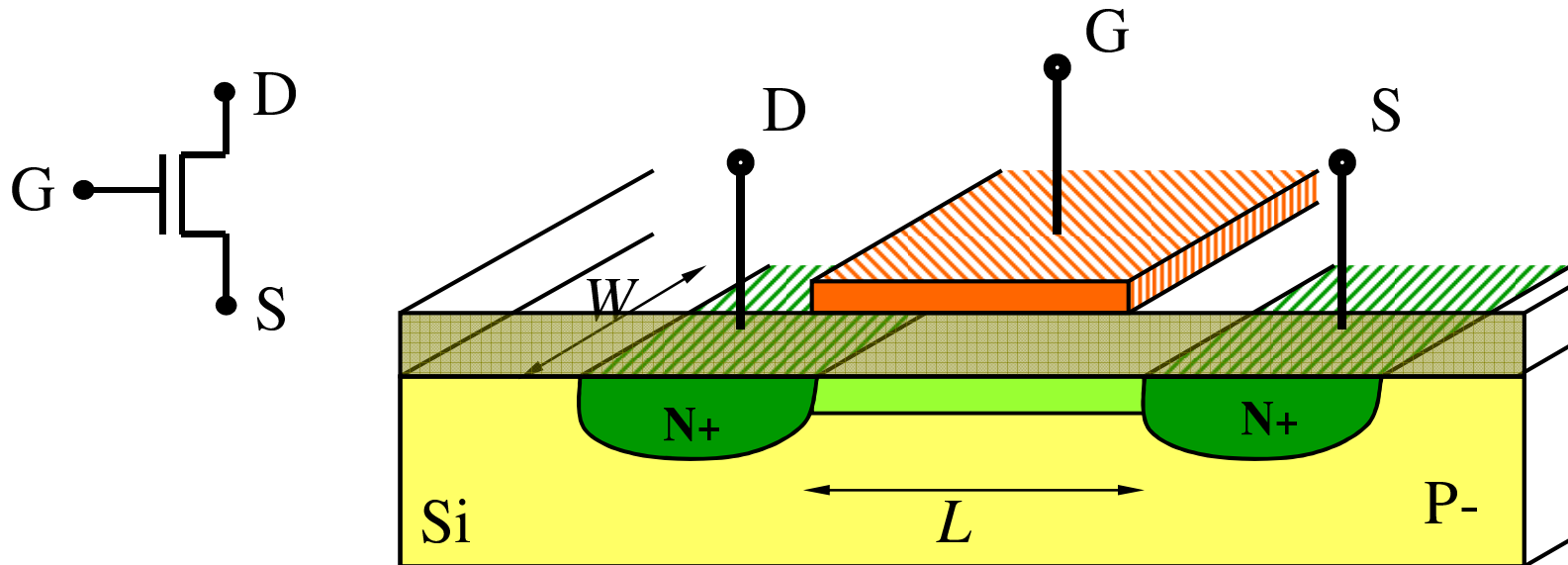


Basic CMOS Gates

● N-MOS transistor

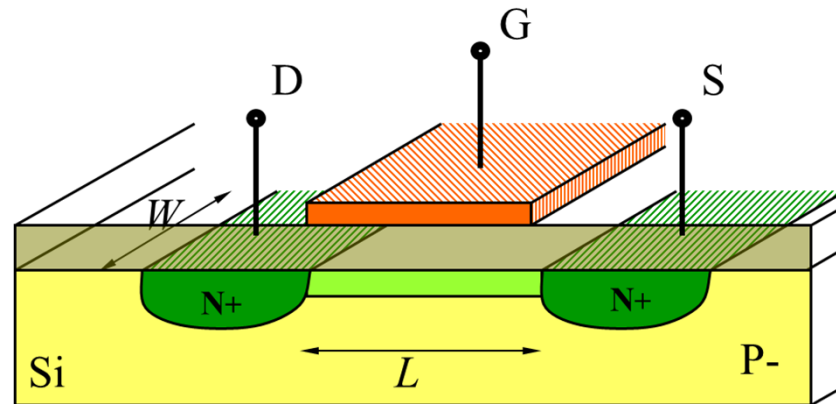
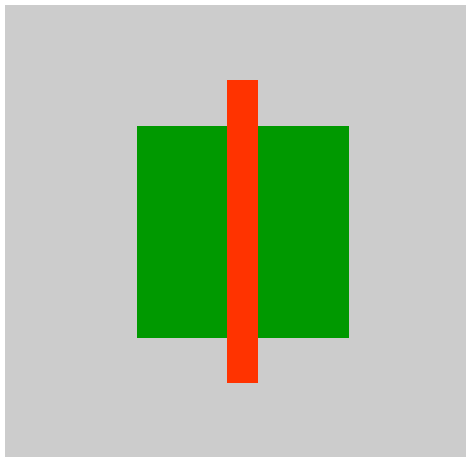



Basic CMOS Gates

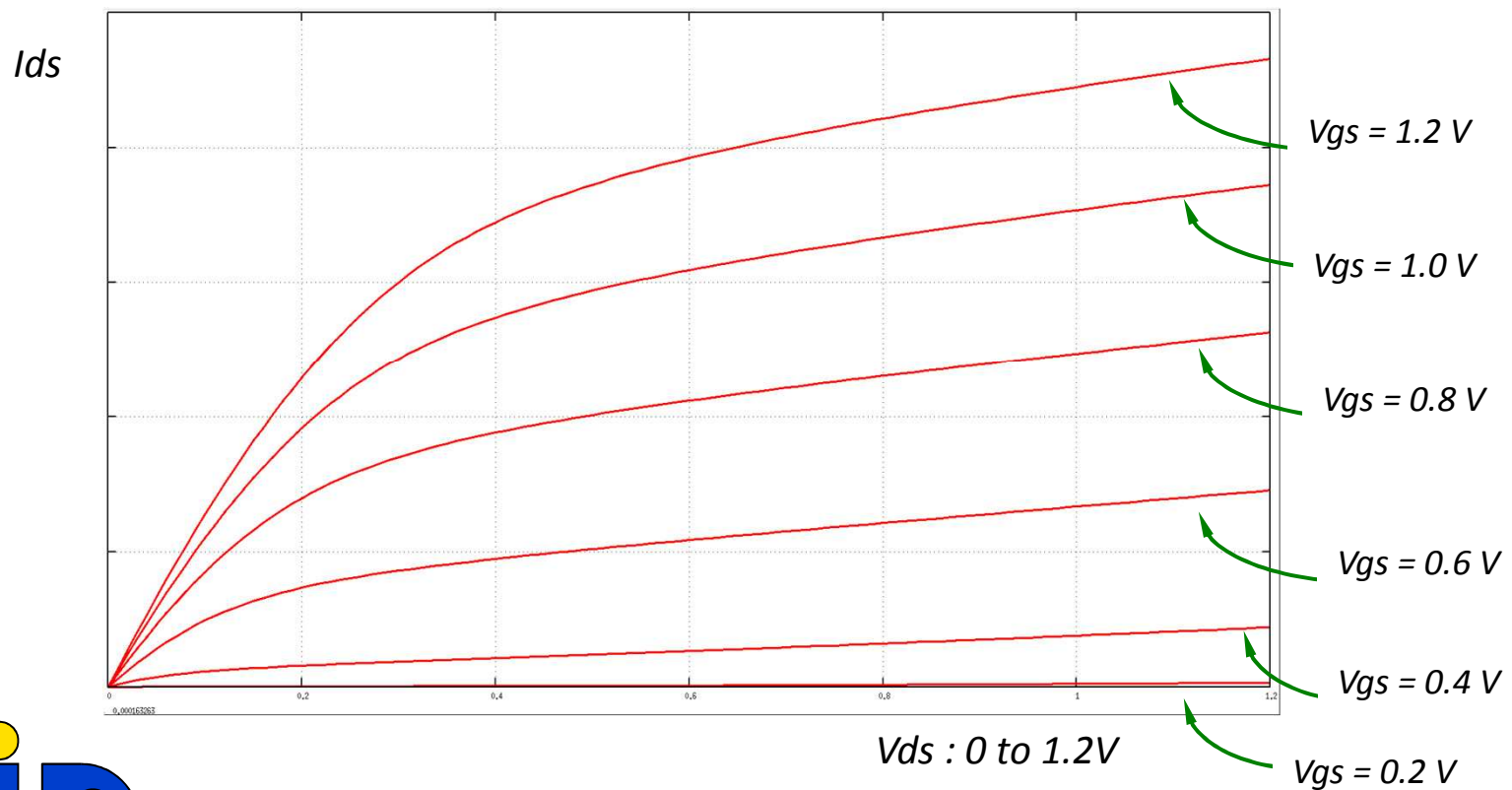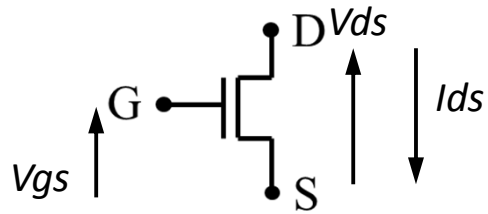


Basic CMOS Gates

● P-MOS transistor

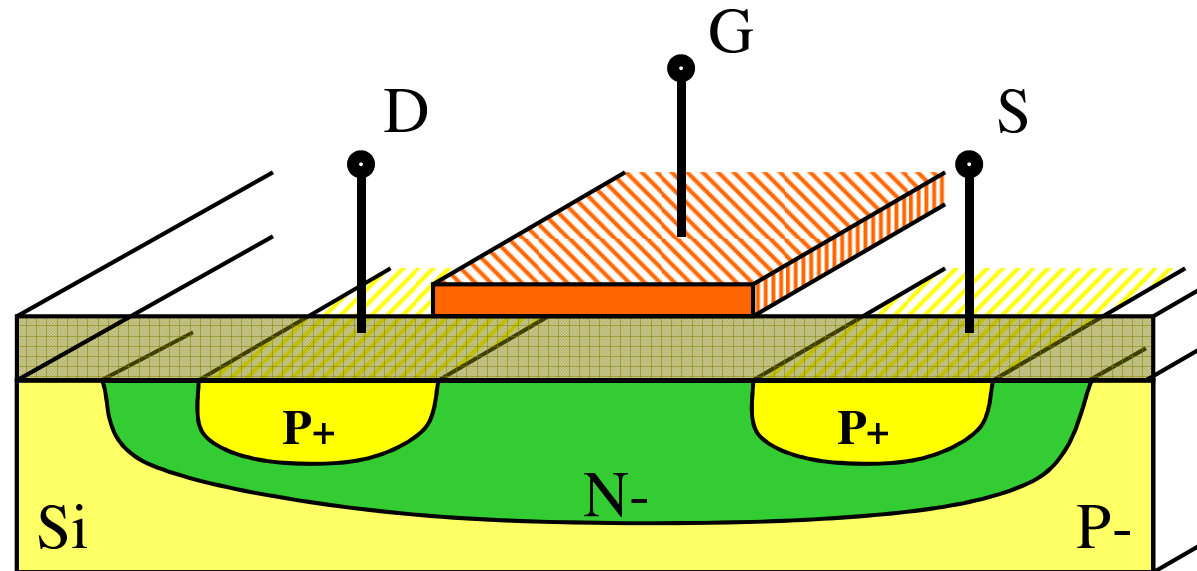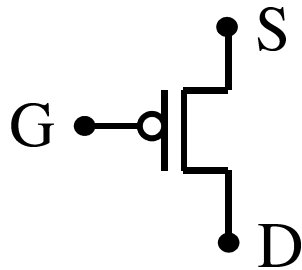

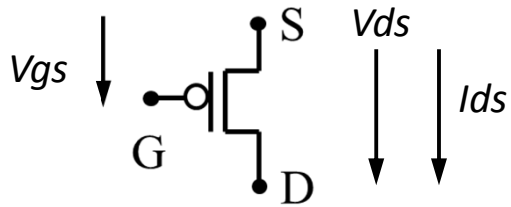

Basic CMOS Gates

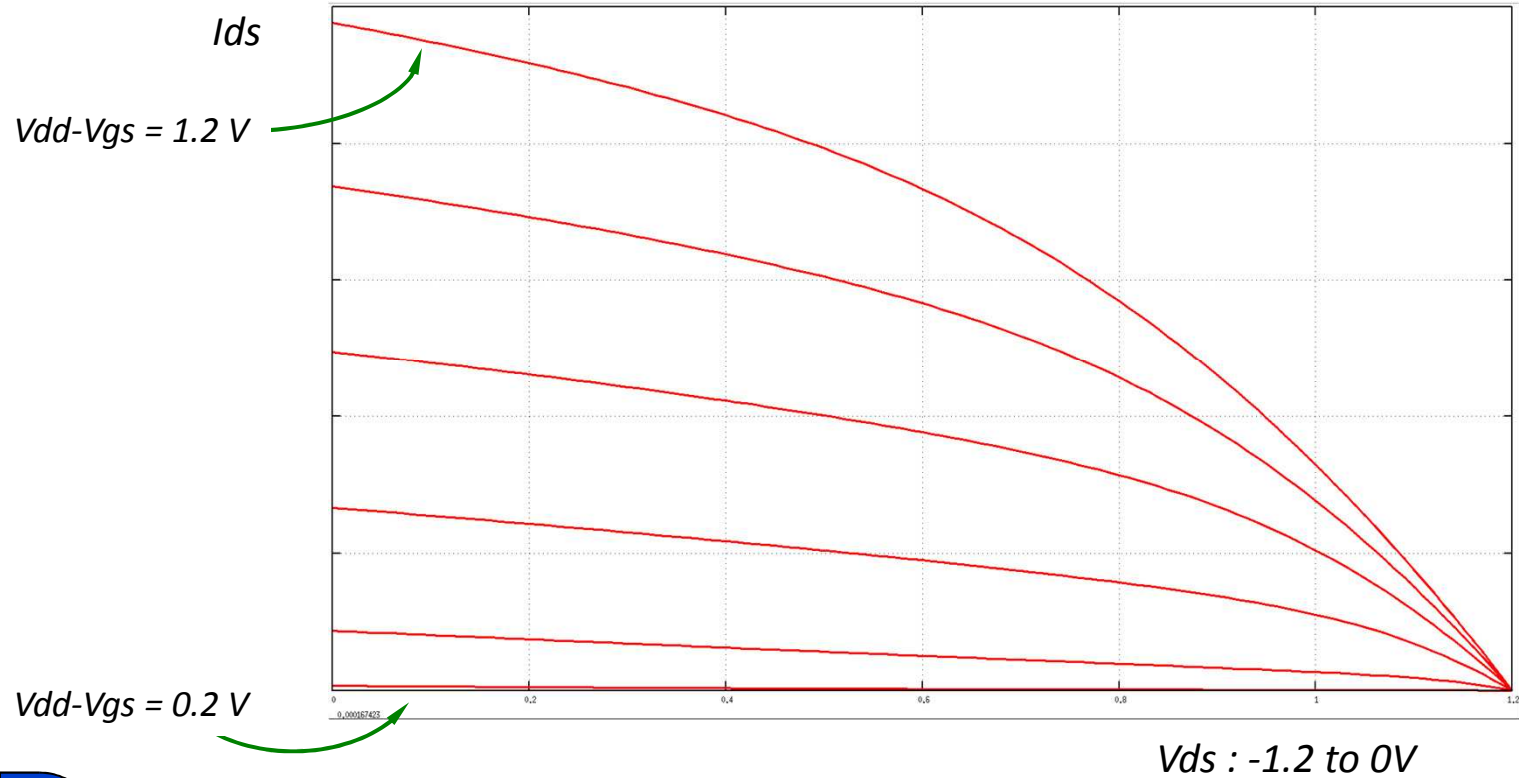

Basic CMOS Gates

The electrical behavior of a MOS transistor
is very complex


Design of a multi-million transistor circuit ?



Basic CMOS Gates


In a digital circuit a MOS transistor can be
seen as a **Switch**

N-MOS

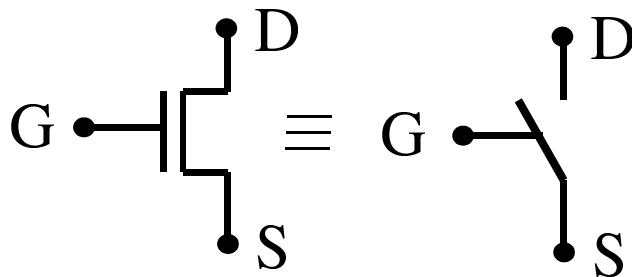

$D = S$ when $G = 1$

P-MOS

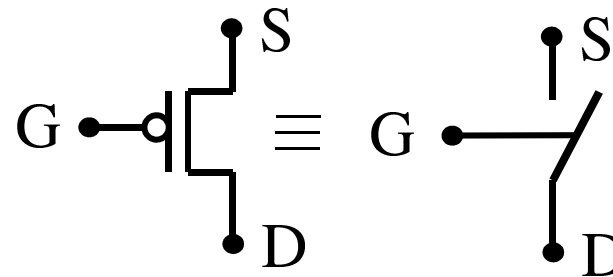

$D = S$ when $G = 0$

Basic CMOS Gates

When driving, a MOS transistor can be seen as a **Resistor**

$$\text{Resistance} \propto \frac{L}{W} \qquad \text{Conductance} \propto \frac{W}{L}$$

For the same size, a P-MOS is twice
more resistive than an N-MOS

Basic CMOS Gates

The N-MOS and P-MOS are not exactly symmetrical


A N-MOS is a good transmitter of 0

A P-MOS is a good transmitter of 1




Basic CMOS Gates



$$y = \text{Not } x$$

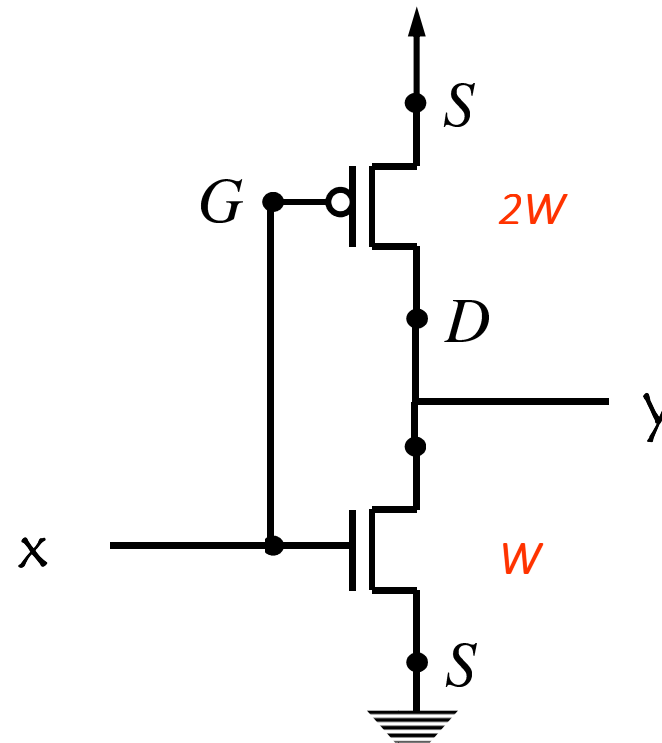

Dual CMOS gate


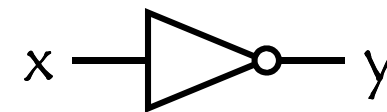


Basic CMOS Gates

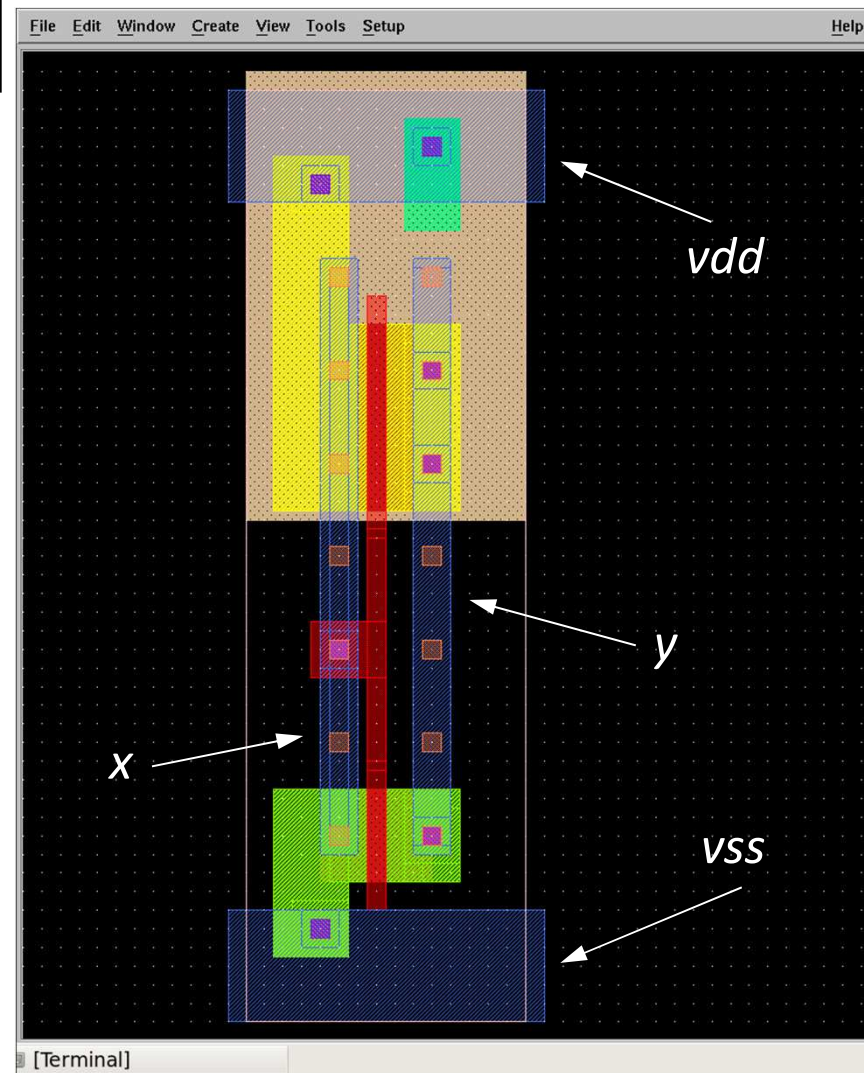
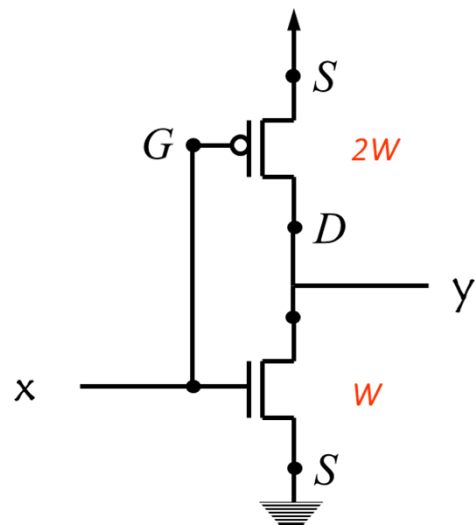


Basic CMOS Gates




$$y = \overline{x_1 \cdot x_2}$$

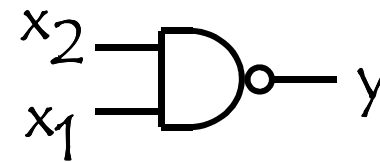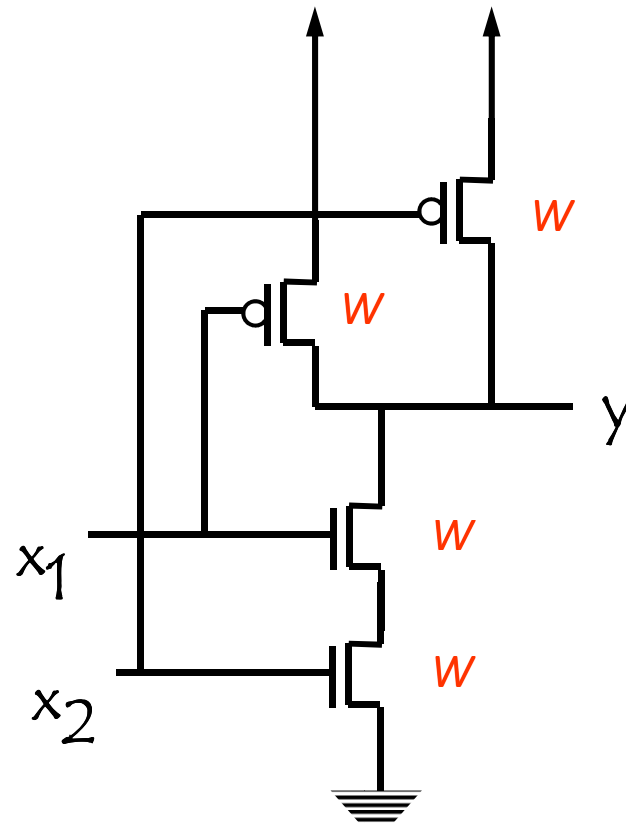

Basic CMOS Gates

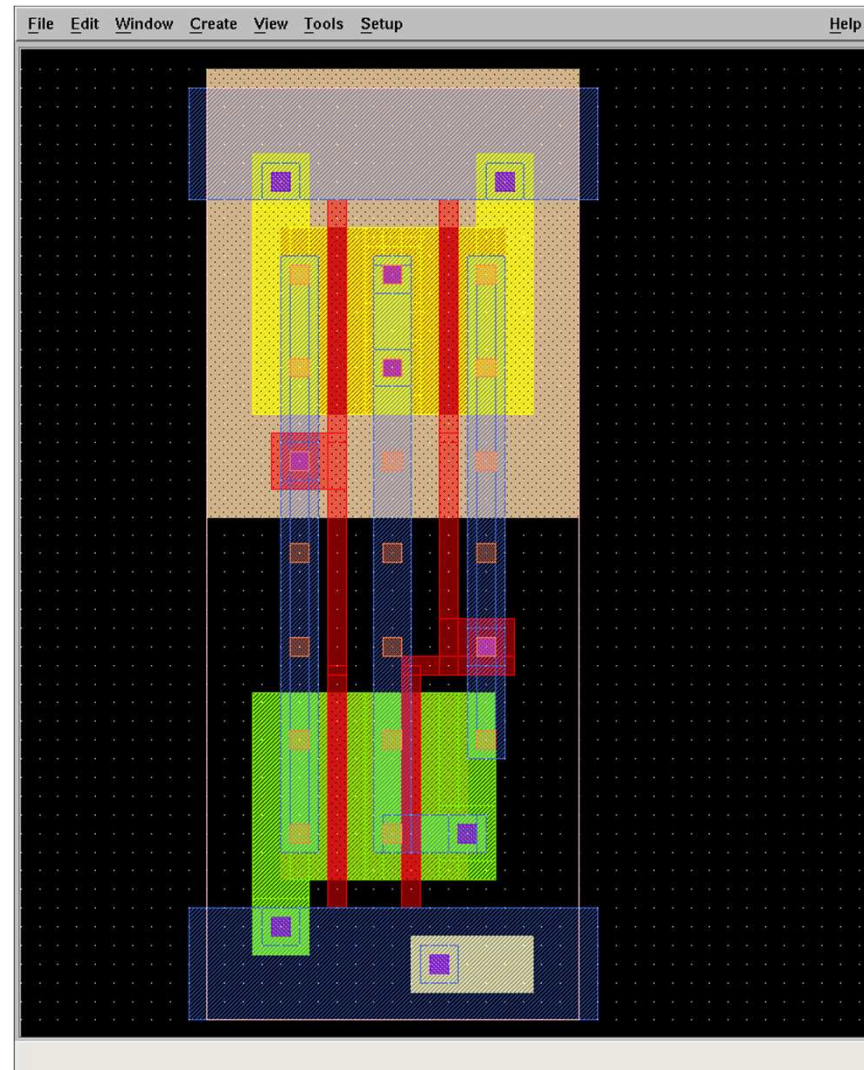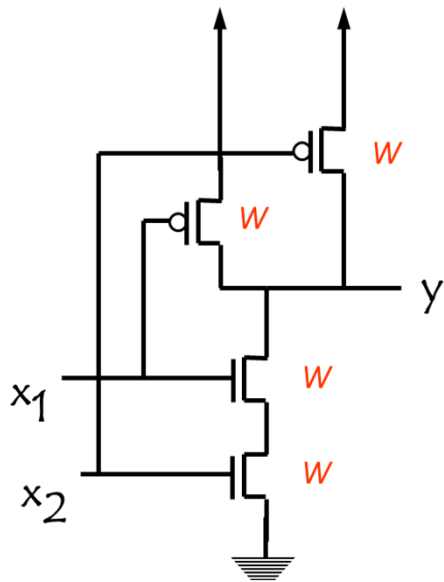


Basic CMOS Gates

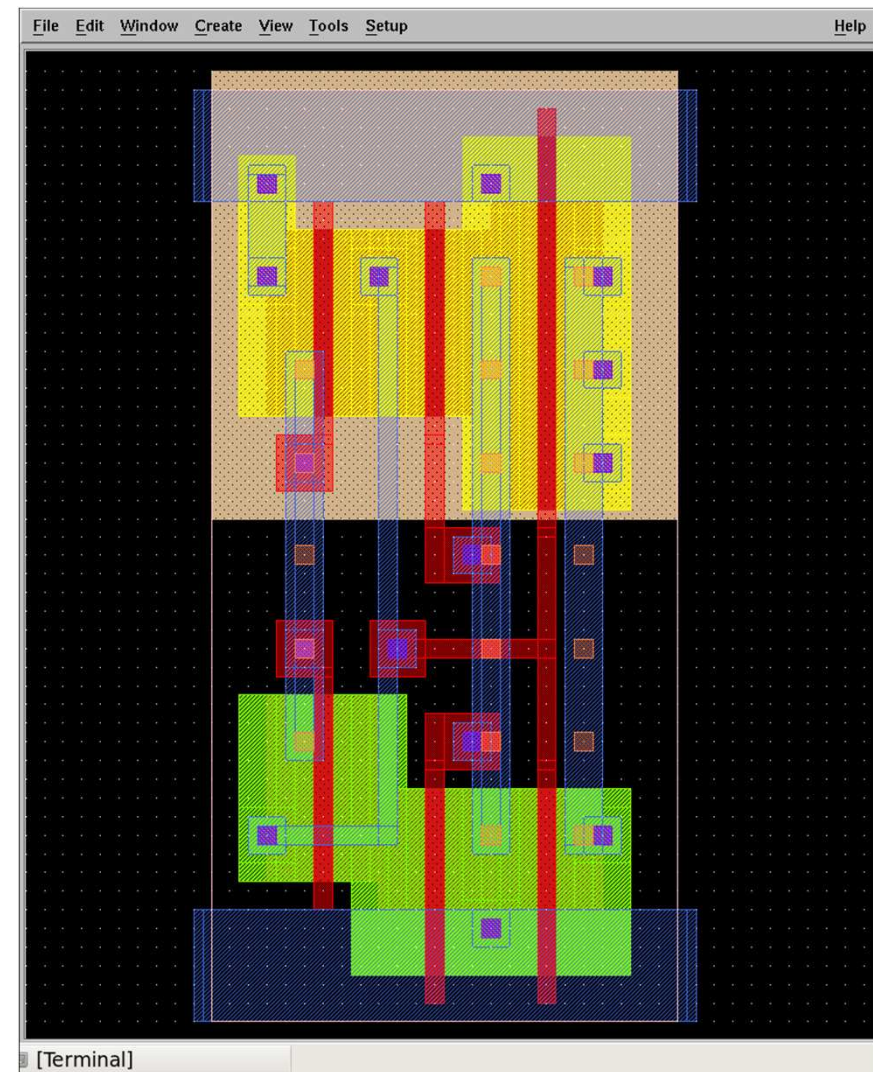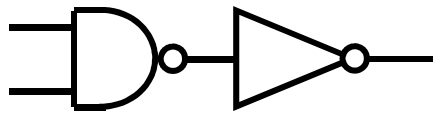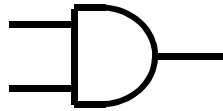

Basic CMOS Gates

Design of a dual gate

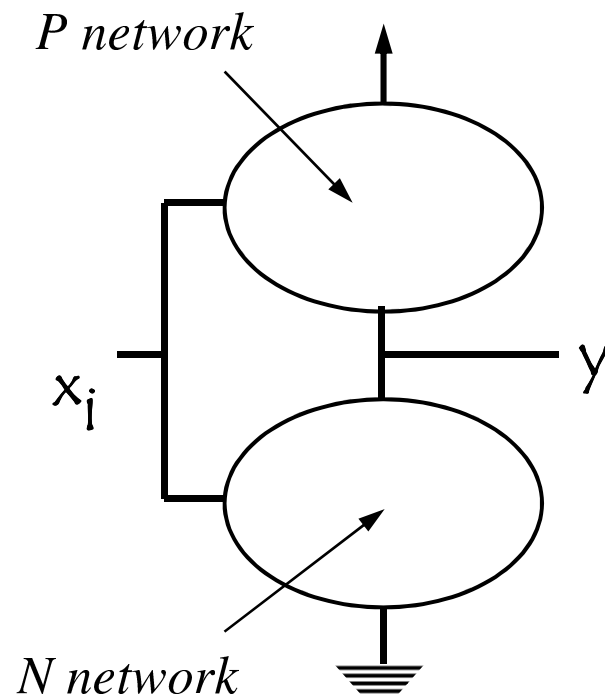

The P-network must be the dual of the N-network


Series \longrightarrow Parallel
Parallel \longrightarrow Series

Take care of the size of transistors

Basic CMOS Gates

- To set the output to **0** a path has to be created through the **N** network
- A series of N-transistor must be conducting

$$\prod x_i = 1$$

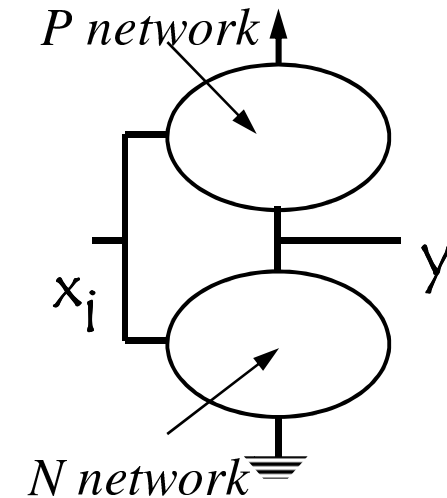

Only negative (inverting) functions can be created

Basic CMOS Gates

Implementing a Boolean function with a CMOS gate ?

- The function must be inverting in regard of all the variables
- Put the function in the form of $f = \overline{g}$
- Design the N-network of g

Basic CMOS Gates

Implementing a Boolean function with a CMOS gate ?

- In the expression of g each $'.'$ are two paths in series
- In the expression of g each $'+'$ are two paths in parallel
- The P-network is the dual network of the N-network
- Avoid putting more than 3 transistors in series

Basic CMOS Gates


Example :

$$f = \bar{a} + (\bar{b} \cdot \bar{c})$$

$$f = \bar{a} + \overline{(b+c)}$$

$$f = \overline{a \cdot (b+c)}$$

$$g = a \cdot (b+c)$$

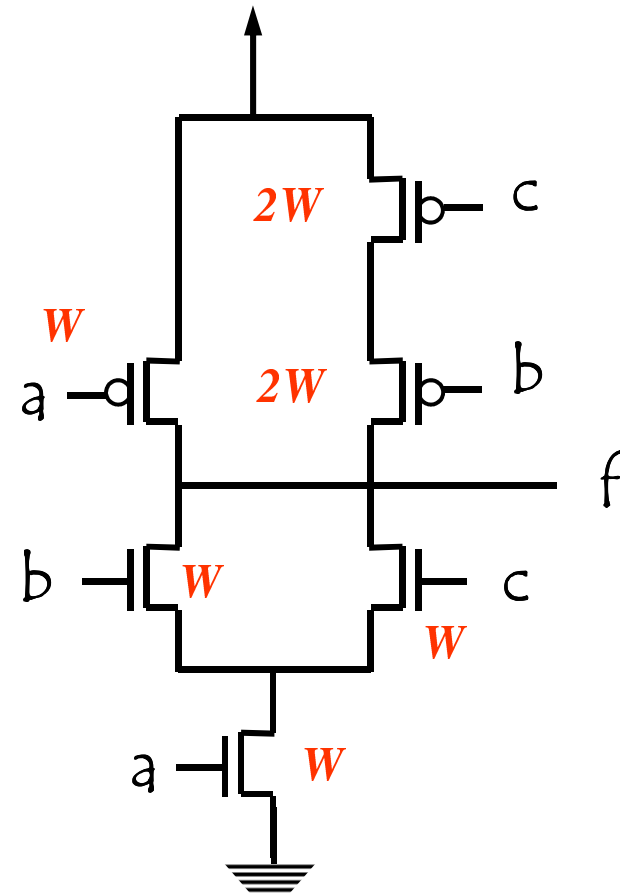



Basic CMOS Gates

Some gates :

Inverter : $f = \overline{a}$

Nand : $f = \overline{a.b}$

Nor : $f = \overline{a+b}$

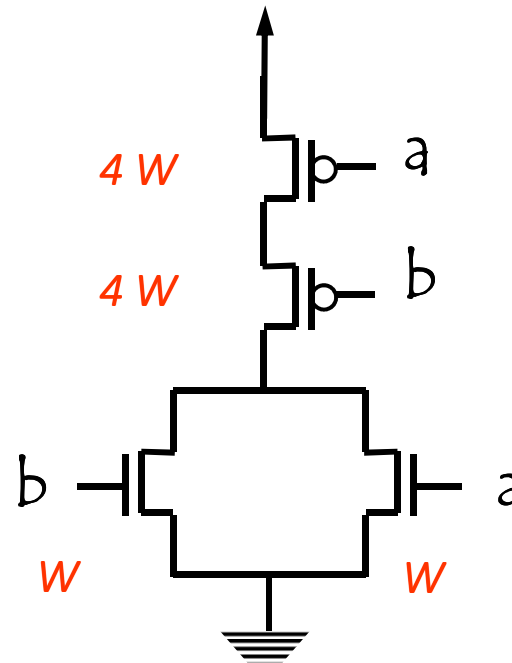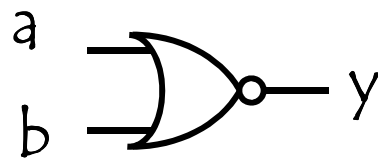

Basic CMOS Gates

Some gates :

Multiplexer :

$$f = \overline{a.s} + b.\overline{s}$$

