

Outline

- Digital CMOS design
 - Boolean algebra
 - Basic digital CMOS gates
 - **Combinational and sequential circuits**
 - Coding - Representation of numbers

CMOS Circuits

- **Combinational logic**

The value of the output can be determined knowing the value of the inputs

- **Sequential logic**

The value of the output depends on the value of the inputs **and the history**

Notion of memory




CMOS Circuits

Memory :

Hold a data (0 or 1)

Write a data (0 or 1)

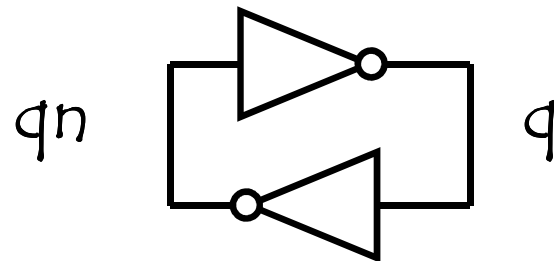


CMOS Circuits

Memory :

Hold a data (0 or 1)

Write a data (0 or 1)

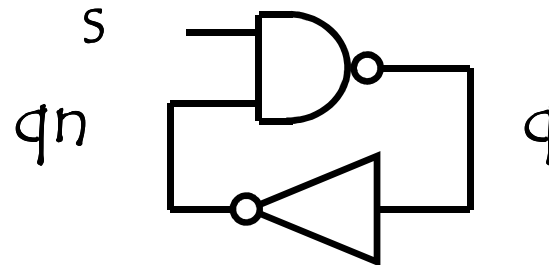


s	q	qn
0	1	0
1	q	qn

CMOS Circuits

Memory :

Hold a data (0 or 1)

Write a data (0 or 1)

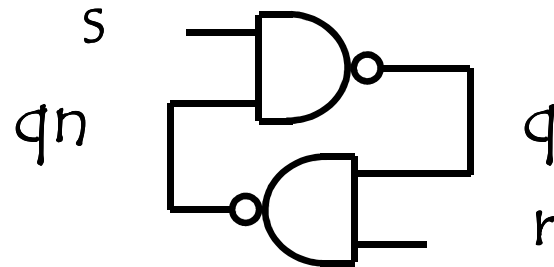


s	r	q	qn
0	1	1	0
1	0	0	1
1	1	q	qn
0	0	1	1

RS flip flop

CMOS Circuits

Synchronous Memory :

Write a data d when the clock $ck = 1$

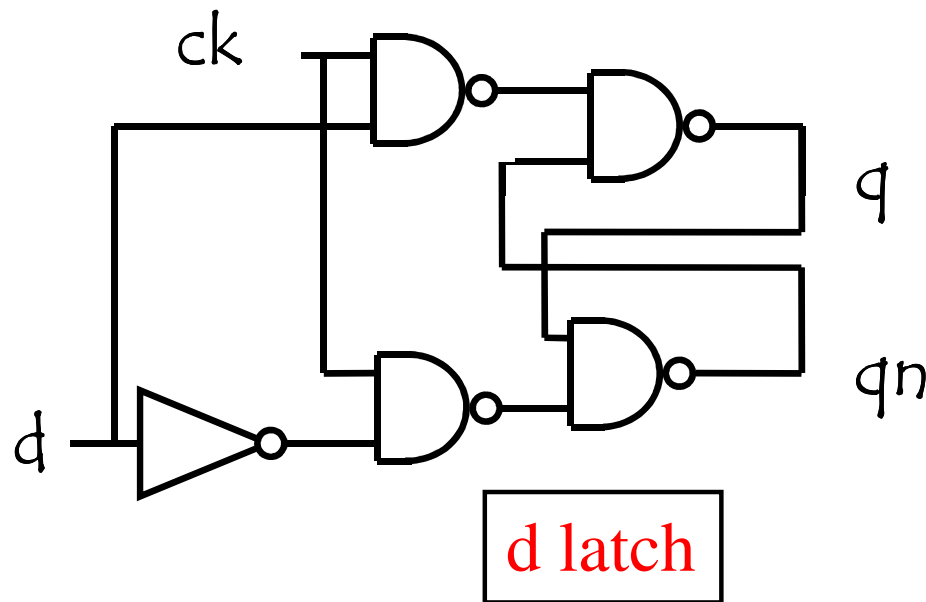

s	r	q	qn
0	1	1	0
1	0	0	1
1	1	q	qn
0	0	1	1



if $ck \cdot d = 1$ $s = 0$

if $ck \cdot \bar{d} = 1$ $r = 0$

CMOS Circuits


Synchronous Memory :

Write a data d when the clock $ck = 1$

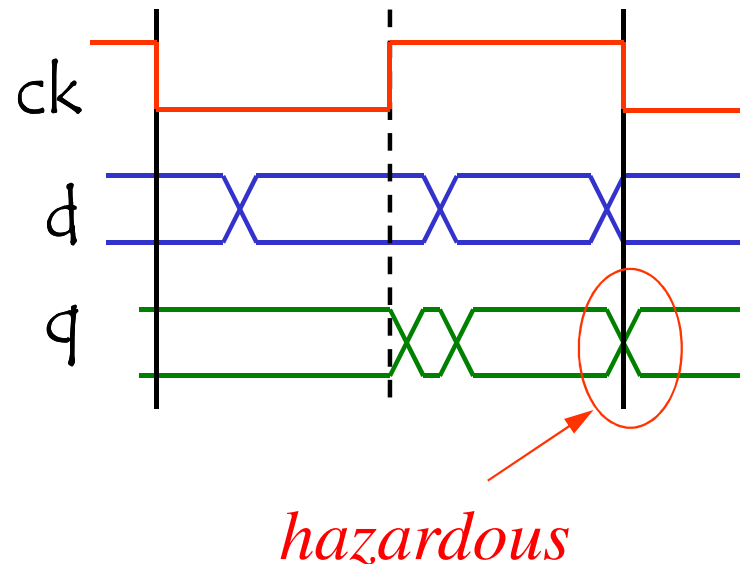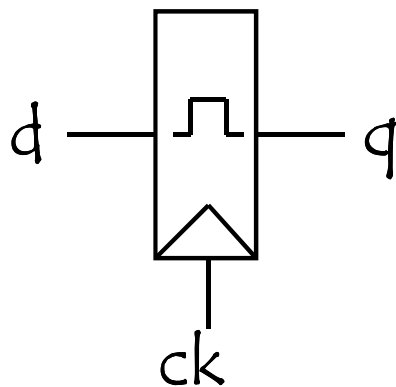

CMOS Circuits



Synchronous Memory :

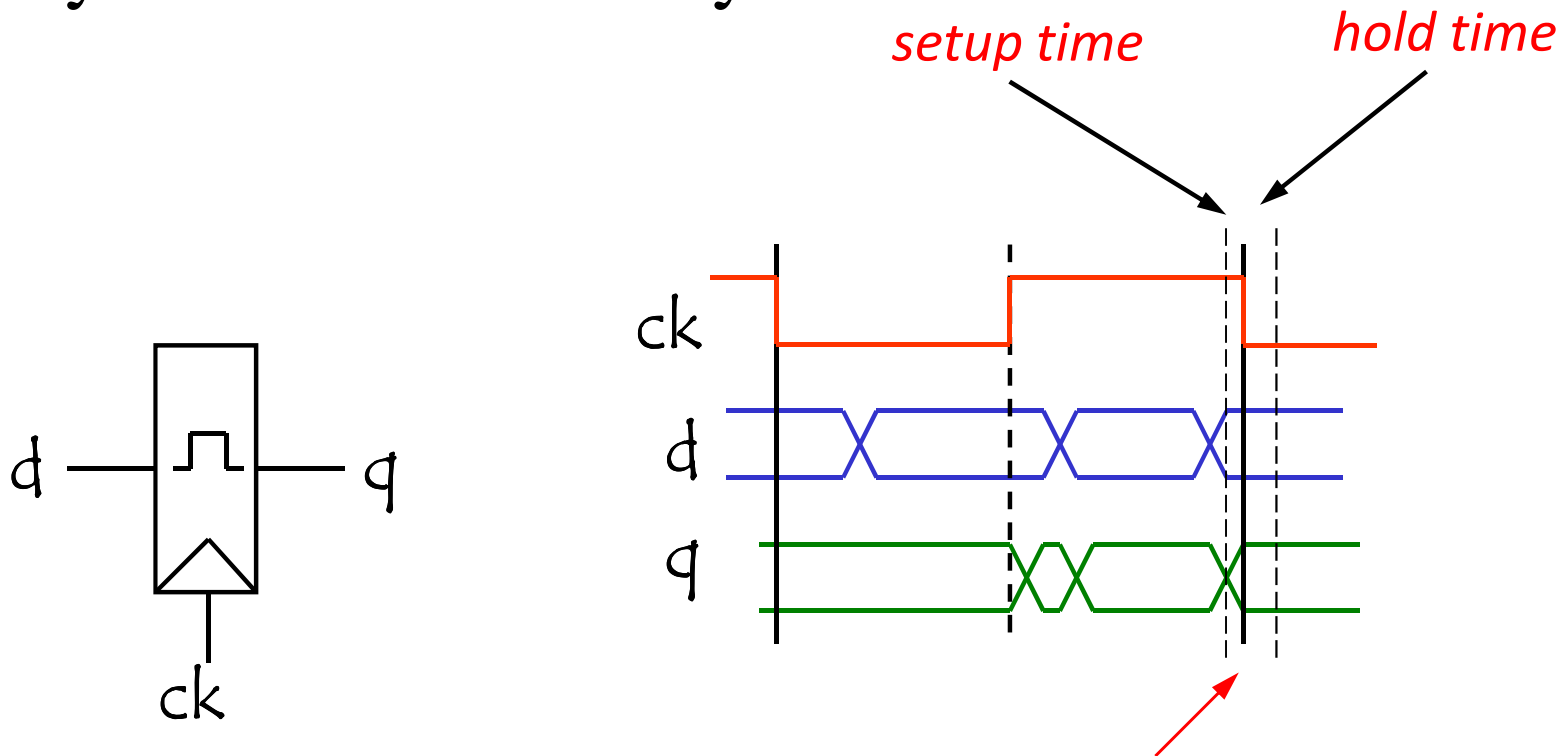

data should not be changed during this period

CMOS Circuits

Memory :

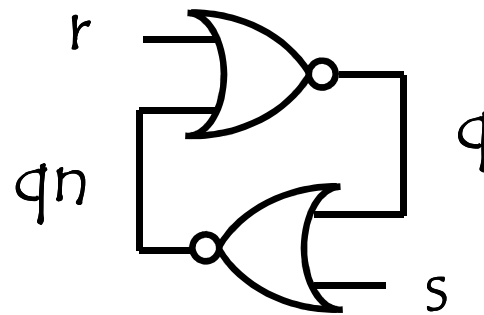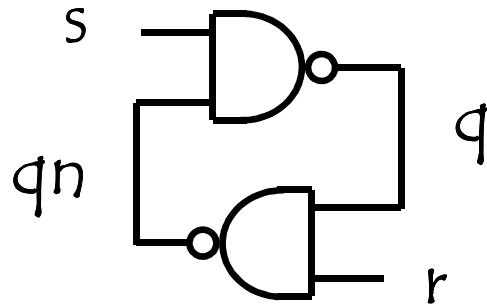


s	r	q	qn
0	1	0	1
1	0	1	0
1	1	0	0
0	0	q	qn

RS flip flop

CMOS Circuits

Synchronous Memory :

Write a data d when the clock $ck = 0$

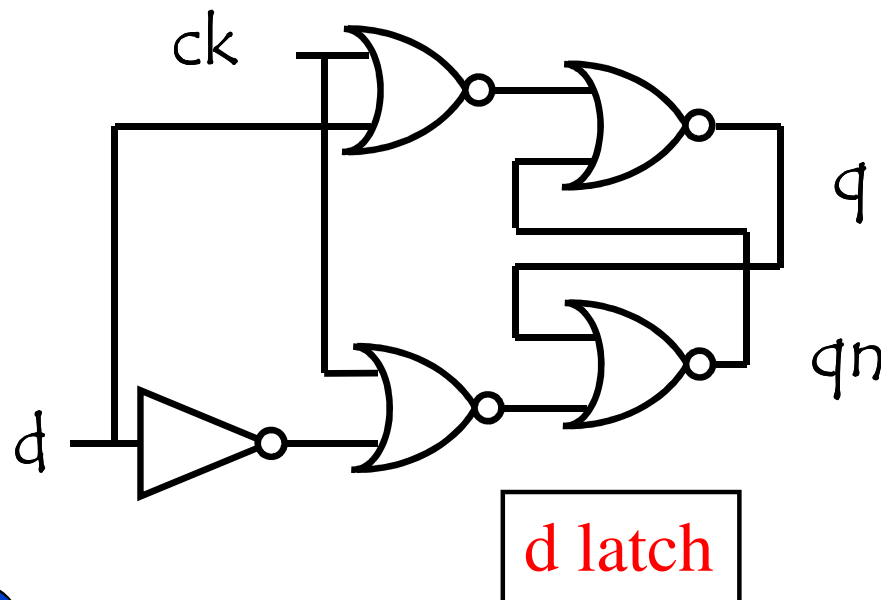

s	r	q	qn
0	1	0	1
1	0	1	0
1	1	0	0
0	0	q	qn



if $\bar{ck}.d = 1$ $s = 1$

if $\bar{ck}.\bar{d} = 1$ $r = 1$

CMOS Circuits

Synchronous Memory :



Write a data d when the clock $ck = 0$

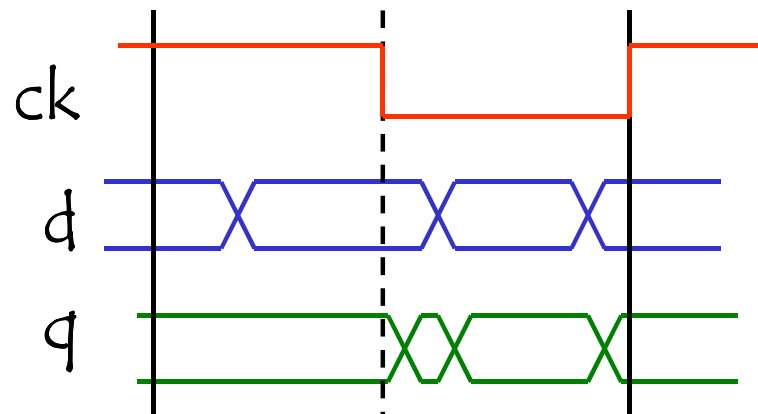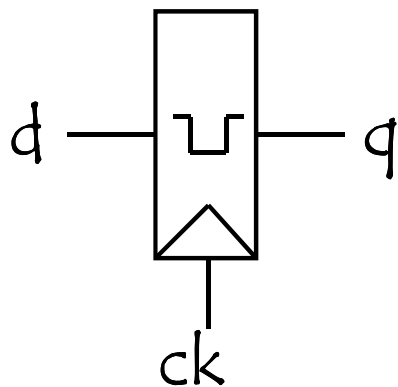

CMOS Circuits

Synchronous Memory :

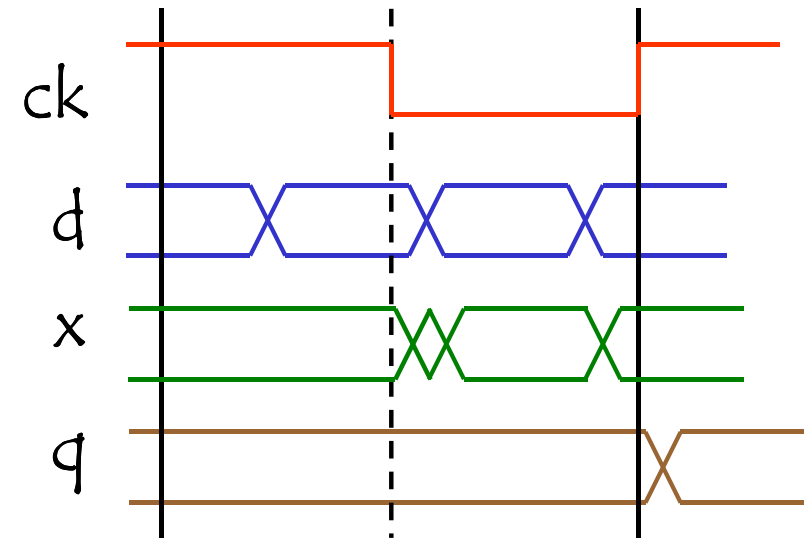
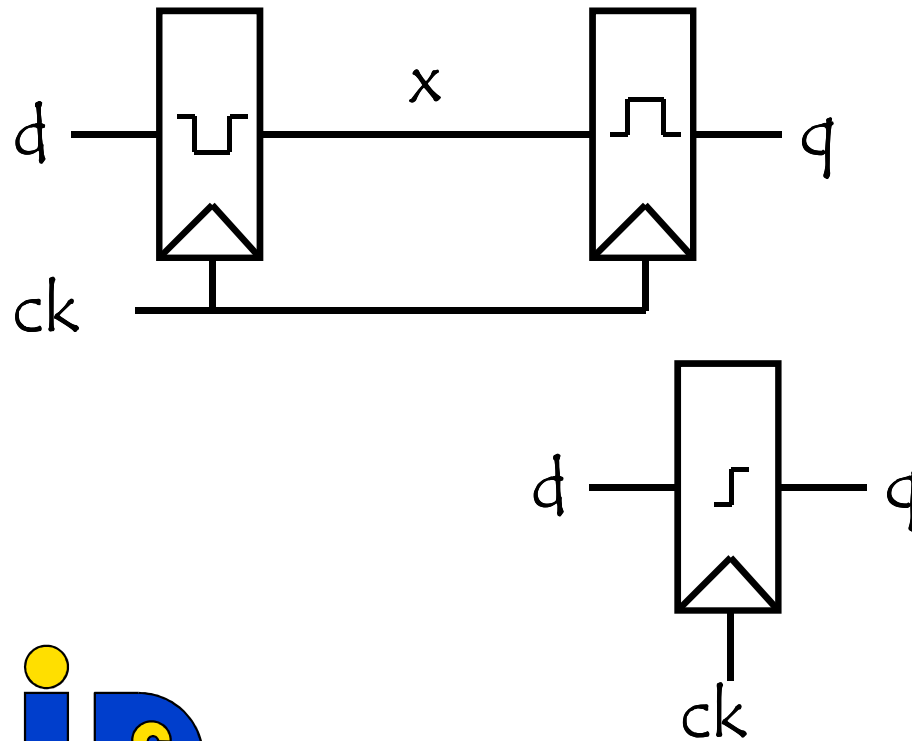
Write a data d on the rising **edge** of the clock ck



CMOS Circuits

Synchronous Memory :

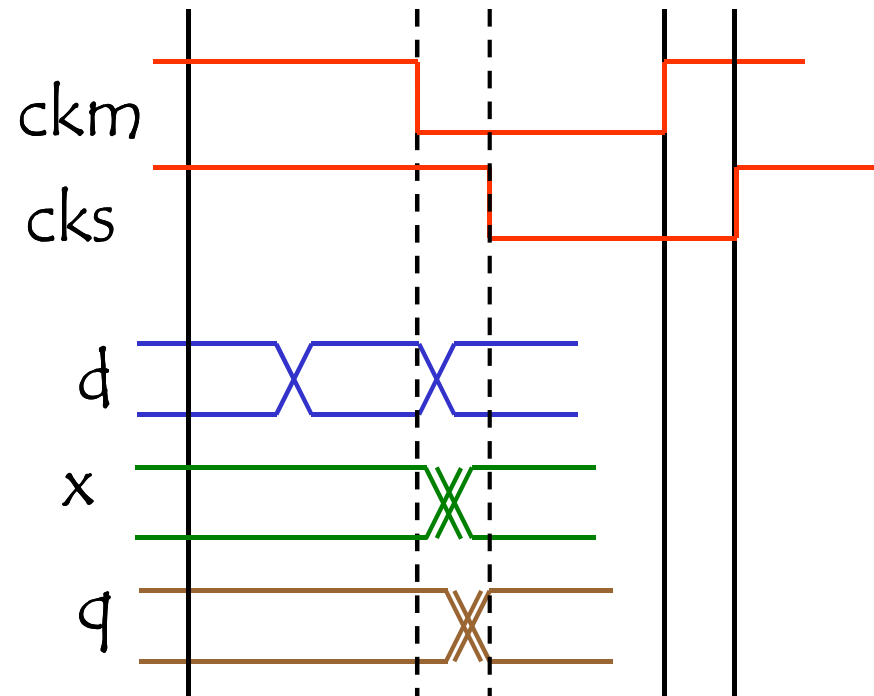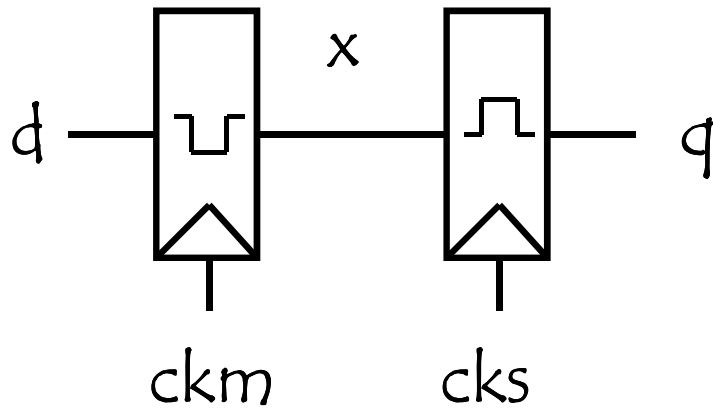
Write a data d on the rising **edge** of the clock ck



CMOS Circuits

Synchronous Memory :


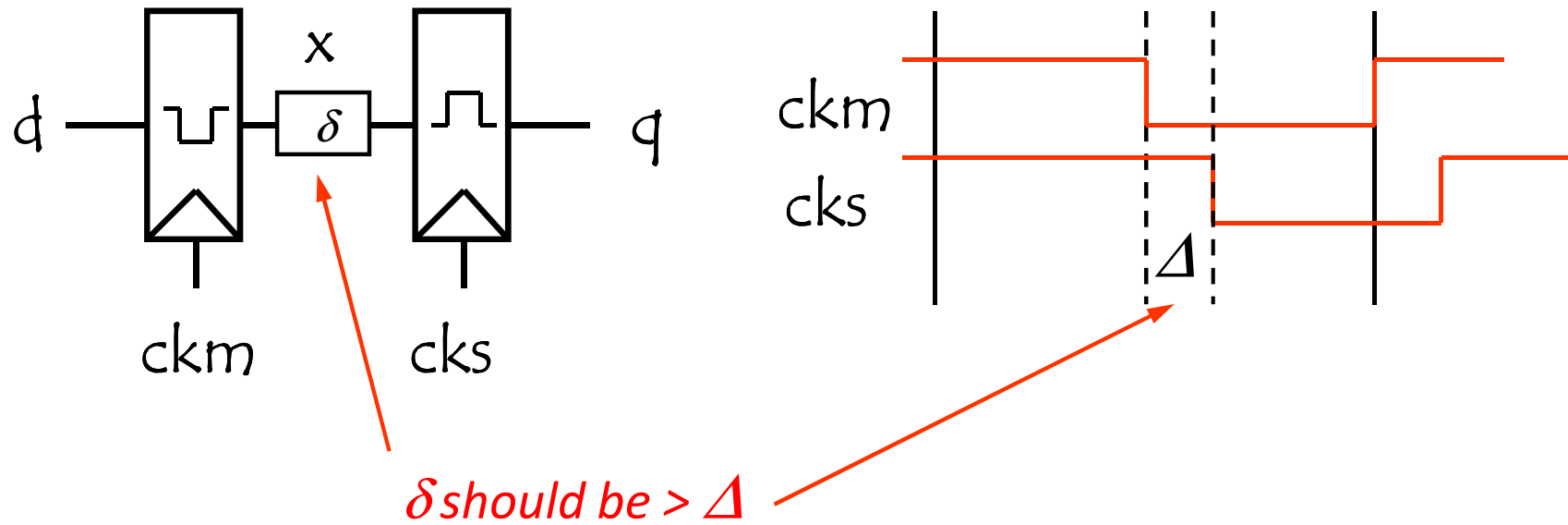
Write a data d on the rising **edge** of the clock ck



CMOS Circuits

Synchronous Memory :

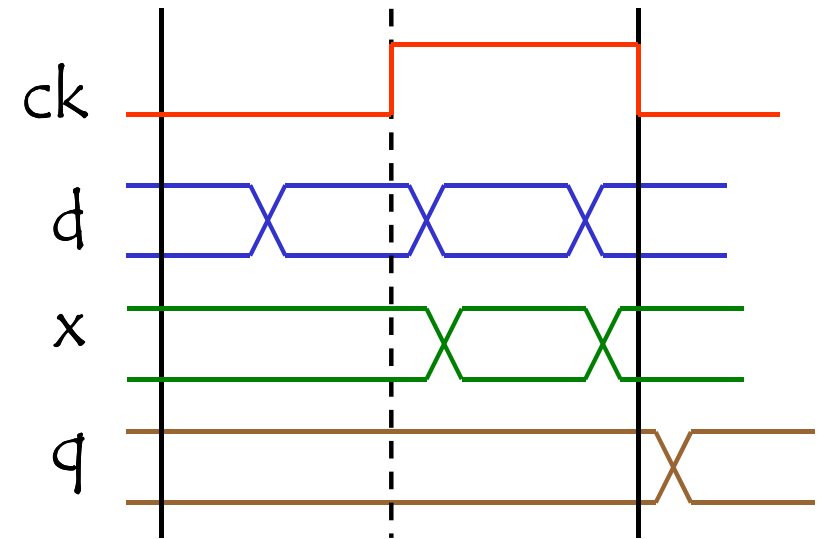
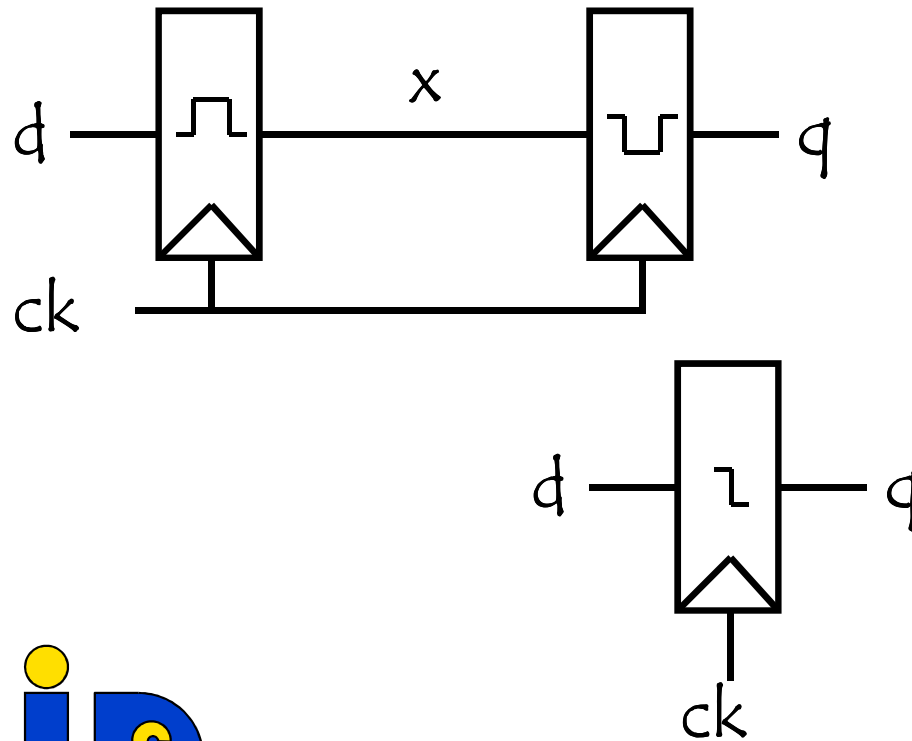
Write a data d on the falling **edge** of the clock ck



CMOS Circuits

Synchronous Memory :

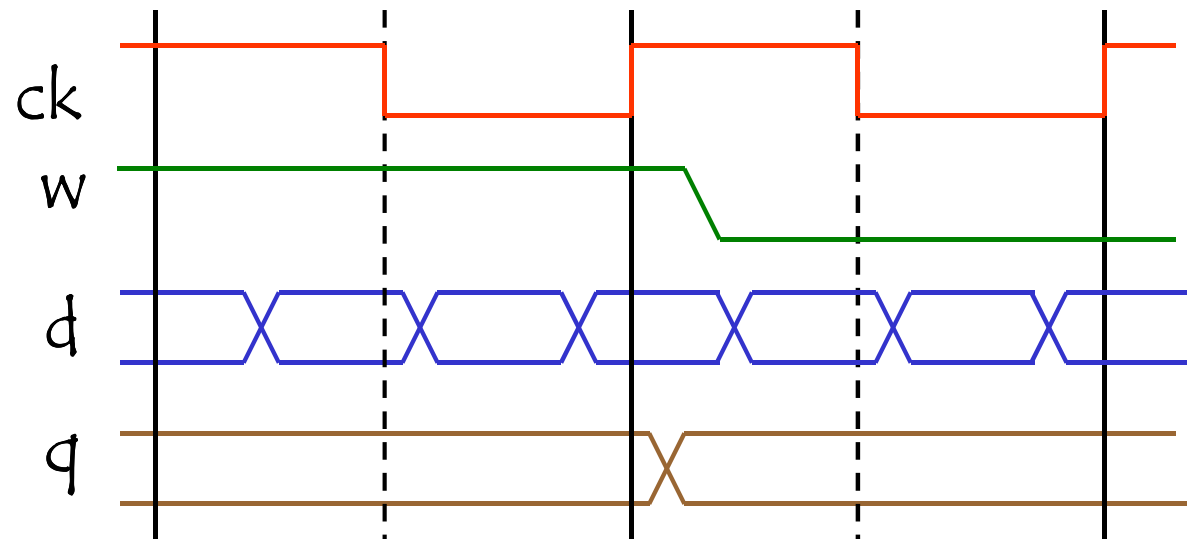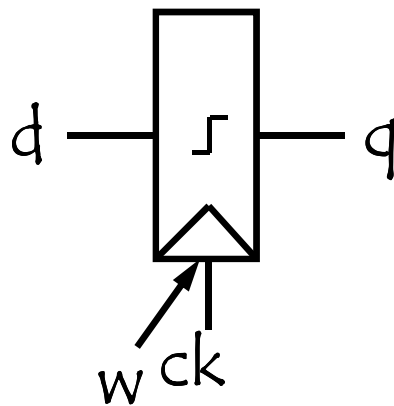Write a data d on the rising **edge** of the clock ck when a condition is true (write enable)



CMOS Circuits

Synchronous Memory :

Write a data d on the rising **edge** of the clock ck when a condition is true (write enable)

