

# Outline

- Digital CMOS design

- Arithmetic operators

  - Adders

  - Comparators


  - Shifters

  - Multipliers
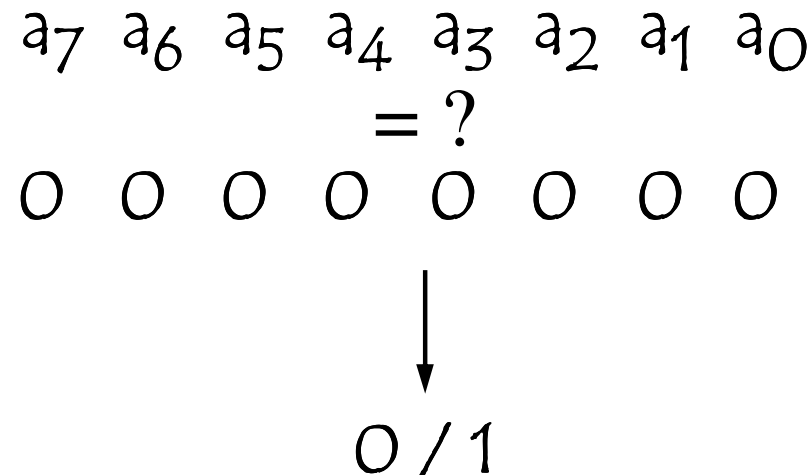
# Comparators

Comparing a natural number to a constant : =

Let consider a natural number  $a$  coded on 8 bits using Natural Binary Code



# Comparators

Comparing a natural number to zero :=

Boolean function

Null = 1 if

$$\bar{a}_7 \cdot \bar{a}_6 \cdot \bar{a}_5 \cdot \bar{a}_4 \cdot \bar{a}_3 \cdot \bar{a}_2 \cdot \bar{a}_1 \cdot \bar{a}_0 = 1$$

---


$$\text{Null} = a_7 + a_6 + a_5 + a_4 + a_3 + a_2 + a_1 + a_0$$



# Comparators

Comparing a natural number to zero : =


## Implementation

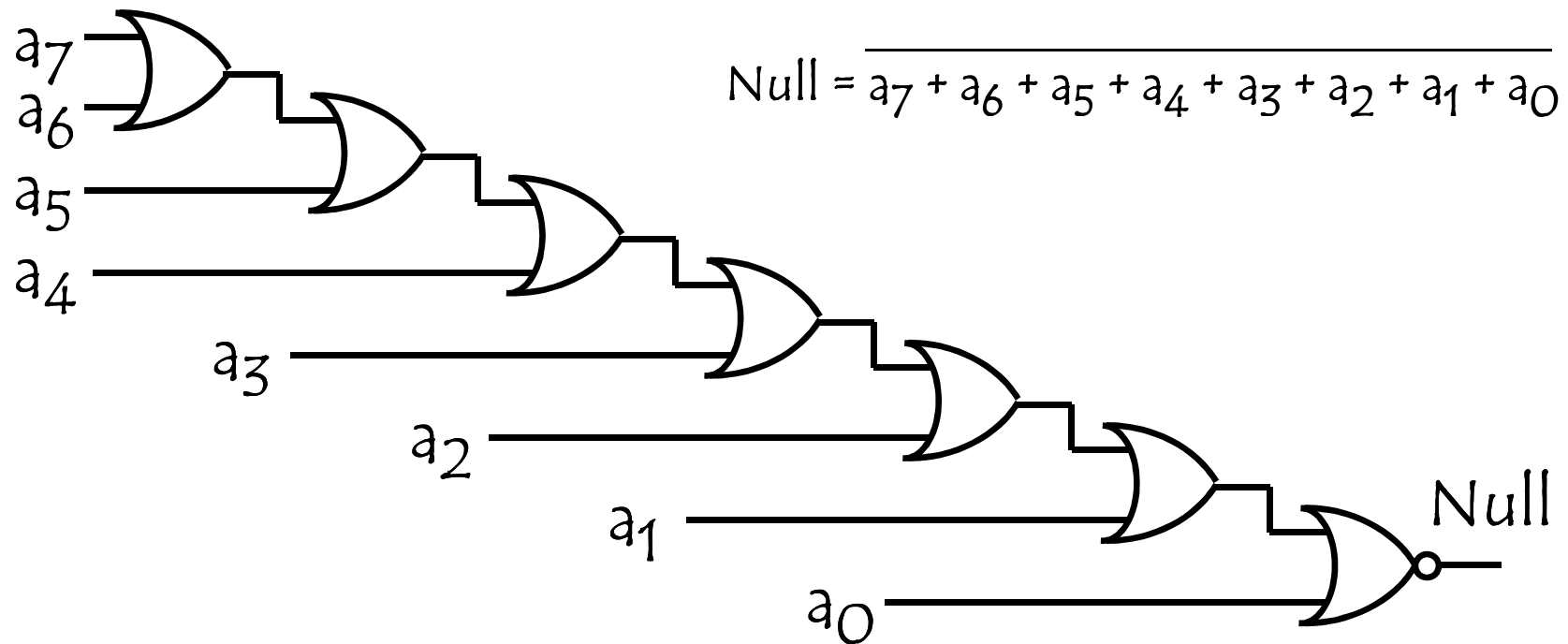

# Comparators

Comparing a natural number to zero :=


Implementation

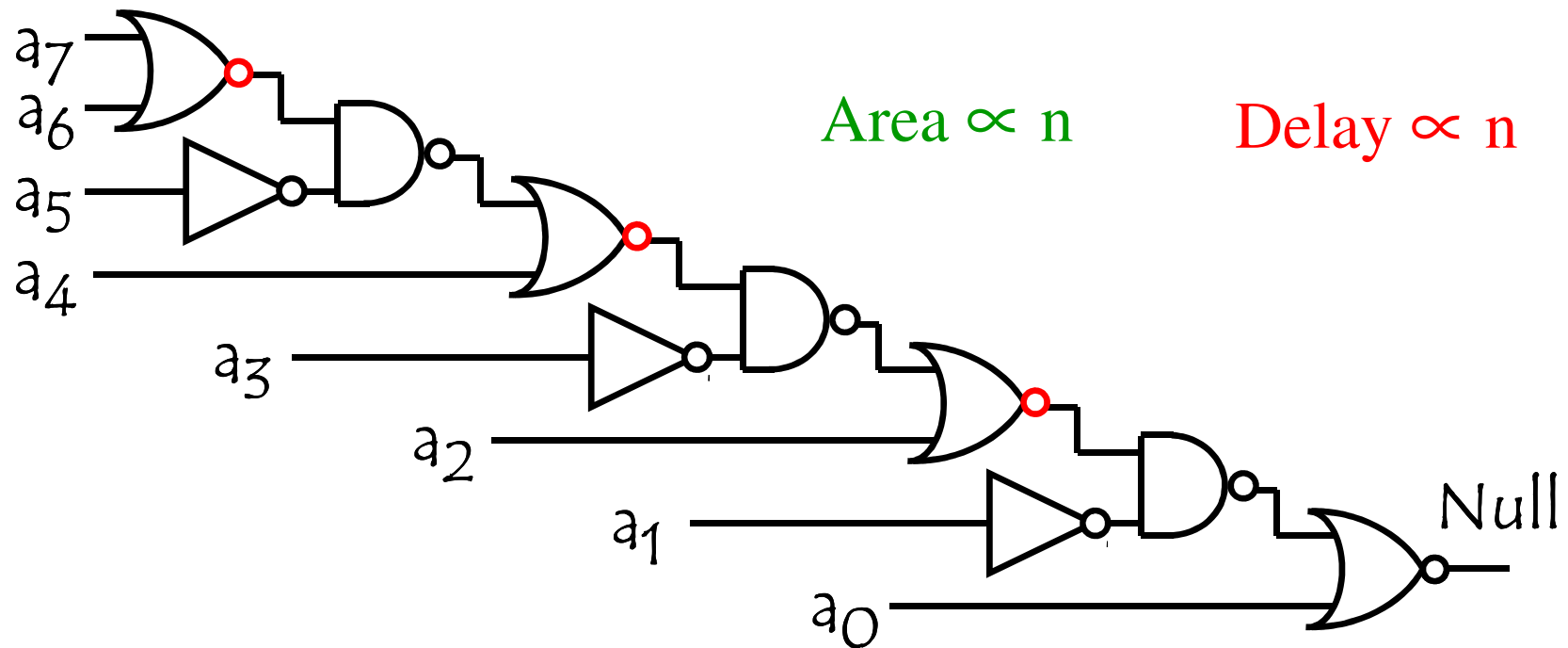

# Comparators

Comparing a natural number to zero : =


Implementation improvement

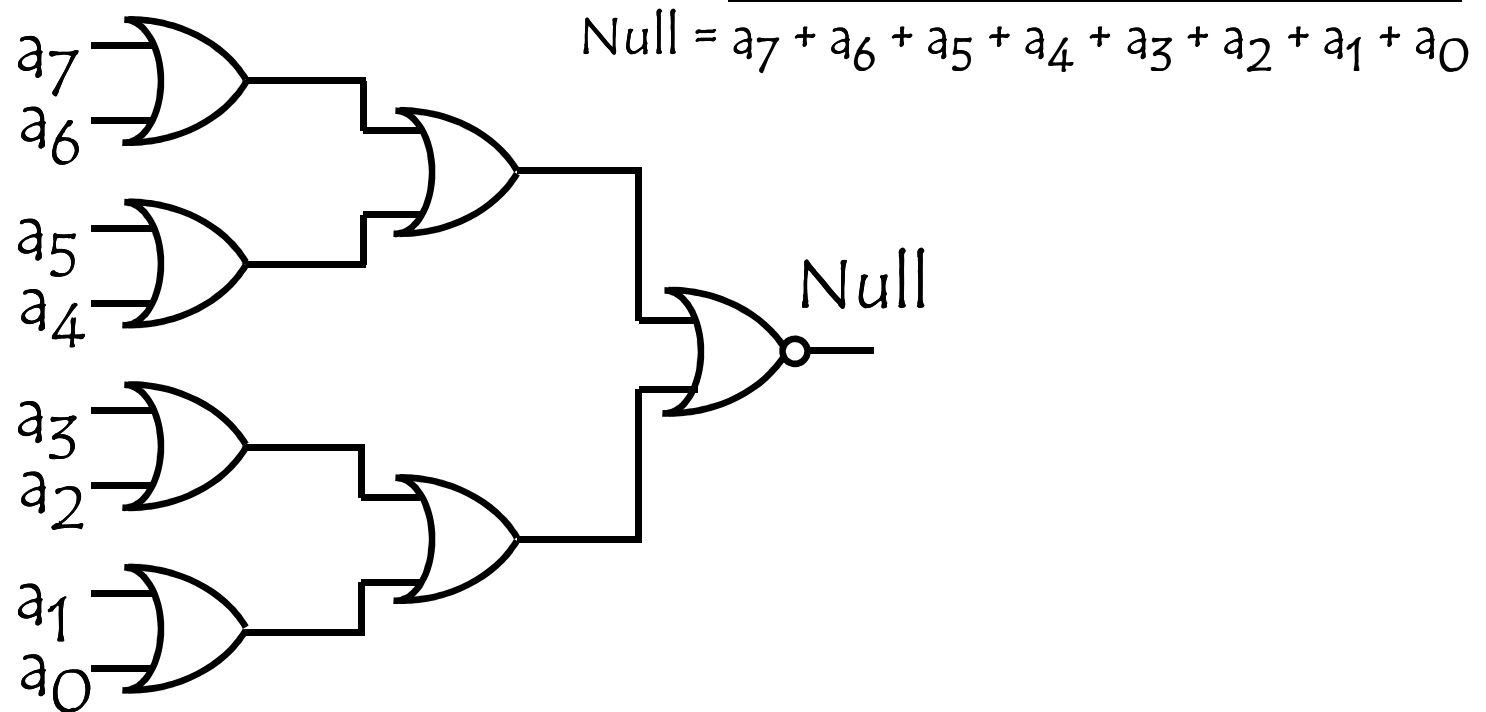

# Comparators

Comparing a natural number to zero :=

Implementation improvement

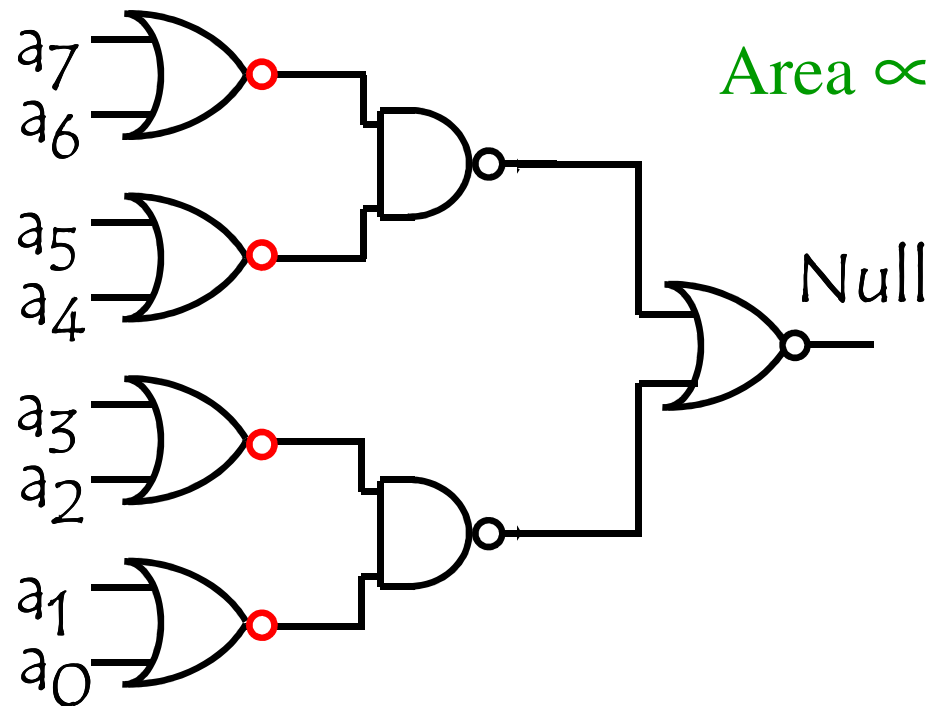

Area  $\propto n$  Delay  $\propto \log(n)$

# Comparators

Comparing two natural numbers : =

Let consider two natural numbers  $a$  and  $b$   
coded on 8 bits using Natural Binary Code

$$\begin{array}{cccccccc} a_7 & a_6 & a_5 & a_4 & a_3 & a_2 & a_1 & a_0 \\ & & & & = ? & & & \\ b_7 & b_6 & b_5 & b_4 & b_3 & b_2 & b_1 & b_0 \end{array}$$

↓

0 / 1



# Comparators

Comparing two natural numbers :=

Boolean function

a Equal b if :  $a_7=b_7$  and  $a_6=b_6$  and ... and  $a_0=b_0$

a Equal b if :  $\overline{(a_7 \oplus b_7)} \cdot \dots \cdot \overline{(a_0 \oplus b_0)} = 1$

Equal =  $\overline{(a_7 \oplus b_7)} + \dots + \overline{(a_0 \oplus b_0)}$

Equal =  $(e_7) + \dots + (e_0)$




# Comparators

Comparing two natural numbers :=

Implementation

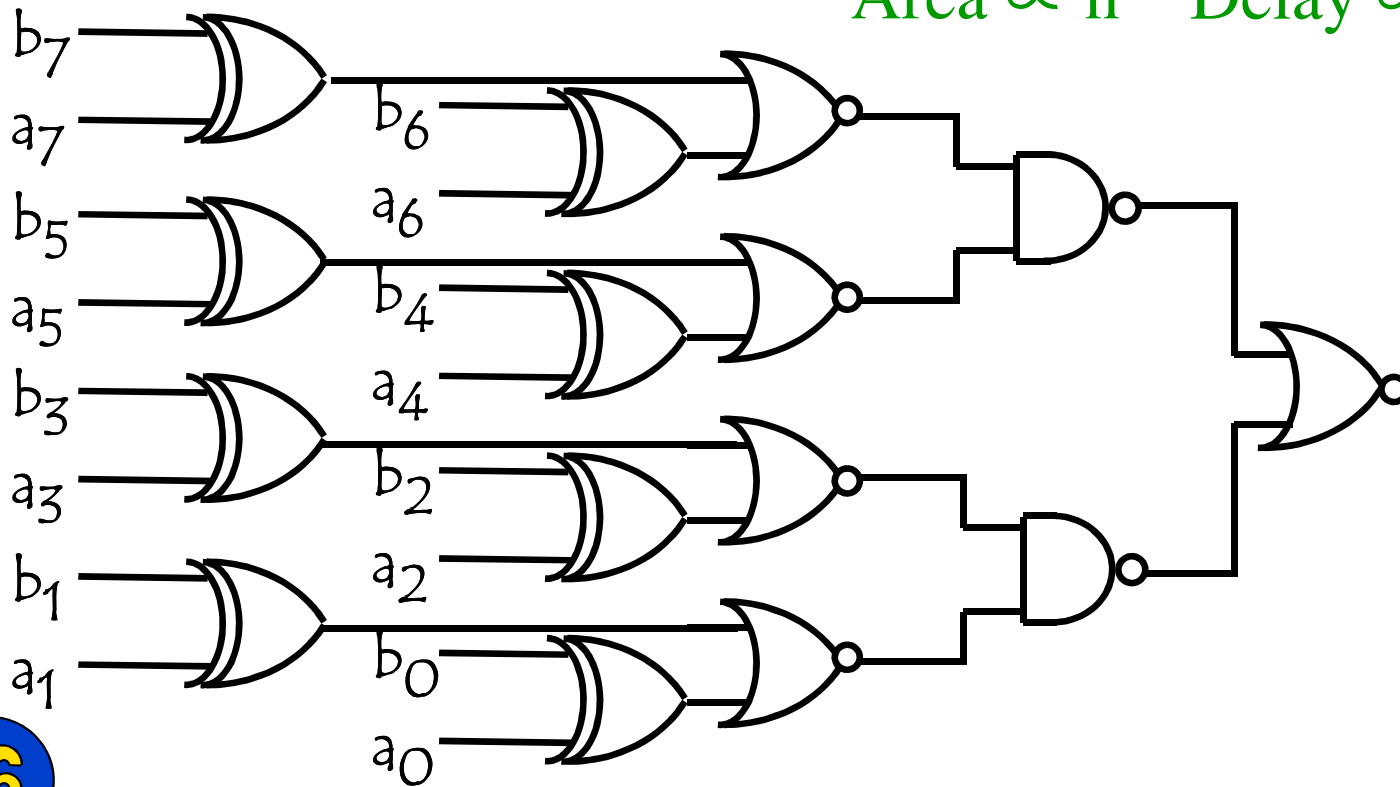
Area  $\propto n$  Delay  $\propto \log(n)$


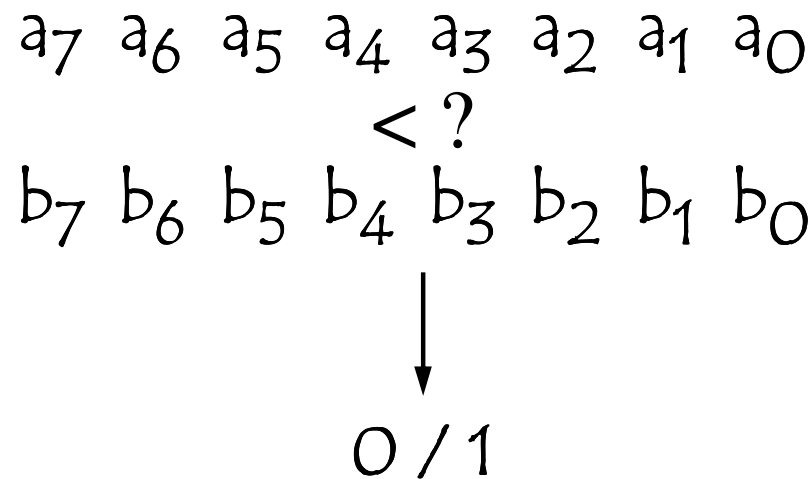
# Comparators

Comparing two natural numbers : <

Let consider two natural numbers  $a$  and  $b$   
coded on 8 bits using Natural Binary Code



# Comparators

Comparing two natural numbers : <

Boolean function

$a < b$  if :  $a_7 < b_7$  or  $(a_7 = b_7$  and  $(a_6 < b_6$  or  $(a_6 = b_6$  and ... )))

$a_7$	$a_6$	$a_5$	$a_4$	$a_3$	$a_2$	$a_1$	$a_0$	
				$< ?$				
$b_7$	$b_6$	$b_5$	$b_4$	$b_3$	$b_2$	$b_1$	$b_0$	
				↓				
				$0 / 1$				

# Comparators

Comparing two natural numbers : <

Boolean function


$a < b$  if :  $a_7 < b_7$  or ( $a_7 = b_7$  and ( $a_6 < b_6$  or ( $a_6 = b_6$  and ... )))

$a < b$  if :  $\overline{a_7}b_7 + ((\overline{a_7 \oplus b_7}) \cdot (\overline{a_6}b_6 + ((\overline{a_6 \oplus b_6}) \cdot \dots )))$



# Comparators

Comparing two natural numbers : <

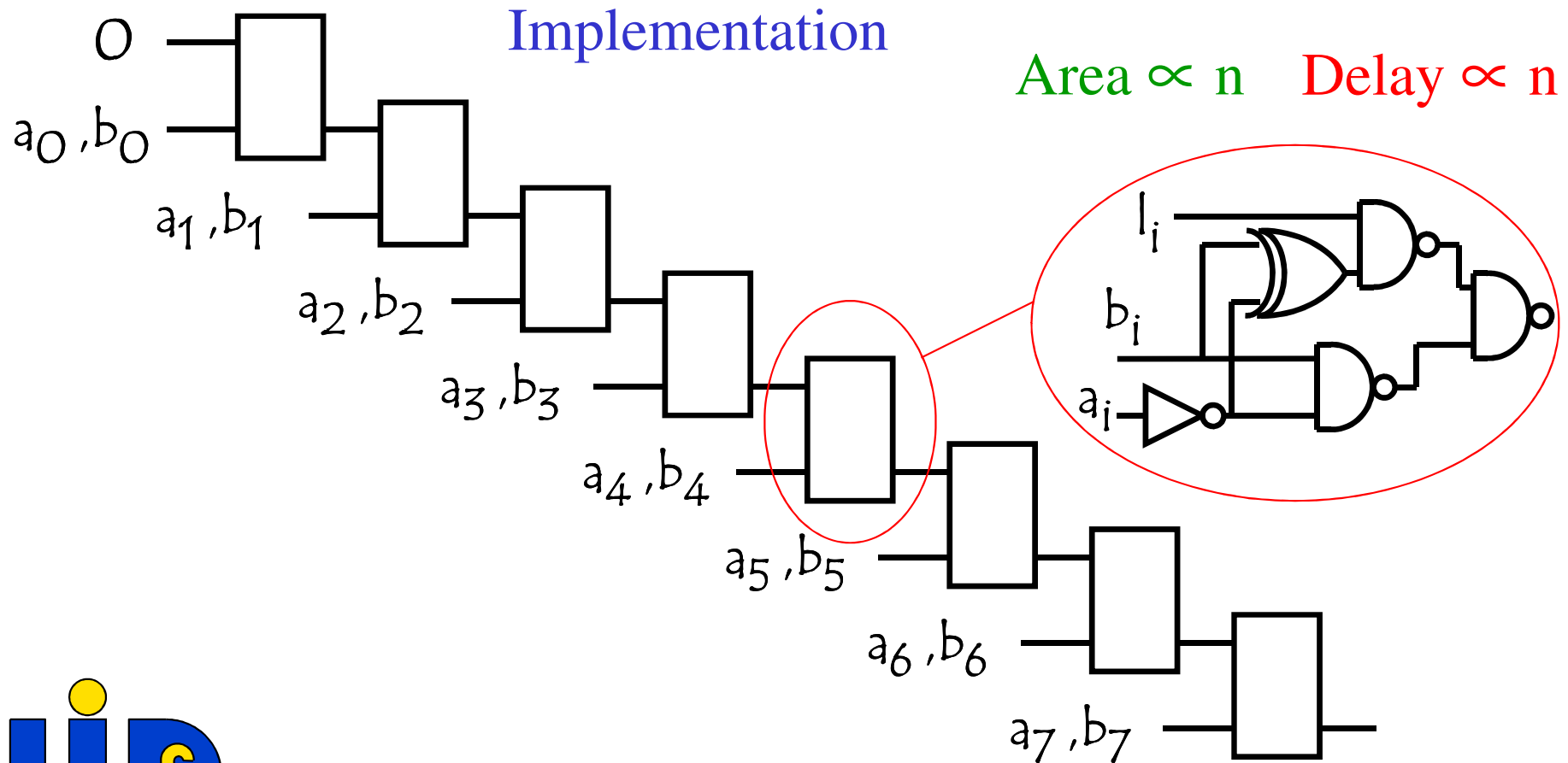

# Comparators

Comparing two natural numbers : <

## Implementation Improvement

$a < b$  if :  $a_7 < b_7$  or ( $a_7 = b_7$  and ( $a_6 < b_6$  or ( $a_6 = b_6$  and ... )))

$a < b$  if :  $\overline{a_7}b_7 + ((\overline{a_7 \oplus b_7}) \cdot (\overline{a_6}b_6 + ((\overline{a_6 \oplus b_6}) \cdot \dots )))$

$$\overline{a_i}b_i + (\overline{a_i \oplus b_i}) \cdot l_i$$


Propagation  
Generation




# Comparators

Comparing two natural numbers : <

## Implementation Improvement

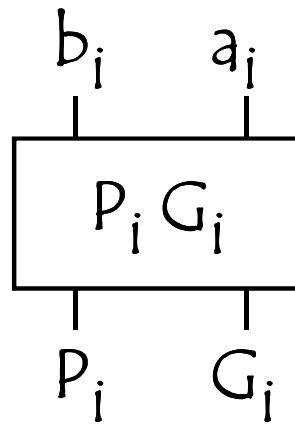

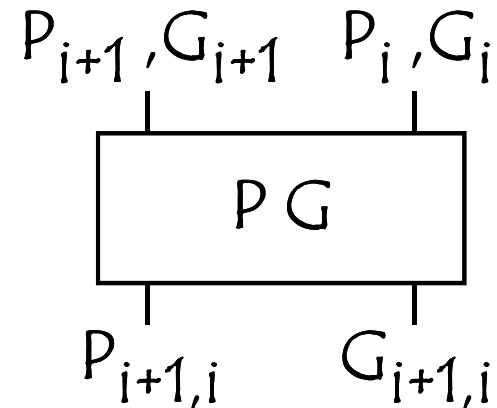
$$G_i = \bar{a}_i b_i$$
$$P_i = \bar{a}_i \oplus b_i$$



$$G_{i+1,i} = G_{i+1} + G_i \cdot P_{i+1}$$
$$P_{i+1,i} = P_i \cdot P_{i+1}$$



# Comparators

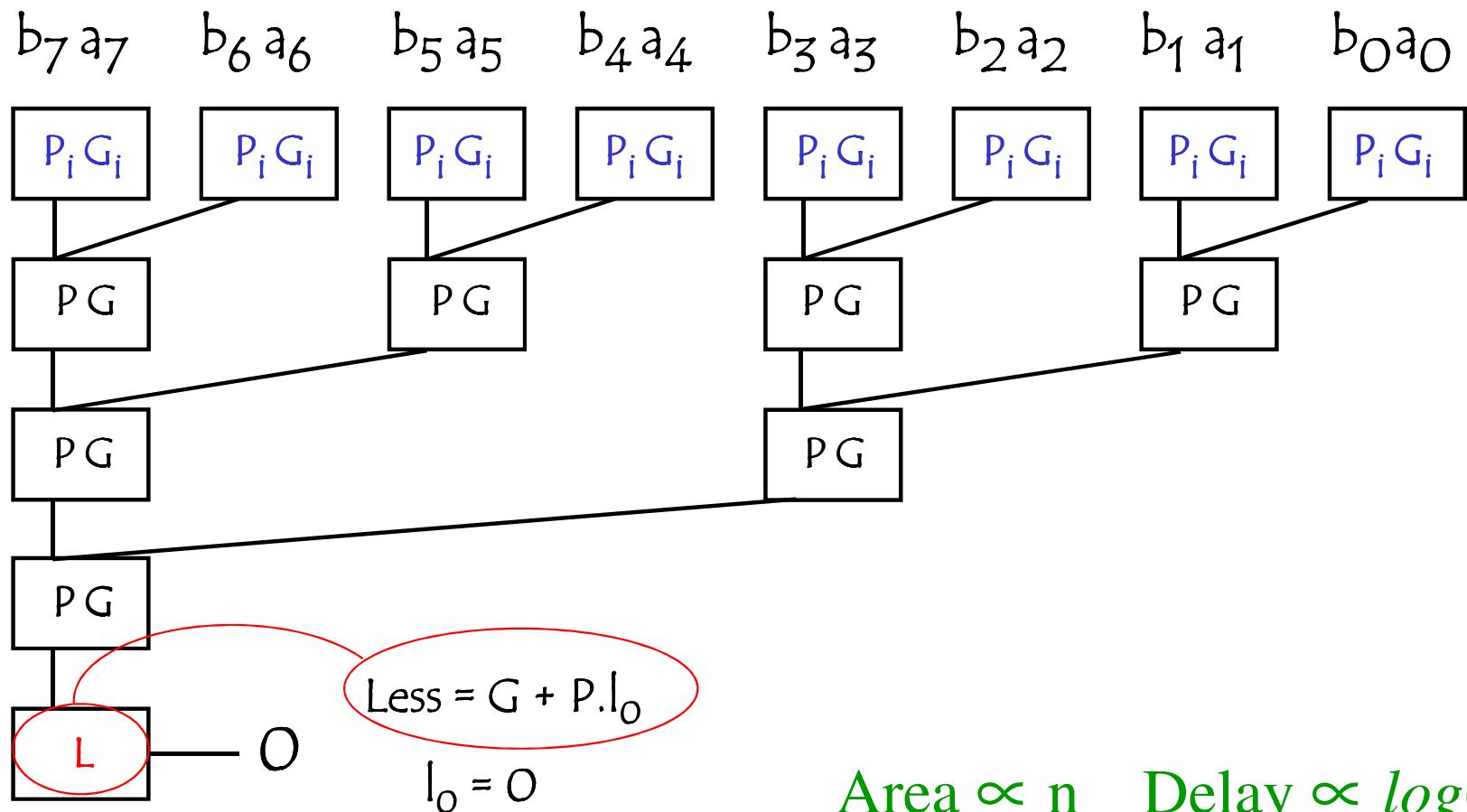

Area  $\propto n$  Delay  $\propto \log(n)$

# Comparators

