

# Outline

## ■ Digital CMOS design


## ■ Arithmetic operators

- Adders
- Comparators
- Shifters
- Multipliers

# Shifters
 
## Shifting a value


Let consider a value  $a$  coded on 8 bits  
 $a$  can be shifted to the left by  $n$  positions ( $0 \leq n < 8$ )



# Shifters
 
## Shifting a value


Let consider a value  $a$  coded on 8 bits  
 $a$  can be shifted to the right by  $n$  positions ( $0 \leq n < 8$ )  
logic



# Shifters
 
## Shifting a value

Let consider a value  $a$  coded on 8 bits  
 $a$  can be shifted to the right by  $n$  positions ( $0 \leq n < 8$ )  
arithmetic




For a **relative** number, shift right is a division by  $2^n$

# Shifters
 
## Shifting a value


Let consider a value  $a$  coded on 8 bits  
 $a$  can be rotated to the left by  $n$  positions ( $0 \leq n < 8$ )



# Shifters
 
## Shifting a value


Let consider a value  $a$  coded on 8 bits  
 $a$  can be rotated to the right by  $n$  positions ( $0 \leq n < 8$ )



# Shifters

## Shifting a value

### Implementation (left shifter)

 

# Shifters

Shifting a value by 1 position to the left

Boolean function

$b$  coded on 1 bit

If  $b = 0$

$$s_i = a_i$$

else


$$s_i = a_{i-1} \text{ assuming } a_{-1} = 0$$

$$s_i = b.a_{i-1} + \bar{b}.a_i \quad \rightarrow \quad \text{2-input Multiplexer}$$

# Shifters

Shifting a value by 1 position to the left

## Implementation

 

# Shifters

Shifting a value by  $b$  positions to the left

$b$  may be  $0 = 000$

$1 = 001$

$2 = 010$

$3 = 011$

$4 = 100$

$5 = 101$


$6 = 110$

$7 = 111$

A combination of  $2^2$ ,  $2^1$ ,  $2^0$


# Shifters

Shifting a value to the left

 

# Shifters



Rotate a value to the left

 

# Shifters

Shift / Rotate a value to the left

*shift-left*

  

# Shifters


Shifting a value

Rotate left by 2

$$6 = -2$$

=  
Rotate right by 6


$$110 = \overline{010} + 1$$

 

# Shifters

## Shifting a value

### Implementation (right shifter)

 

# Shifters

Shifting a value

Rotate right by  $b$


=  
Rotate left by  $-b$

=  
Rotate left by  $(\bar{b} + 1)$

=  
Rotate left by  $\bar{b}$  followed by a 1 position rotate



# Shifters

Rotate a value to the **right**

 


# Shifters

Rotate a value to the **left / right**

  


# Shifters

Shift logic a value to the right

 


# Shifters

Shift / Rotate a value to the right

 


 shift-r-log.  
(shift-r-ari .  $a_{i.}$  +  
shift-r-ari .  $a_7$ )


 
# Shifters

Shift / Rotate a value to the left / right



# Shifters

Shift / Rotate a value to the left / right *optimized*

