

Outline

■ Digital CMOS Design

■ Arithmetic Operators

- Adders
- Comparators
- Shifters
- Multipliers

Multipliers


Two natural numbers a and b coded on n bits

the result of $a \times b$ is coded on $2n$ bits

Classic method as learned in primary school




Multipliers

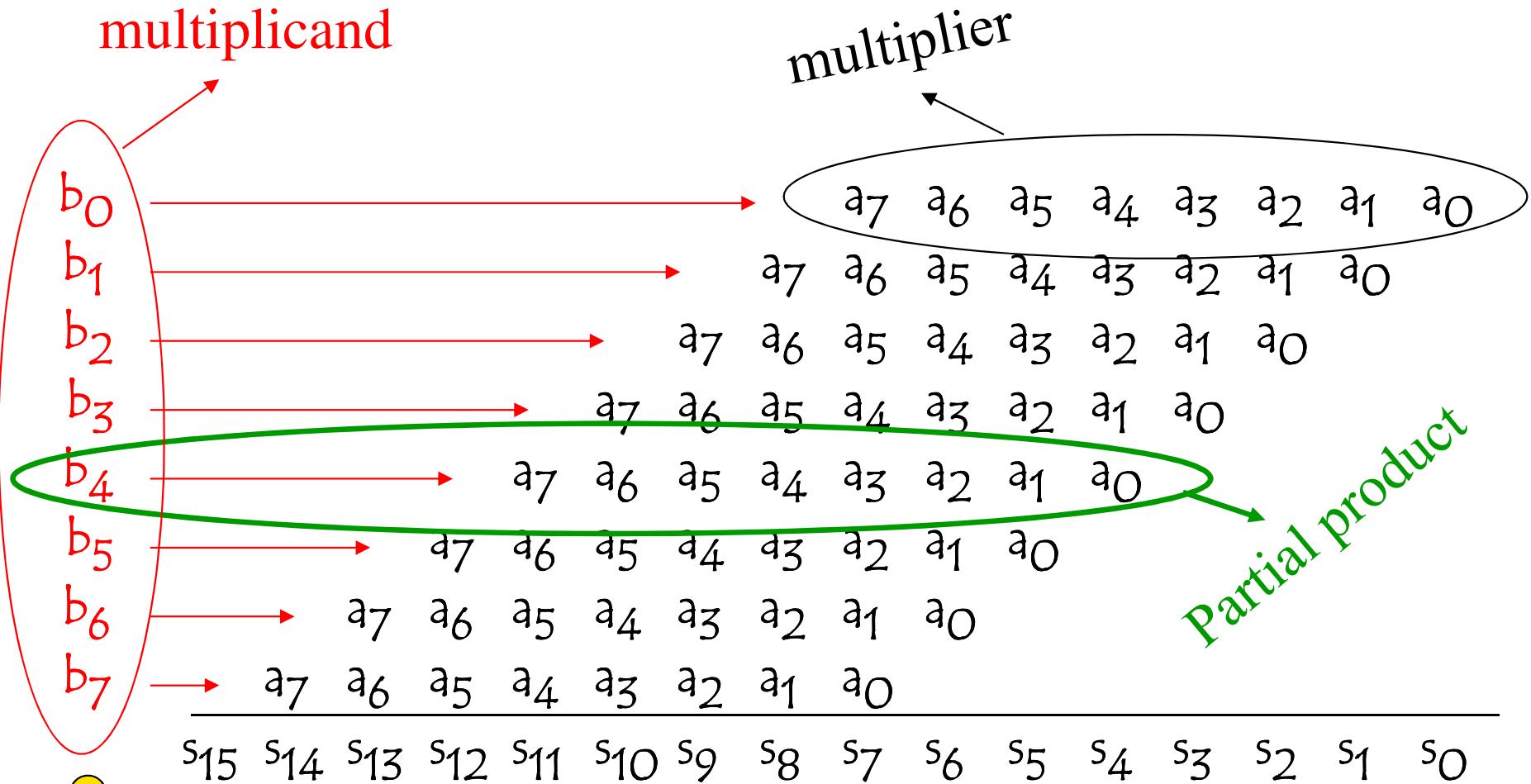


Multipliers

Implementation : sequential multiplier

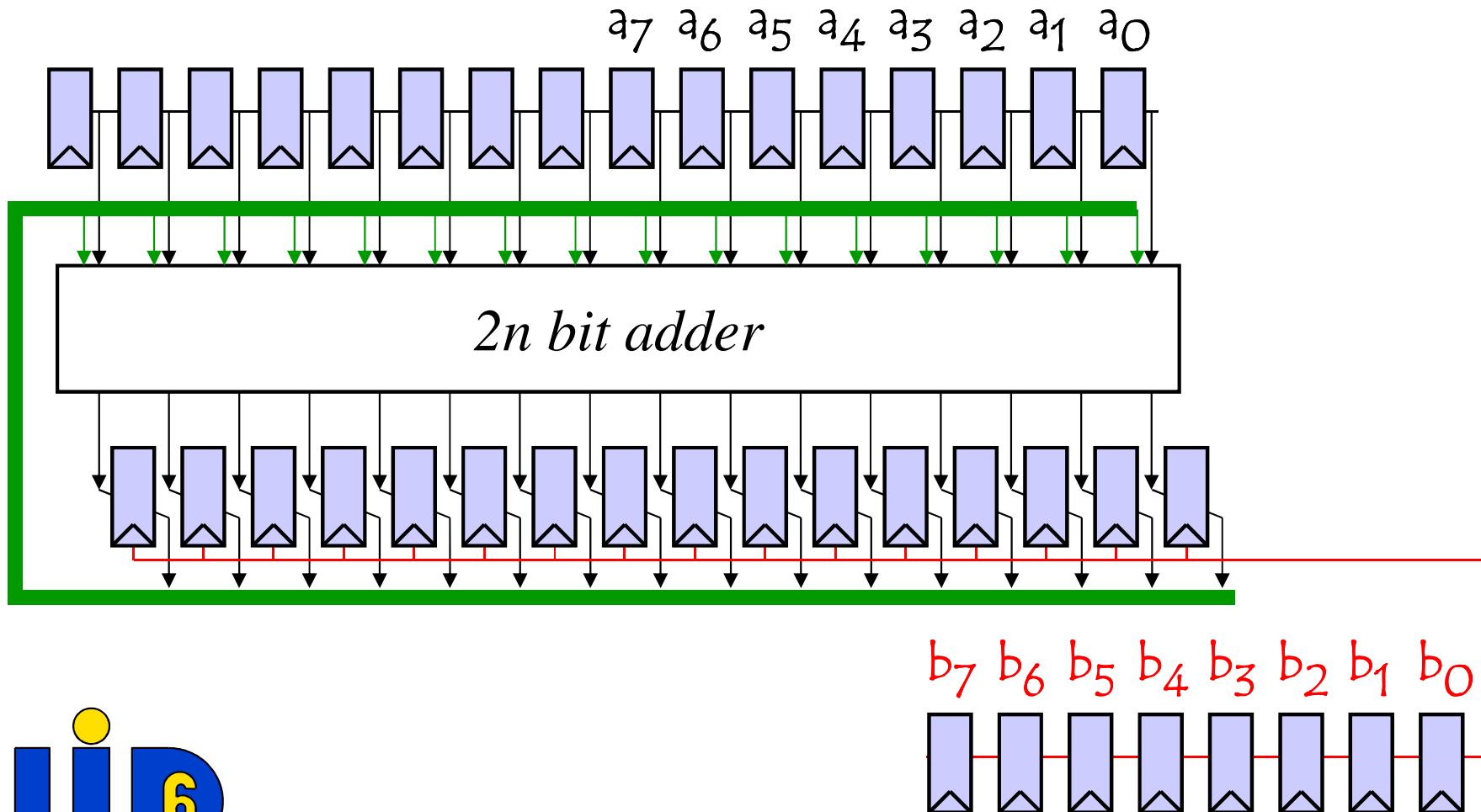


Multipliers

Implementation : sequential multiplier

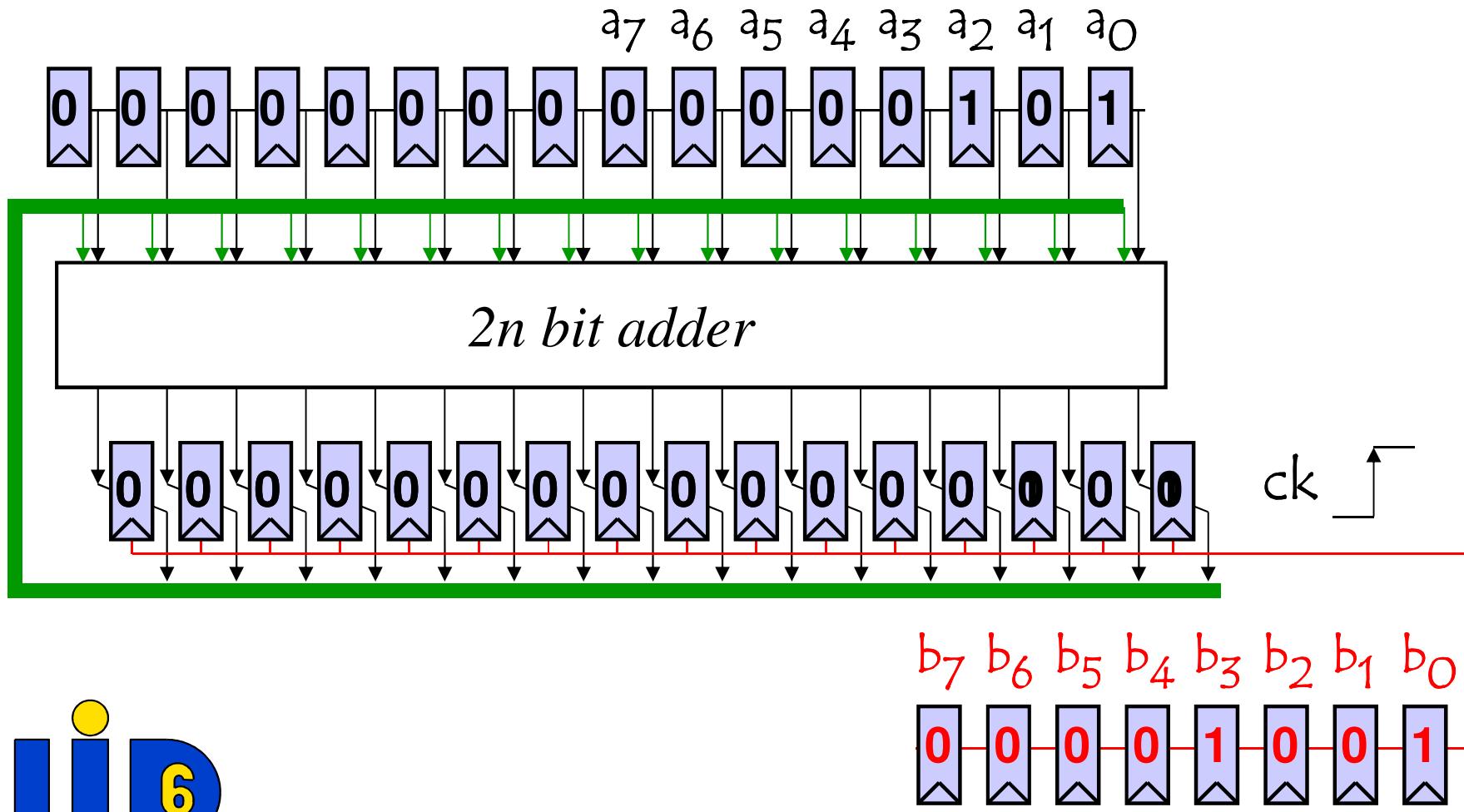


Multipliers

Implementation : sequential multiplier

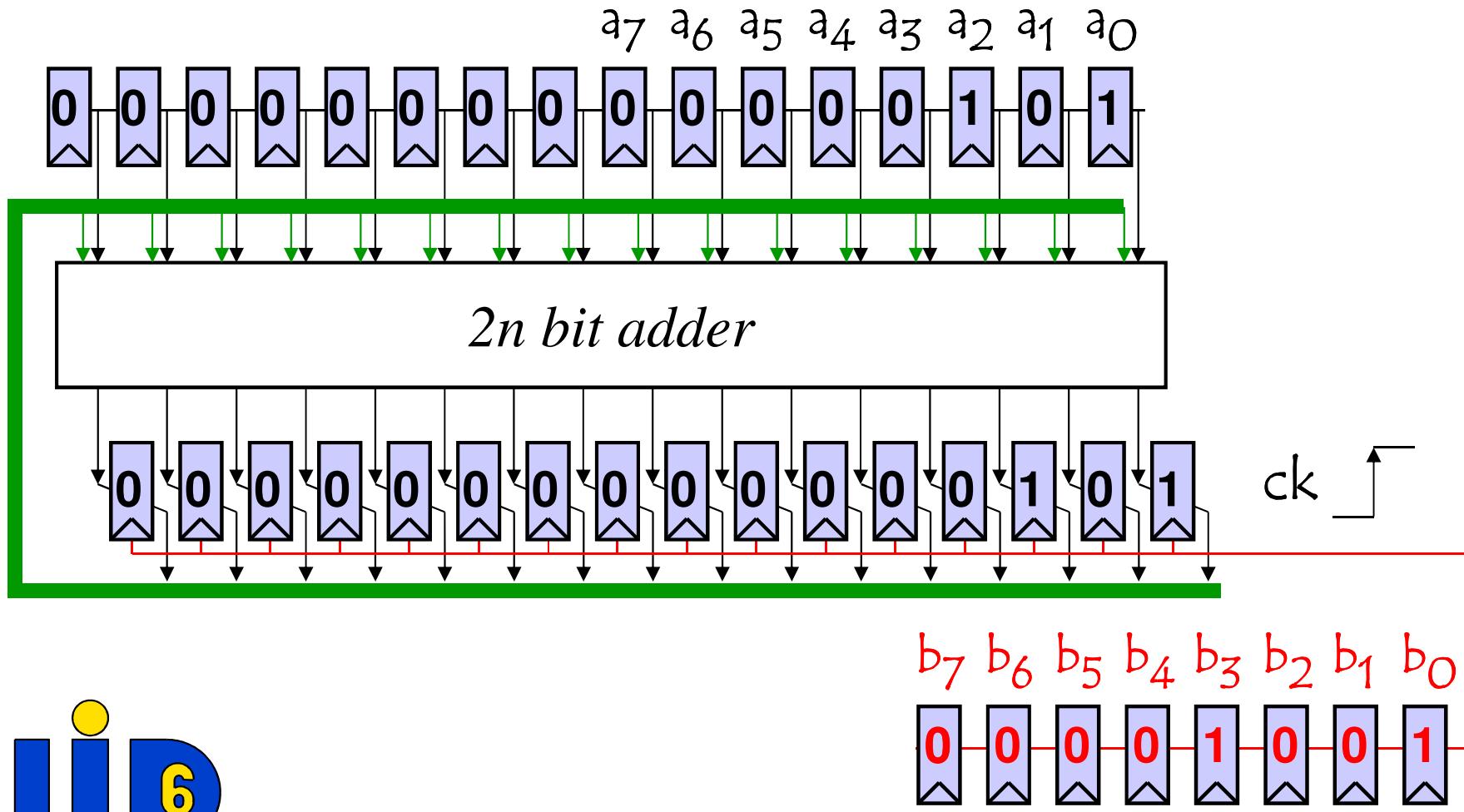


Multipliers

Implementation : sequential multiplier

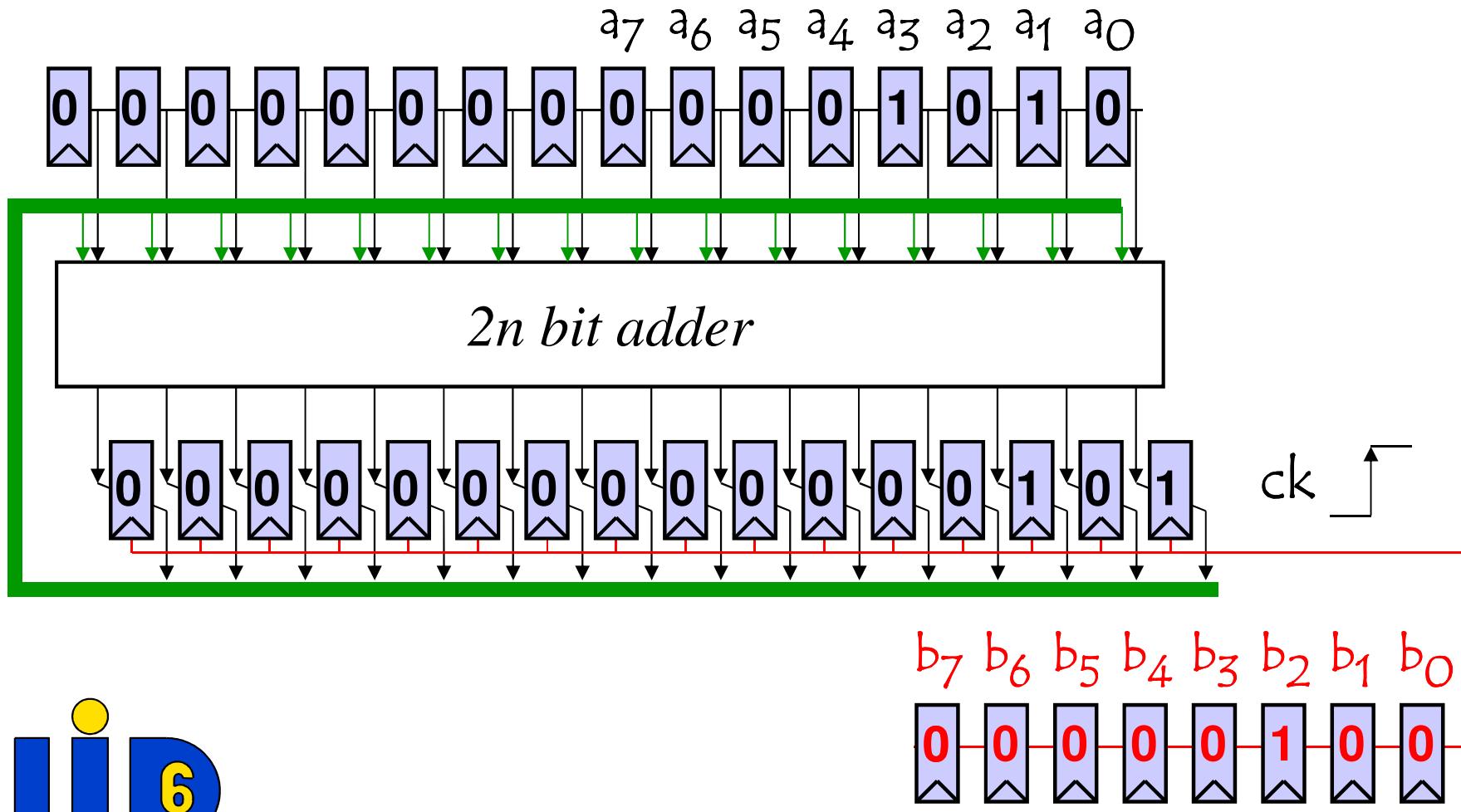


Multipliers

Implementation : sequential multiplier

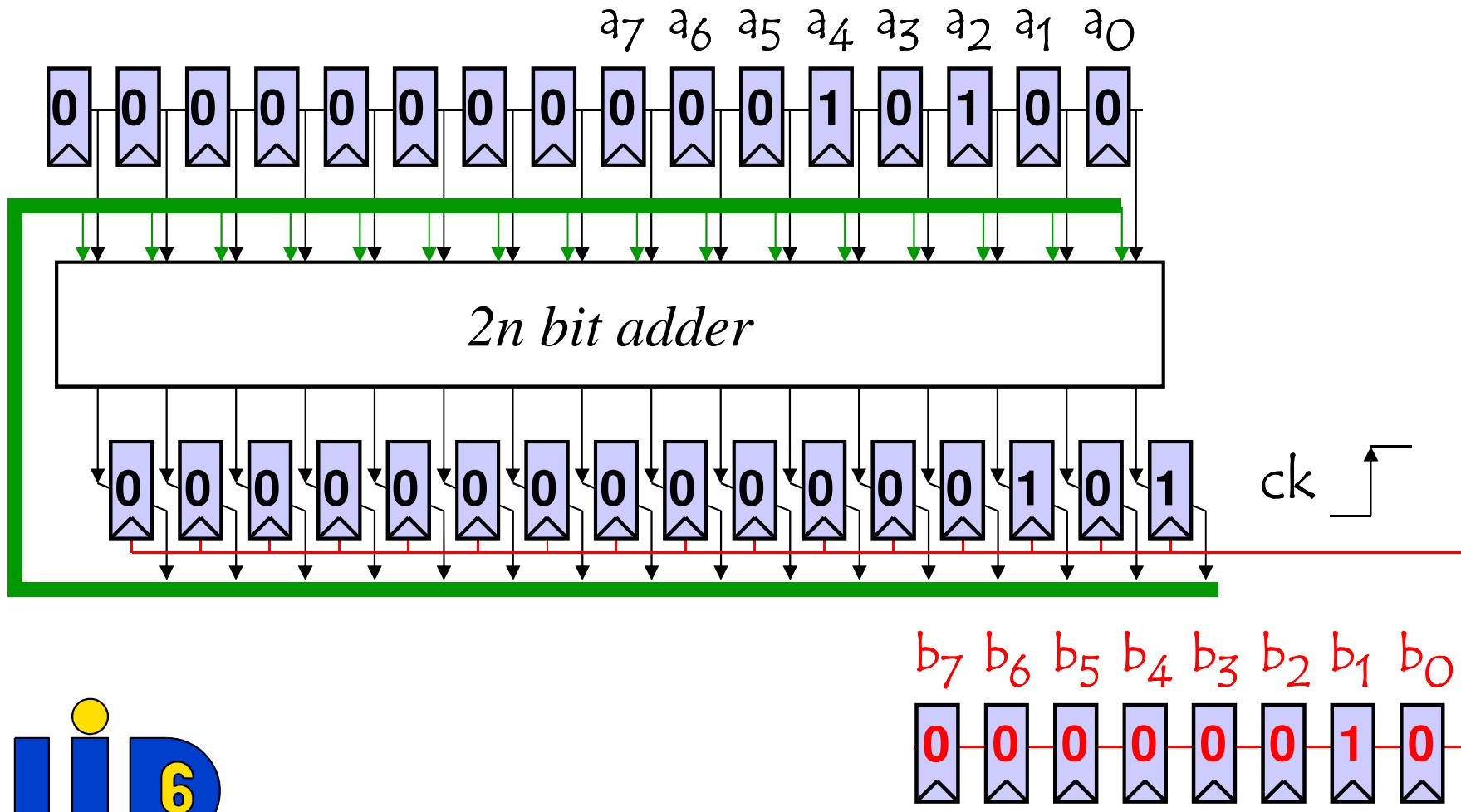


Multipliers

Implementation : sequential multiplier

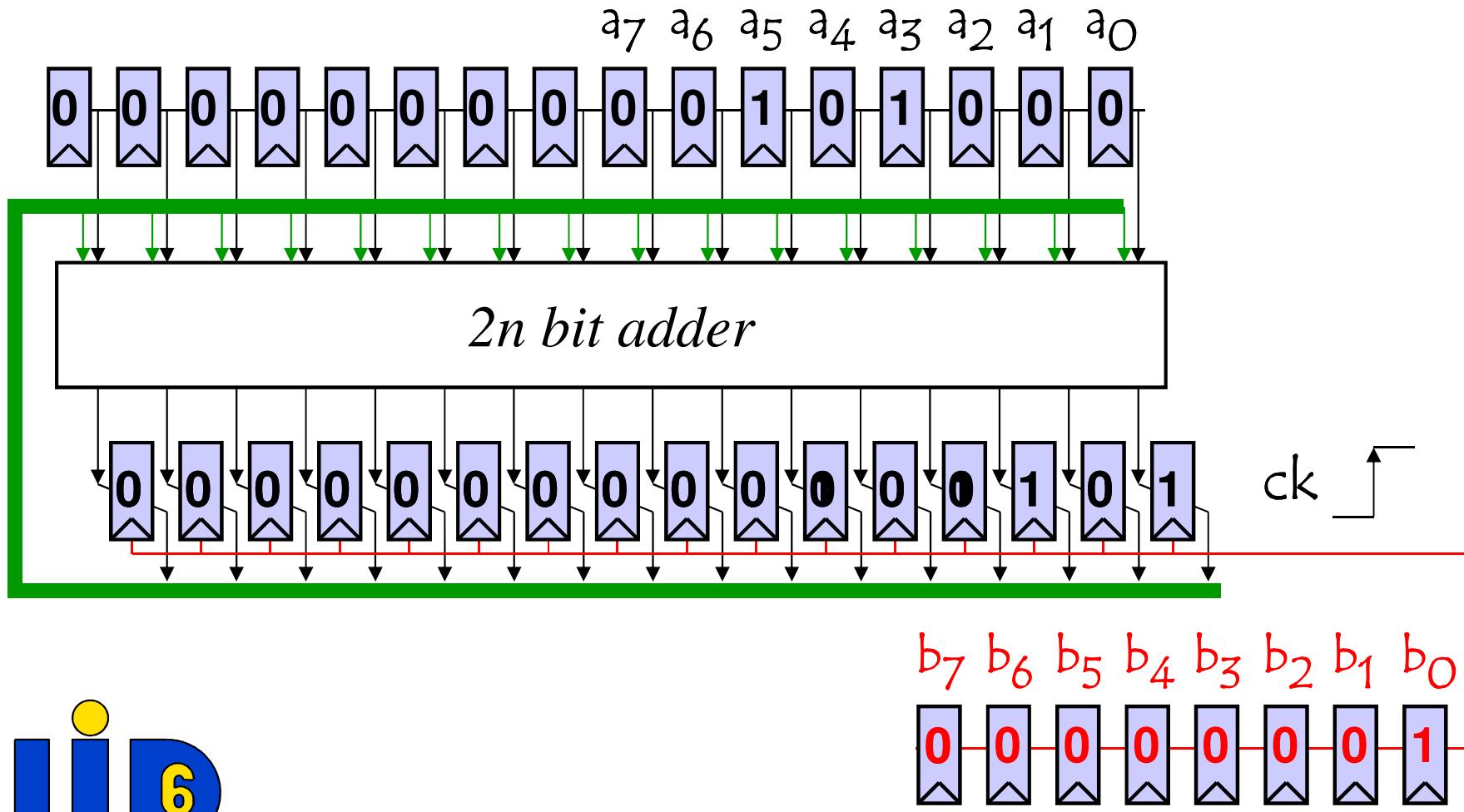

Multipliers


Implementation : parallel multiplier

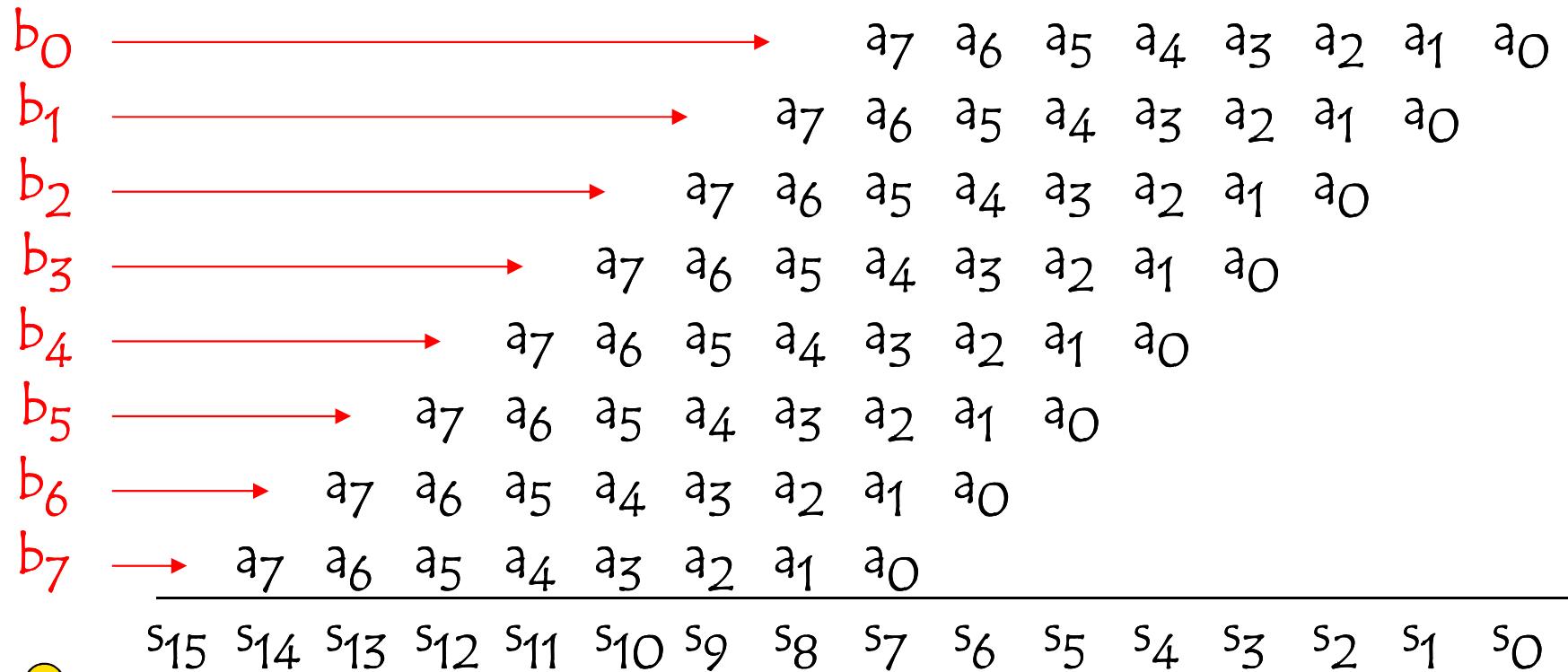

Multipliers

Implementation : parallel multiplier

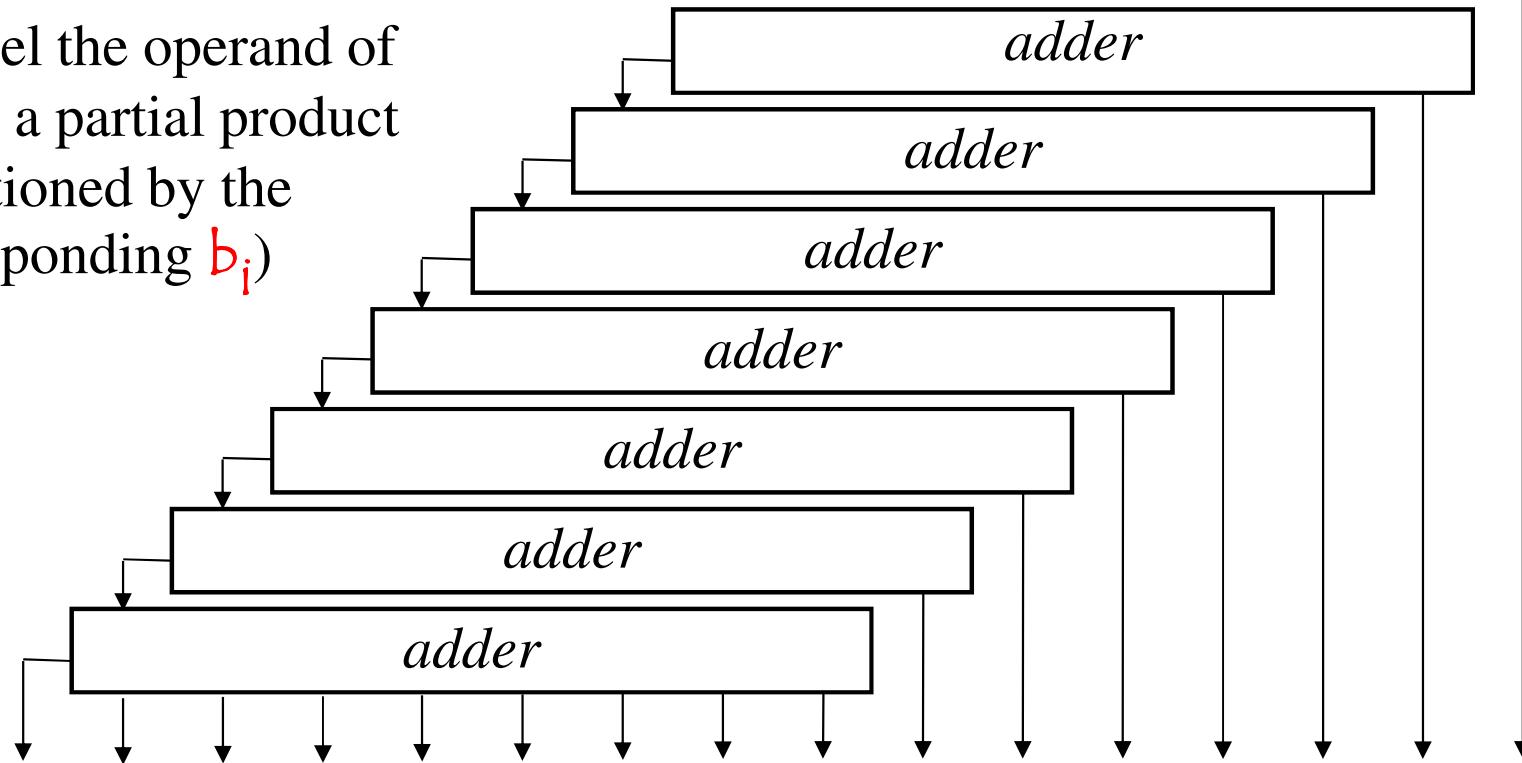At each level the operand of the adder is a partial product (conditioned by the corresponding b_i)



Multipliers


Implementation : parallel multiplier

Improvement : Reduce the number of partial products

$$x = \sum_{i=0}^{n-1} x_i \times 2^i \quad x_i \in \{0, 1\}$$

$$x = \sum_{i=0}^{n/2-1} (x_{2i} + 2x_{2i+1}) \times 2^{2i}$$

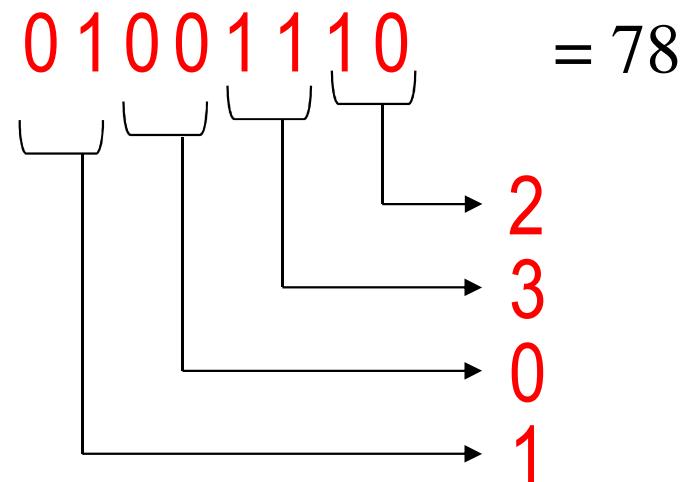half less terms \Rightarrow
half less partial products



$$x = 2 \times 2^0 + 3 \times 2^2 + 0 \times 2^4 + 1 \times 2^6 = 78$$

Multipliers

Implementation : parallel multiplier

Improvement : Reduce the number of partial products

$$x = \sum_{i=0}^{n-1} x_i \times 2^i \quad x = x_0 \times 2^0 + x_1 \times 2^1 +$$
$$x_2 \times 2^2 + x_3 \times 2^3 +$$
$$x_4 \times 2^4 + x_5 \times 2^5 +$$
$$x_6 \times 2^6 + x_7 \times 2^7$$

$$x = (x_0 + x_1 \times 2) \times 2^0 +$$
$$(x_2 + x_3 \times 2) \times 2^2 +$$
$$(x_4 + x_5 \times 2) \times 2^4 +$$
$$(x_6 + x_7 \times 2) \times 2^6$$



Multipliers

Implementation : parallel multiplier

Improvement : Reduce the number of partial products

$$x = \sum_{i=0}^{n-1} x_i \times 2^i \quad x_i \in \{0, 1\}$$

$$x = \sum_{i=0}^{n/2-1} (x_{2i} + 2x_{2i+1}) \times 2^{2i} \quad \in \{0, 1, 2, 3\}$$

2 = 4 - 2

$$x = \sum_{i=0}^{n/2-1} (x_{2i} + 4x_{2i+1} - 2x_{2i+1}) \times 2^{2i}$$

Multipliers

Implementation : parallel multiplier

Improvement : Reduce the number of partial products

$$x = \sum_{i=0}^{n/2-1} (x_{2i} + 4x_{2i+1} - 2x_{2i+1}) \times 2^{2i}$$

$$\begin{aligned} x = & (x_0 + 4x_1 - 2x_1) + \\ & (x_2 + 4x_3 - 2x_3) \times 4 + \\ & (x_4 + 4x_5 - 2x_5) \times 16 + \dots \end{aligned}$$

$$\begin{aligned} x = & (x_0 + 0 - 2x_1) + \\ & (x_2 + x_1 - 2x_3) \times 4 + \\ & (x_4 + x_3 - 2x_5) \times 16 + \dots \end{aligned}$$

Multipliers

Implementation : parallel multiplier

Improvement : Reduce the number of partial products

$$x = \sum_{i=0}^{n-1} x_i \times 2^i \quad x_i \in \{0, 1\}$$

$$x = \sum_{i=0}^{n/2-1} (x_{2i} + 4x_{2i+1} - 2x_{2i+1}) \times 2^{2i} \quad \text{next weight}$$

previous
weight

$$x = \sum_{i=0}^{n/2} (x_{2i-1} + x_{2i} - 2x_{2i+1}) \times 2^{2i}$$

$$x = \sum_{i=0}^{n/2} x'_{2i} \times 2^{2i}$$

$$x'_i \in \{-2, -1, 0, 1, 2\}$$




Multipliers

Implementation : parallel multiplier

Improvement : Reduce the number of partial products

$$x = \sum_{i=0}^{n/2} (x_{2i-1} + x_{2i} - 2x_{2i+1}) \times 2^{2i}$$

Booth encoding

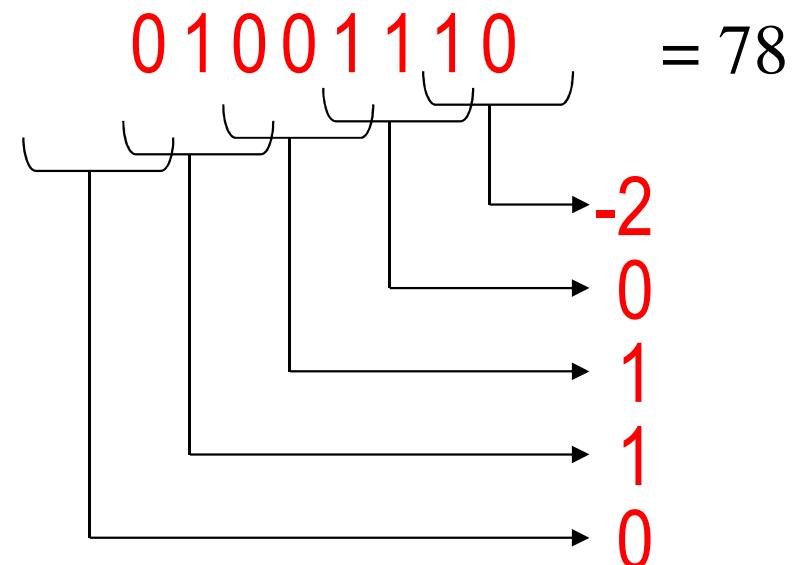


$$x = -2 \times 2^0 + 0 \times 2^2 + 1 \times 2^4 + 1 \times 2^6 + 0 \times 2^8 = 78$$

Multipliers

Implementation : parallel multiplier

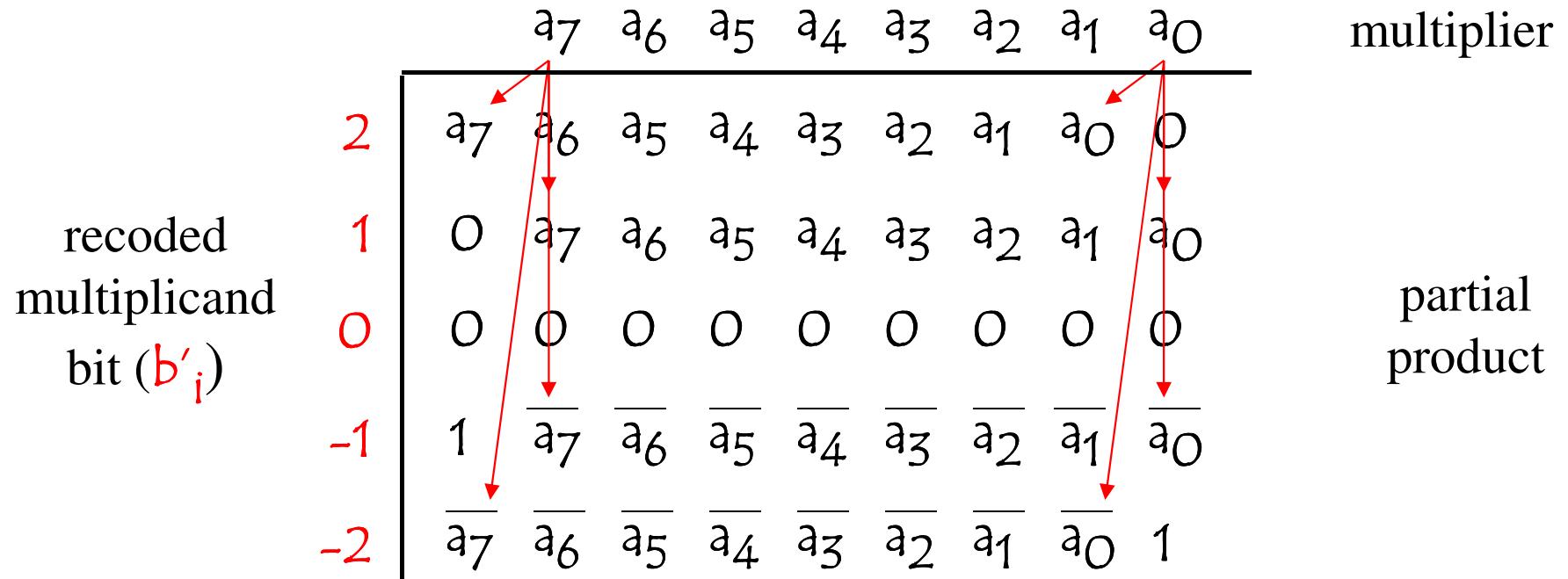Improvement : Reduce the number of partial products




$$a'_8 \ a'_7 \ a'_6 \ a'_5 \ a'_4 \ a'_3 \ a'_2 \ a'_1 \ a'_0$$

Multipliers

Implementation : parallel multiplier


Improvement : Reduce the number of partial products

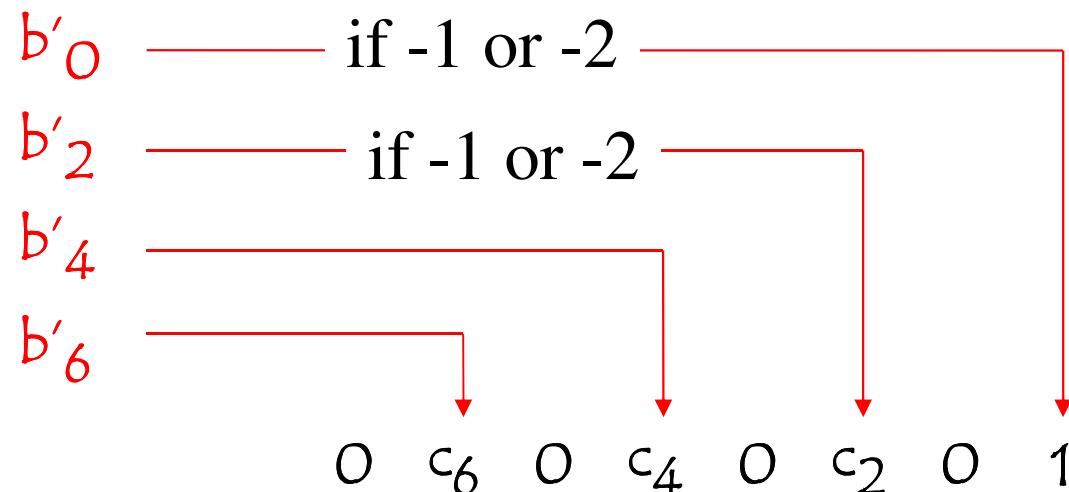An additional partial product is generated to take into account the input carry in case of subtraction



Multipliers

Implementation : parallel multiplier

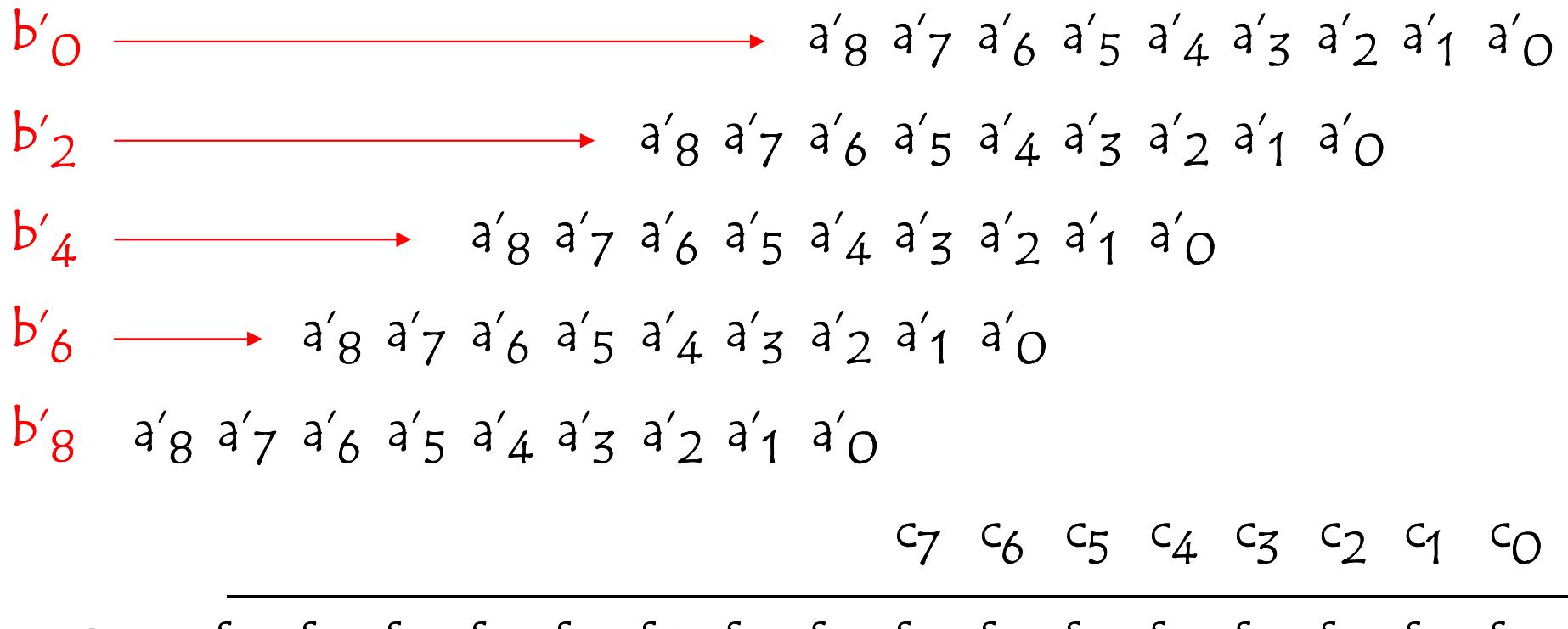


Multipliers

Implementation : parallel multiplier

Each partial product is conditioned by the corresponding Booth encoded multiplicand

bit b'_i

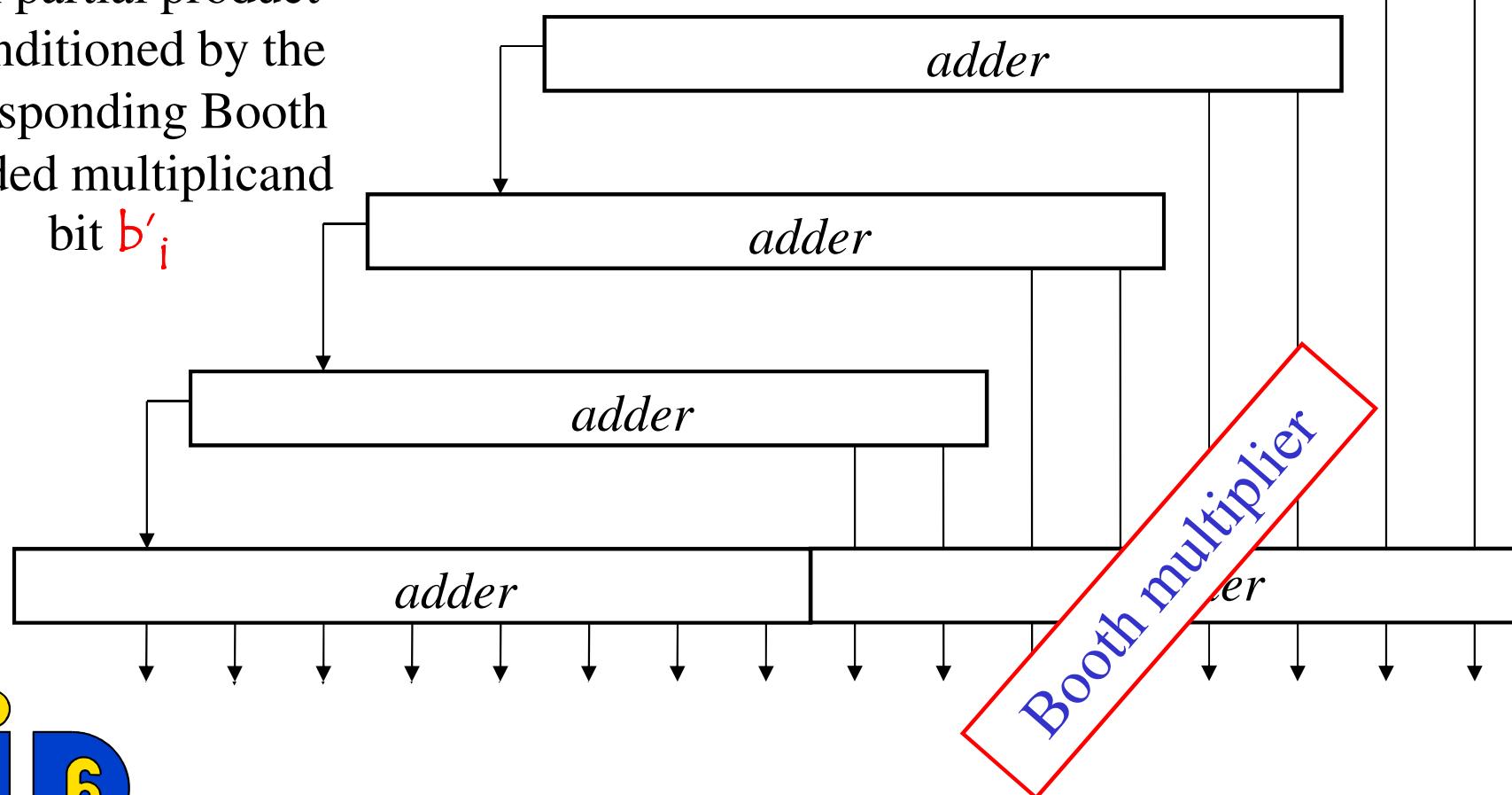

Multipliers


Implementation : fast parallel multiplier

Basically for a $n \times n$ multiplication,
we have to add n partial products
($2n$ -bit numbers)



Multipliers

Adding **three** natural numbers

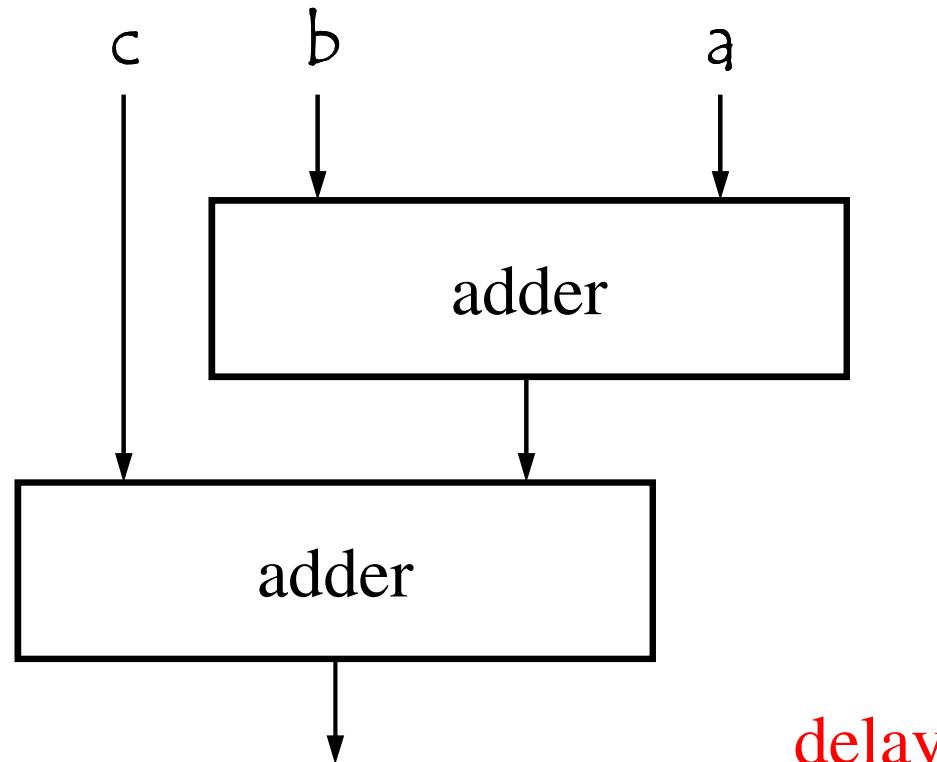


Multipliers

Adding **three** natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$

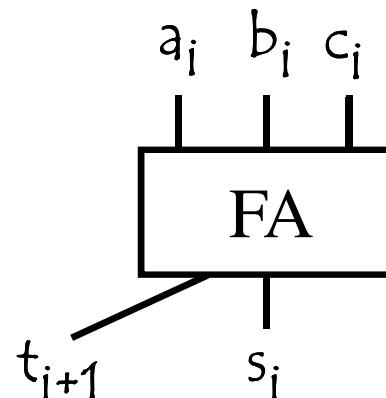the expressions are symmetrical in regard of a, b and c




A full adder creates 2
numbers from 3

Multipliers

Adding **three** natural numbers


Carry Save Adder (CSA)

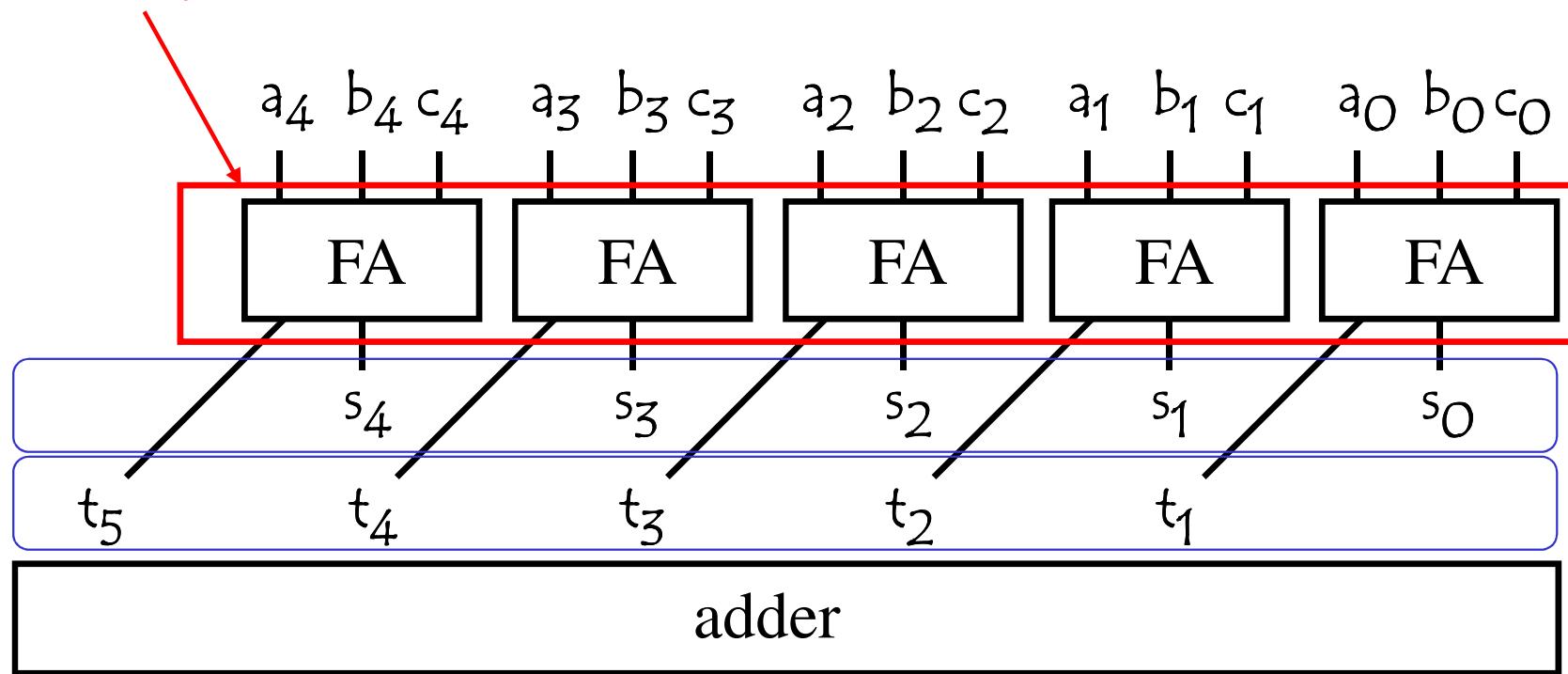

Multipliers

Implementation : fast parallel multiplier

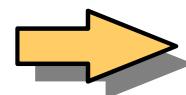Basically for a $n \times n$ multiplication,
we have to add n partial products
($2n$ -bit numbers)




Use CSA (Carry Save Adder)
to reduce 3 partial products
into 2

Multipliers

Implementation : fast parallel multiplier

8 partial products

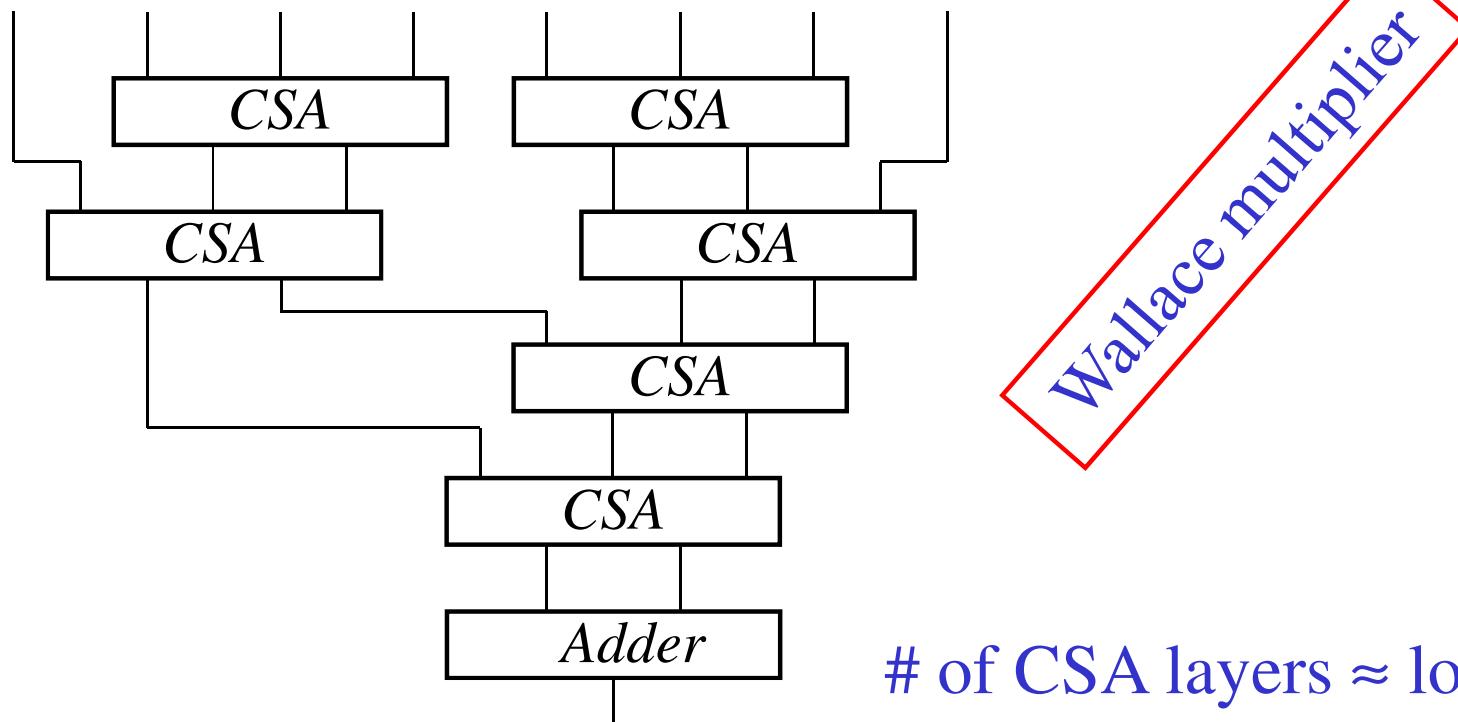


Multipliers

Implementation : fast parallel multiplier

32×32 bits multiplier $32 \rightarrow 22 \rightarrow 15 \rightarrow 10 \rightarrow 7 \rightarrow 5 \rightarrow 4 \rightarrow 3 \rightarrow 2$

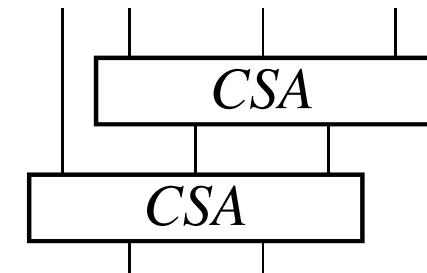Using $4 \rightarrow 2$ reduction leads to a more regular hardware implementation



32×32 bits multiplier $32 \rightarrow 16 \rightarrow 8 \rightarrow 4 \rightarrow 2$

of CSA layers $\approx 2 \log (n/2)$

Multipliers

Implementation : fast parallel multiplier

32×32 bits multiplier $32 \rightarrow 22 \rightarrow 15 \rightarrow 10 \rightarrow 7 \rightarrow 5 \rightarrow 4 \rightarrow 3 \rightarrow 2$

$42 \rightarrow 28 \rightarrow 19 \rightarrow 13 \rightarrow 9 \rightarrow 6 \rightarrow 4 \rightarrow 3 \rightarrow 2$

The margin on the number of ‘partial products’ can be used to extended the functionality of the multiplier

Multipliers

Two relative numbers a and b coded on n bits

$$p = a \times b$$

How it works if $b < 0$?

$$\begin{aligned} p = a \times b &= (-a) \times (-b) = (\bar{a} + 1) \times (\bar{b} + 1) \\ &= \bar{a} \times \bar{b} + \bar{a} + \bar{b} + 1 \end{aligned}$$

Multipliers

Multiply and add

$$p = a \times b + c$$

if $b < 0$

$$\begin{aligned} p = a \times b + c &= (-a) \times (-b) + c &= (\bar{a} + 1) \times (\bar{b} + 1) + c \\ &&= \bar{a} \times \bar{b} + \bar{a} + \bar{b} + 1 + c \end{aligned}$$

Multipliers

Multiply and subtract

$$p = c - a \times b$$

if $b > 0$

$$\begin{aligned} p = c - a \times b &= c + a \times (-b) \\ &= c + a \times (\bar{b} + 1) \\ &= c + a \times \bar{b} + a \end{aligned}$$