

# Designing a Low-cost LED Sun Photometer

*Edoardo Milotti, Department of Physics, University of Trieste*




The Abdus Salam  
**International Centre  
for Theoretical Physics**



**UNIVERSITÀ  
DEGLI STUDI DI TRIESTE**

# A little analog electronics: negative feedback and OP-AMPS

## Basic feedback scheme

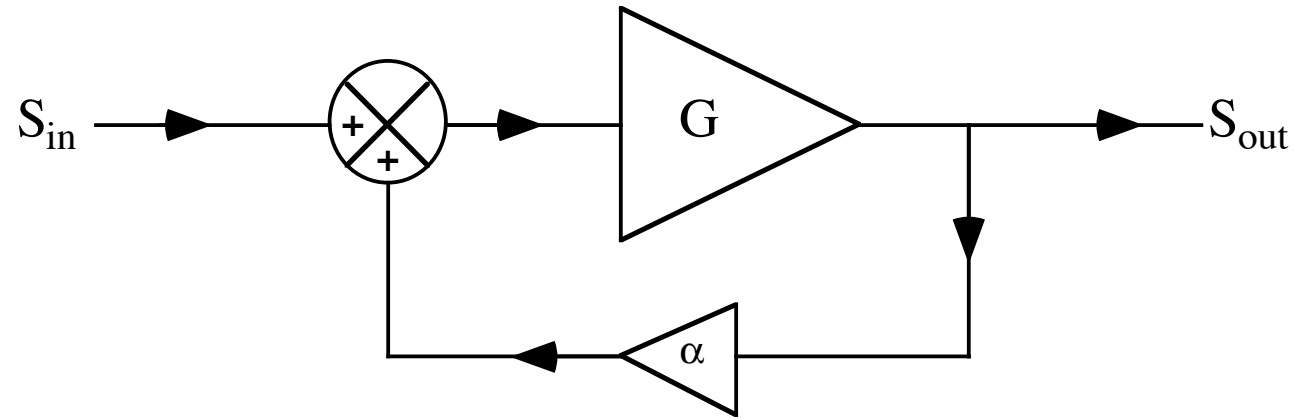

$$S_{out} = G \cdot (S_{in} + \alpha S_{out})$$

$$\Rightarrow S_{out} = \frac{G}{1 - \alpha G} S_{in} \quad \Rightarrow G' = \frac{G}{1 - \alpha G}$$

$$G' = \frac{G}{1 - \alpha G}$$


1.  $1 - \alpha G > 1$  (i.e.,  $\alpha G < 0$ ) then *negative feedback*
2.  $1 - \alpha G < 1$  (i.e.,  $\alpha G > 0$ ) then *positive feedback*
3.  $1 - \alpha G = 0$  *self oscillation*

## Negative feedback enhances stability

$$G = G(p) \quad \text{gain may depend on one or more parameters}$$

but ...


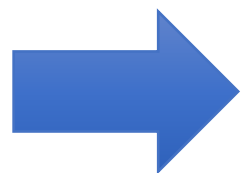
$$\begin{aligned} \frac{\partial G'}{\partial p} &= \frac{\partial}{\partial p} \left( \frac{G}{1 - \alpha G} \right) = \frac{\partial G}{\partial p} \cdot \frac{1}{1 - \alpha G} + \frac{\partial G}{\partial p} \cdot \frac{\alpha G}{(1 - \alpha G)^2} = \\ &= \frac{\partial G}{\partial p} \cdot \frac{1}{(1 - \alpha G)^2} \end{aligned}$$



$$\frac{1}{G'} \frac{\partial G'}{\partial p} = \frac{1}{(1 - \alpha G)} \left( \frac{1}{G} \frac{\partial G}{\partial p} \right)$$

**Negative feedback reduces fractional gain change, i.e., it enhances stability.**


# Enter the Operational Amplifiers

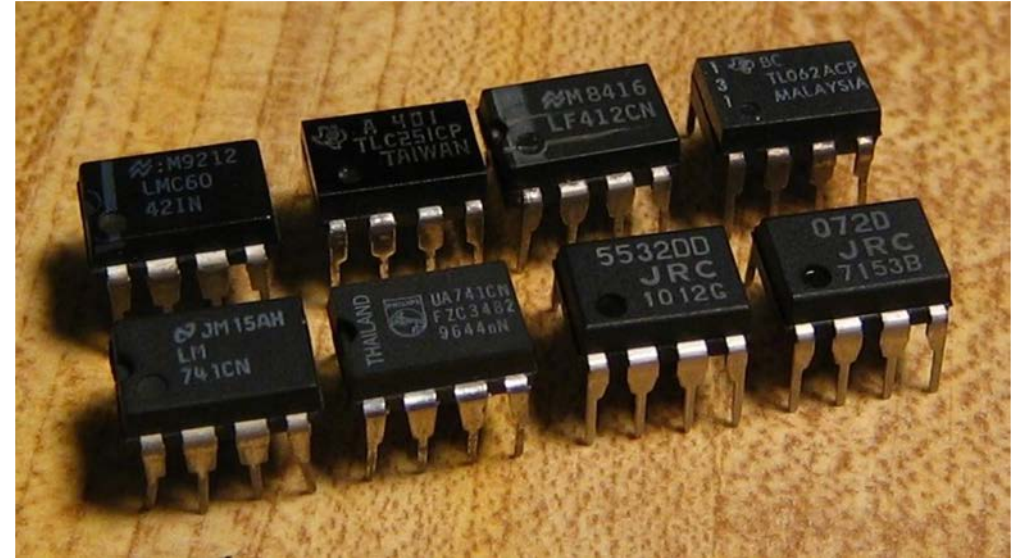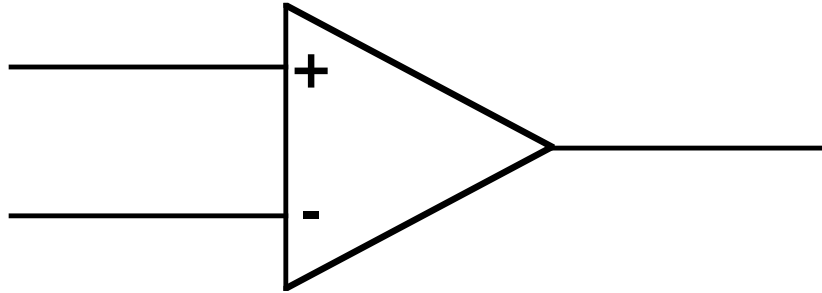


**The Operational Amplifiers (OP-AMPS) are differential amplifiers with a huge input impedance (greater than 1 M $\Omega$ , often as large as 1 G $\Omega$ ).**

A differential amplifier outputs a voltage that is proportional to the (signed) voltage difference between the inputs.
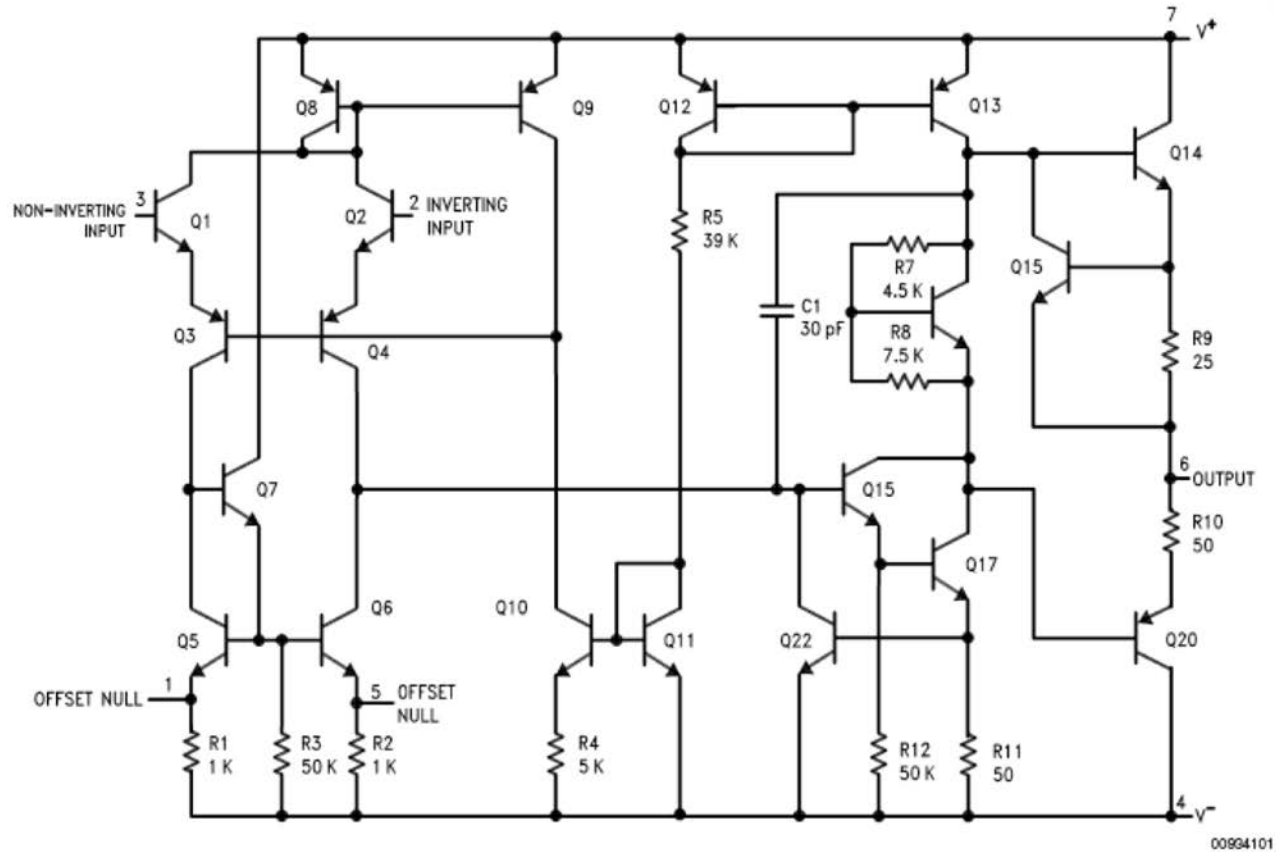
# The first highly-successful OP-AMP : the $\mu$ A741 (Bob Widlar: 1968)



## Dual-In-Line or S.O. Package

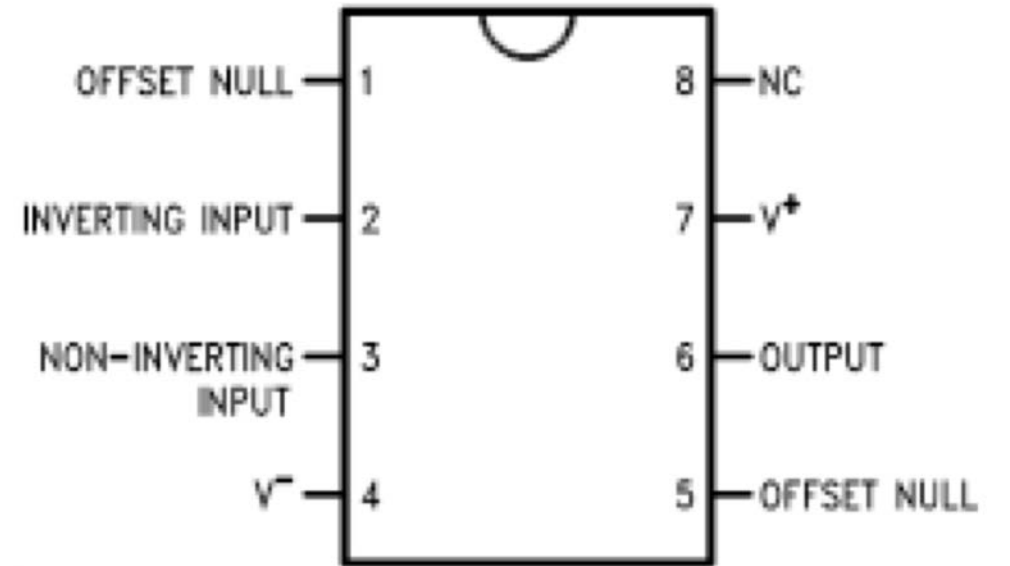

20 transistors in a small, optimized design, in a simple-to-use packaging

The OP-AMPs are normally used in a negative feedback configuration, and since they have a very high open-loop gain

$$G' = \frac{G}{1 - \alpha G} \rightarrow -\frac{1}{\alpha}$$

Then, the input signal becomes "negligible" (this means that the voltage difference between inputs is very close to 0 V)


$$S_{in} + \alpha S_{out} \approx S_{in} + \alpha \left( -\frac{1}{\alpha} \right) S_{in} = 0$$

This takes us to the two basic (approximate) "golden rules":

1. An OP-AMP draws very little current (0.2 nA for the LF411, very high input impedance)
2. The voltage difference between the inputs is negligible (feedback)


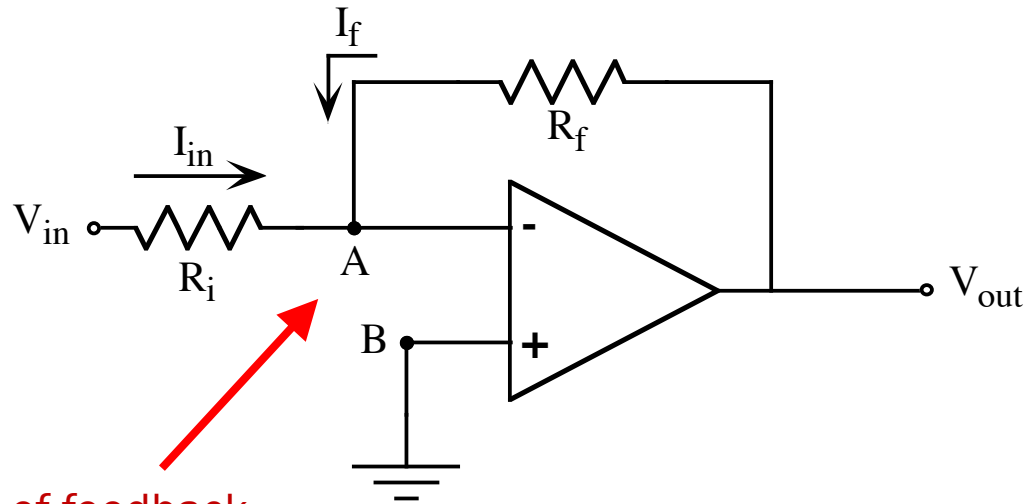
# A very basic circuit: the inverting amplifier




$$I_{in} = V_{in} / R_i$$

$$I_f = V_{out} / R_f$$

$$I_{in} + I_f = 0 \quad (\text{very large input impedance})$$

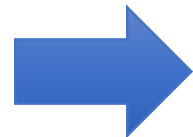because of feedback,  
A is a virtual ground




$$V_{in} / R_i + V_{out} / R_f = 0$$



$$V_{out} = -\frac{R_f}{R_i} V_{in}$$


output voltage  
depends only on the  
feedback network

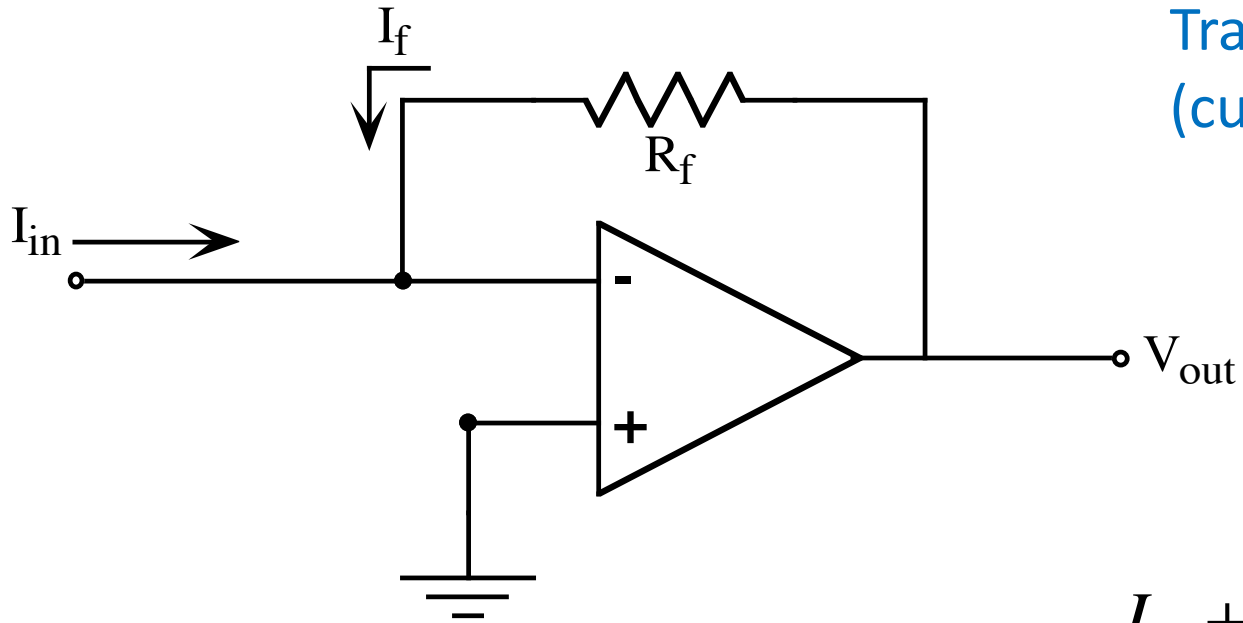Transimpedance amplifier  
(current-to-voltage converter)



$$I_{in} + I_f = 0$$

$$I_{in} + V_{out} / R_f = 0$$

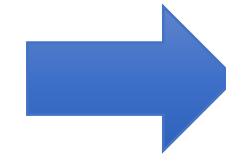

$$V_{out} = -R_f I_{in}$$



Using a 10M $\Omega$  feedback resistor the amplifier converts a 1  $\mu$ A into a 10 V voltage.

**THIS IS THE BASIC TEMPLATE FOR MANY PREAMPLIFIERS.**


The transimpedance amplifier configuration is used with photodiodes and other detectors that behave like current generators.

The BPW34 is a common and accurate photodiode.

fotodiodi BPW34

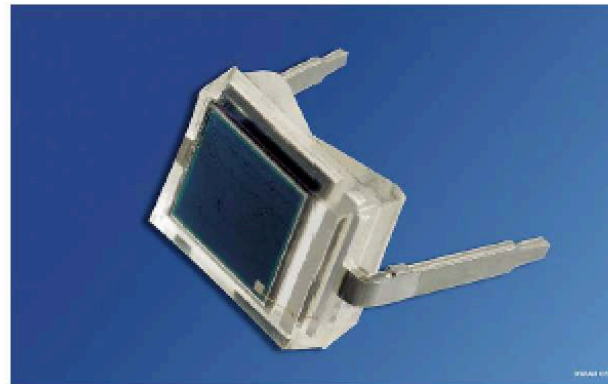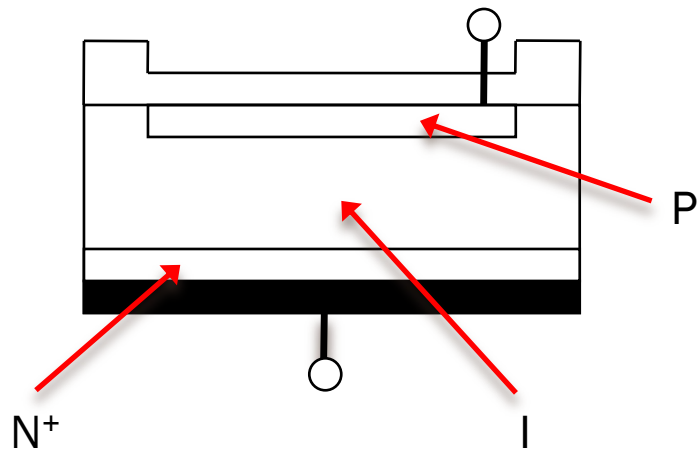

BPW 34 B

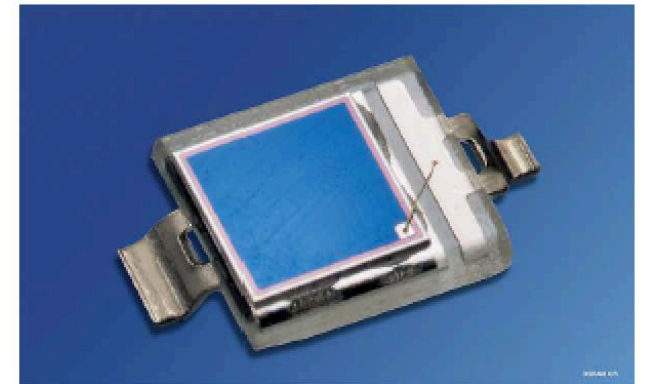

BPW 34 BS

## Silicon PIN Photodiode


### Description


The BPW34 is a high speed and high sensitive PIN photodiode in a miniature flat plastic package. Its top view construction makes it ideal as a low cost replacement of TO-5 devices in many applications.

Due to its waterclear epoxy the device is sensitive to visible and infrared radiation. The large active area combined with a flat case gives a high sensitivity at a wide viewing angle.

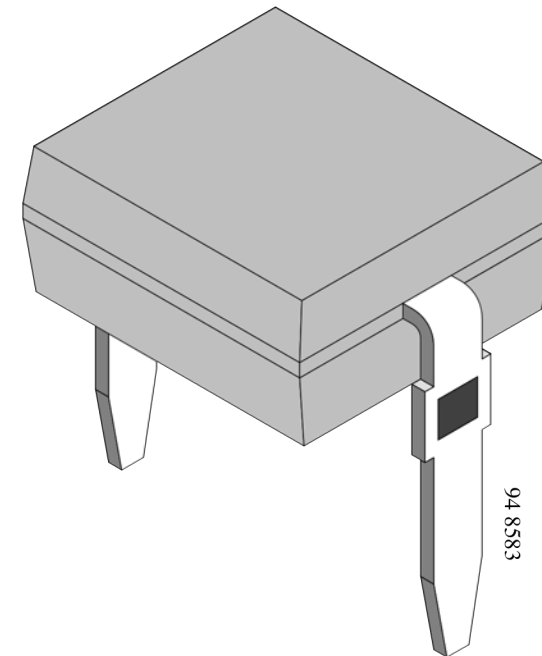
### Features

- Large radiant sensitive area ( $A=7.5 \text{ mm}^2$ )
- Wide angle of half sensitivity  $\varphi = \pm 65^\circ$
- High photo sensitivity
- Fast response times
- Small junction capacitance
- Suitable for visible and near infrared radiation



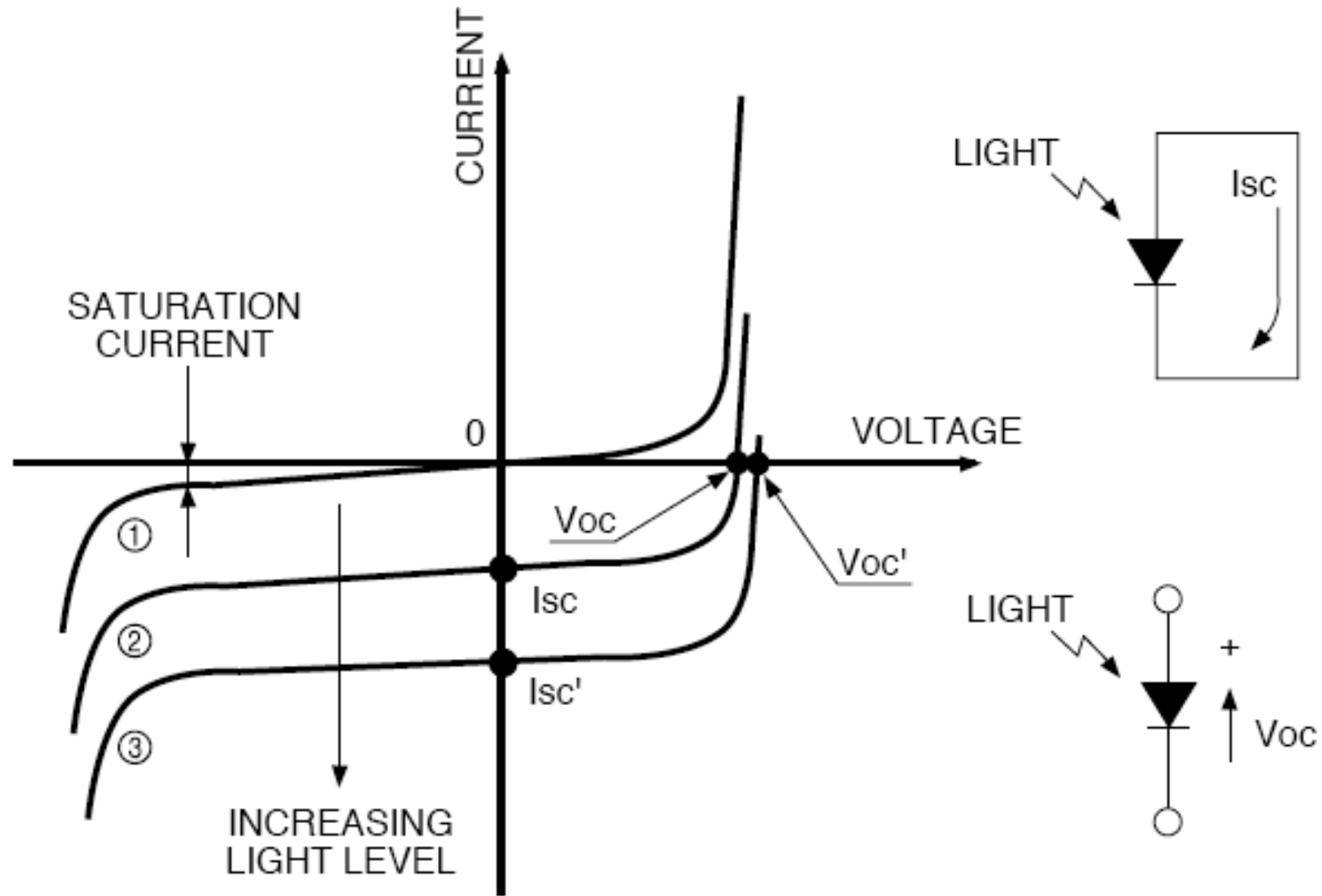


Spectral sensitivity of BPW-34

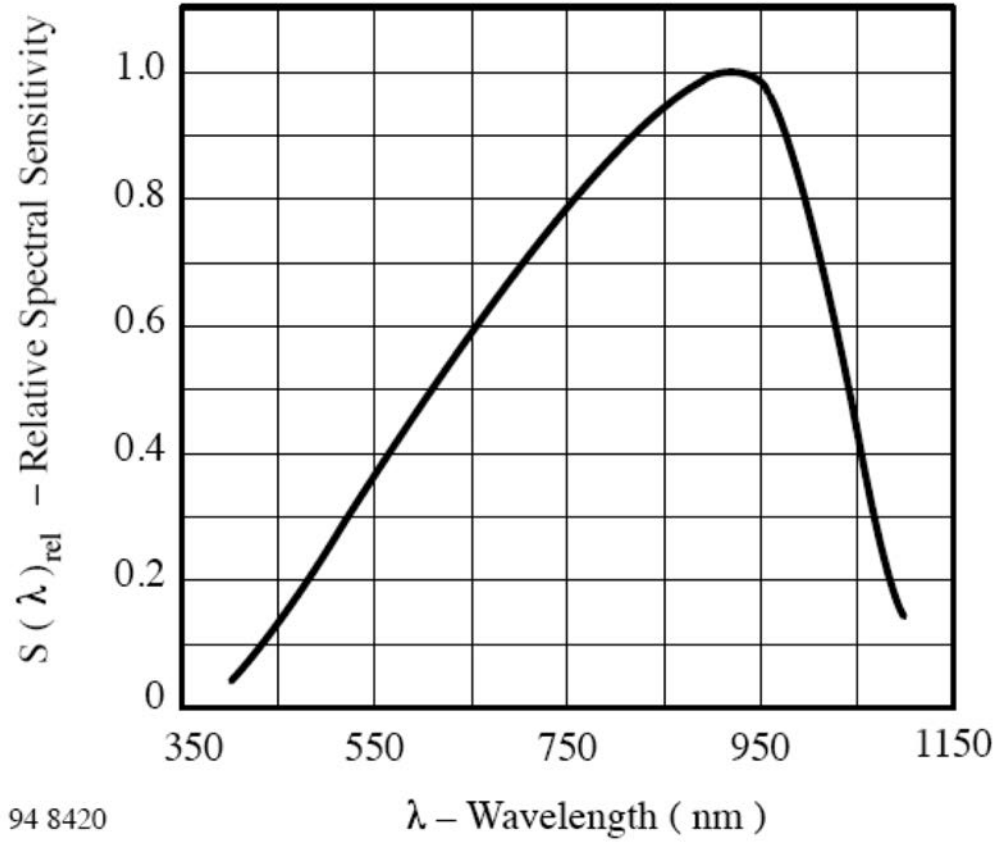


94 8420

Spectral sensitivity of BPW-34B

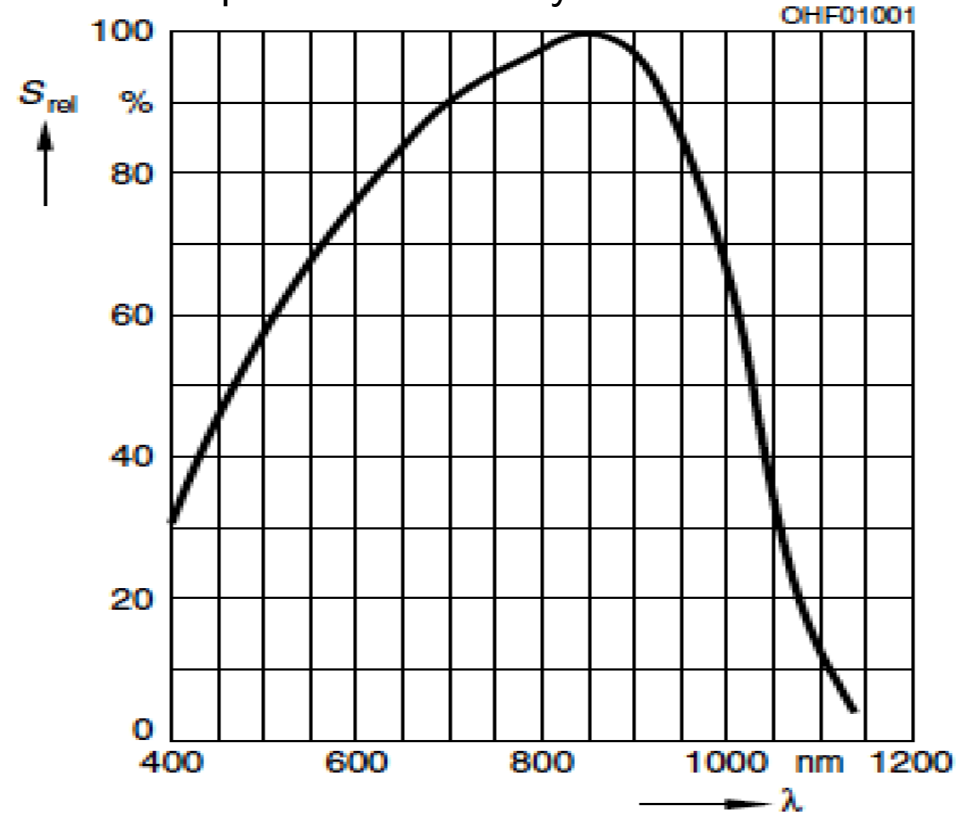

# Photo Voltaic-Cell Amplifier

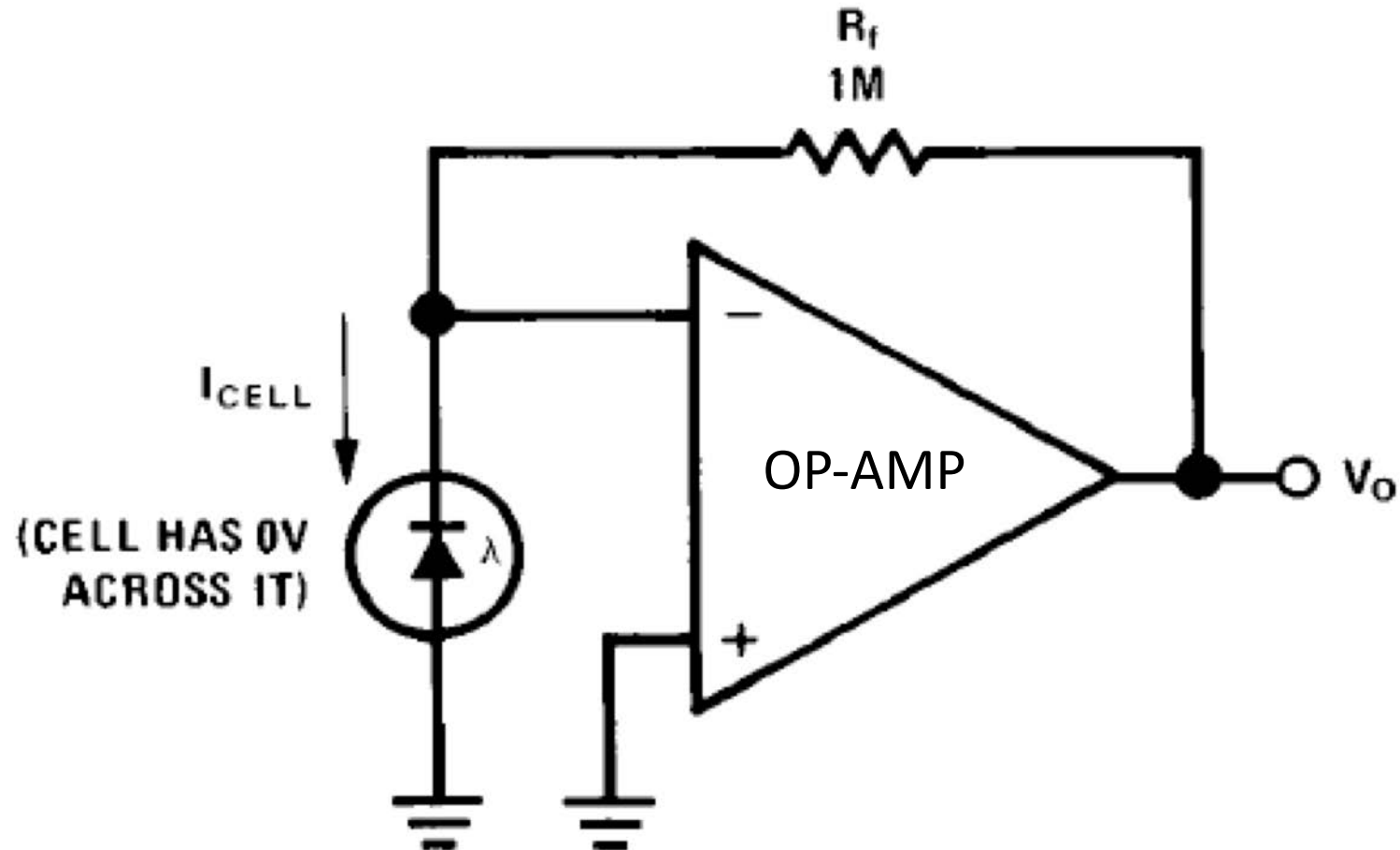


TLC251, TLC251A, TLC251B, TLC251Y  
 LinCMOS™ PROGRAMMABLE  
 LOW-POWER OPERATIONAL AMPLIFIERS  
 SLOS001F – JULY 1983 – REVISED MARCH 2001


Schematics of a simple  
 TLC251C based photometer

- Wide Range of Supply Voltages  
1.4-V to 16-V
- True Single-Supply Operation
- Common-Mode Input Voltage Range  
Includes the Negative Rail
- Low Noise . . . 30 nV/√Hz Typ at 1-kHz  
(High Bias)
- ESD Protection Exceeds 2000 V Per  
MIL-STD-833C, Method 3015.1


D OR P PACKAGE  
 (TOP VIEW)

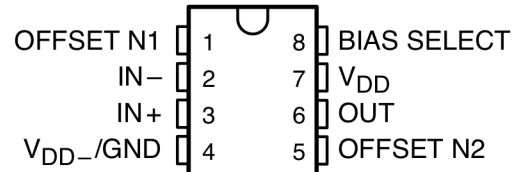

symbo

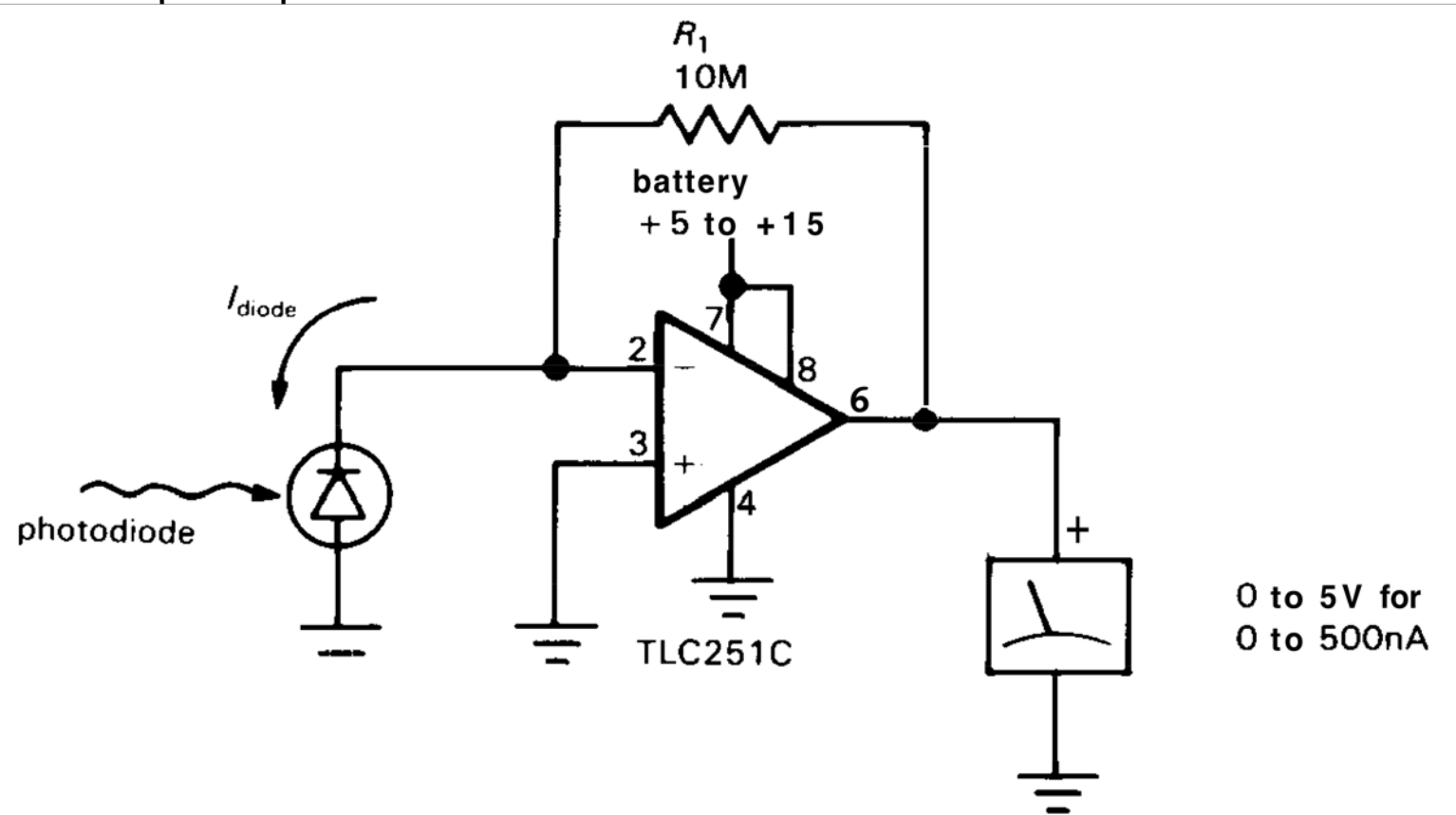



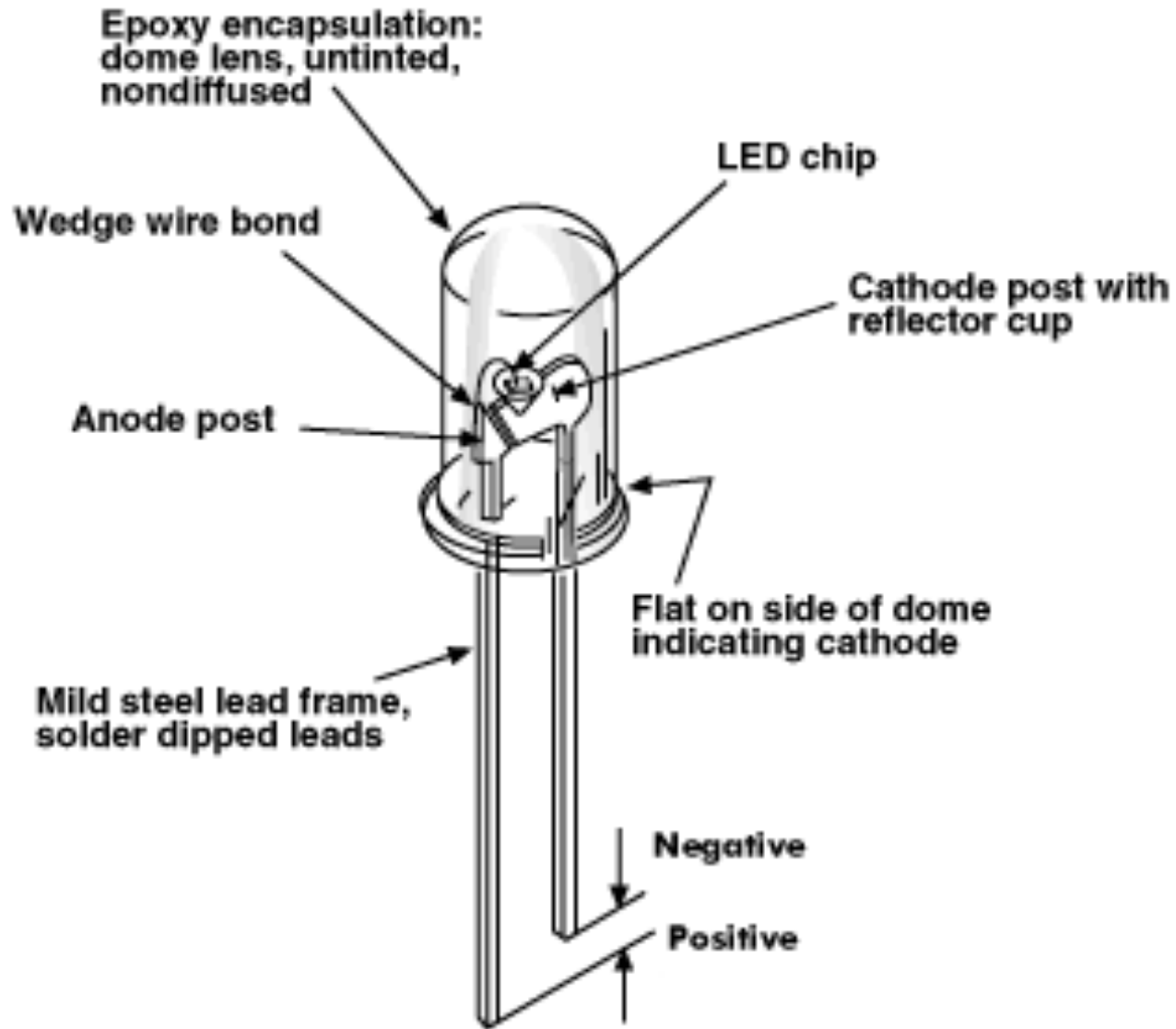


...

At about 2¢ each in large quantities, LEDs cost about five times as much as diodes, but they are much more sensitive as photocells. With the sun falling directly on it, the photocurrent of a red 5-mm LED (1000 mCd @ 20 mA) is over 20  $\mu$ A; in the sunny tropics this might keep a clock battery charged. They're not well-suited for power generation, but LEDs are convenient photodetectors at about 10% of the price of purpose-made ones.

...

from J.Bryant, Analog Dialog, 108 (Aug. 2014)


<http://www.analog.com/en/analog-dialogue/raqs/raq-issue-108.html>

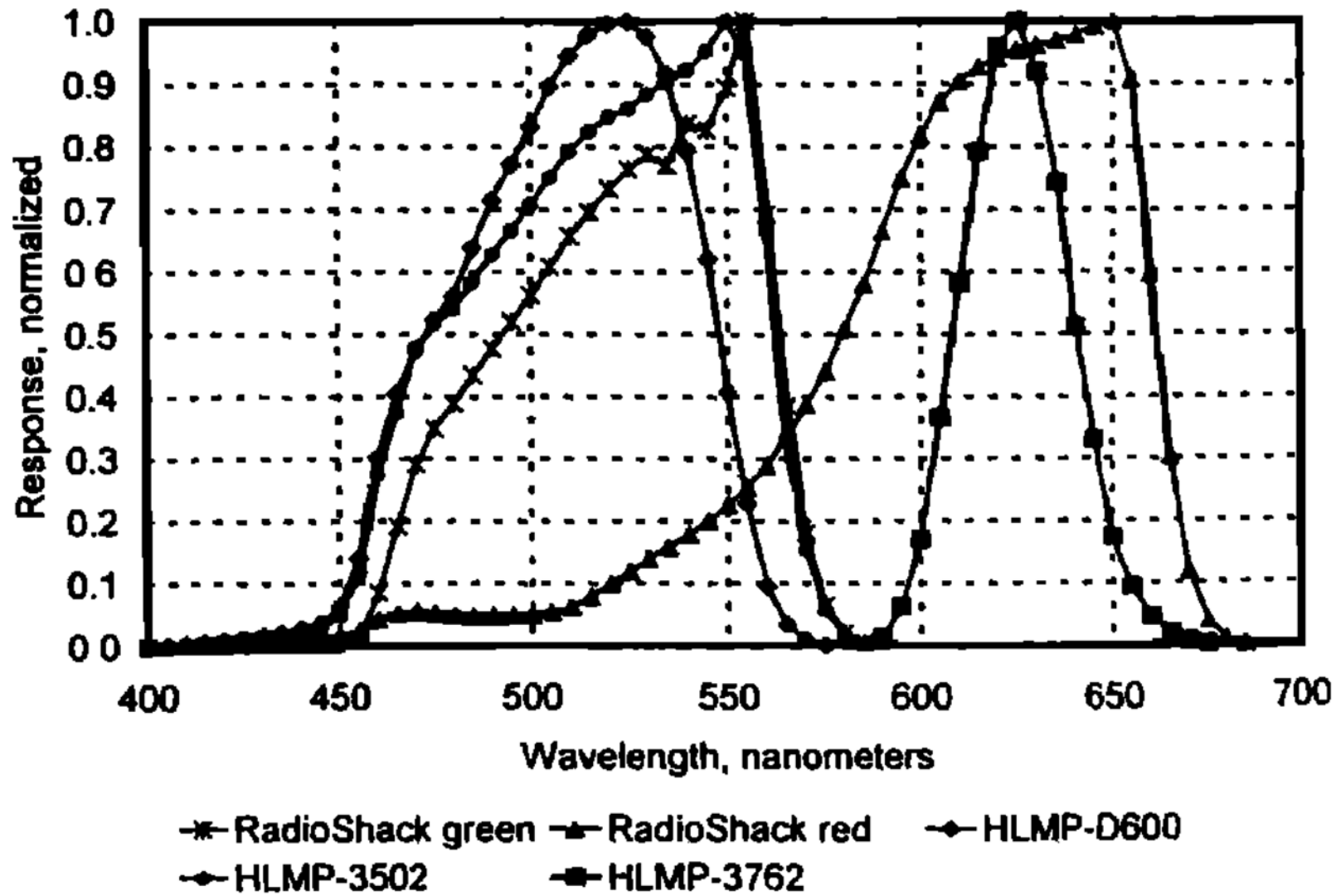

**Figure 2.** Spectral response of selected LEDs.
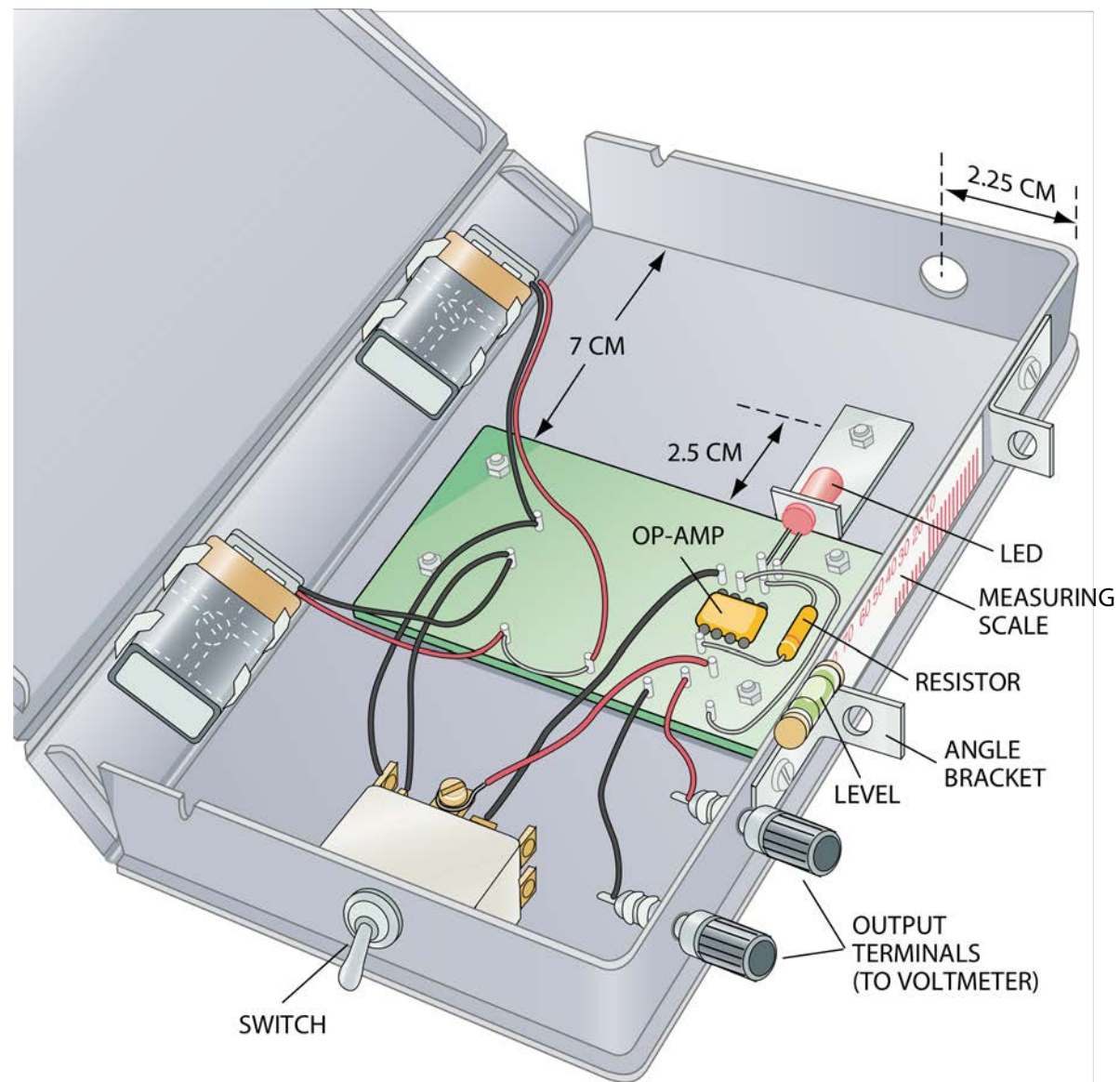
# The sun photometer

(scheme from Carlson, Sci. Am., May 1997, 107)



## HAZE SENSOR

*fits neatly into a videocassette case. Angle brackets align the case to the sun. They can also be used with the level to calculate the sun angle.*

# The Langley plot

$$I_{\lambda}(m) = I_0(\lambda) \exp(-\alpha_{\lambda} m)$$

Irradiance at the photometer position, at wavelength  $\lambda$ , with an airmass  $m$


Solar irradiance above the atmosphere at wavelength  $\lambda$

Attenuation coefficient at wavelength  $\lambda$

Airmass


Langley plot
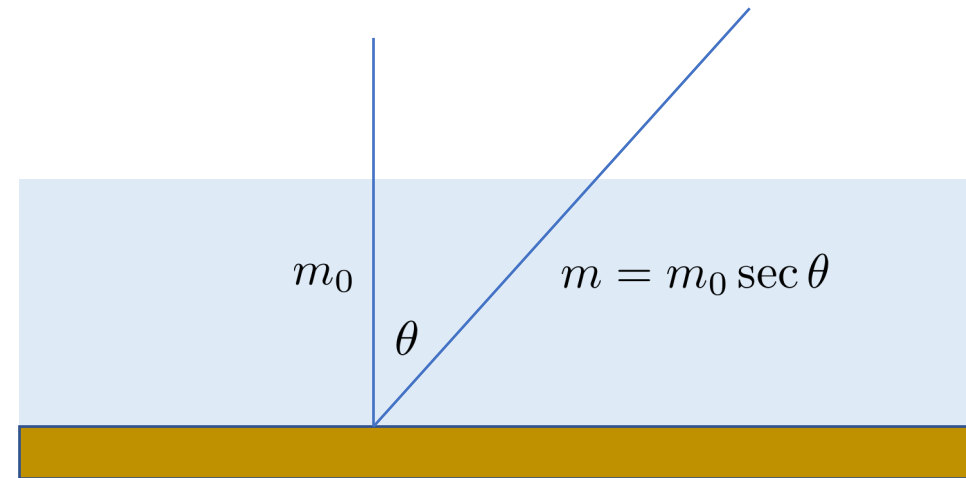
$$\ln I_{\lambda}(m) = \ln I_0(\lambda) - \alpha_{\lambda} m$$



The solar spectrum is widely variable, and it is advisable to define the wavelength with a narrowband filter (a LED detector is a reasonable approximation)

# Solar Radiation Spectrum

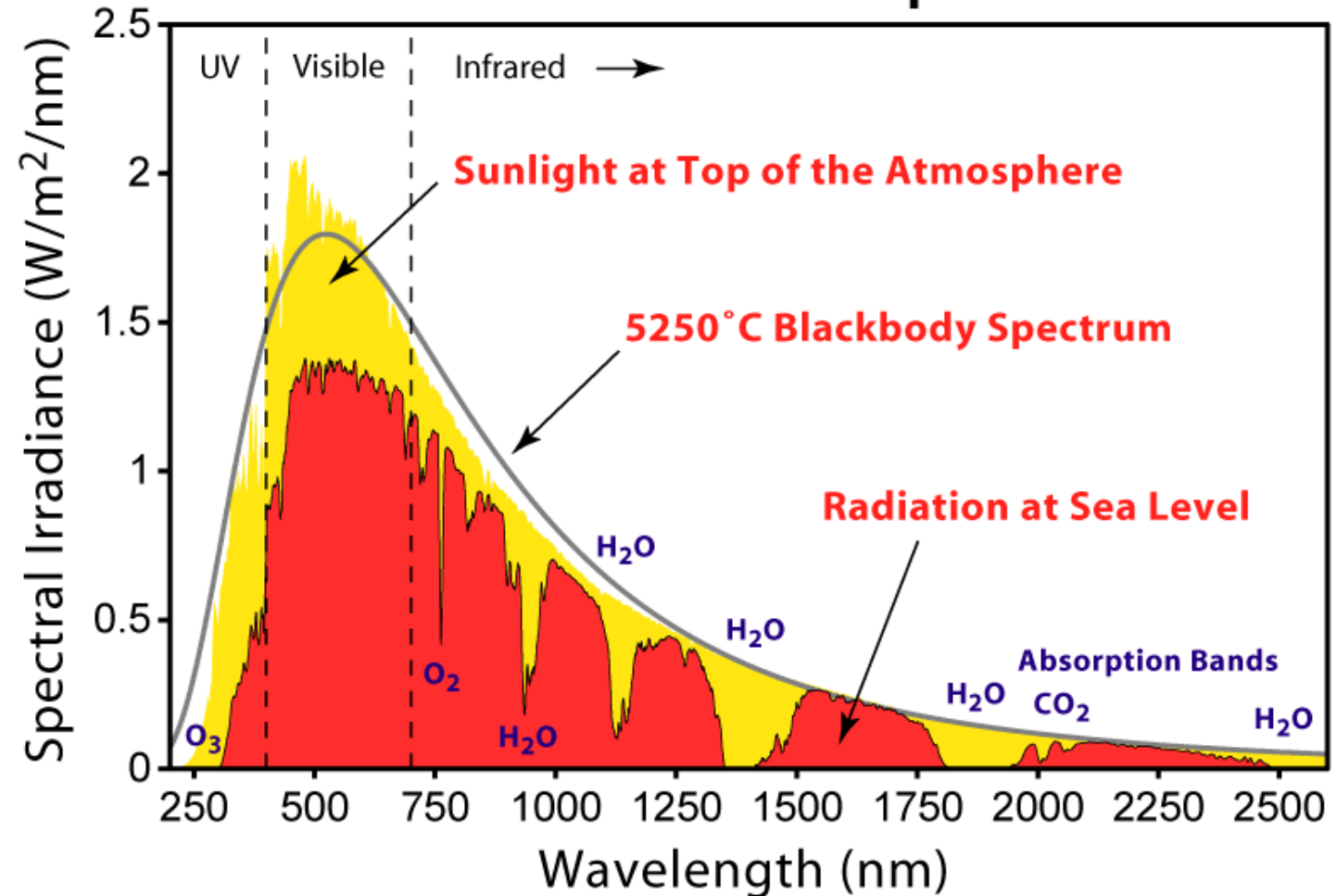


<https://physics.stackexchange.com/questions/152963/solar-spectrum-units>

## Langley plot

$$\ln I_{\lambda}(m) = \ln I_0(\lambda) - \alpha_{\lambda} m \approx \ln I_0(\lambda) - (\alpha_{\lambda} m_0) \sec \theta$$

The absorption coefficient can be split in two parts: one that depend on the haze and the other that depends on Rayleigh scattering (which is pressure-dependent)

$$\alpha_{\lambda} = \alpha_H + \alpha_R \frac{P}{P_0}$$

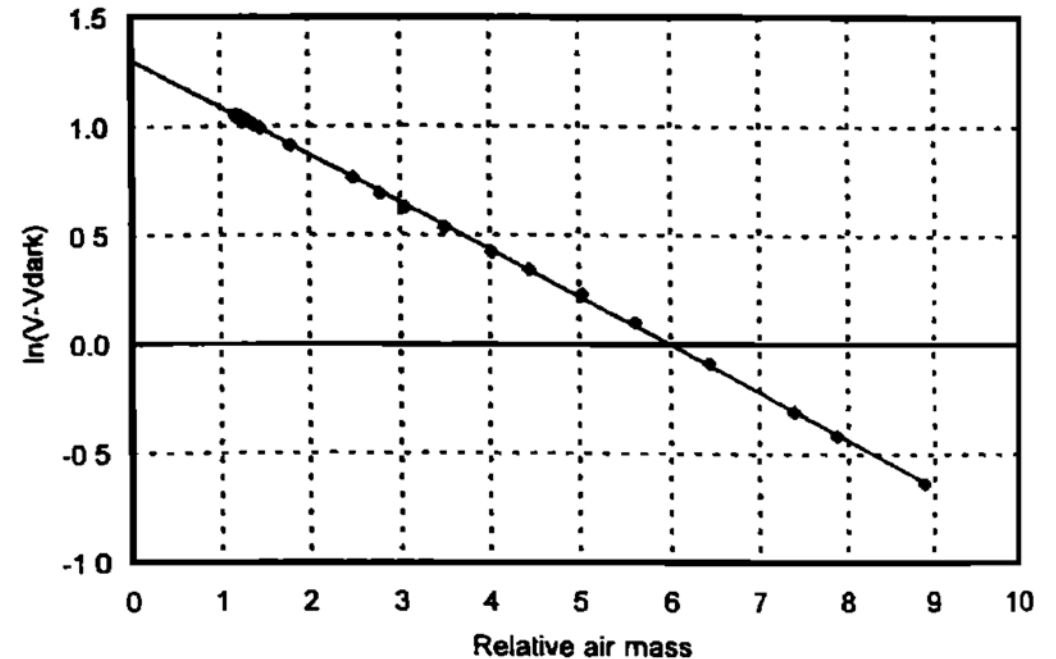

**Figure 1.** Langley plot calibration for a light-emitting diode (LED) based Sun photometer, from Seguin, Texas, March 9, 1999 (unpublished data from Mims).


from Brooks & Mims, J. Geophys. Res. **106** 4733 (2001)

## Langley's plot *after* amplification

$$V_{\lambda}(\theta) = V_0(\lambda) \exp \left[ - \left( \alpha_H + \alpha_R \frac{P}{P_0} \right) m_0 \sec \theta \right] + V_D$$

a "solar constant"

"dark" voltage

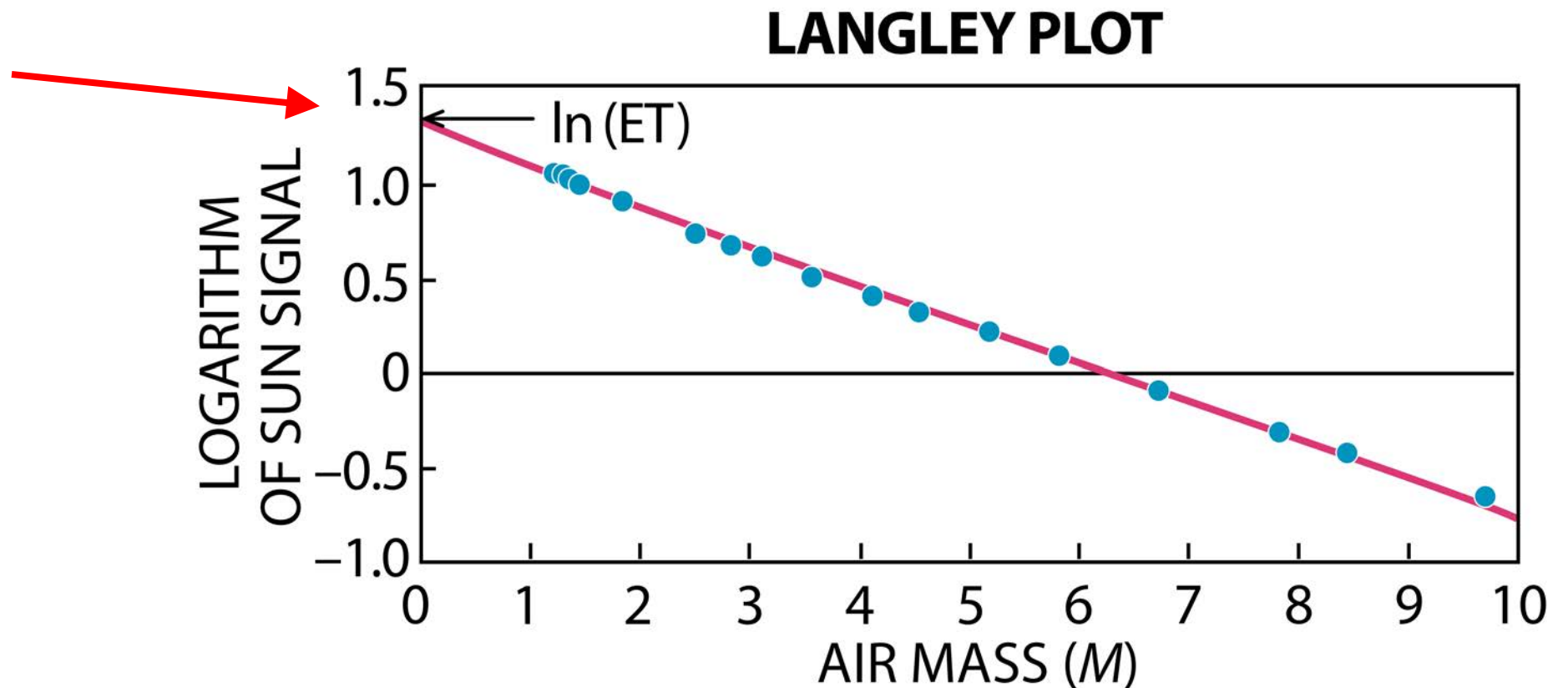

$$\ln (V_{\lambda}(\theta) - V_D) = \ln V_0(\lambda) - \left( \alpha_H + \alpha_R \frac{P}{P_0} \right) m_0 \sec \theta$$

$$\text{AOT} = \alpha_H = \frac{\ln V_0(\lambda) - \ln(V_{\lambda}(\theta) - V_D) - \alpha_R (P/P_0) m_0 \sec \theta}{m_0 \sec \theta}$$

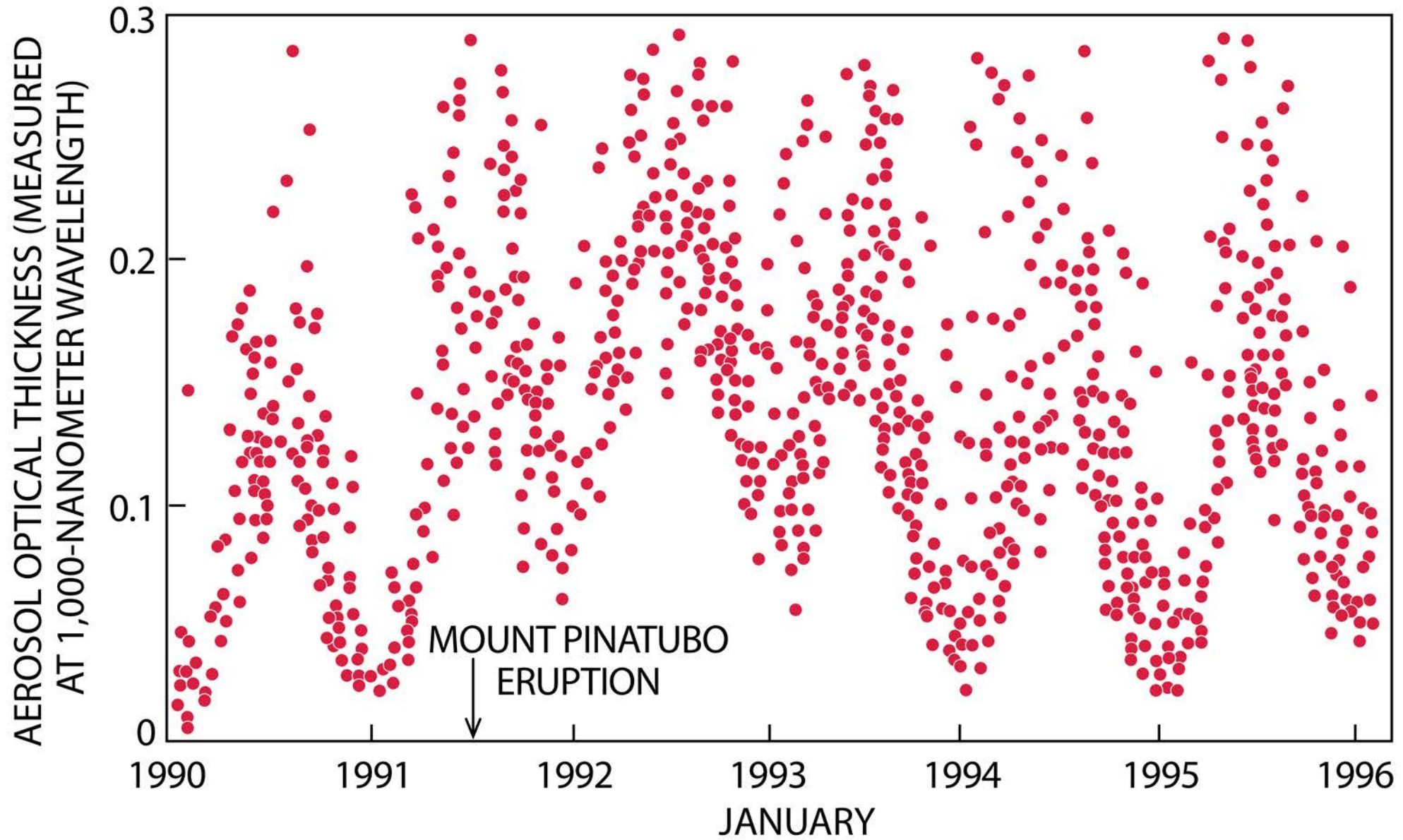
**AOT = Aerosol Optical Thickness**

$$\text{AOT} = \alpha_H = \frac{\ln V_0(\lambda) - \ln(V_\lambda(\theta) - V_D) - \alpha_R(P/P_0)m_0 \sec \theta}{m_0 \sec \theta}$$

ET = ExtraTerrestrial constant, the signal that would be measured just outside the atmosphere.







More details (and a few misprints ... )  
in this paper

## Development of an inexpensive handheld LED-based Sun photometer for the GLOBE program

David R. Brooks

Department of Mathematics and Computer Science, Drexel University, Philadelphia, Pennsylvania

Forrest M. Mims III

Sun Photometer Atmospheric Network, Seguin, Texas

See also <https://www.globe.gov>



The Global Learning and Observations to Benefit the Environment (GLOBE) Program is an international science and education program that provides students and the public worldwide with the opportunity to participate in data collection and the scientific process, and contribute meaningfully to our understanding of the Earth system and global environment. Announced by the U.S. Government on Earth Day in 1994, GLOBE launched its worldwide implementation in 1995.

# Now we are ready to build and use a sun photometer !

Lower resistance (3.9 MΩ) resistor suggested

