


### Outline

- Digital CMOS design
- Arithmetic operators
  - Adders
  - Comparators
  - Shifters
  - Multipliers



Pirouz Bazargan Sabet      Digital Design      February 2010


### Adders

Adding two natural numbers

At each stage, I need to sum 3 single bit numbers  $a_i, b_i, c_i$   
 The carry out of the stage  $i$  is the input carry of the next stage

$$\begin{array}{r} c_{i+1}c_i \\ a_i \\ + \\ b_i \\ \hline s_i \end{array}$$

$s_i$  and  $c_{i+1}$  are Boolean functions of  $a_i, b_i, c_i$




Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers

Let consider two natural numbers  $A$  and  $B$  coded on 8 bits using Natural Binary Code

$$\begin{array}{r} c_7 c_6 c_5 c_4 c_3 c_2 c_1 \\ a_7 a_6 a_5 a_4 a_3 a_2 a_1 a_0 + \\ b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0 \\ \hline s_7 s_6 s_5 s_4 s_3 s_2 s_1 s_0 \end{array}$$



Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders


Adding two natural numbers

	00	01	11	10	$a_i b_i$
0	0	1	0	1	
1	1	0	1	0	
$c_i$					$s_i$

$$s_i = \bar{a}_i \cdot \bar{b}_i \cdot c_i + \bar{a}_i \cdot b_i \cdot \bar{c}_i + a_i \cdot b_i \cdot c_i + a_i \cdot \bar{b}_i \cdot \bar{c}_i$$

$$s_i = \bar{a}_i (b_i \cdot c_i + \bar{b}_i \cdot \bar{c}_i) + a_i (b_i \cdot c_i + \bar{b}_i \cdot \bar{c}_i)$$

$$s_i = a_i \oplus b_i \oplus c_i \qquad s_i = \bar{a}_i (b_i \oplus c_i) + a_i (b_i \oplus c_i)$$



Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers

	00	01	11	10	$a_i$	$b_i$
0	0	1	0	1		
1	1	0	1	0		

	00	01	11	10	$a_i$	$b_i$
0	0	0	1	0		
1	0	1	1	1		

$c_i$   
 $s_i$   
 $s_i = a_i \oplus b_i \oplus c_i$

$c_i$   
 $c_{i+1}$   
 $c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$

Pirouz Bazargan Sabet    Digital Design    February 2010

### Adders

Adding two natural numbers  
Considering the delay

Pirouz Bazargan Sabet    Digital Design    February 2010

### Adders

Adding two natural numbers

$s_i = a_i \oplus b_i \oplus c_i$

$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$   
 $c_{i+1} = a_i \cdot (b_i + c_i) + b_i \cdot c_i$

Pirouz Bazargan Sabet    Digital Design    February 2010

### Adders

Adding two natural numbers

$s_i = a_i \oplus b_i \oplus c_i$

$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$   
 $c_{i+1} = a_i \cdot (b_i + c_i) + b_i \cdot c_i$

Addition delay depends on the delay of  $c_i$  to  $c_{i+1}$

Pirouz Bazargan Sabet    Digital Design    February 2010

### Adders

Adding two natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$

$$c_{i+1} = a_i \cdot b_i + (a_i + b_i) \cdot c_i$$

Pirouz Bazargan Sabet
Digital Design
February 2010

### Adders

Adding two natural numbers

The circuit generating  $s_i$  and  $c_{i+1}$  is called a Full Adder (FA)

Pirouz Bazargan Sabet
Digital Design
February 2010

### Adders

Adding two natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$

$$c_{i+1} = a_i \cdot b_i + (a_i + b_i) \cdot c_i$$

$$c_{i+1} = a_i \cdot b_i + (a_i \oplus b_i + a_i \cdot b_i) \cdot c_i$$

$$c_{i+1} = a_i \cdot b_i + (a_i \oplus b_i) \cdot c_i$$

Pirouz Bazargan Sabet
Digital Design
February 2010

### Adders

Adding two natural numbers

At each stage, I need to sum 3 single bit numbers  $a_i, b_i, c_i$

The carry out of the stage  $i$  is the input carry of the next stage

Pirouz Bazargan Sabet
Digital Design
February 2010

### Adders

Adding two natural numbers

Ripple Carry Adder (RCA)

Area  $\propto n$       Delay  $\propto n$

Timing should be improved

Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers

Carry Select Adder (CSLA)

Area  $\propto 3^{\log(n)} = n^{\log(3)} = n^{1.585}$       Delay  $\propto \log(n)$

Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers

Acceleration technics

Carry Select Adder (CSLA)

Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers

Acceleration technics

	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$c_i$

	00	01	11	10
absorption				
propagation				
generation				
propagation				

$a_i b_i$

carry out depends on carry in

carry out does not depend on carry in

Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers  
Acceleration technics

	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$a_i b_i$

	00	01	11	10
absorption				
propagation				
generation				
propagation				

$a_i b_i$

$$G_i = a_i b_i$$

$$P_i = a_i \oplus b_i$$

$$c_{i+1} = G_i + P_i c_i$$

$$s_i = P_i \oplus c_i$$

Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers  
Acceleration technics

Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers  
Acceleration technics

$b_i$   $a_i$

	00	01	11	10
absorption				
propagation				
generation				
propagation				

$$G_i = a_i b_i$$

$$P_i = a_i \oplus b_i$$

$$c_{i+1} = G_i + P_i c_i$$

$$s_i = P_i \oplus c_i$$

Pirouz Bazargan Sabet      Digital Design      February 2010

### Adders

Adding two natural numbers  
Acceleration technics




$b_{i+1}$   $a_{i+1}$   $b_i$   $a_i$

$G_{i+1} = a_{i+1} b_{i+1}$	$G_i = a_i b_i$
$P_{i+1} = a_{i+1} \oplus b_{i+1}$	$P_i = a_i \oplus b_i$

$$G_{i+1, i} = G_{i+1} + G_i \cdot P_{i+1}$$

$$P_{i+1, i} = P_i \cdot P_{i+1}$$

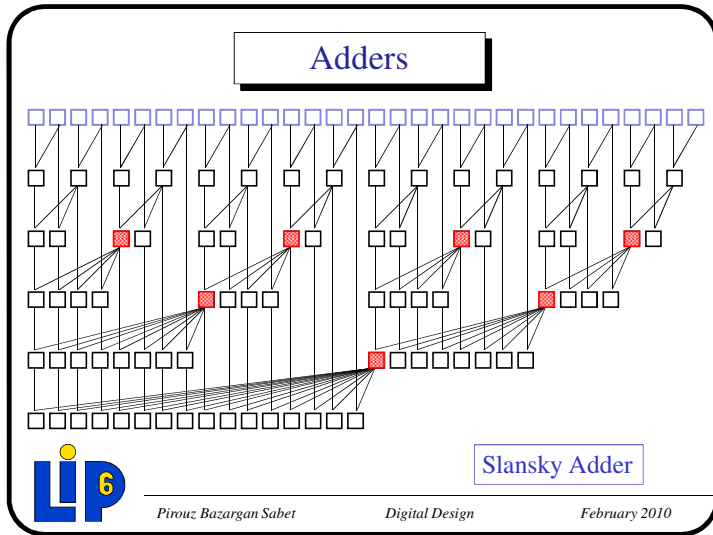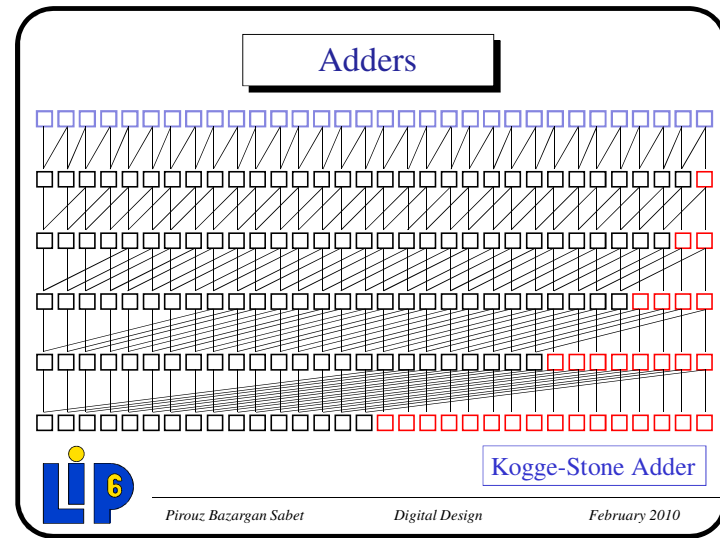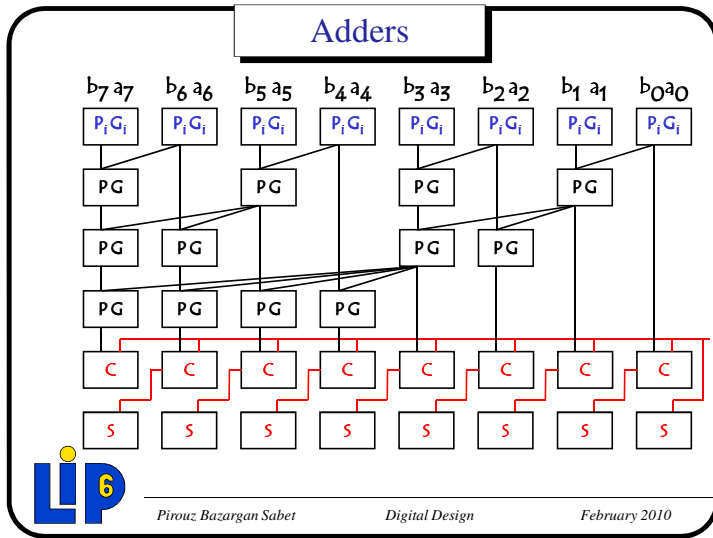Pirouz Bazargan Sabet      Digital Design      February 2010



### Adders

Adding two natural numbers (summary)

	Area	Delay
Ripple Carry (RCA)	$n$	$n$
Carry Select (CSLA)	$3 \log(n)$	$\log(n)$
Carry Lookahead (CLA)	$n \log(n)$	$\log(n)$

Pirouz Bazargan Sabet
Digital Design
February 2010