

Outline

❑ Digital CMOS design

- Boolean algebra
- Basic digital CMOS gates
- **Combinational and sequential circuits**
- Coding - Representation of numbers



CMOS Circuits

How can I design a digital circuit ?

- A set of gates (cell library)

combinational gates

memory elements



CMOS Circuits

How can I design a digital circuit ?

- Method to design combinational circuits

Karnaugh table (local optimization)

no method for global optimization

→ synthesis tools



CMOS Circuits

How can I design a digital circuit ?

- Specify the circuit


Combinational circuit : Boolean functions

Sequential circuit ?



CMOS Circuits


- Combinational logic

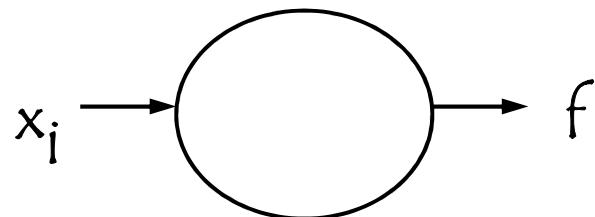

$$f(x_1, \dots, x_i, \dots, x_n)$$

CMOS Circuits

- Sequential logic

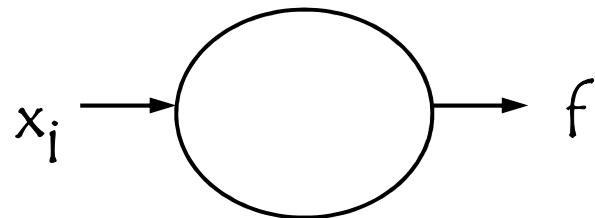


$$f(x_1, \dots, x_i, \dots, x_n, m_1, \dots, m_k, \dots, m_p)$$

$$m_k(x_1, \dots, x_i, \dots, x_n, m_1, \dots, m_k, \dots, m_p)$$

CMOS Circuits


- Sequential logic

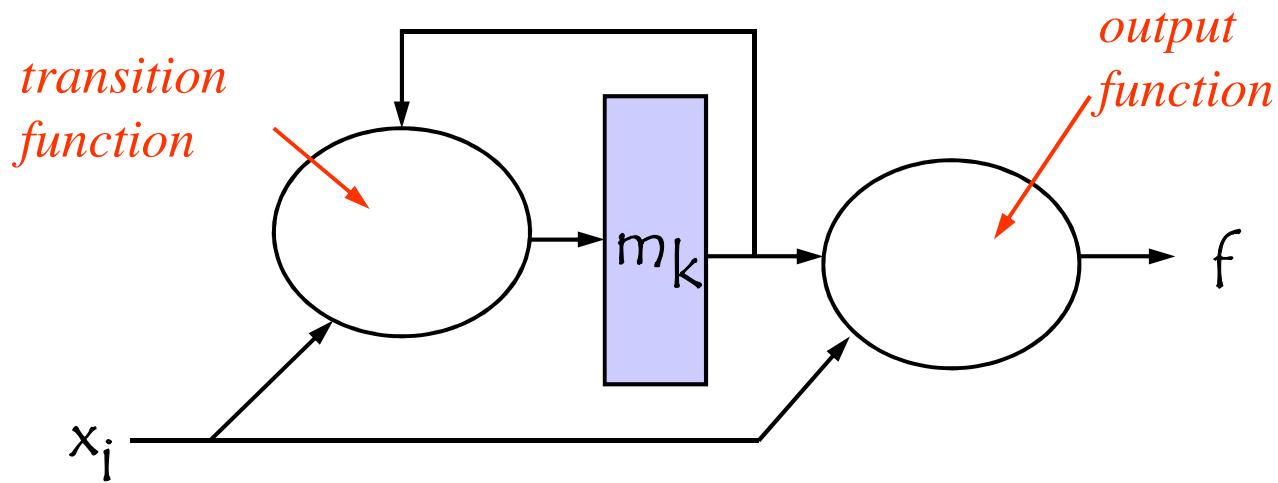

Finite State Machine (FSM)


CMOS Circuits

Finite State Machine

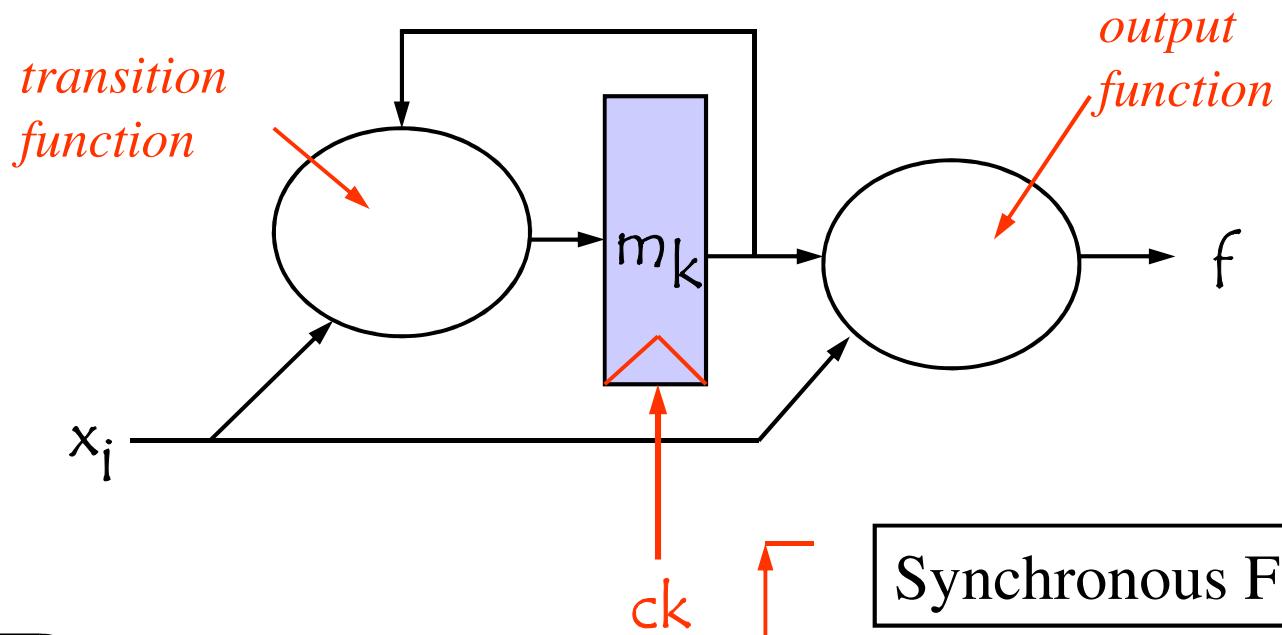

CMOS Circuits


- Finite State Machine

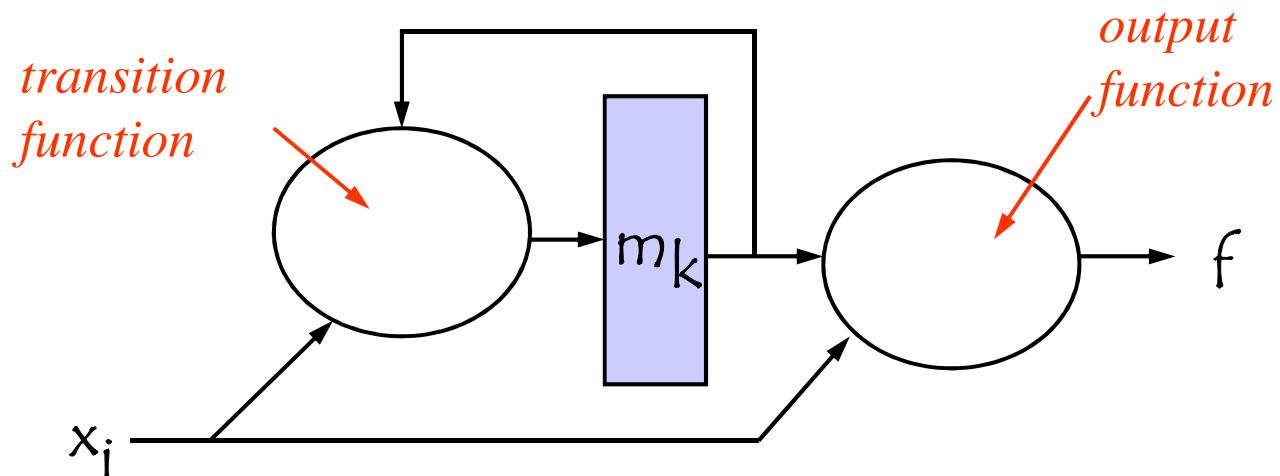

Mealy FSM

CMOS Circuits


Finite State Machine

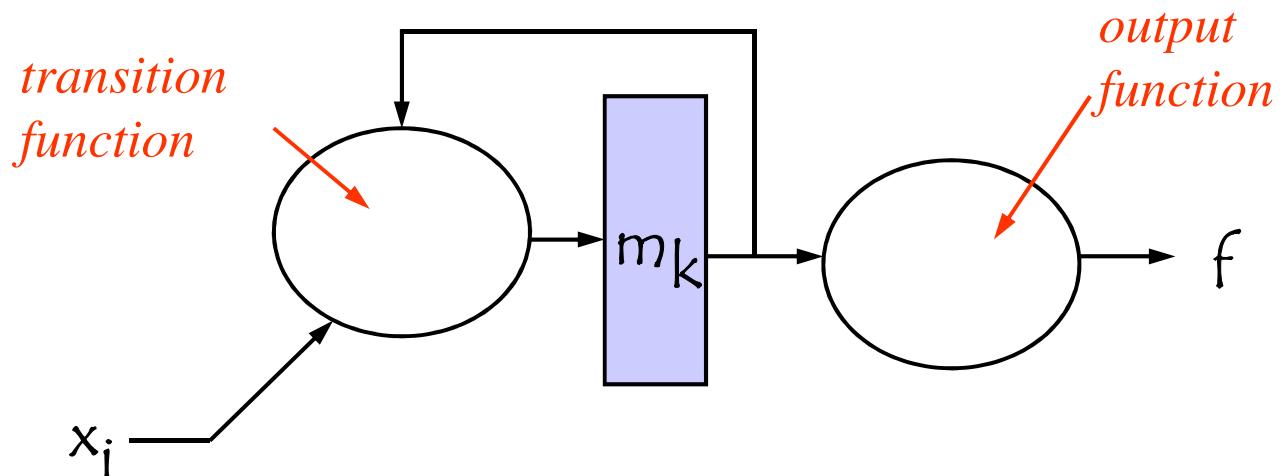

Moore FSM

Sequential Circuits


- Sequential Circuit

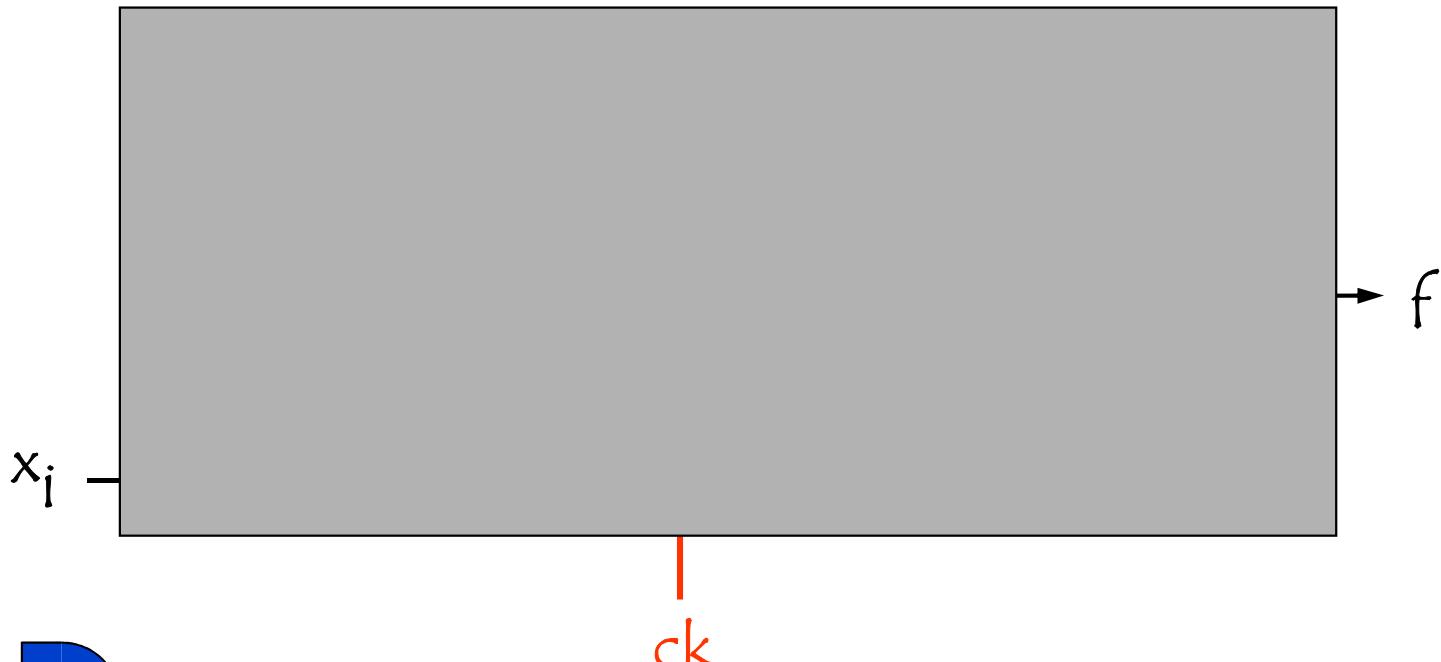

Sequential Circuits

How can I design a sequential circuit ?

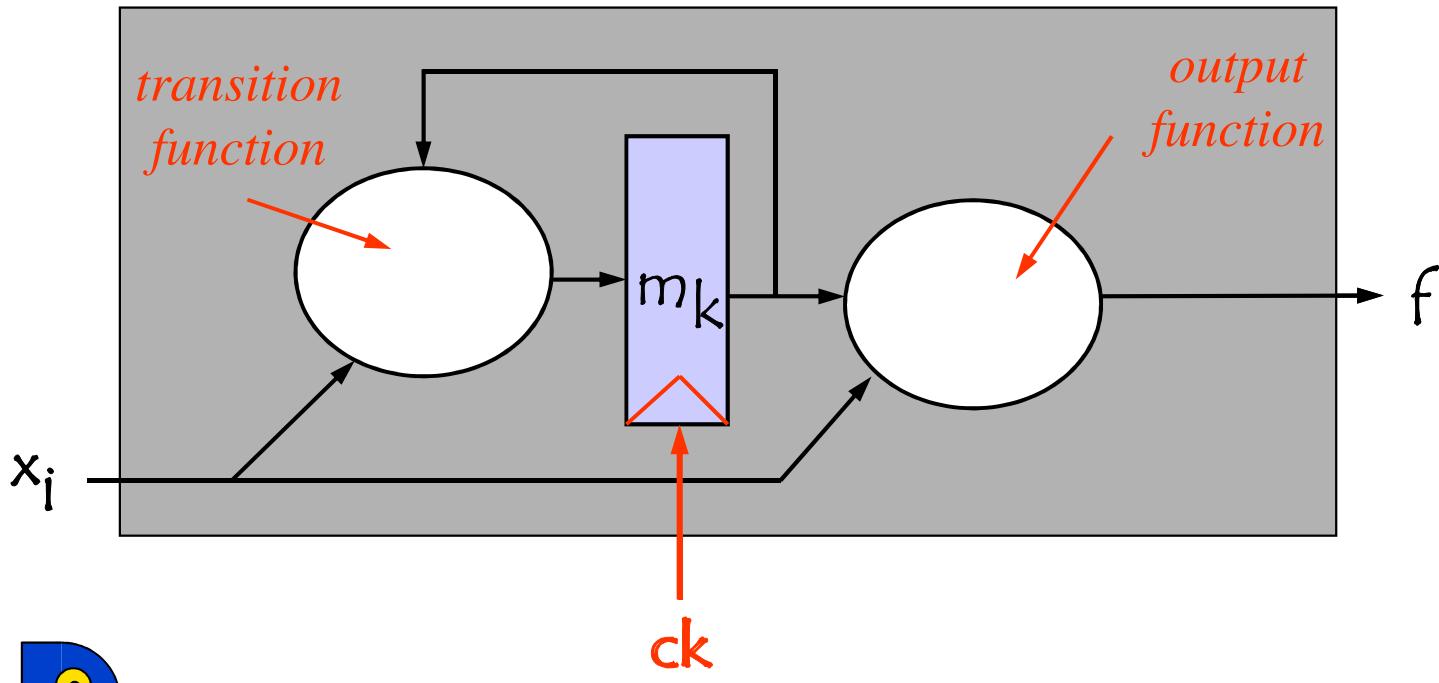I need a method to go from a black box to a white box



Sequential Circuits

How can I design a sequential circuit ?

The starting point (what I know)

What the circuit is supposed to do

Capture this knowledge into a
representation that can be
transposed into Boolean functions

The aim

How it will do it

number of required
memory elements



Sequential Circuits

Representation of a sequential circuit ?

- State graph

$$G = (X, Y, S, T, O)$$

- X : input variables
- Y : output variables
- S : states
- T : transitions
- O : output set conditions



Sequential Circuits

- $G = (X, Y, S, T, O)$

T : set of transitions

$t \in T, \quad t = (s, s', f)$

$s \in S$: source state

$s' \in S$: target state

$f \in B_n$: transition condition



Sequential Circuits

- $G = (X, Y, S, T, O)$

O : output set conditions

$$o \in O, \quad o = (y, s, c)$$

$y \in Y$: output variable

$s \in S$: state


$c \in B_n$: output set condition



Sequential Circuits

- Let consider a graph $G = (X, Y, S, T, O)$

Graphic representation of G

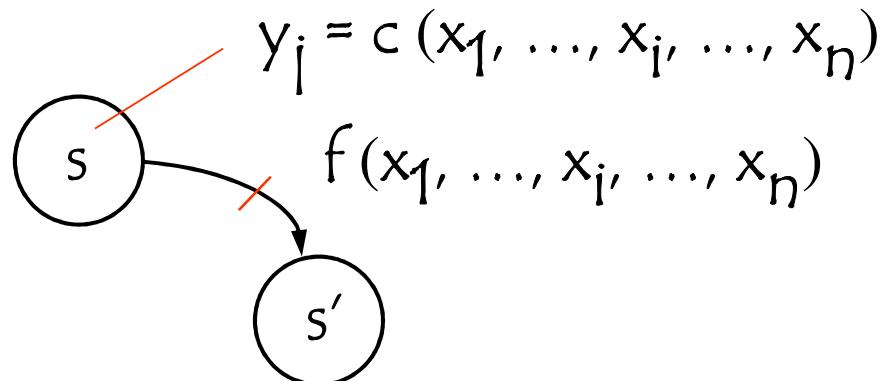

Sequential Circuits

Representation of a sequential circuit ?

- State graph

Transpose into a graphic representation the expected behavior of a sequential system

$$G = (X, Y, S, T, O)$$



Sequential Circuits

Example


Two signals a, b each transmitting a series of bits (1 bit at a cycle)

Design a system that sets a flag d if the value transmitted by a is different than b



Sequential Circuits

- Example

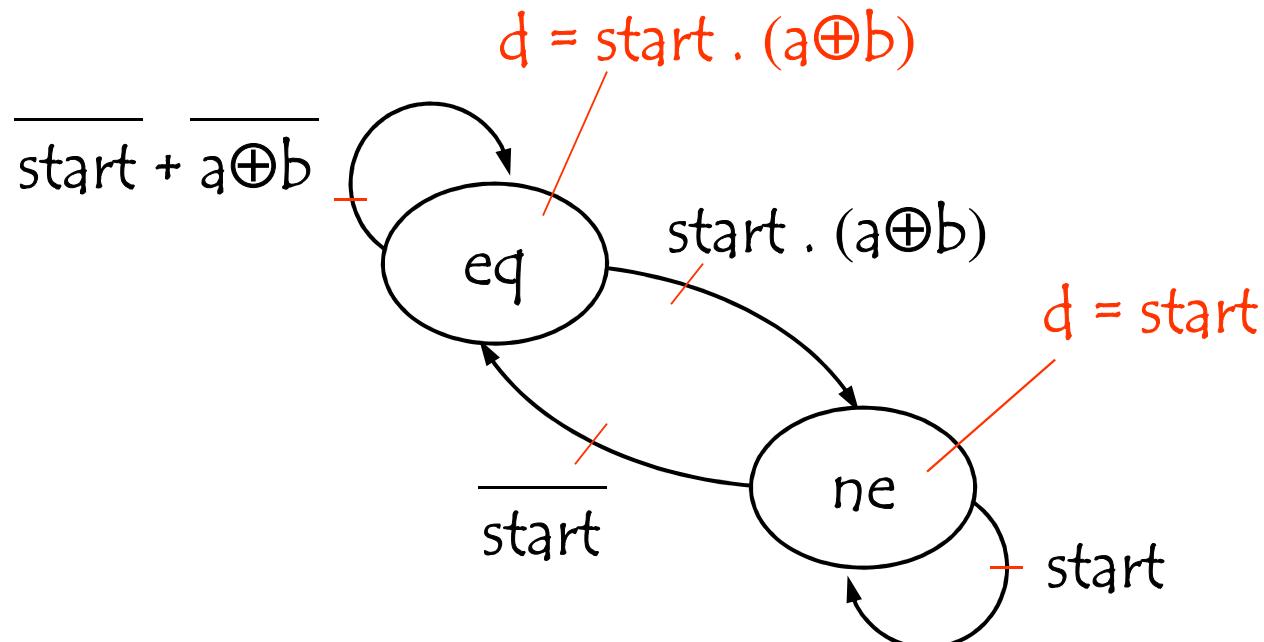

Sequential Circuits

Representation of a sequential circuit ?

- State graph


$$G = (X, Y, S, T, O)$$

define the number of memory elements
required to represent $S : M$



Sequential Circuits

- Example

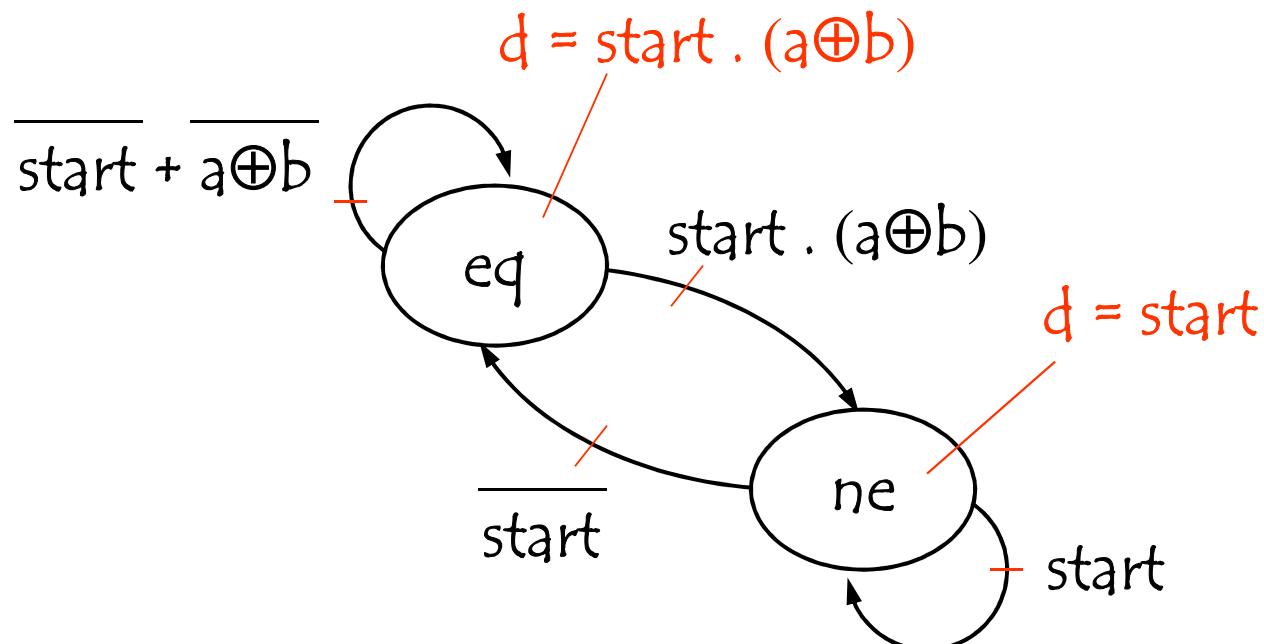

2 states \longrightarrow 1 memory element

Sequential Circuits

Representation of a sequential circuit ?

- State graph

$$G = (X, Y, S, T, O)$$


define the number of memory elements
required to represent $S : M$

represent each state s by a vector of M



Sequential Circuits

- Example

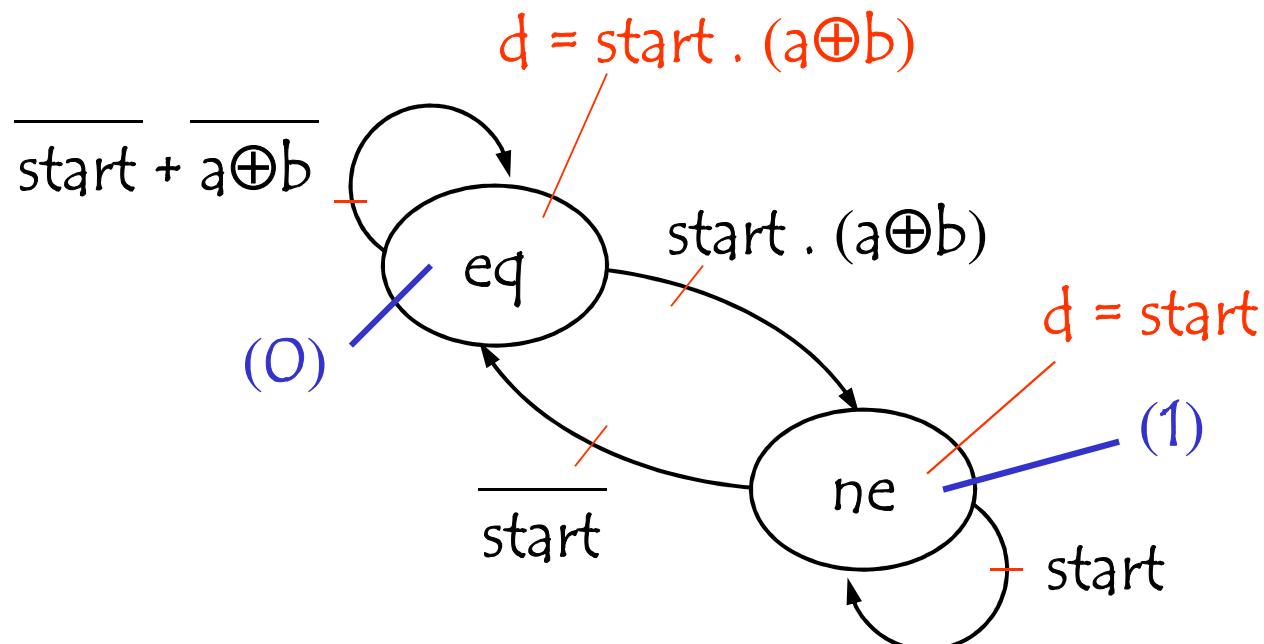

2 states \rightarrow 1 memory element

Sequential Circuits

Representation of a sequential circuit ?

- State graph

$$G = (X, Y, S, T, O)$$


define the *transition function* : m_k

m_k = sum of the Boolean function of the transitions
that have as target a state where $m_k=1$



Sequential Circuits

- Example

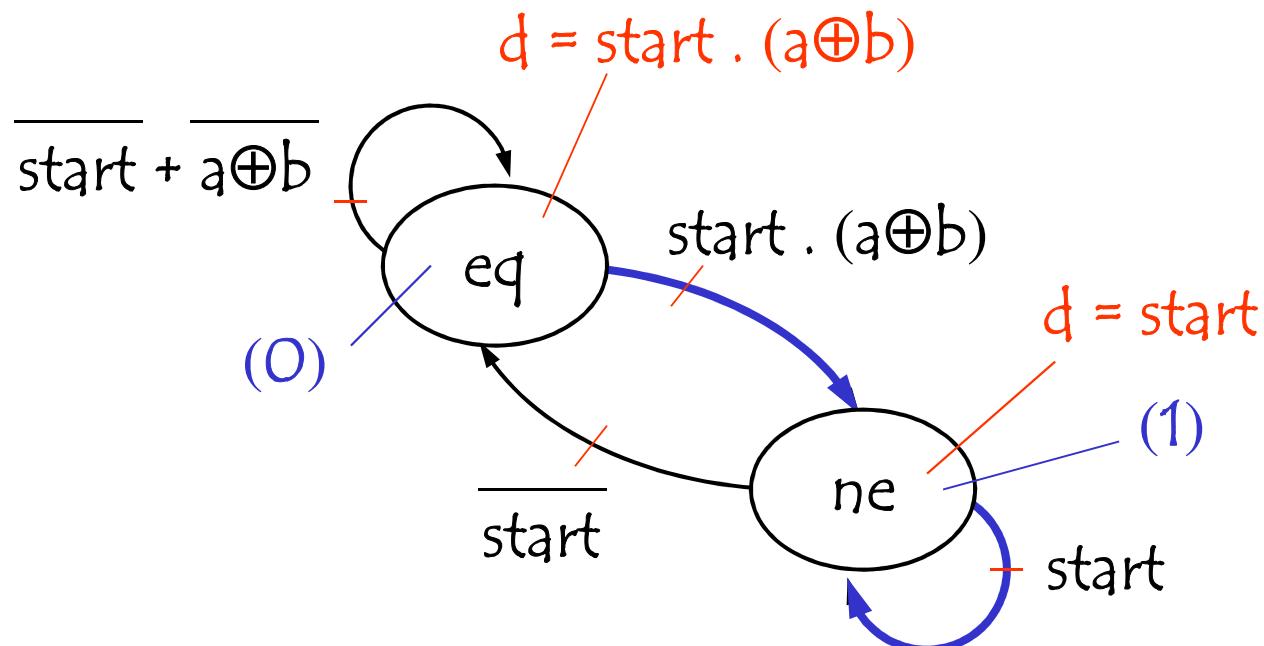

$$m_1 = \overline{m_1} \cdot \text{start} \cdot (a \oplus b) + m_1 \cdot \text{start}$$

Sequential Circuits

Representation of a sequential circuit ?

- State graph

$$G = (X, Y, S, T, O)$$


define the *output function* : y_j

y_j = sum of the output conditions concerning y_j



Sequential Circuits

Example

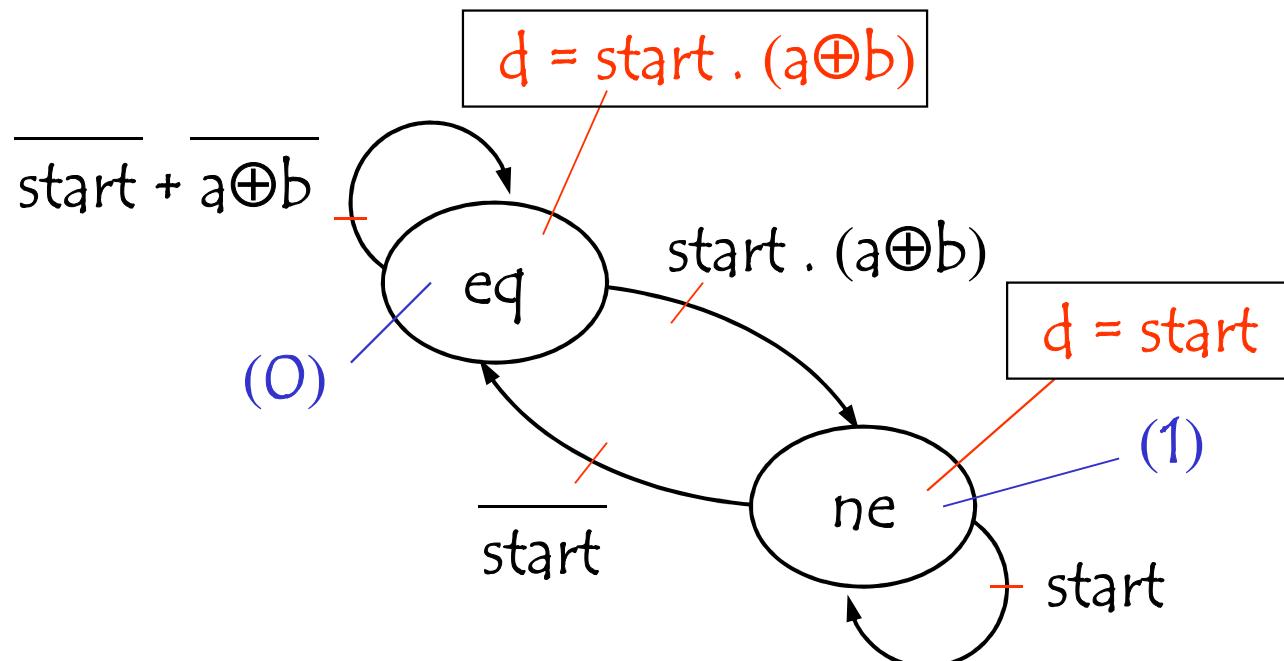

$$d = \overline{m_1} \cdot \text{start} \cdot (a \oplus b) + m_1 \cdot \text{start}$$

Sequential Circuits

Representation of a sequential circuit ?

- State graph

$$G = (X, Y, S, T, O)$$

implement the Boolean functions : m_k, y_j




Sequential Circuits

Example

$$m_1 = \overline{m_1} \cdot \text{start} \cdot (a \oplus b) + m_1 \cdot \text{start}$$

$$d = \overline{m_1} \cdot \text{start} \cdot (a \oplus b) + m_1 \cdot \text{start}$$
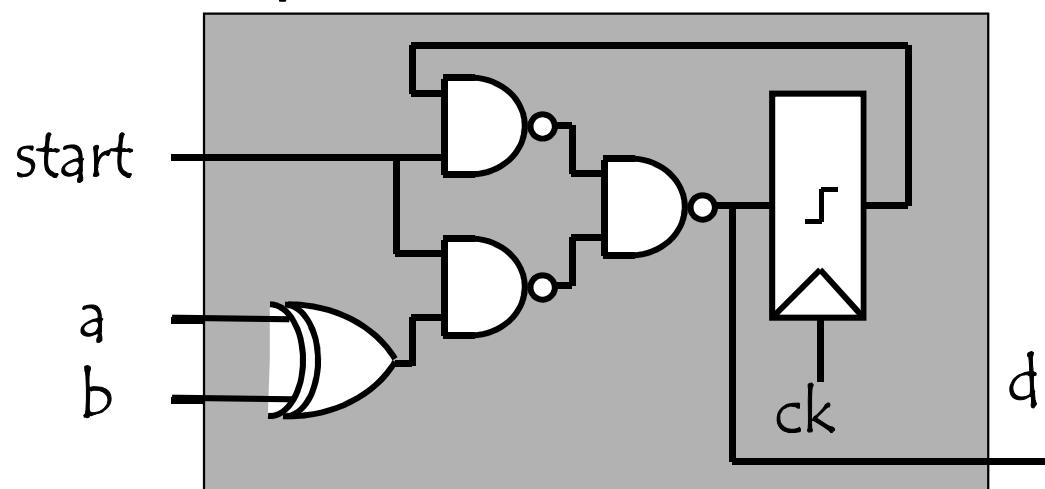
$$m_1 = \text{start} \cdot (a \oplus b) + \text{start} \cdot m_1$$



Sequential Circuits

How can I design a sequential circuit (summary) ?

$$\bullet G = (X, Y, S, T, O)$$

- graphic representation of the behavior
- define the number of memory elements required to represent $S : M$
- represent each state by a vector of M
- define the *transition function*
- define the *output function*
- implement the Boolean functions

Sequential Circuits

How can I design a sequential circuit (summary) ?

○ $G = (X, Y, S, T, O)$

- check the completeness
for each state s :

$$\sum_{t_i=(s, s'_i, f_i)} f_i = 1$$

- check the exclusivity

for each state s :

$$\sum_{\substack{t_i=(s, s'_i, f_i) \\ t_j=(s, s'_j, f_j) \\ i \neq j}} f_i \cdot f_j = 0$$

