

301/1352

**MCIROPROCESSOR LABORATORY SEVENTH COURSE  
ON  
BASIC VLSI DESIGN TECHNIQUES**

**29 October - 23 November 2001**

---

***ADDENDUM TO LECTURE NOTES***

*by*

Sandro CENTRO  
Dipartimento di Fisica "G. Galilei"  
Universita' degli Studi di Padova  
Via F. Marzolo 8  
35131 Padova  
ITALY


---

These are preliminary lecture notes intended only for distribution to participants.



## INTRODUCTION

ANY AMPLIFIER COULD BE THOUGH AS A:

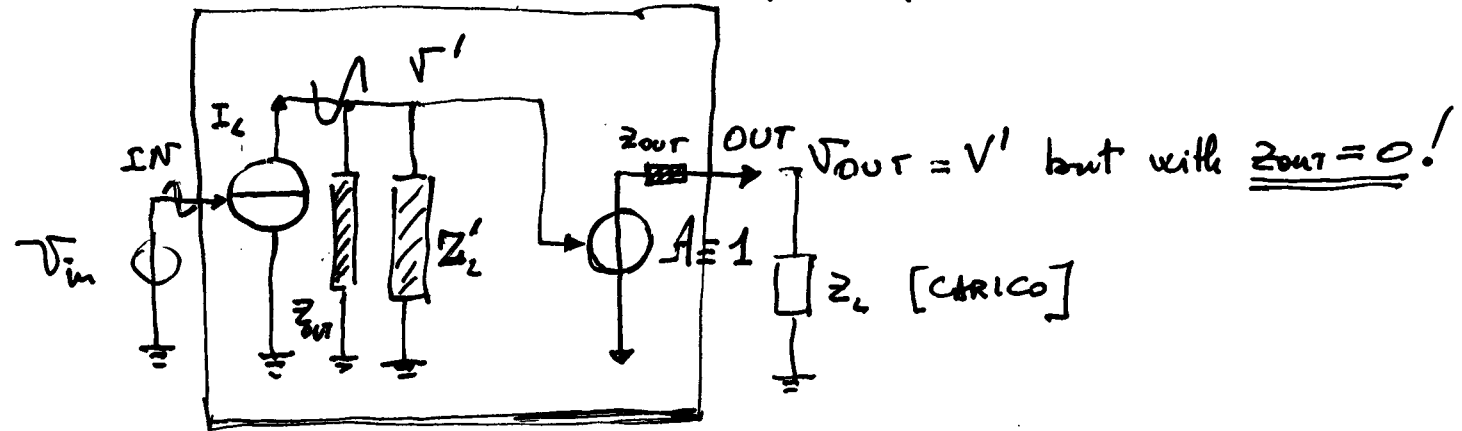

VOLTAGE CONTROLLED CURRENT GENERATOR, THAT  
CAN BE FOLLOWED BY VOLTAGE CONTROLLED VOLTAGE  
GENERATOR, NORMALLY WITH GAIN "1"



$$\boxed{\frac{I_L}{V_{in}} = g_m}$$

$$V' = I_L \cdot Z = V_{OUT}$$

TRANSCONDUCTANCE [mho, siemens]

$$\boxed{\frac{V_{OUT}}{V_{in}} = g_m \frac{Z'}{Z}} \quad [Z_{OUT} = \infty]$$

## BASIC ENGINES TO MAKE AMPLIFIERS:

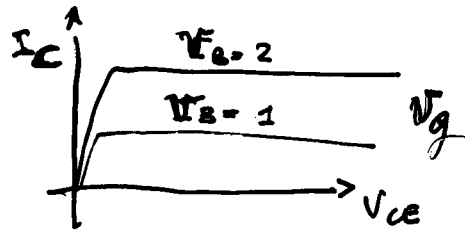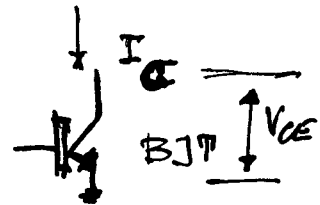

$$\frac{I_C}{V_g} = g_T = \frac{1}{r_e}$$

$$r_e = \frac{K T}{q} \cdot \frac{1}{I_C} = \frac{25 \text{ mV}}{I_C [\text{mA}]}$$



$1.38 \cdot 10^{-23} \text{ JK}^{-1}$

$1.6 \cdot 10^{-19} \text{ C}$

$$= 5 \div 250 \Omega$$



$$g_T = \underline{4 \div 200 \text{ mS}}$$

1 (ma Zinficeste)

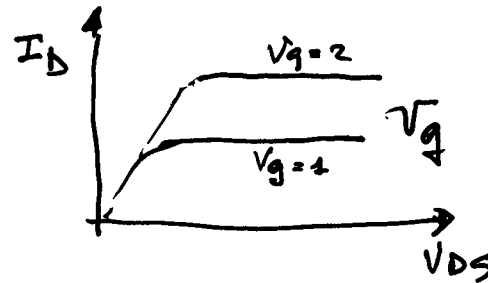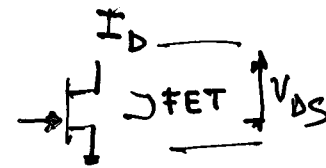

$$\frac{I_D}{V_g} = g_m$$
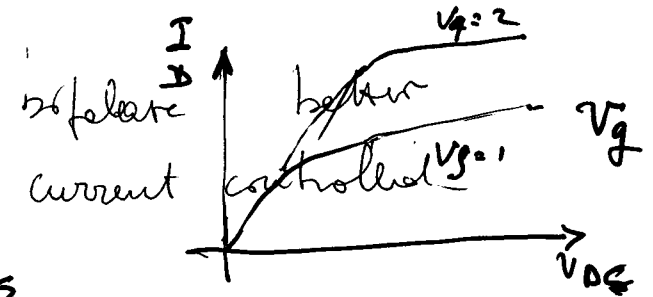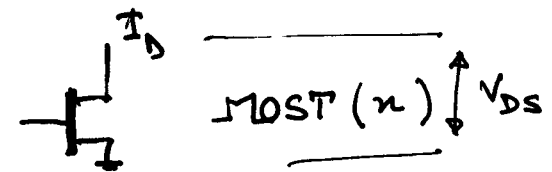
$$g_m = \underline{.5 \div 20 \text{ mS}}$$




$$\frac{I_D}{V_g} = g_m$$

$$g_m = \underline{.05 \div 2 \text{ mS}}$$

1/10 (ma Zinficeste)

1/100 (ma Zinficeste)

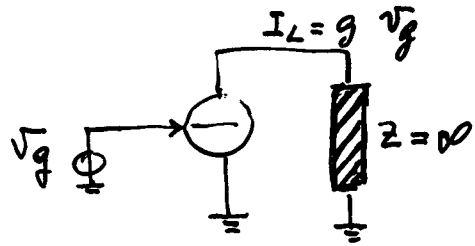WHICH IS THE LIMIT FOR THE AMPLIFICATION OF A SINGLE ENGINE ??



THEN

$$Z_{MAX} = Z_{OUT} \text{ OF THE ELEMENT.}$$

BIPOLAR  $Z_{OUT} \rightarrow 10^5 \div 10^6 \Omega$

J-FET  $Z_{OUT} \rightarrow 10^5 \div 10^6 \Omega$


CMOS  $Z_{OUT} \rightarrow 10^4 \div 10^5 \Omega$

A<sub>LIMIT</sub>

400 ÷ 200'000

50 ÷ 20'000

.5 ÷ 200

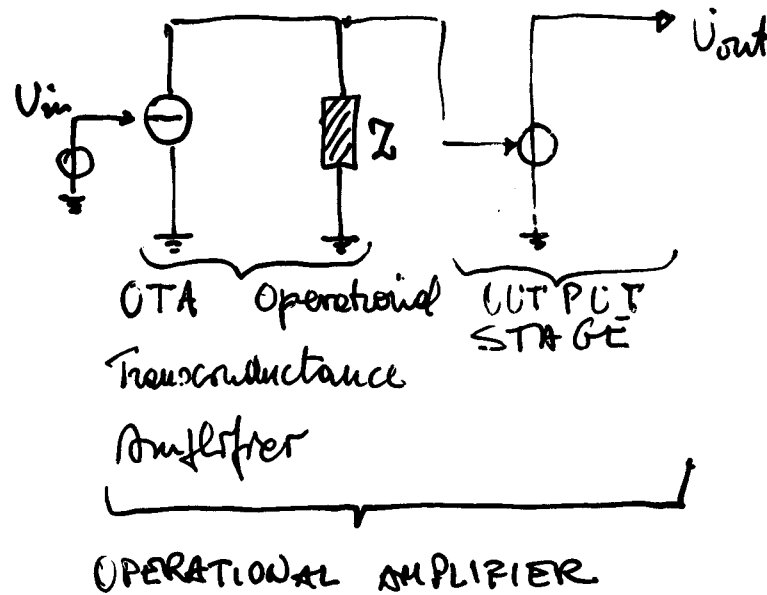

THERE ARE ALSO

$A_i = \frac{I_{out}}{I_{in}}$  OCA  $\rightarrow$  OP. Current Amp.

$A_f = \frac{V_{out}}{I_{in}}$  CMA  $\rightarrow$  Current Mode Amp.


$$A_V = \frac{V_{out}}{V_{in}}$$

$$BW = f_T$$

$$NB @ f_T \quad A_V = 1$$

$$GBW = A_V f_L = K (\text{constant}) = f_T \cdot 1$$

## OP. AMP. REQUIREMENTS :

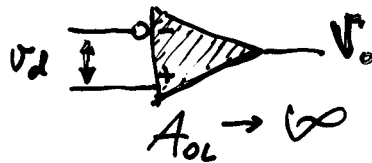


$$(10^4 \div 10^5)$$

$$A_{OL} = \frac{v_o}{v_d}$$

$$R_{inOL} \rightarrow \infty \quad (10^5 \div 10^8) \Omega$$

$$Z_{outOL} \rightarrow 0 \quad (50 \div 200) \Omega$$

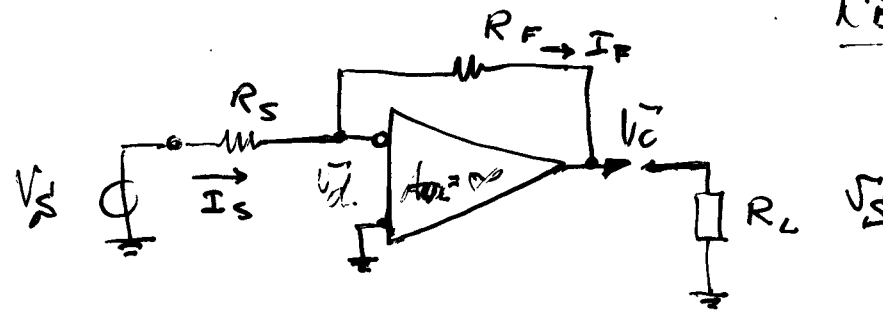IDEAL  $\uparrow$  $\downarrow$  REAL LIFE

$$\frac{v_o}{v_d} \rightarrow \infty$$

THAT  
MEANS  
 $v_d \rightarrow 0$

$$\frac{v_s - v_d}{R_s} = \frac{v_d - v_o}{R_f}$$

$$\text{COMBINING WITH } v_d = -\frac{v_o}{A_{OL}}$$

$$\boxed{A_f} = \frac{v_o}{v_s} = \frac{A_{OL} R_f}{R_f + R_s - A_{OL} R_s} \xrightarrow{A_{OL} \rightarrow \infty} -\frac{R_f}{R_s} = \boxed{A_{f,ideal}}$$

$$\sum v_d = 0$$

VIRTUAL GROUND  $\& S \quad I_s \equiv I_f$ 

$$\text{BECAUSE } Z_{inf} = \frac{R_f Z_{inOL}}{(1-A) Z_{inOL} + R_f} \approx \frac{R_f}{1-A} \xrightarrow{A \rightarrow \infty} 0$$


IS INFINITE  $A_{OL}$  GAIN NECESSARY TO HAVE

$$A_f = A_{f,ideal} = -R_F / R_S \quad ?$$


REMININDG THAT

$$\begin{aligned} A_f &= \frac{A_{OL} R_F}{R_F + R_S - A_{OL} R_S} = \frac{A_{OL} R_F / R_S}{R_F / R_S + 1 - A_{OL}} \\ &= \frac{A_{OL} A_{fi}}{A_{OL} - 1 + A_{fi}} = \frac{A_{fi}}{1 - \frac{1}{A_{OL}} + \frac{A_{fi}}{A_{OL}}} \end{aligned}$$
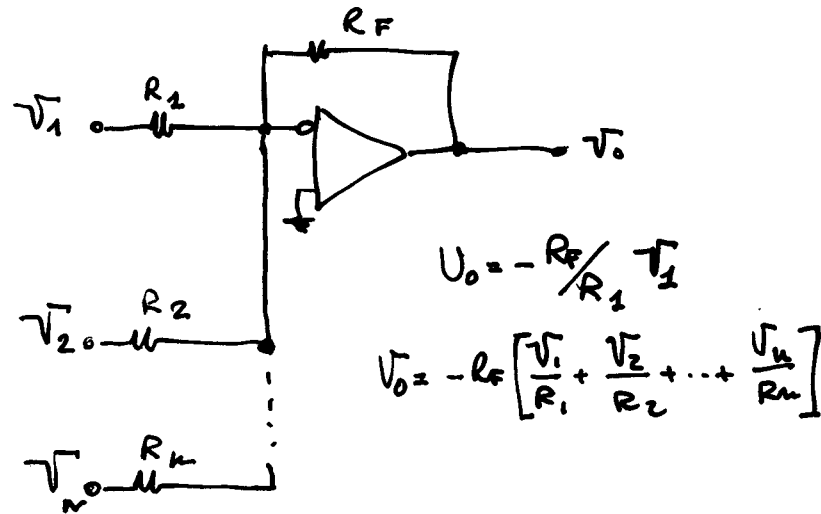
$$\approx \frac{A_{fi}}{1 + A_{fi}/A_{OL}} \xrightarrow{A_{OL} \rightarrow \infty} A_{fi} \quad \text{OR FOR } A_{OL} \gg A_{fi} !$$



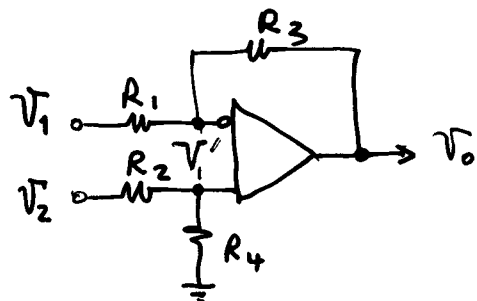$\Sigma$  WITHOUT COUPLING OF  $V_x$ , AS THE SUMMING NODE AS ZERO VOLTAGE.



FROM  $V' = \frac{V_2}{R_2 + R_4} * R_4$



$$\frac{V_1 - V'}{R_1} = \frac{V' - V_0}{R_3}$$

$$V_0 = V_2 \frac{R_4}{R_2 + R_4} \frac{R_1 + R_3}{R_1} - V_1 \frac{R_3}{R_1}$$

IF  $R_1 = R_2 = R_i$

$R_3 = R_4 = R$

$$V_0 = (V_2 - V_1) R / R_i$$

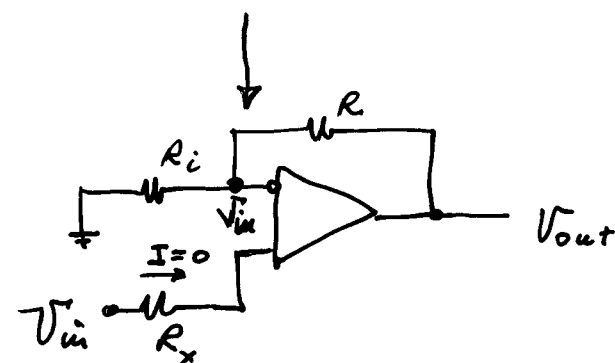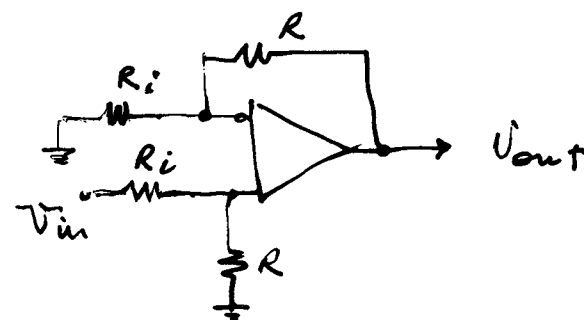

$$\frac{V_{out} - V_{in}}{R} = \frac{V_{in}}{R_i}$$

$$V_{out} = (1 + R/R_i) V_{in}$$


$$Z_{in} \Rightarrow \infty$$

$$A_{f+} = 1 + R_F/R_S \gg 1$$


WHILE

$$A_{f-} = -R_S/R_S \quad \text{NEGATIVE BUT "ANY" VALUE}$$

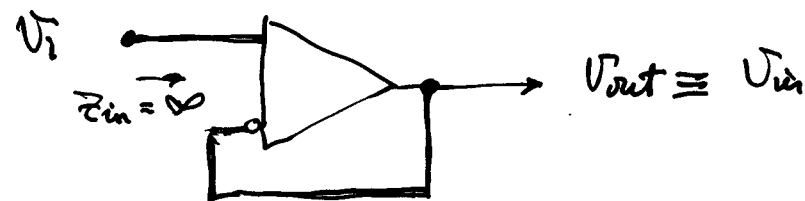$A_{f+} = 1$  if  $R_F/R_S$  THAT MEANS  $R_S = \infty$  THEN  $R_F$   
DON'T CARE, THEN:



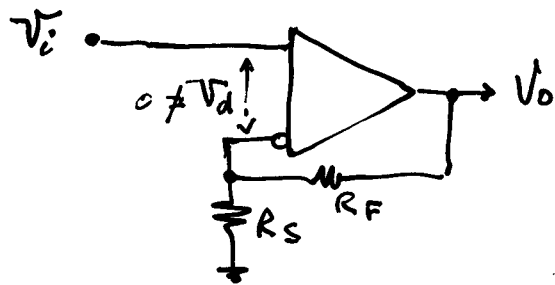AGAIN IN THE ASSUMPTION  $A_{OL} = \infty$ . DO WE NEED IT?



$$A_{fi} = \frac{R_S + R_F}{R_S} = 1 + \frac{R_F}{R_S}$$

$$V_d = V_i - \frac{V_O}{R_S + R_F} \cdot R_S$$

$$V_{out} = A_{OL} V_d = A_{OL} V_i - A_{OL} \frac{V_O}{R_S + R_F} R_S$$

$$A_{fi} = \frac{V_{out}}{V_{in}} = \frac{A_{OL}}{1 + A_{OL} \frac{R_S}{R_S + R_F}} \xrightarrow{A_{OL} \rightarrow \infty} = \frac{R_S + R_F}{R_S} = A_{fi}$$

$$A_{fi} = \frac{A_{OL}}{1 + A_{OL}/A_{fi}}$$

$$A_{fi} = A_{fi} \quad \text{IF } A_{OL} \rightarrow \infty \quad \text{OR } A_{fi} \ll A_{OL}$$

LET'S CALCULATE THE REAL UNITY GAIN FOR  $A_{OL} = 5 \times 10^4$


$$A_f = \frac{A_{OL}}{1 + A_{OL}} = \frac{5 \times 10^4}{1 + 5 \times 10^4} = .9999800004 \approx$$

AND FOR  $A_{OL} = 1000$

$$A_f = \frac{10^3}{1 + 10^3} = .99900 \quad \text{STILL QUITE GOOD.}$$

CAN WE MAKE NON INVERTING SUM ?

YES, BUT...

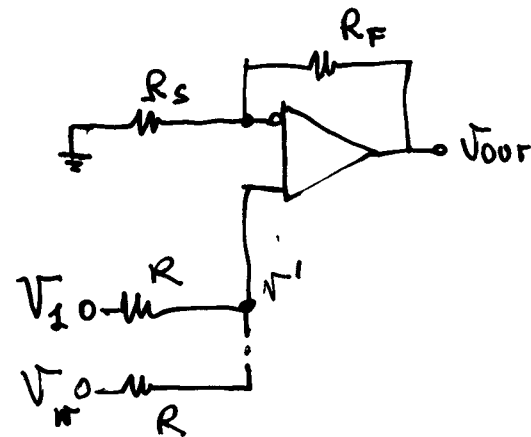

$$V_1' = \frac{V_1}{R + \frac{R}{N-1}} \cdot \frac{R}{N-1} = \frac{V_1}{N}$$

...


$$V_N' = \frac{V_N}{N}$$

$$V_o = \left(1 + \frac{R_F}{R_S}\right) \frac{1}{N} (V_1 + V_2 + \dots + V_N)$$

EACH GENERATOR  $V_i$  SEES THE OTHERS, SO ITS  
LOAD IS NOT CONSTANT!

LET'S USE ANOTHER METHOD TO CALCULATE MORE  
PRECISELY THE  $Z_{inf}$ , INPUT IMPEDANCE WITH  
FEEDBACK.


WE USE THE MILLER EFFECT

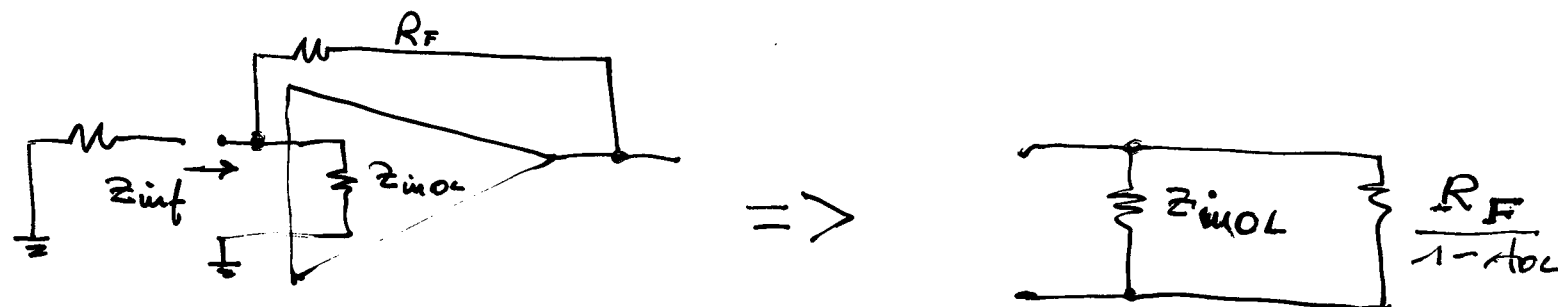

$$Z_{inf} = Z_{inOL} \parallel \left[ \frac{R_F}{1 - A_{OL}} \right]$$

$$= \frac{Z_{inOL} R_F}{R_F + Z_{inOL} (1 - A_{OL})} \rightarrow \frac{R_F}{1 - A_{OL}} \rightarrow \phi$$

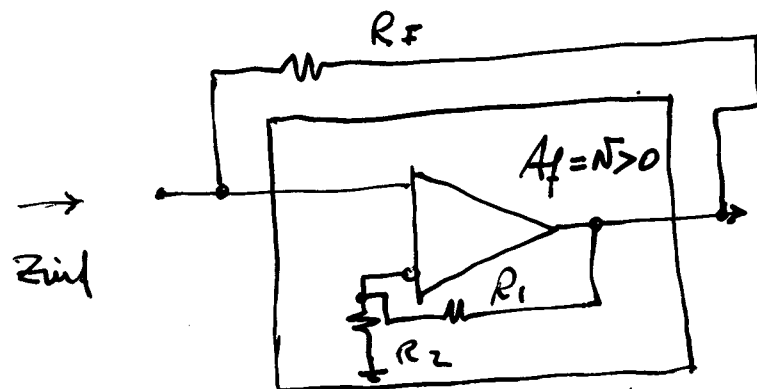BUT THIS HOLDS FOR ANY SIGN OF  $A_{OL}$   
EVEN FOR  $A_{OL} > 0 \dots$




$$A_f = 1 + R_F/R_2 \geq 1$$

$$Z_{inf} = \frac{Z_{inOL} R_F}{R_F + Z_{inOL} (1 - A_{OL})}$$


$Z_{inOL} = \infty$  NOW AND  $A_{OL} = N > 0$  THEN (REMEMBER  $A_{OL} > 1$  ALSO)

$$Z_{inf} = \frac{-R_F}{N-1} \leq \phi !$$

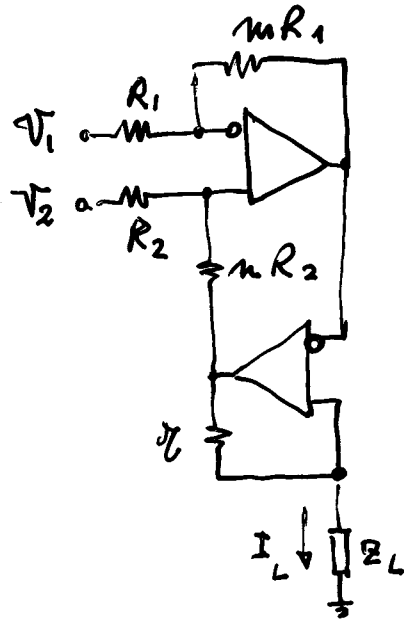WE CAN USE IT TO GENERATE INFINITE IMPEDANCES!



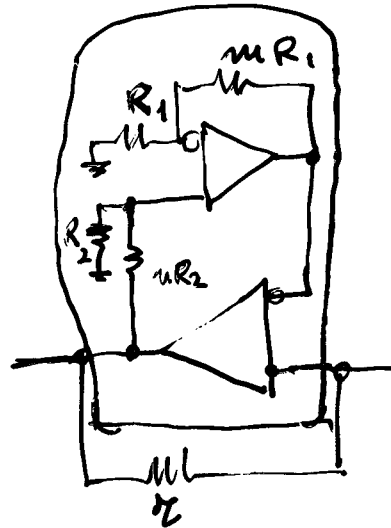WE WANT TO MAKE A VOLTAGE  $(V_2 - V_1)$  CURRENT GENERATOR.  
THE IMPEDANCE SEEN FROM LOAD  $Z_L$  MUST BE  $\infty$ .



$$Z_{in} = \frac{Z_{in} R_F}{R_F + Z_{in} (1 - A_{OL})}$$


$$R_F = R \quad Z_{in} = \infty$$

$$Z_{in} = \frac{R}{1 - A_{OL}} \quad \text{TO HAVE } Z_{in} = \infty$$

$$A_{OL} \text{ MUST BE } = 1$$

THAT MEANS  $m = m$   
HAVE  $I_L$  INDEPENDENT  
THE VALUE OF  $I_L$  ?

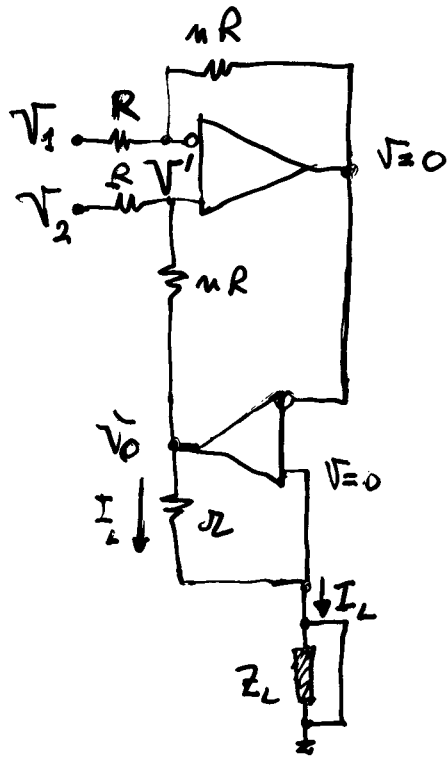CONDITION TO  
FROM  $Z_L$ . BUT WHICH IS




$$V_1' = \frac{V_1}{R+nR} \cdot nR = \frac{V_1 n}{1+n}$$

$$V_2' = \frac{V_2 - V_0}{R+nR} \cdot nR + V_0 = \frac{V_2 - V_0}{1+n} n + V_0$$

$$\begin{aligned} V_1' \frac{n}{1+n} &= \frac{V_2 n}{1+n} - V_0 \left[ \frac{n}{1+n} - 1 \right] \\ &= \frac{V_2 n}{1+n} + V_0 \left[ \frac{1}{1+n} \right] \end{aligned}$$

$$V_0 = (V_1 - V_2) n$$

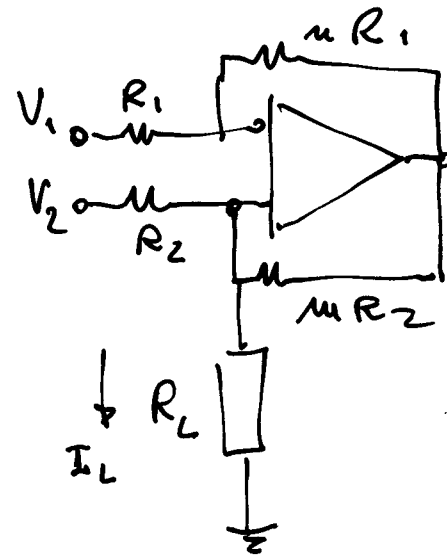
$$I_L = \frac{V_0}{Z_L} = \frac{V_1 - V_2}{Z_L} n$$




TRY TO FIND THE CONDITION  
TO HAVE  $I_L = f(V_1, V_2)$

OR

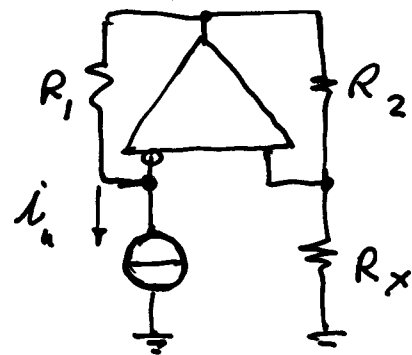④ CALCULATE  $I_L$  ON  $R_x$  AS A FUNCTION OF  
 $R_1$  &  $R_2$




Single pole system

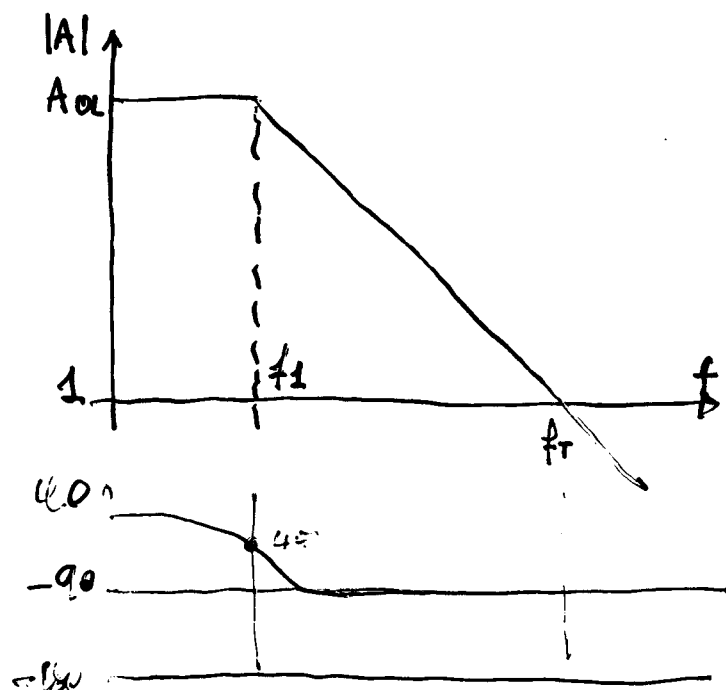


$$A = \frac{A_0}{1 + j f/f_1}$$

Two pole system

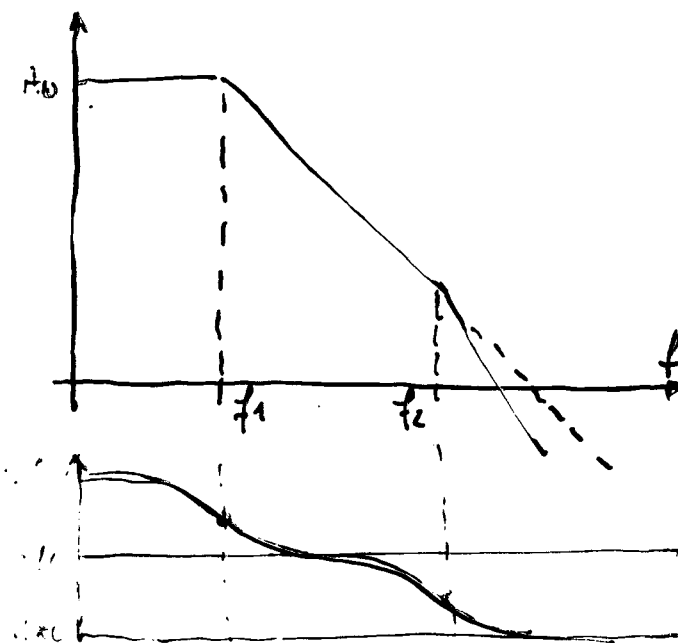

$$\frac{A_0}{(1 + j f/f_1)(1 + j f/f_2)}$$


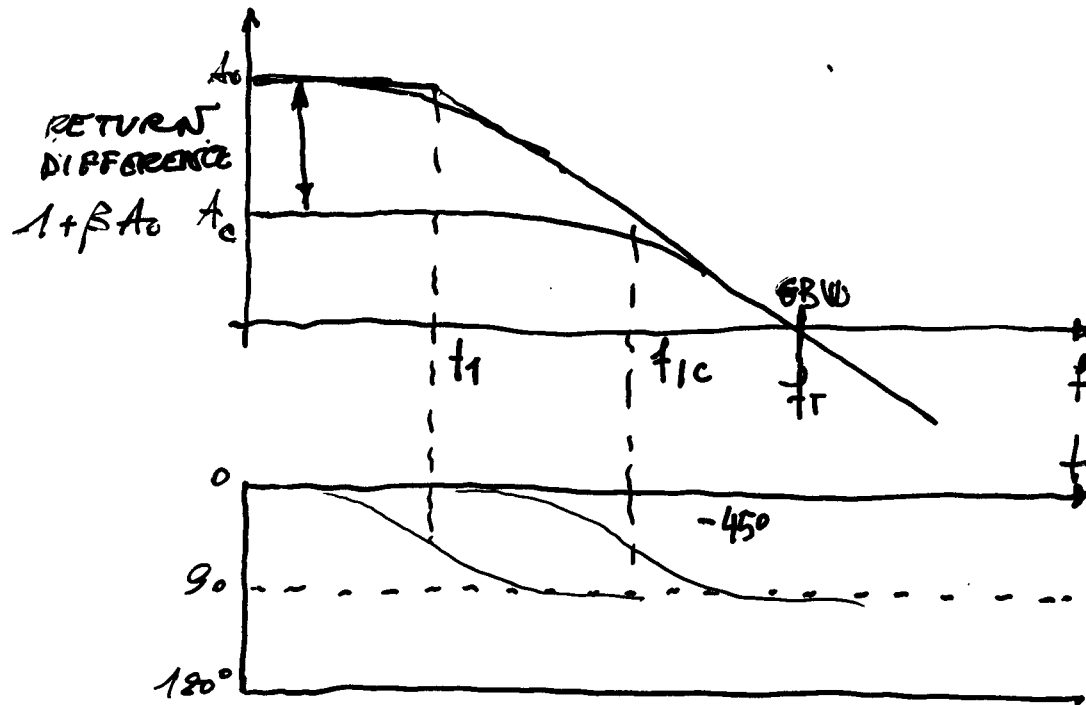
CLOSED LOOP GAIN  $A_c$  IN A ONE-POLE SYSTEM



$$A_0 f_1 = 1 * f_T \quad \text{GBW}$$

$$A_c f_{1c} = f_T$$
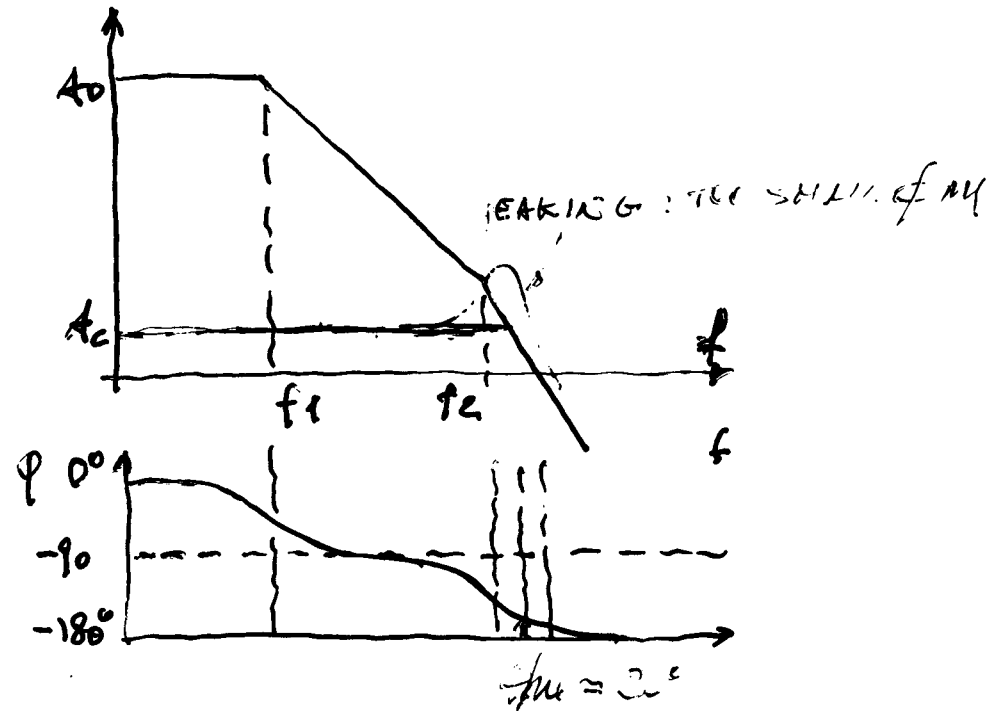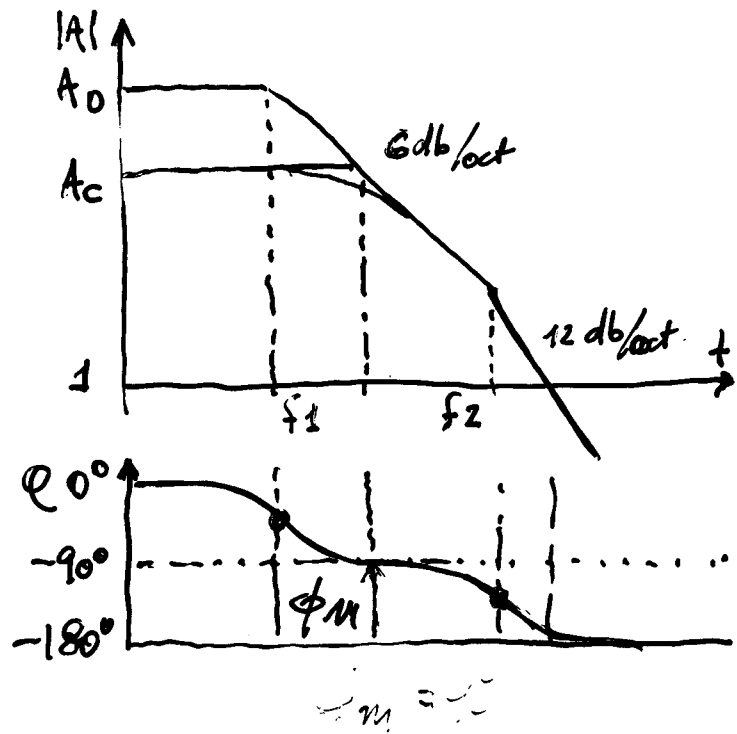
# TWO POLES SYSTEM WITH DIFFERENT CLOSED LOOP GAINS $A_c$



ALMOST READY TO OSCILLATE

THE CRITERION FOR STABILITY AGAINST OSCILLATION IN CLOSED LOOP IS:

THE OPEN LOOP PHASE SHIFT MUST BE LESS THAN  $180^\circ$   
AT THE FREQUENCY AT WHICH THE LOOP GAIN (IN THE  
FEEDBACK CONFIGURATION) IS UNITY.

$$\text{NB } A_c = \frac{A_o}{1 + \beta A_o}$$

$$\frac{1 + \beta A_o}{\beta A}$$

RETURN DIFFERENCE  
LOOP GAIN

$$\underset{A_o \rightarrow \infty}{\approx} \frac{1}{\beta}$$

THE HARDEST CONDITION IS WHEN THE AMPLIFIER CONNECTED AS  
FOLLOWER AS LOOP GAIN EQUALS THE OPEN LOOP GAIN AT THE  
 $\frac{1}{\beta}$  WHERE THE PHASE SHIFT IS  $180^\circ$ .