



***ICTP-UNU-Microprocessor Laboratory
Fifth Course on Basic VLSI Design Techniques***

9 November - 4 December 1998

**ANALOGUE VLSI DESIGN
Part 9**


Sandro CENTRO
Dipartimento di Fisica "G. Galilei"
Universita' degli Studi di Padova
via Marzolo, 8
35131 Padova
Italy

These are preliminary lecture notes intended only for distribution to participants

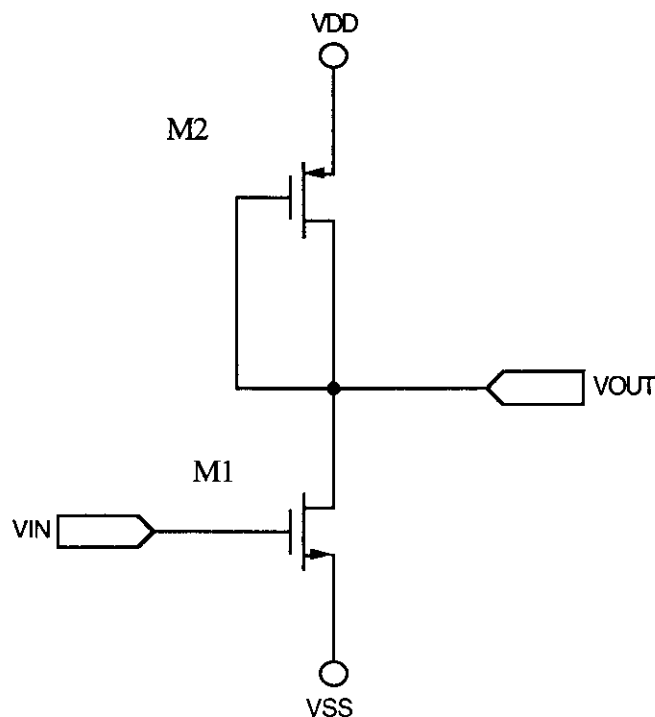9. SIMPLE AMPLIFIERS

- The inverter is the basic gain stage of CMOS circuits. Typically the inverter uses the common source configuration with either a resistor for a load or a current sink/source as an active load.


A very common circuit is given in the following figure.



- The current through M2 is found from (5.5) assuming that


$$V_{DS} = V_{GS} - V_T$$

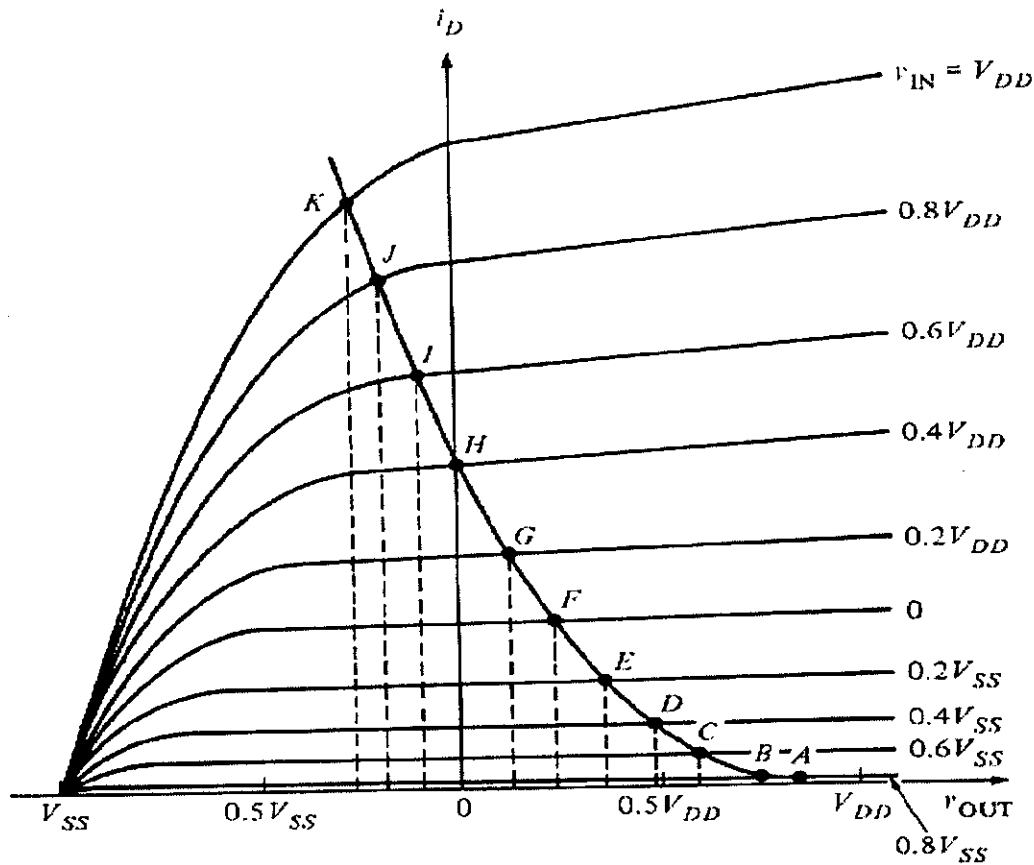In the graph the working point is given as the intersection between the **M1** characteristic and **M2** load curve.



• From the following equivalent circuit one can obtain the small signal gain as
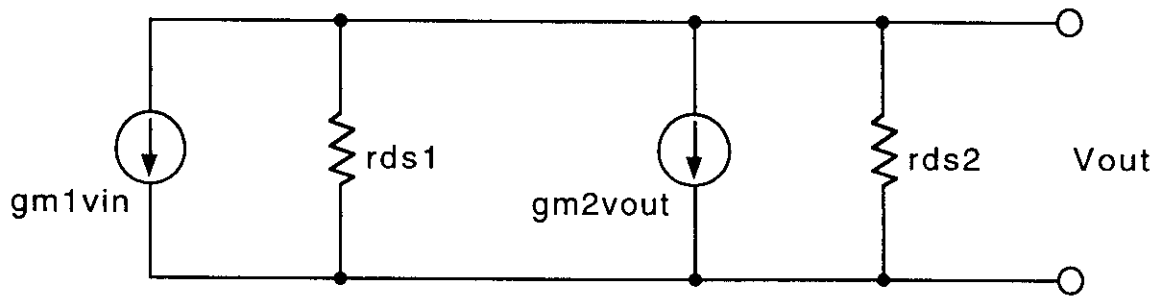
$$\begin{aligned} \frac{v_{OUT}}{v_{IN}} &= \frac{-g_{m1}}{g_{ds1} + g_{ds2} + g_{m2}} \cong \frac{g_{m1}}{g_{m2}} \\ &= -\frac{K'_N W_1 L_2}{K'_P W_2 L_1} \end{aligned}$$



•A modified version of the inverter is shown in the following figure where the load is a current generator, that could mirror another current.



The small signal equivalent circuit misses now the second current generator and the small signal gain is obtained, using (6.1a) and (6.3a), as

$$\frac{v_{OUT}}{v_{IN}} = \frac{-g_{m1}}{g_{ds1} + g_{ds2}} = \sqrt{\frac{2K_N' W_1}{L_1 I_D}} \left(\frac{-1}{\lambda_1 + \lambda_2} \right) \quad (9.1)$$



We see that the gain increases as the current I_D decreases. This holds true until the transistor work in the saturation region.

Gains of -500 and little more can be obtained by this stage.

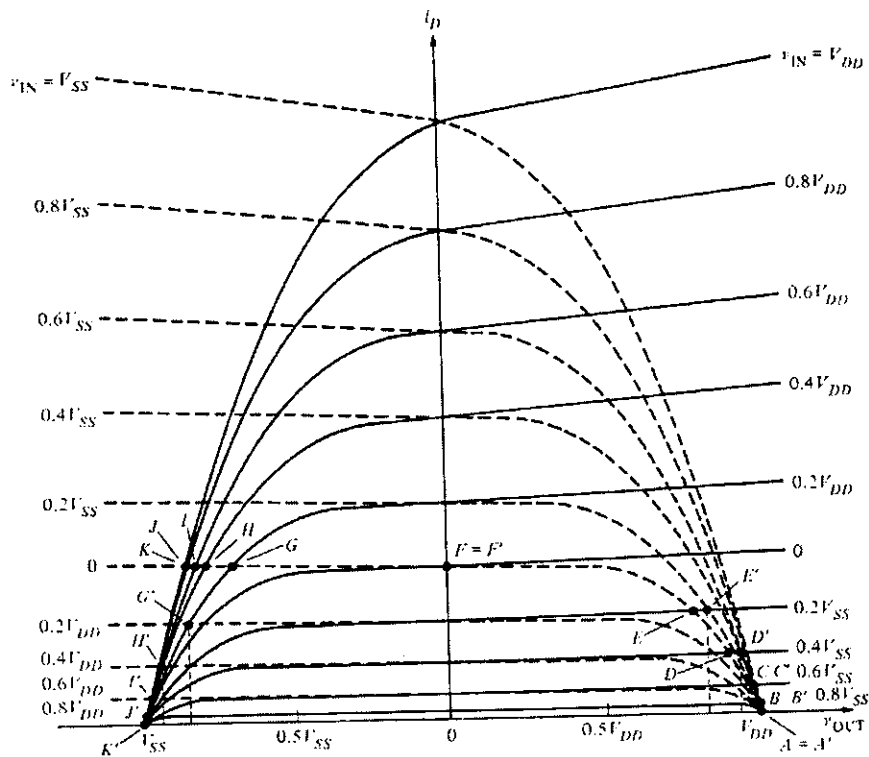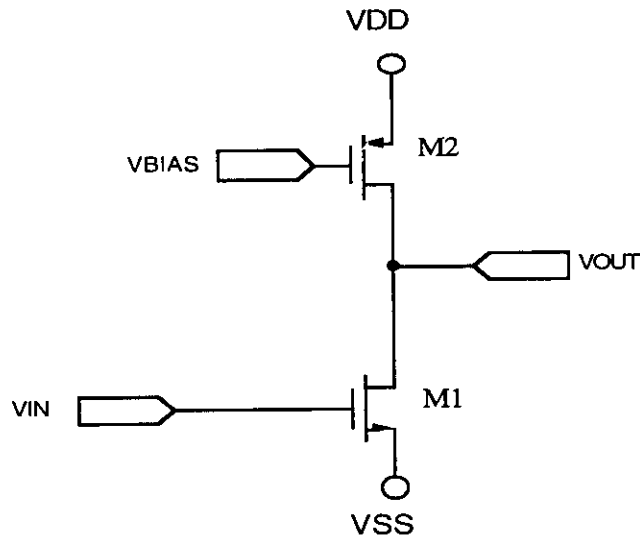The graph gives the transfer characteristic of this type of inverter.



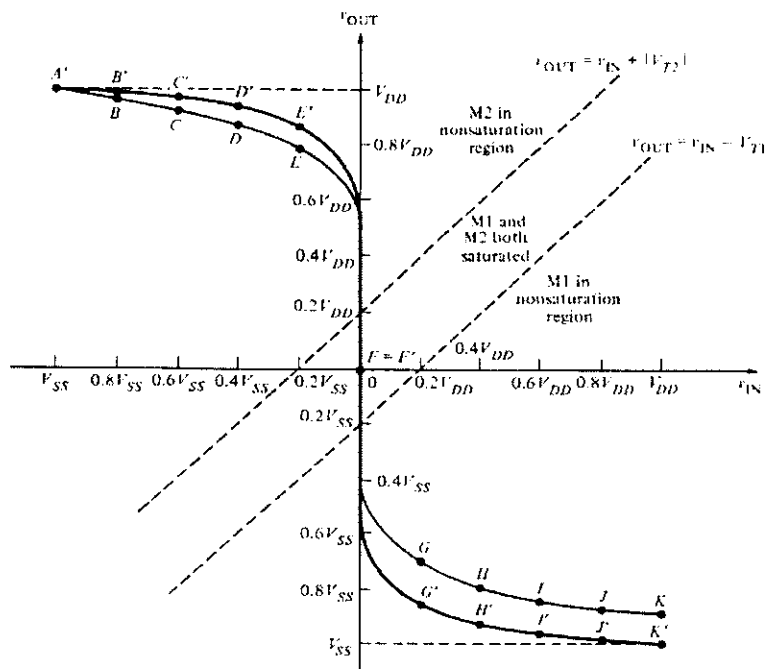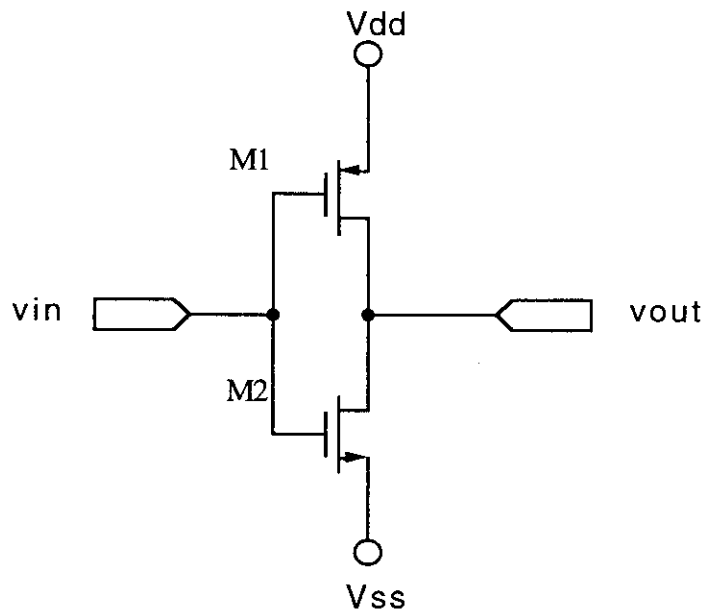- Another type of inverter is the push-pull inverter given in the figure.



Transfer characteristics of CMOS inverters ($V_{T1} = |V_{T2}| = 0.2 V_{DD}$)


The gain, using the small signal equivalent circuit and the already used formulas, is given by


$$\frac{v_{OUT}}{v_{IN}} = \frac{-g_{m1} - g_{m2}}{g_{ds1} + g_{ds2}}$$

$$= \sqrt{2/I_D} \left(\sqrt{\frac{K_N' W_1}{L_1}} + \sqrt{\frac{K_P' W_2}{L_2}} \right) \left(\frac{-1}{\lambda_1 + \lambda_2} \right) \quad (9.2)$$

Gains in the order of -1000 can be easily obtained.

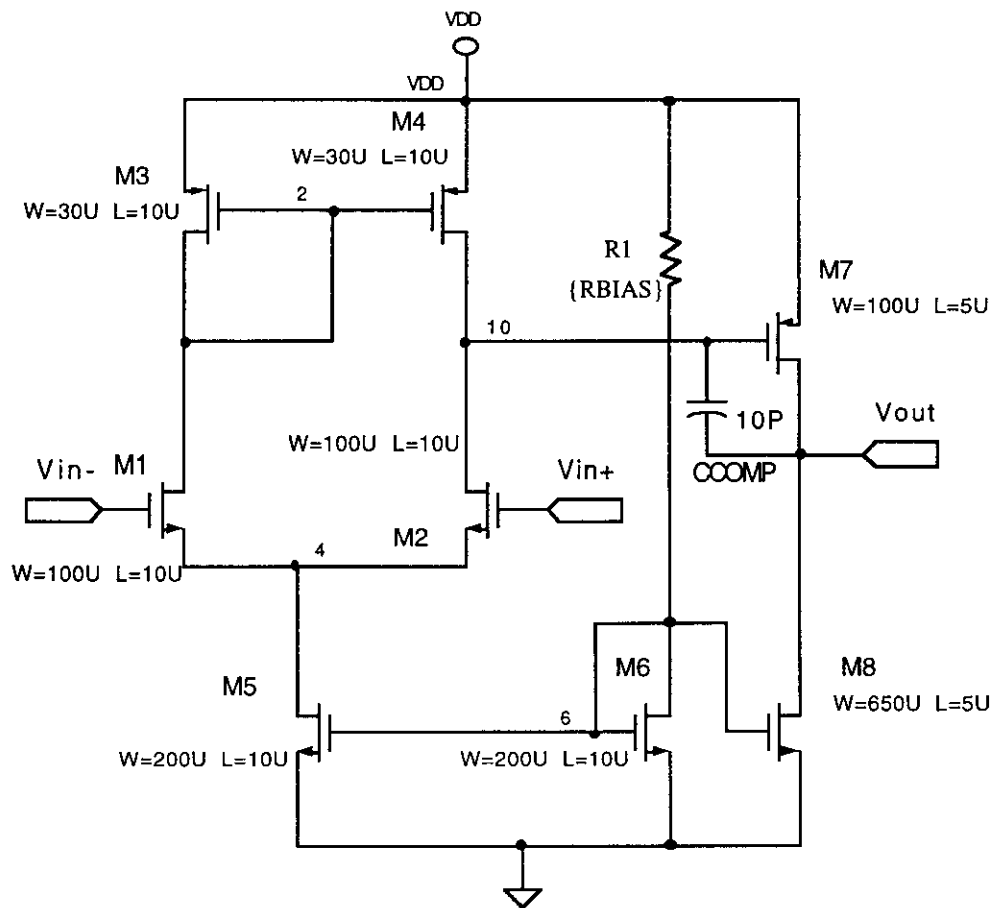- Differential amplifiers can be designed with CMOS technology. In the following figures two different structures are shown: one uses n-type input stage while the second uses the p-type input.



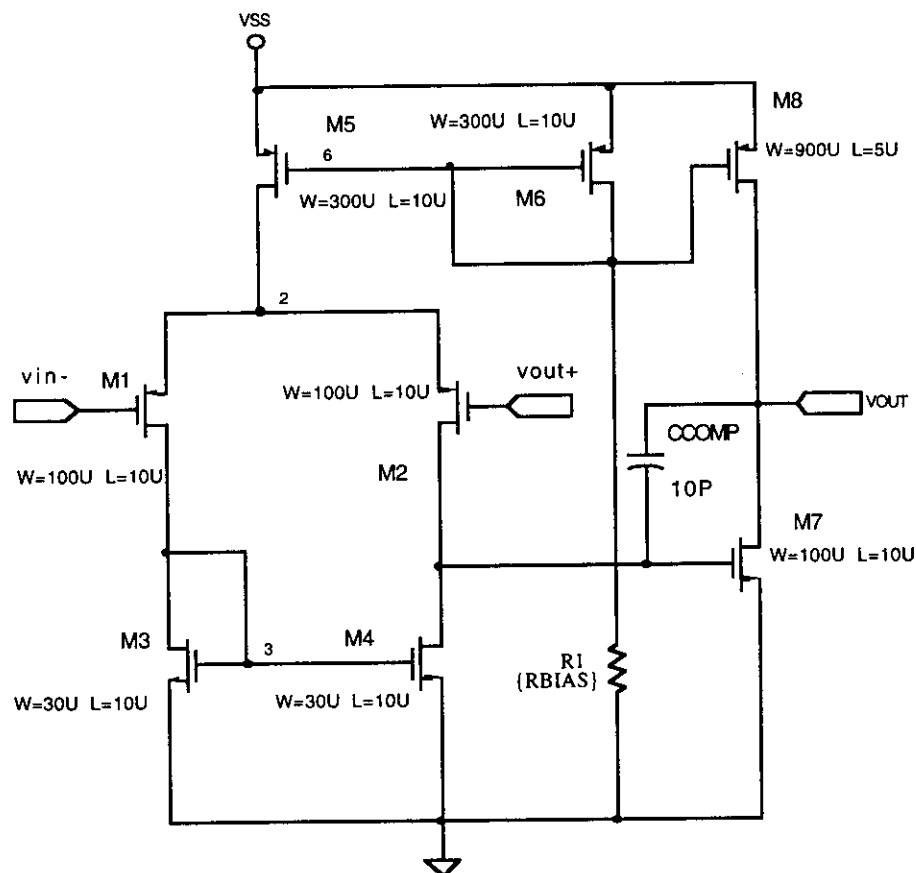

The two circuits have been simulated with models **LEVEL2** and the sub circuits given in the section 7.

The SPICE listing of the two amplifiers is given.

SUBCIRCUITS and MODELs have been written and put in a library CUBA.lib.

```

.SUBCKT AMP_CUBA_n VIN+ VIN- VDD VSS VOUT PARAMS: RBIAS=200K
X1 2 VIN- 4 VSS TN_2_CUBAQb PARAMS: WN=100U LN=10U
X2 10 VIN+ 4 VSS TN_2_CUBAQb PARAMS: WN=100U LN=10U
X3 2 2 VDD VDD TP_2_CUBAQb PARAMS: WP=30U LP=10U
X4 10 2 VDD VDD TP_2_CUBAQb PARAMS: WP=30U LP=10U
X5 4 6 VSS VSS TN_2_CUBAQb PARAMS: WN=200U LN=10U
X6 6 6 VSS VSS TN_2_CUBAQb PARAMS: WN=200U LN=10U
X7 VOUT 10 VDD VDD TP_2_CUBAQb PARAMS: WP=100U LP=10U
X8 VOUT 6 VSS VSS TN_2_CUBAQb PARAMS: WN=650U LN=5U
CCOMP VOUT 10 10PF
R1 VDD 6 {RBIAS}
.ENDS AMP_CUBA_n
*****

.SUBCKT AMP_CUBA_p VIN+ VIN- VDD VSS VOUT PARAMS: RBIAS=200K
*
*
X1 3 VIN- 2 VDD TP_2_CUBAQb PARAMS: WP=100U LP=10U
X2 10 VIN+ 2 VDD TP_2_CUBAQb PARAMS: WP=100U LP=10U
X3 3 3 VSS VSS TN_2_CUBAQb PARAMS: WN=30U LN=10U
X4 10 3 VSS VSS TN_2_CUBAQb PARAMS: WN=30U LN=10U
X5 2 6 VDD VDD TP_2_CUBAQb PARAMS: WP=300U LP=10U
X6 6 6 VDD VDD TP_2_CUBAQb PARAMS: WP=300U LP=10U
X7 VOUT 10 VSS VSS TN_2_CUBAQb PARAMS: WN=100U LN=10U
X8 VOUT 6 VDD VDD TP_2_CUBAQb PARAMS: WP=900U LP=5U
CCOMP VOUT 10 10PF
R1 VSS 6 {RBIAS}
.ENDS AMP_CUBA_p
*****

.SUBCKT TN_2_CUBAQb      D      G      S      BK      PARAMS:  WN=3U
      LN=2U
M1      D      G      S      BK      2_CUBAQN W={WN} L={LN}
+AD={2U*WN} AS={2U*WN} PD={2U+(2*WN)} PS={2U+(2*WN)}
+NRD={2U/WN} NRS={2U/WN}
.ENDS TN_2_CUBAQb
*****
* PMOS_CAE
.SUBCKT TP_2_CUBAQb      D      G      S      BK      PARAMS:  WP=3U
      LP=2U
M1      D      G      S      BK      2_CUBAQP W={WP} L={LP}
+AD={2U*WP} AS={2U*WP} PD={2U+(2*WP)} PS={2U+(2*WP)}
+NRD={2U/WP} NRS={2U/WP}
.ENDS TP_2_CUBAQb
*****
*
*      2_CUBAQ 2um CMOS
*****
* typical parameters
*
.MODEL 2_CUBAQN NMOS LEVEL=2
+ CGSO =0.560E-09 CGDO =0.560E-09 CGBO =0.165E-09
+ CJ   =0.400E-03 MJ   =0.500E+00 CJSW =0.390E-09 MJSW =0.060E+00
+ JS   =0.020E-03 PB   =0.860E+00 RSH  =30.00E+00 XQC  =1E+00
+ TOX  =31.10E-09 XJ   =0.054E-06 LD   =0.338E-06 WD   =0.644E-06
+ VTO  =0.770E+00 NSUB =33.10E+15 NFS  =0.293E+12 NEFF =3.560E+00
+ UO   =582.0E+00 UCRIT=20.90E+04 UEXP =0.235E+00 UTRA  =0.000E+00
+ VMAX =86.00E+03 DELTA=0E+00
*
.MODEL 2_CUBAQP PMOS LEVEL=2
+ CGSO =0.560E-09 CGDO =0.560E-09 CGBO =0.165E-09


```

```

+ CJ  =0.360E-03 MJ  =0.500E+00 CJSW =0.310E-09 MJSW =0.010E+00
+ JS  =0.040E-03 PB  =0.790E+00 RSH  =81.00E+00 XQC  =1E+00
+ TOX  =31.10E-09 XJ  =0.021E-06 LD   =0.315E-06 WD   =0.731E-06
+ VTO  =-.804E+00 NSUB =11.80E+15 NFS  =0.337E+12 NEFF =2.030E+00
+ UO   =180.0E+00 UCRIT =19.70E+04 UEXP =0.219E+00 UTRA  =0.000E+00
+ VMAX =41.20E+03 DELTA =1.040E+00
*****

```

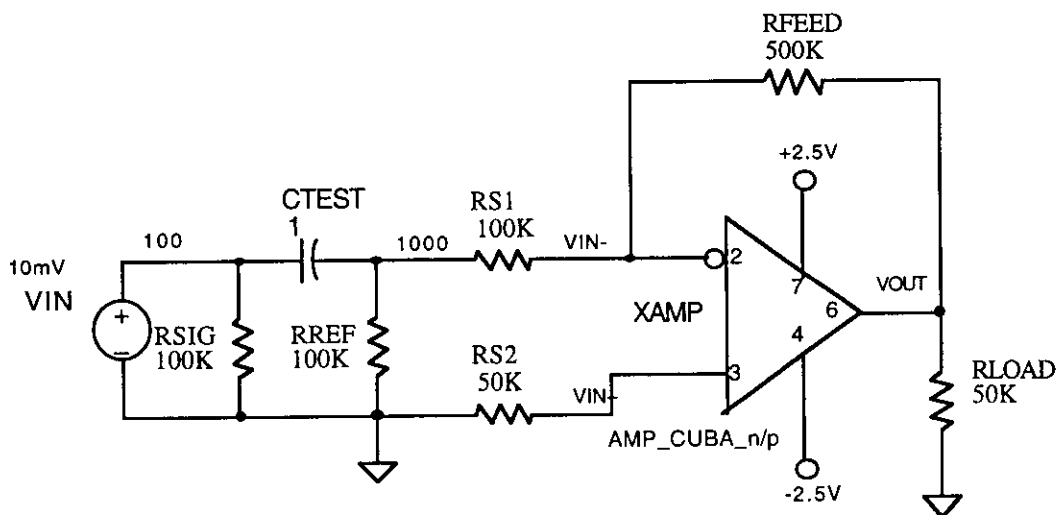- Then the following circuit has been simulated both for the n-type and p-type to find the AC and TRAN responses.



9.11

SPICE File_1

*****ANALISYS OF DIFF_AMP N_TYPE

.lib CUBA.lib

.TRAN 1U 400u

.AC dec 10 10 20MEG

Vin 100 0 ac 10m pwl(0 0V 100u 0V 110u -100mV 200u -100mV 210u 0 250U 0V

+260U 100mV 360u 100mV 370u 0v 10m 0)

.PROBE

.OP

.TEMP 25

.PARAM RBIAS=400K

.STEP PARAM RBIAS LIST 100K, 200K,400K, 800K

*power supply (simmetrical)

V10 VDD 0 2.5V

V20 0 VSS 2.5V

XAMP VIN+ VIN- VDD VSS VOUT AMP_CUBA_n PARAMS: RBIAS={RBIAS}

*FEEDBACK & LOAD NETWORK

RFEED VOUT VIN- 500K

RS1 VIN+ 0 100K

RS2 VIN- 1000 50K

RLAOD VOUT 0 50K

*SIGNAL NETWORK

RSIG 100 0 100K

RREF 1000 0 100K

CTEST 100 1000 1

.END

SPICE File_2

.lib CUBA.lib

*****ANALISYS OF DIFF_AMP P_TYPE

.TRAN 1U 400u

.AC dec 10 10 20MEG

Vin 100 0 ac 10m pwl(0 0V 100u 0V 110u -100mV 200u -100mV 210u 0 250U 0V

+260U 100mV 360u 100mV 370u 0v 10m 0)

.PROBE

.OP

.TEMP 25

.PARAM RBIAS=400K

.STEP PARAM RBIAS LIST 100K, 200K,400K, 800K

*

*power supply (simmetrical)

V10 VDD 0 2.5V

V20 0 VSS 2.5V

XAMP VIN+ VIN- VDD VSS VOUT AMP_CUBA_p PARAMS: RBIAS={RBIAS}

*FEEDBACK & LOAD NETWORK

RFEED VOUT VIN- 500K

RS1 VIN+ 0 100K


RS2 VIN- 1000 50K


RLAOD VOUT 0 50K


*SIGNAL NETWORK

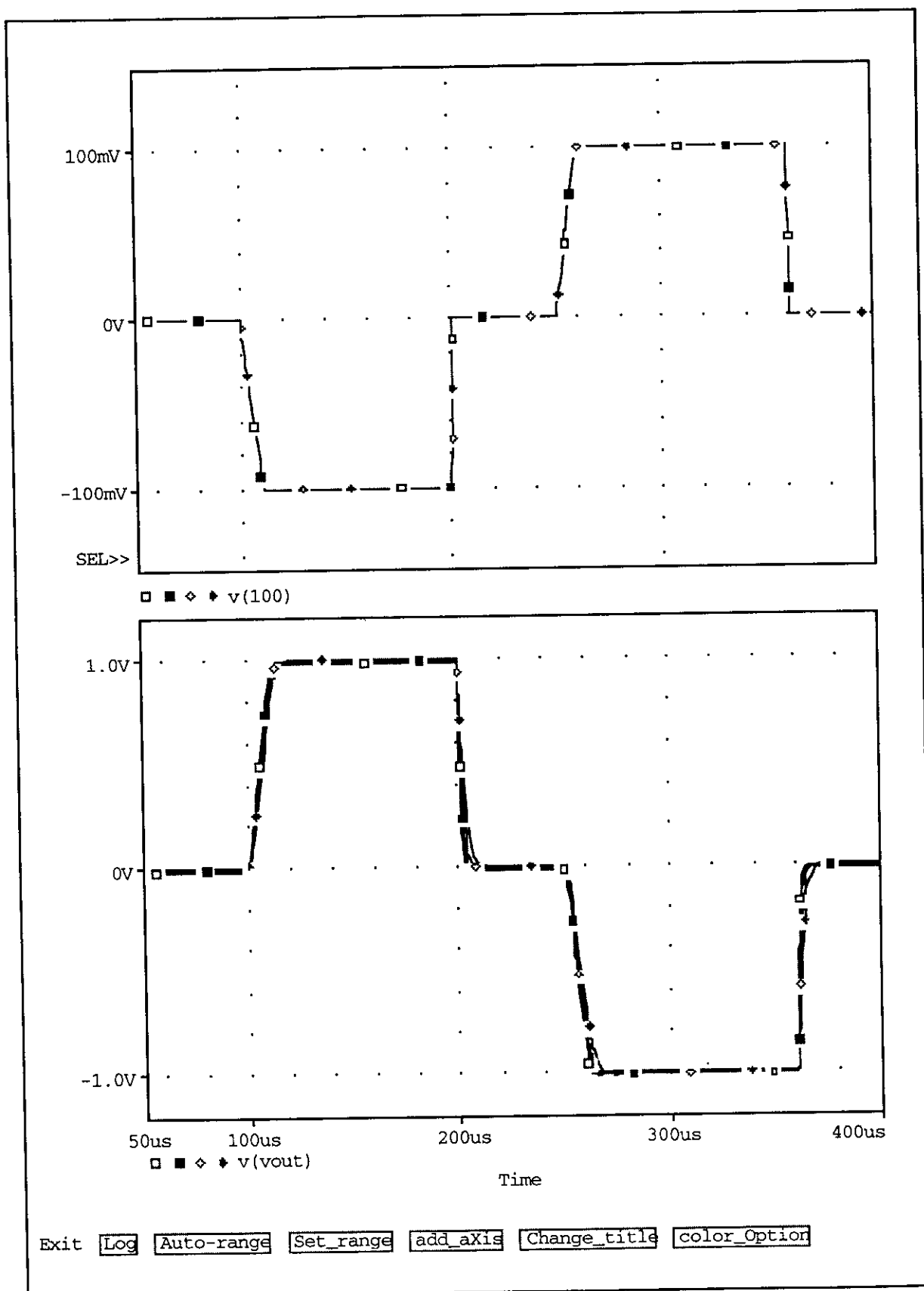9.12

```
RSIG 100 0 100K
RREF 1000 0 100K
CTEST 100 1000 1
.END
```



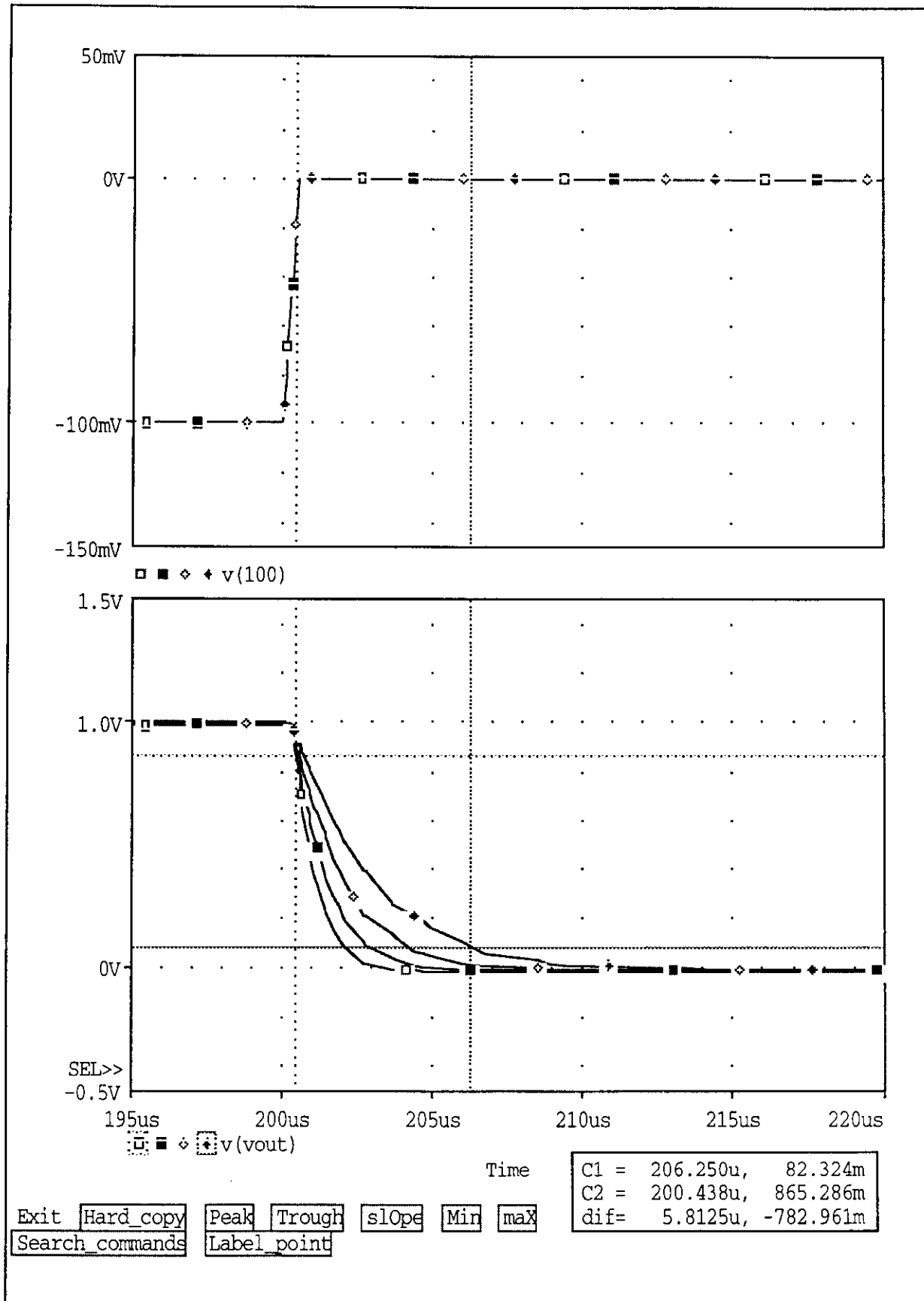

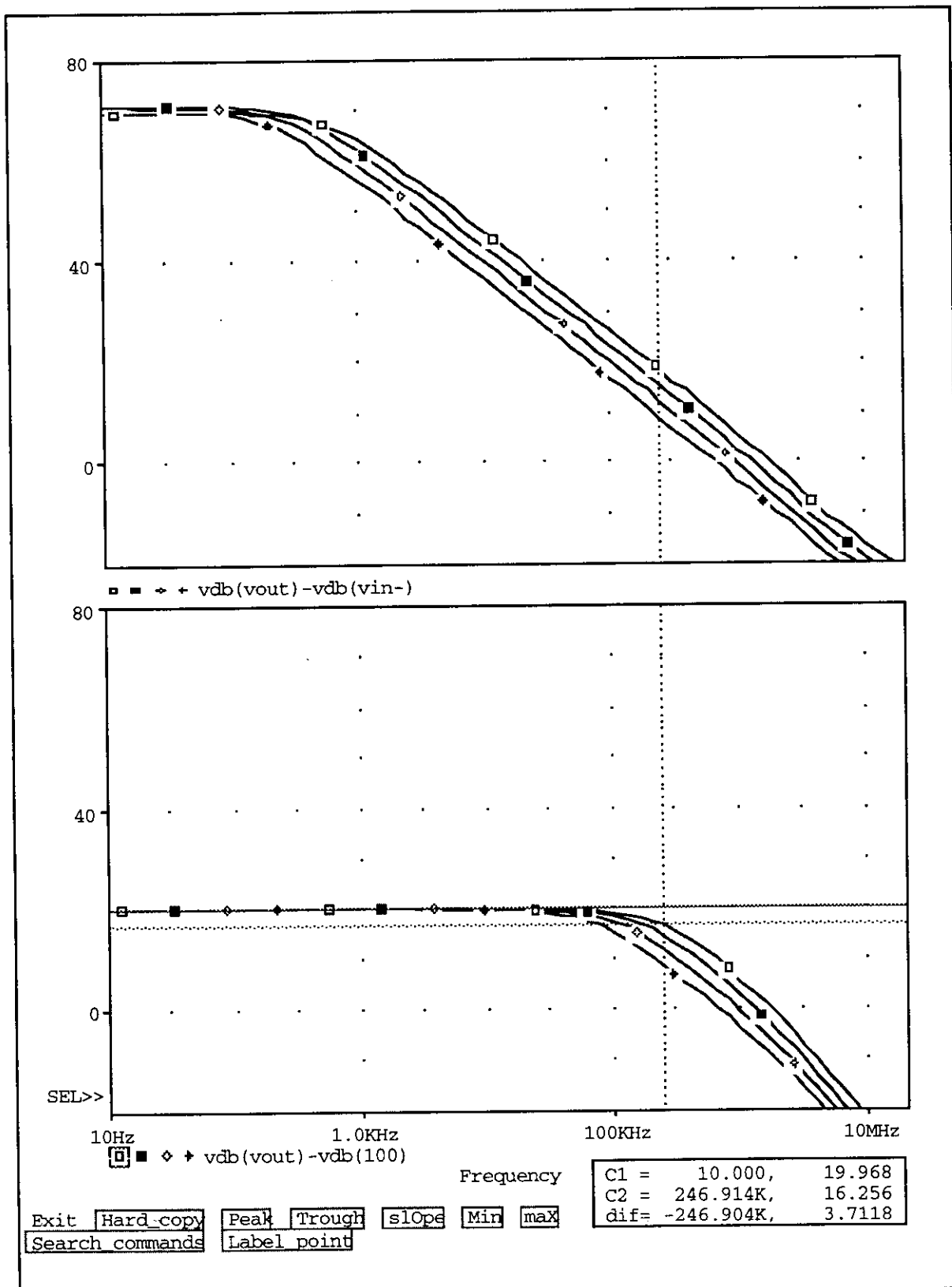

**** MOSFET MODEL PARAMETERS

	2_CUBAQP PMOS	2_CUBAQN NMOS
LEVEL	2	2
L	100.000000E-06	100.000000E-06
W	100.000000E-06	100.000000E-06
LD	315.000000E-09	338.000000E-09
WD	731.000000E-09	644.000000E-09
VTO	-.804	.77
KP	19.986040E-06	64.621530E-06
GAMMA	.563673	.944061
PHI	.703995	.75735
RSH	81	30
JS	40.000000E-06	20.000000E-06
PB	.79	.86
PBSW	.79	.86
CJ	360.000000E-06	400.000000E-06
CJSW	310.000000E-12	390.000000E-12
MJSW	.01	.06
CGSO	560.000000E-12	560.000000E-12
CGDO	560.000000E-12	560.000000E-12
CGBO	165.000000E-12	165.000000E-12
NSUB	11.800000E+15	33.100000E+15
NFS	337.000000E+09	293.000000E+09
TOX	31.100000E-09	31.100000E-09
XJ	21.000000E-09	54.000000E-09
UO	180	582
UCRIT	197.000000E+03	209.000000E+03
UEXP	.219	235
VMAX	41.200000E+03	86.000000E+03
NEFF	2.03	3.56
DELTA	1.04	

**** MOSFET MODEL PARAMETERS

NAME	VTO	PHI	PB	IS(JS)	KP	UO
2_CUBAQP	-8.074E-01	7.078E-01	7.932E-01	2.934E-05	2.019E-05	1.818E+02
2_CUBAQN	7.733E-01	7.608E-01	8.627E-01	1.467E-05	6.527E-05	5.879E+02

**** 01/21/96 19:25:38 ***** PSpice 6.0 (Jan 1994) ***** ID# 53788
 * * * *

SPICE File_1

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 25.000 DEG C

**** CURRENT STEP PARAM RBIAS = 100.0000E+03

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(100)	0.0000	(VDD)	2.5000	(VSS)	-2.5000	(1000)	-.0021
(VIN+)	0.0000	(VIN-)	-.0032	(VOUT)	-.0137	(XAMP.2)	.7966
(XAMP.4)	-1.4707	(XAMP.6)	-1.4446	(XAMP.10)	-.2187		

**** MOSFETS

NAME	XAMP.X1.M1	XAMP.X2.M1	XAMP.X3.M1	XAMP.X4.M1	XAMP.X5.M1
MODEL	2_CUBAQN	2_CUBAQN	2_CUBAQP	2_CUBAQP	2_CUBAQN
ID	1.96E-05	1.98E-05	-1.96E-05	-1.98E-05	3.94E-05
VGS	1.47E+00	1.47E+00	-1.70E+00	-1.70E+00	1.06E+00
VDS	2.27E+00	1.25E+00	-1.70E+00	-2.72E+00	1.03E+00
VBS	-1.03E+00	-1.03E+00	0.00E+00	0.00E+00	0.00E+00
VTH	1.24E+00	1.24E+00	-8.51E-01	-8.50E-01	8.14E-01
VDSAT	2.03E-01	2.05E-01	-6.92E-01	-6.93E-01	1.92E-01
GM	1.44E-04	1.44E-04	4.39E-05	4.45E-05	2.72E-04
GDS	2.00E-07	2.62E-07	2.59E-07	1.91E-07	5.28E-07
GMB	4.82E-05	4.83E-05	1.21E-05	1.23E-05	1.36E-04
CBD	1.08E-13	1.15E-13	3.11E-14	2.92E-14	2.57E-13
CBS	1.29E-13	1.29E-13	4.08E-14	4.08E-14	3.16E-13
CGSOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGDOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGBOV	1.54E-15	1.54E-15	1.55E-15	1.55E-15	1.54E-15
CGS	6.81E-13	6.81E-13	1.98E-13	1.98E-13	1.37E-12
CGD	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00

NAME	XAMP.X6.M1	XAMP.X7.M1	XAMP.X8.M1
MODEL	2_CUBAQN	2_CUBAQP	2_CUBAQN
ID	3.94E-05	-3.13E-04	3.14E-04
VGS	1.06E+00	-2.72E+00	1.06E+00
VDS	1.06E+00	-2.51E+00	2.49E+00
VBS	0.00E+00	0.00E+00	0.00E+00
VTH	8.14E-01	-8.49E-01	8.00E-01
VDSAT	1.92E-01	-1.49E+00	2.01E-01
GM	2.72E-04	2.93E-04	2.07E-03
GDS	5.22E-07	3.93E-06	5.60E-06
GMB	1.36E-04	6.59E-05	1.01E-03
CBD	2.57E-13	9.69E-14	7.31E-13
CBS	3.16E-13	1.34E-13	1.03E-12
CGSOV	1.11E-13	5.52E-14	3.63E-13
CGDOV	1.11E-13	5.52E-14	3.63E-13
CGBOV	1.54E-15	1.55E-15	7.13E-16
CGS	1.37E-12	6.83E-13	2.08E-12
CGD	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00

9.17

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 25.000 DEG C

**** CURRENT STEP PARAM RBIAS = 200.0000E+03

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(100)	0.0000	(VDD)	2.5000	(VSS)	-2.5000	(1000)	-.0012
(VIN+)	0.0000	(VIN-)	-.0019	(VOUT)	-.0080	(XAMP.2)	1.0497
(XAMP.4)	-1.4113	(XAMP.6)	-1.5274	(XAMP.10)	.3020		

**** MOSFETS

NAME	XAMP.X1.M1	XAMP.X2.M1	XAMP.X3.M1	XAMP.X4.M1	XAMP.X5.M1
MODEL	2_CUBAQN	2_CUBAQN	2_CUBAQP	2_CUBAQP	2_CUBAQN
ID	1.00E-05	1.01E-05	-1.00E-05	-1.01E-05	2.02E-05
VGS	1.41E+00	1.41E+00	-1.45E+00	-1.45E+00	9.73E-01
VDS	2.46E+00	1.71E+00	-1.45E+00	-2.20E+00	1.09E+00
VBS	-1.09E+00	-1.09E+00	0.00E+00	0.00E+00	0.00E+00
VTH	1.26E+00	1.26E+00	-8.51E-01	-8.50E-01	8.14E-01
VDSAT	1.46E-01	1.47E-01	-4.95E-01	-4.95E-01	1.37E-01
GM	1.03E-04	1.03E-04	3.13E-05	3.16E-05	1.94E-04
GDS	1.23E-07	1.44E-07	1.40E-07	1.09E-07	3.12E-07
GMB	3.42E-05	3.43E-05	9.02E-06	9.10E-06	9.89E-05
CBD	1.07E-13	1.11E-13	3.18E-14	3.01E-14	2.55E-13
CBS	1.28E-13	1.28E-13	4.08E-14	4.08E-14	3.16E-13
CGSOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGDOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGBOV	1.54E-15	1.54E-15	1.55E-15	1.55E-15	1.54E-15
CGS	6.81E-13	6.81E-13	1.98E-13	1.98E-13	1.37E-12
CGD	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00

NAME	XAMP.X6.M1	XAMP.X7.M1	XAMP.X8.M1
MODEL	2_CUBAQN	2_CUBAQP	2_CUBAQN
ID	2.01E-05	-1.66E-04	1.66E-04
VGS	9.73E-01	-2.20E+00	9.73E-01
VDS	9.73E-01	-2.51E+00	2.49E+00
VBS	0.00E+00	0.00E+00	0.00E+00
VTH	8.14E-01	-8.49E-01	8.00E-01
VDSAT	1.37E-01	-1.08E+00	1.46E-01
GM	1.94E-04	2.40E-04	1.50E-03
GDS	3.29E-07	1.82E-06	3.51E-06
GMB	9.87E-05	6.09E-05	7.46E-04
CBD	2.59E-13	9.69E-14	7.31E-13
CBS	3.16E-13	1.34E-13	1.03E-12
CGSOV	1.11E-13	5.52E-14	3.63E-13
CGDOV	1.11E-13	5.52E-14	3.63E-13
CGBOV	1.54E-15	1.55E-15	7.13E-16

9.18

CGS	1.37E-12	6.83E-13	2.08E-12
CGD	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 25.000 DEG C

**** CURRENT STEP PARAM RBIAS = 400.0000E+03

NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE

(100)	0.0000	(VDD)	2.5000	(VSS)	-2.5000	(1000)	-760.5E-06
(VIN+)	0.0000	(VIN-)	-.0011	(VOUT)	-.0049	(XAMP.2)	1.2334
(XAMP.4)	-1.3687	(XAMP.6)	-1.5872	(XAMP.10)			.6755

**** MOSFETS

NAME	XAMP.X1.M1	XAMP.X2.M1	XAMP.X3.M1	XAMP.X4.M1	XAMP.X5.M1
MODEL	2_CUBAQN	2_CUBAQN	2_CUBAQP	2_CUBAQP	2_CUBAQN
ID	5.11E-06	5.15E-06	-5.11E-06	-5.15E-06	1.03E-05
VGS	1.37E+00	1.37E+00	-1.27E+00	-1.27E+00	9.13E-01
VDS	2.60E+00	2.04E+00	-1.27E+00	-1.82E+00	1.13E+00
VBS	-1.13E+00	-1.13E+00	0.00E+00	0.00E+00	0.00E+00
VTH	1.27E+00	1.27E+00	-8.51E-01	-8.51E-01	8.14E-01
VDSAT	1.04E-01	1.05E-01	-3.53E-01	-3.53E-01	9.79E-02
GM	7.34E-05	7.36E-05	2.22E-05	2.24E-05	1.38E-04
GDS	7.77E-08	8.65E-08	7.60E-08	6.19E-08	1.92E-07
GMB	2.43E-05	2.44E-05	6.64E-06	6.69E-06	7.12E-05
CBD	1.06E-13	1.09E-13	3.24E-14	3.09E-14	2.54E-13
CBS	1.27E-13	1.27E-13	4.08E-14	4.08E-14	3.16E-13
CGSOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGDOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGBOV	1.54E-15	1.54E-15	1.55E-15	1.55E-15	1.54E-15
CGS	6.81E-13	6.81E-13	1.98E-13	1.98E-13	1.37E-12
CGD	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00

NAME	XAMP.X6.M1	XAMP.X7.M1	XAMP.X8.M1
MODEL	2_CUBAQN	2_CUBAQP	2_CUBAQN
ID	1.02E-05	-8.85E-05	8.86E-05
VGS	9.13E-01	-1.82E+00	9.13E-01
VDS	9.13E-01	-2.51E+00	2.50E+00
VBS	0.00E+00	0.00E+00	0.00E+00
VTH	8.14E-01	-8.49E-01	8.00E-01
VDSAT	9.77E-02	-7.89E-01	1.07E-01
GM	1.38E-04	1.75E-04	1.09E-03
GDS	2.11E-07	9.10E-07	2.27E-06
GMB	7.10E-05	4.69E-05	5.50E-04
CBD	2.61E-13	9.70E-14	7.31E-13

9.19

CBS	3.16E-13	1.34E-13	1.03E-12
CGSOV	1.11E-13	5.52E-14	3.63E-13
CGDOV	1.11E-13	5.52E-14	3.63E-13
CGBOV	1.54E-15	1.55E-15	7.13E-16
CGS	1.37E-12	6.83E-13	2.08E-12
CGD	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 25.000 DEG C

**** CURRENT STEP PARAM RBIAS = 800.0000E+03

NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE

(100) 0.0000 (VDD) 2.5000 (VSS) -2.5000 (1000)-486.7E-06
(VIN+) 0.0000 (VIN-) -730.1E-06 (VOUT) -.0032 (XAMP.2) 1.3657
(XAMP.4) -1.3382 (XAMP.6) -1.6301 (XAMP.10) .9441


**** MOSFETS

NAME	XAMP.X1.M1	XAMP.X2.M1	XAMP.X3.M1	XAMP.X4.M1	XAMP.X5.M1
MODEL	2_CUBAQN	2_CUBAQN	2_CUBAQP	2_CUBAQP	2_CUBAQN
ID	2.59E-06	2.61E-06	-2.59E-06	-2.61E-06	5.20E-06
VGS	1.34E+00	1.34E+00	-1.13E+00	-1.13E+00	8.70E-01
VDS	2.70E+00	2.28E+00	-1.13E+00	-1.56E+00	1.16E+00
VBS	-1.16E+00	-1.16E+00	0.00E+00	0.00E+00	0.00E+00
VTH	1.28E+00	1.28E+00	-8.51E-01	-8.51E-01	8.14E-01
VDSAT	7.42E-02	7.45E-02	-2.51E-01	-2.51E-01	6.96E-02
GM	5.23E-05	5.25E-05	1.58E-05	1.59E-05	9.81E-05
GDS	5.07E-08	5.47E-08	4.15E-08	3.51E-08	1.23E-07
GMB	1.72E-05	1.73E-05	4.84E-06	4.87E-06	5.10E-05
CBD	1.05E-13	1.07E-13	3.29E-14	3.15E-14	2.53E-13
CBS	1.27E-13	1.27E-13	4.08E-14	4.08E-14	3.16E-13
CGSOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGDOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGBOV	1.54E-15	1.54E-15	1.55E-15	1.55E-15	1.54E-15
CGS	6.81E-13	6.81E-13	1.98E-13	1.98E-13	1.37E-12
CGD	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00

NAME	XAMP.X6.M1	XAMP.X7.M1	XAMP.X8.M1
MODEL	2_CUBAQN	2_CUBAQP	2_CUBAQN
ID	5.16E-06	-4.79E-05	4.79E-05
VGS	8.70E-01	-1.56E+00	8.70E-01
VDS	8.70E-01	-2.50E+00	2.50E+00
VBS	0.00E+00	0.00E+00	0.00E+00
VTH	8.14E-01	-8.49E-01	8.00E-01
VDSAT	6.94E-02	-5.80E-01	7.86E-02
GM	9.77E-05	1.28E-04	8.03E-04
GDS	1.38E-07	4.79E-07	1.52E-06
GMB	5.08E-05	3.59E-05	4.08E-04
CBD	2.63E-13	9.70E-14	7.31E-13
CBS	3.16E-13	1.34E-13	1.03E-12
CGSOV	1.11E-13	5.52E-14	3.63E-13
CGDOV	1.11E-13	5.52E-14	3.63E-13
CGBOV	1.54E-15	1.55E-15	7.13E-16
CGS	1.37E-12	6.83E-13	2.08E-12

CGD	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00

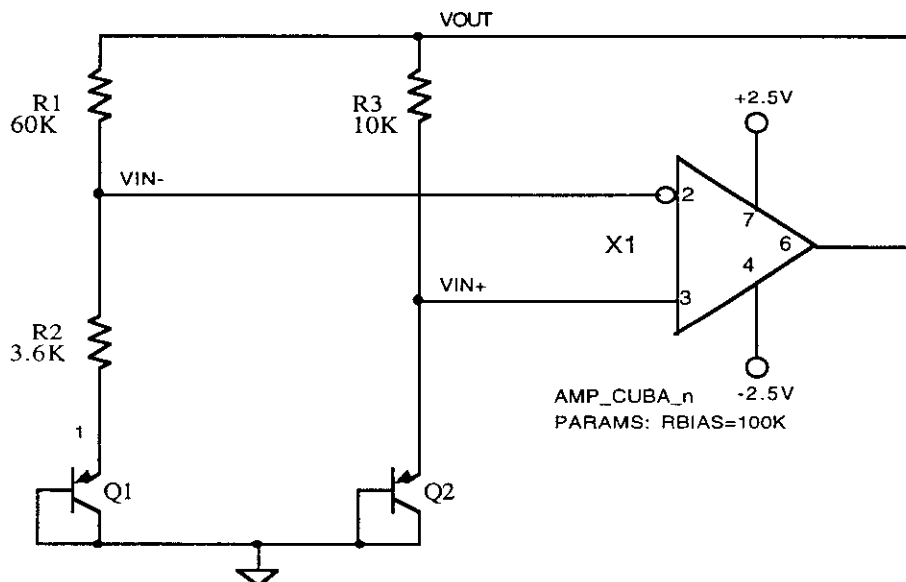- Based on the previous amplifier we can built a precise ***bandgap voltage reference***.
- The principle is trying to generate a voltage reference with zero *tempco*, adding in a proper way two voltage sources with opposite ***tempco***.
- The structure is the one in the following scheme.



- Let's analyze the simple circuit assuming that **X1** has infinite gain (op.amp.):

$$\frac{V_{OUT} - V_{IN-}}{R_1} = \frac{V_{IN-} - V_{B1}}{R_2}$$

(9.3)

Being

$$V_{IN-} = V_{IN+} = V_{B2} \quad (9.4)$$

we get

$$V_{OUT} = \frac{R_1}{R_2} (V_{B2} - V_{B1}) + V_{B2} \quad (9.5)$$

Remembering, (2.3), that

$$I_{D1} \approx I_S e^{V_{B1}/V_T}$$

and

$$I_{D2} \approx I_S e^{V_{B2}/V_T}$$

taking into account the ratio

$$I_{D2} = nI_{D1}$$

we can compute the difference ($V_{B2}-V_{B1}$) between the two junction voltages and the (9.5) becomes

$$V_{OUT} = \frac{R_1}{R_2} V_T \ln(n) + V_{B2} \quad (9.6)$$

It is worth to remind that

$$V_T = \frac{kT}{q} \quad (9.7)$$

and n is the ratio between the currents through R_3 and R_1 . In fact n is also the ratio of the two resistances.

•The requirement is to have zero *tempco* for V_{OUT} , that means to have the derivative zero.

$$\frac{\partial V_{OUT}}{\partial T} = \frac{R_1}{R_2} \frac{\partial V_T}{\partial T} \ln(n) - 2.2 * 10^{-3} = 0 \quad (9.8)$$

$$\frac{R_1}{R_2} \frac{k}{q} \ln(n) = 2.2 * 10^{-3} \quad (9.9)$$

$$\frac{R_1}{R_2} \ln(n) = 2.2 * 10^{-3} \frac{1.6 * 10^{-19}}{1.38 * 10^{-23}} = 25.6 \quad (9.10)$$

- In this conditions we have

$$V_{OUT} = 25.6 * 26mV + 600mV = 1.24V \quad (9.11)$$

that corresponds to the *bandgap voltage* V_{GO} .

- We just remind here the definition of bandgap voltage, V_{GO} .

- The junction voltage V_{BE} , can be expressed by

$$V_{BE} \cong V_{GO} - \frac{kT}{q} \ln \frac{const}{I_C} \quad (9.11)$$


that can be easily compared with (9.6), from which we understand that

$$V_{OUT} = V_{GO} \quad (9.12)$$

- In our case we would have

$$V_{OUT} = \frac{60}{3.65} * 26mV \ln(6) + 600mV \approx 1.3V$$

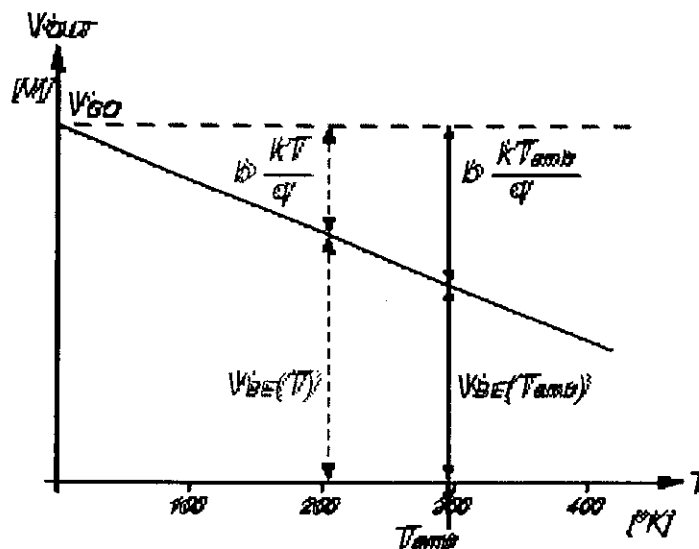The correct value will be obtained with simulation. V_{GO} is the extrapolated value of V_{BE} at $T[^\circ K]=0$.



- It should be noted that pnp transistors are obtained in CMOS technology with the so called ***lateral bipolar***. The base is the n-well (p substrate) while source and drain are emitter and collector (or viceversa). To control the value n one can also play with the transistor dimensions, changing the current density through the emitter base junction.

- The SPICE circuit description follows.

```

SPICE File_1
.PROBE
.OP
.TRAN 10N 2u
.TEMP 0, 25, 50
.LIB CUBA.LIB
.LIB MY-BJT.LIB
Q1 0 0 1 QBFT92
Q2 0 0 VIN+ QBFT92
R1 VOUT VIN- 60K
R2 VIN- 1 3.5K
R3 VOUT VIN+ 10K
X1 VIN+ VIN- VDD VSS VOUT AMP_CUBA_n PARAMS: RBIAS=100K
** POWER SPPLY
V1 VDD 0 2.5
V2 0 VSS 2.5
.END *****

```

```

SPICE File_2
.PROBE
.OP
.TRAN 10N 2u
.TEMP 0, 25, 50
.LIB CUBA.LIB
.LIB MY-BJT.LIB
Q1 0 0 1 QBFT92
Q2 0 0 VIN+ QBFT92
R1 VOUT VIN- 60K
R2 VIN- 1 3.6536K
R3 VOUT VIN+ 10K
X1 VIN+ VIN- VDD VSS VOUT AMP_CUBA_n PARAMS: RBIAS=100K
** POWER SPPLY
V1 VDD 0 2.5
V2 0 VSS 2.5
.END *****

```

```


SPICE File_3
.PROBE
.OP
.TRAN 10N 3u
.TEMP 0, 25, 50
.LIB CUBA.LIB
.LIB MY-BJT.LIB
Q1 0 0 1 QBFT92
Q2 0 0 VIN+ QBFT92
R1 VOUT VIN- 60K
R2 VIN- 1 3.85K
R3 VOUT VIN+ 10K
X1 VIN+ VIN- VDD VSS VOUT AMP_CUBA_n PARAMS: RBIAS=100K
** POWER SPPLY

```

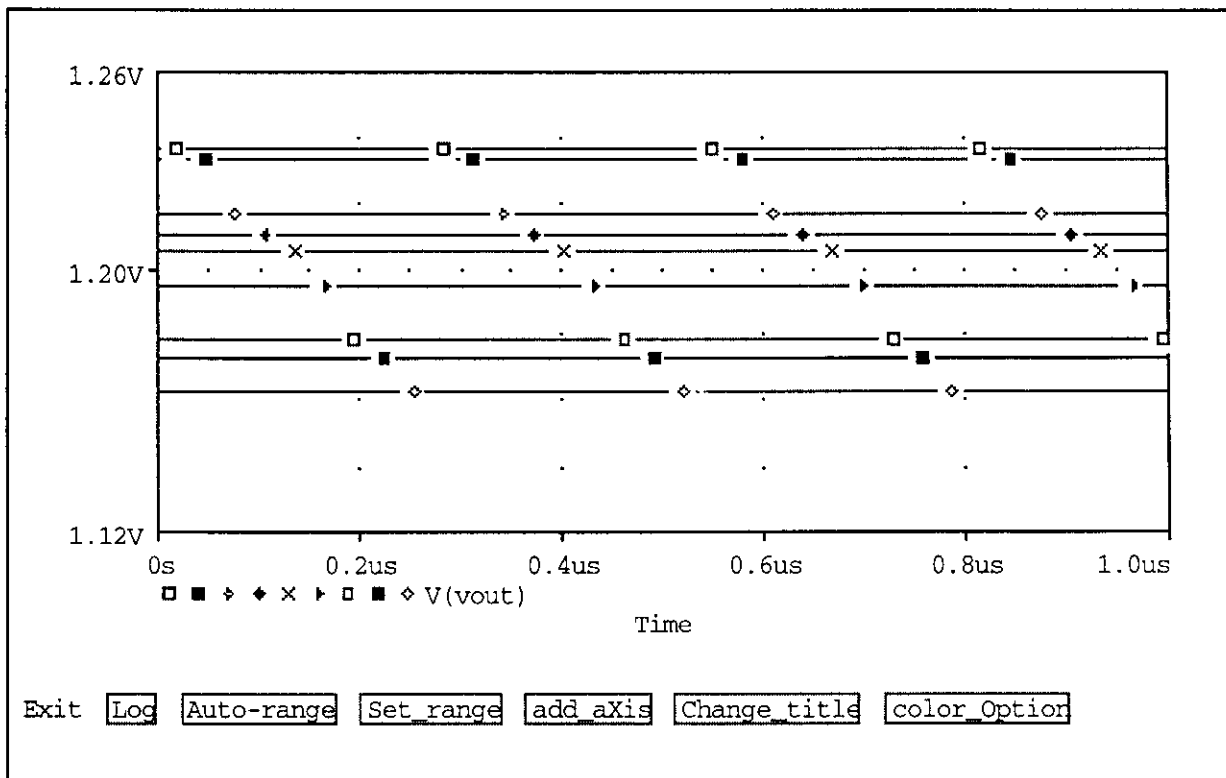9.27

```
V1 VDD 0 2.5
V2 0 VSS 2.5
.END *****
```

- The three listings differ only for **R2** value. The circuit has been simulated for three different temperatures and the one with the **R2=3.6536K** has the lowest tempo.



The tempco's are $-400\mu\text{V}/^{\circ}\text{C}$, $-300\mu\text{V}/^{\circ}\text{C}$, $-330\mu\text{V}/^{\circ}\text{C}$.

The nominal value at 25°C is 1.2062V .

The biasing for the best value, at 25°C , is given below.

**** 01/30/96 12:04:29 ***** PSpice 6.0 (Jan 1994) ***** ID# 53788
 * * * *

SPICE File_2

**** OPERATING POINT INFORMATION TEMPERATURE = 25.000 DEG C

**** BIPOLAR JUNCTION TRANSISTORS

NAME	Q1	Q2
MODEL	QBFT92	QBFT92
IB	-3.05E-07	-1.82E-06
IC	-1.09E-05	-6.49E-05
VBE	-4.94E-01	-5.39E-01
VBC	0.00E+00	0.00E+00
VCE	-4.94E-01	-5.39E-01
BETADC	3.57E+01	3.57E+01
GM	4.23E-04	2.52E-03
RPI	8.42E+04	1.41E+04
RX	0.00E+00	0.00E+00
RO	2.21E+06	3.70E+05
CBE	1.33E-12	1.43E-12
CBC	1.04E-12	1.04E-12
CBX	0.00E+00	0.00E+00
CJS	0.00E+00	0.00E+00
BETAAC	3.57E+01	3.57E+01
FT	2.84E+07	1.62E+08

**** MOSFETS

NAME	X1.X1.M1	X1.X2.M1	X1.X3.M1	X1.X4.M1	X1.X5.M1
MODEL	2_CUBAQN	2_CUBAQN	2_CUBAQP	2_CUBAQP	2_CUBAQN
ID	1.97E-05	2.00E-05	-1.97E-05	-2.00E-05	3.96E-05
VGS	1.60E+00	1.60E+00	-1.70E+00	-1.70E+00	1.06E+00
VDS	1.86E+00	4.18E-01	-1.70E+00	-3.15E+00	1.44E+00
VBS	-1.44E+00	-1.44E+00	0.00E+00	0.00E+00	0.00E+00
VTH	1.37E+00	1.37E+00	-8.51E-01	-8.50E-01	8.14E-01
VDSAT	2.06E-01	2.08E-01	-6.93E-01	-6.94E-01	1.93E-01
GM	1.45E-04	1.46E-04	4.40E-05	4.47E-05	2.73E-04
GDS	2.24E-07	4.32E-07	2.59E-07	1.76E-07	4.48E-07
GMB	4.42E-05	4.42E-05	1.21E-05	1.23E-05	1.37E-04
CBD	1.08E-13	1.19E-13	3.11E-14	2.86E-14	2.46E-13
CBS	1.23E-13	1.23E-13	4.08E-14	4.08E-14	3.16E-13
CGSOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGDOV	5.53E-14	5.53E-14	1.60E-14	1.60E-14	1.11E-13
CGBOV	1.54E-15	1.54E-15	1.55E-15	1.55E-15	1.54E-15
CGS	6.81E-13	6.81E-13	1.98E-13	1.98E-13	1.37E-12

9.29

CGD	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00

NAME	X1.X6.M1	X1.X7.M1	X1.X8.M1
MODEL	2_CUBAQN	2_CUBAQP	2_CUBAQN
ID	3.94E-05	-3.98E-04	3.20E-04
VGS	1.06E+00	-3.15E+00	1.06E+00
VDS	1.06E+00	-1.29E+00	3.71E+00
VBS	0.00E+00	0.00E+00	0.00E+00
VTH	8.14E-01	-8.50E-01	7.99E-01
VDSAT	1.92E-01	-1.82E+00	2.02E-01
GM	2.72E-04	2.23E-04	2.10E-03
GDS	5.22E-07	1.48E-04	4.57E-06
GMB	1.36E-04	5.15E-05	1.03E-03
CBD	2.57E-13	1.06E-13	6.85E-13
CBS	3.16E-13	1.34E-13	1.03E-12
CGSOV	1.11E-13	5.52E-14	3.63E-13
CGDOV	1.11E-13	5.52E-14	3.63E-13
CGBOV	1.54E-15	1.55E-15	7.13E-16
CGS	1.37E-12	5.39E-13	2.08E-12
CGD	0.00E+00	4.34E-13	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00

**** 01/30/96 12:04:29 ***** PSpice 6.0 (Jan 1994) ***** ID# 53788

SPICE File_2

**** INITIAL TRANSIENT SOLUTION TEMPERATURE = 25.000 DEG C

NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE

(1)	.4935 (VDD)	2.5000 (VSS)	-2.5000 (VIN+)	.5394
(VIN-)	.5344 (VOUT)	1.2062 (X1.2)	.7953 (X1.4)	-1.0639
(X1.6)	-1.4446 (X1.10)	-1.6456		

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
------	---------

V1	-4.769E-04
V2	-3.990E-04

TOTAL POWER DISSIPATION 2.19E-03 WATTS

