

301/1152-9

Microprocessor Laboratory
Sixth Course on Basic VLSI Design Techniques
8 November - 3 December 1999


ADDITIONAL MATERIAL FOR LECTURE NOTES
by

Sandro CENTRO
Dipartimento di Fisica "G. Galilei"
Universita' degli Studi di Padova
via Marzolo, 8
35131 Padova
ITALY

These are preliminary lecture notes intended only for distribution to participants.

INTRODUCTION

ANY AMPLIFIER COULD BE THOUGH AS A:

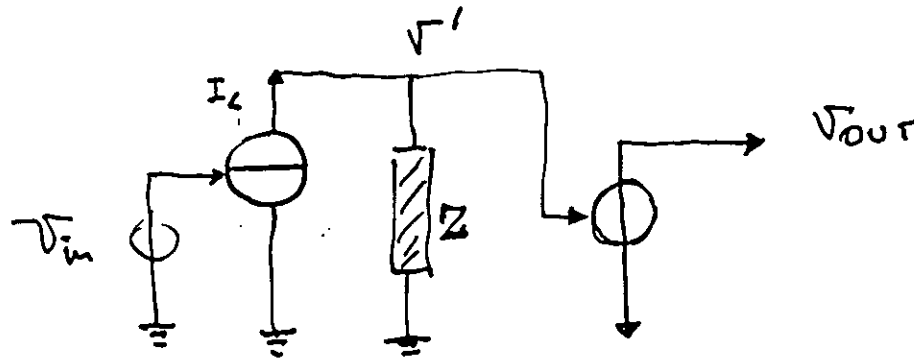


VOLTAGE CONTROLLED CURRENT GENERATOR, THAT
CAN BE FOLLOWED BY VOLTAGE CONTROLLED VOLTAGE
GENERATOR, NORMALLY WITH GAIN "1"

$$\frac{I_L}{V_{in}} = g_m \quad \text{TRANSCONDUCTANCE [mho, siemens]}$$

$$V' = I_L * Z = V_{out}$$

$$\frac{V_{out}}{V_{in}} = g_m Z$$

BASIC ENGINES TO MAKE AMPLIFIERS:


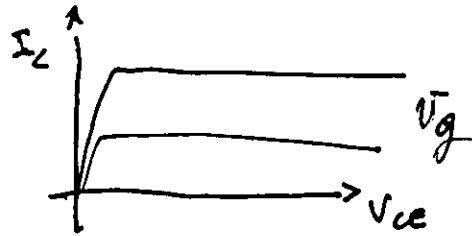


$$\frac{I_C}{V_{BE}} = g_T = \frac{1}{r_e}$$

$$r_e = \frac{kT}{q} \frac{1}{I_C} = \frac{25 \text{ mV}}{I_C [\text{mA}]}$$



$$= 5 \div 250 \Omega$$

$$g_T = 4 \div 200 \text{ mS}$$

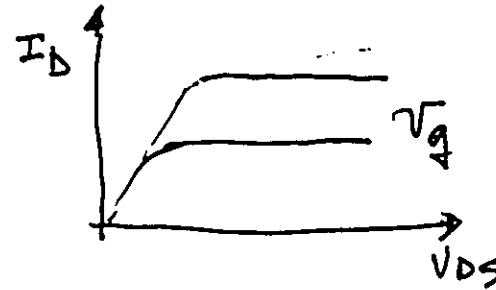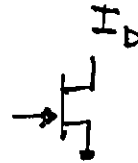

$$\frac{I_D}{V_{GS}} = g_m$$

$$g_m = .5 \div 20 \text{ mS}$$

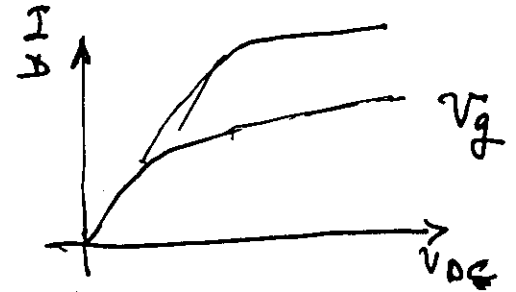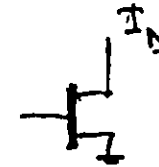


$$\frac{I_D}{V_{GS}} = g_m$$

$$g_m = .05 \div 2 \text{ mS}$$

WHICH IS THE LIMIT FOR THE AMPLIFICATION OF A SINGLE ENGINE ??

3

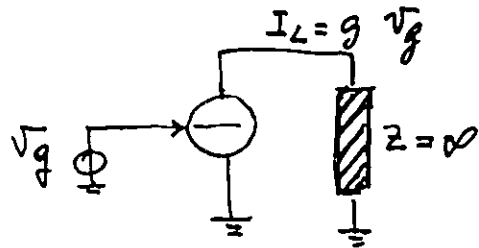

THEN

$Z_{MAX} = Z_{OUT}$ OF THE ELEMENT.

BIPOLAR $Z_{OUT} \rightarrow 10^5 \div 10^6 \Omega$

J-FET $Z_{OUT} \rightarrow 10^5 \div 10^6 \Omega$


CMOS $Z_{OUT} \rightarrow 10^4 \div 10^5 \Omega$

A_{LIMIT}

400 ÷ 200'000

50 ÷ 20'000

.5 ÷ 200

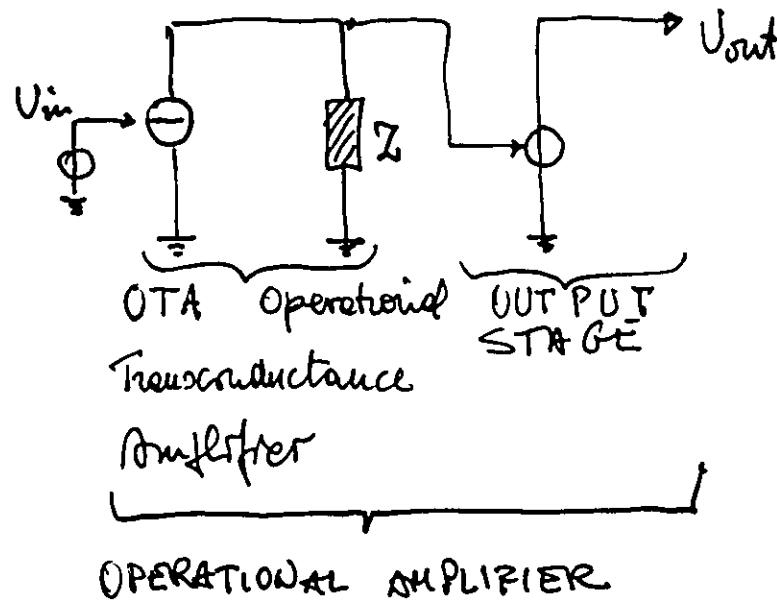

THERE ARE ALSO

$A_i = \frac{I_{out}}{I_{in}}$ OCA $\rightarrow$ OP. Current Amp.

$A_r = \frac{V_{out}}{I_{in}}$ CMA $\rightarrow$ Current Mode Amp.

$$A_v = V_{out} / V_{in}$$

$$BW = f_T$$

$$NB @ f_T \quad A_v = 1$$

$$GBW = A_v f_L = K (\text{constant}) = f_T$$

OP. AMP. REQUIREMENTS :

5




$$A_{OL} \rightarrow \infty \quad (10^4 \div 10^5)$$

$$R_{inOL} \rightarrow \infty \quad (10^5 \div 10^8)$$

$$Z_{outOL} \rightarrow 0 \quad (50 \div 200)$$

IDEAL $\uparrow$ $\uparrow$ REAL LIFE

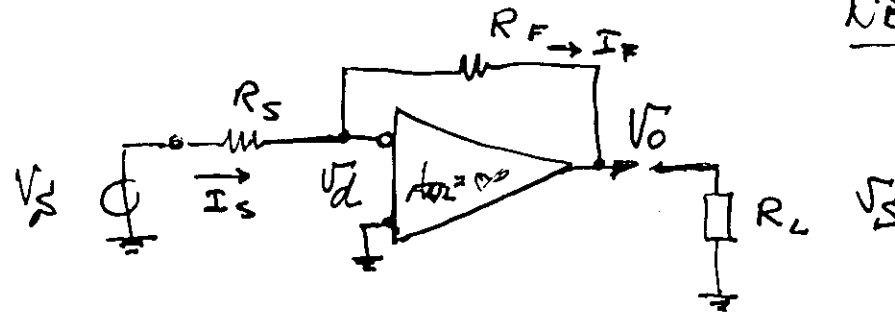

NB

$$\frac{V_O}{V_d} \rightarrow \infty$$

THAT MEANS

$$V_d \rightarrow 0$$

$$\frac{V_S - V_d}{R_S} = \frac{V_d - V_O}{R_F}$$

COMBINING WITH $V_d = -\frac{V_O}{A_{OL}}$

$$\boxed{A_f} = \frac{V_O}{V_S} = \frac{A_{OL} R_F}{R_F + R_S - A_{OL} R_S} \xrightarrow{A_{OL} \rightarrow \infty} -\frac{R_F}{R_S} = \boxed{A_{f,ideal}}$$

$$\sum V_d = 0$$

VIRTUAL GROUND $\& S \ I_S \equiv I_F$

IS INFINITE A_{OL} GAIN NECESSARY TO HAVE


$$A_f = A_{ideal} = -R_F / R_S \quad ?$$

REMINING THAT

$$A_f = \frac{A_{OL} R_F}{R_F + R_S - A_{OL} R_S} = \frac{A_{OL} R_F / R_S}{R_F / R_S + 1 - A_{OL}}$$

$$= \frac{A_{OL} A_{fi}}{A_{OL} - 1 + A_{fi}} = \frac{A_{fi}}{1 - \frac{1}{A_{OL}} + \frac{A_{fi}}{A_{OL}}}$$

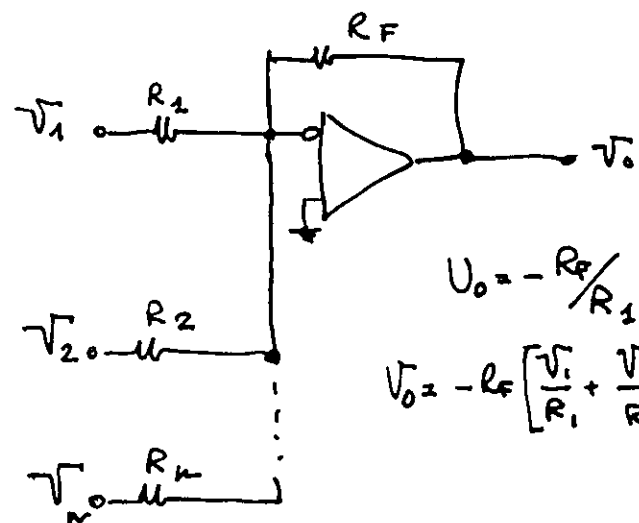
$$\approx \frac{A_{fi}}{1 + A_{fi}/A_{OL}} \xrightarrow{A_{OL} \rightarrow \infty} A_{fi} \quad \text{OR FOR } A_{OL} \gg A_{fi} !$$



$$U_0 = -R_F / R_1 \cdot V_1$$

$$V_0 = -R_F \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right]$$

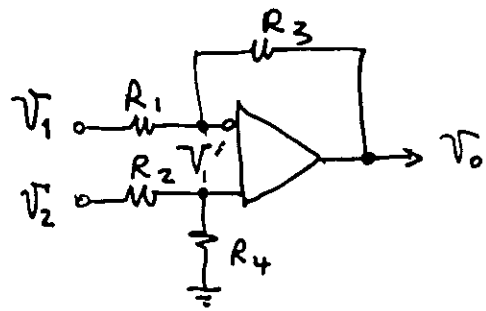Σ WITHOUT COUPLING OF V_x , AS THE SUMMING NODE AS ZERO VOLTAGE.



FROM $V' = \frac{V_2}{R_2 + R_4} * R_4$



$$\frac{V_1 - V'}{R_1} = \frac{V' - V_0}{R_3}$$

$$V_0 = V_2 \frac{R_4}{R_2 + R_4} \frac{R_1 + R_3}{R_1} - V_1 \frac{R_3}{R_1}$$

IF $R_1 = R_2 = R_i$

$R_3 = R_4 = R$

$$V_0 = (V_2 - V_1) R / R_i$$

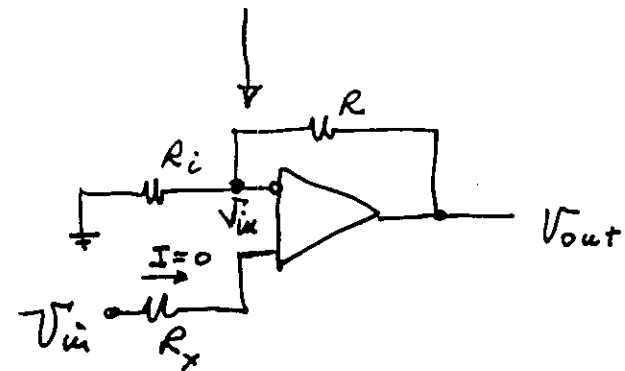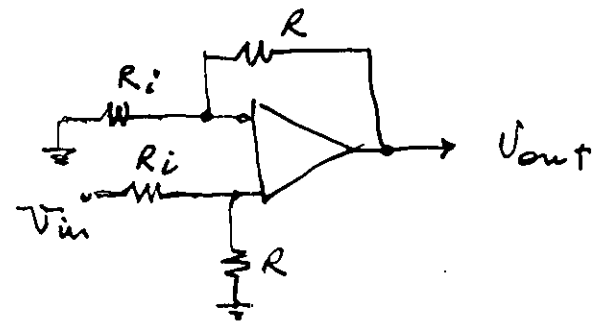

$$\frac{V_{out} - V_{in}}{R} = \frac{V_{in}}{R_i}$$

$$V_{out} = (1 + R/R_i) V_{in}$$


$$Z_{in} \Rightarrow \infty$$

$$A_{f+} = 1 + R_F/R_S \geq 1$$


WHILE

$$A_{f-} = -R_S/R_S \quad \text{NEGATIVE BUT "ANY" VALUE}$$

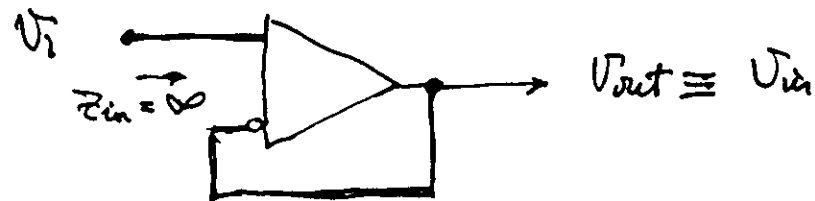$A_{f+} = 1$ if R_F/R_S THAT MEANS $R_S = \infty$ THEN R_F
DON'T CARE, THEN:



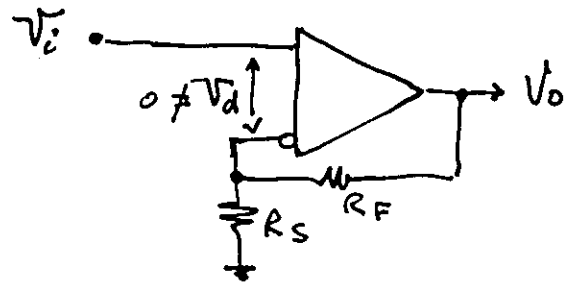AGAIN IN THE ASSUMPTION $A_{OL} = \infty$. DO WE NEED IT?



$$V_d = V_i - \frac{V_o}{R_S + R_F} \cdot R_S$$

$$V_{out} = A_{OL} V_d = A_{OL} V_i - A_{OL} \frac{V_o}{R_S + R_F} R_S$$

$$A_{f+} = \frac{V_{out}}{V_{in}} = \frac{A_{OL}}{1 + A_{OL} \frac{R_S}{R_S + R_F}} \xrightarrow{A_{OL} \rightarrow \infty} = \frac{R_S + R_F}{R_S} = A_{fi}$$

$$A_{f+} = \frac{A_{OL}}{1 + A_{OL}/A_{fi}}$$

$$A_{f+} = A_{fi} \quad \text{IF } A_{OL} \rightarrow \infty \quad \text{OR } A_{fi} \ll A_{OL}$$

LET'S CALCULATE THE REAL UNITY GAIN FOR $A_{OL} = 5 \times 10^4$


$$A_f = \frac{A_{OL}}{1 + A_{OL}} = \frac{5 \times 10^4}{1 + 5 \times 10^4} = .9999800004 \approx$$

AND FOR $A_{OL} = 1000$

$$A_f = \frac{10^3}{1 + 10^3} = .99900 \quad \text{STILL QUITE GOOD.}$$

CAN WE MAKE NON INVERTING SUM ?

YES, BUT...

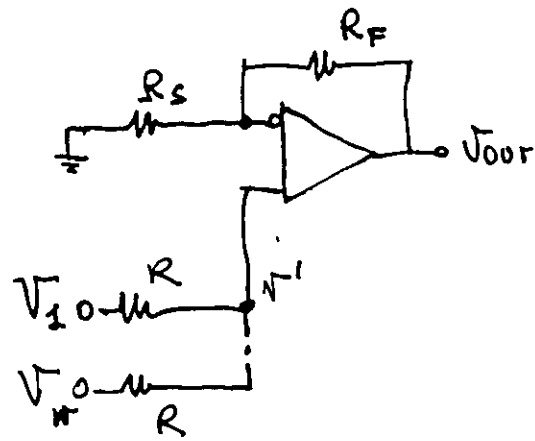

$$V'_1 = \frac{V_1}{R + \frac{R}{N-1}} = \frac{V_1}{N}$$

...


$$V'_N = \frac{V_N}{N}$$

$$V_o = \left(1 + \frac{R_F}{R_s}\right) \frac{1}{N} (V_1 + V_2 + \dots + V_N)$$

EACH GENERATOR V_N SEES THE OTHERS, SO ITS
LOAD IS NOT CONSTANT!

LET'S USE ANOTHER METHOD TO CALCULATE MORE PRECISELY THE Z_{inf} , INPUT IMPEDANCE WITH FEEDBACK.


WE USE THE MILLER EFFECT

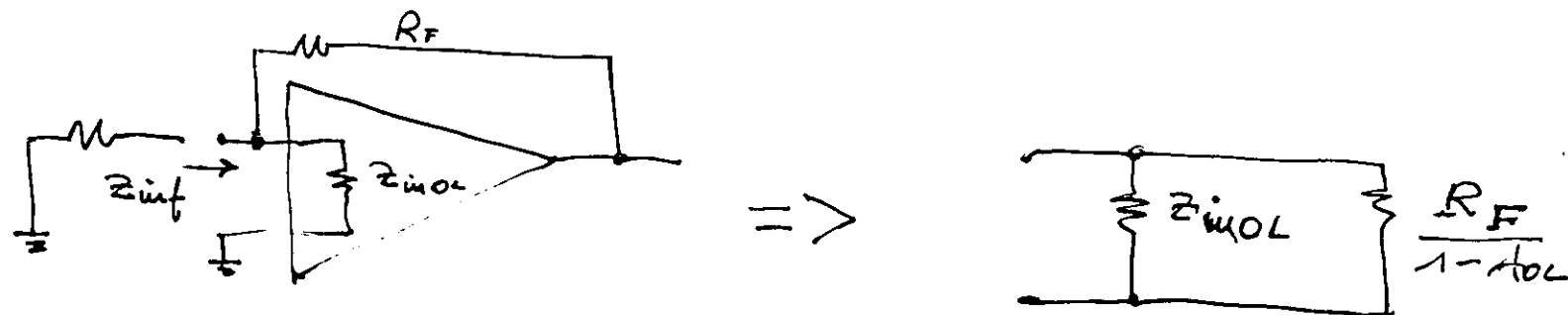

$$Z_{inf} = Z_{inol} \parallel \left[\frac{R_F}{1 - A_{OL}} \right]$$

$$= \frac{Z_{inol} R_F}{R_F + Z_{inol} (1 - A_{OL})} \rightarrow \frac{R_F}{1 - A_{OL}} \rightarrow \phi$$

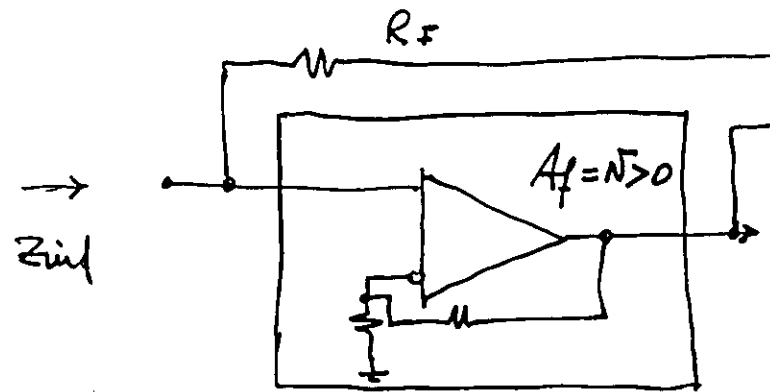BUT THIS HOLDS FOR ANY SIGN OF A_{OL}
EVEN FOR $A_{OL} > 0 \dots$




16

$$Z_{in} = \frac{Z_{inOL} R_F}{R_F + Z_{inOL} (1 - A_{OL})}$$


$Z_{inOL} = \infty$ NOW AND $A_{OL} = N > 0$ THEN (REMEMBER $A_{OL} > 1$ ALSO)

$$Z_{in} = \frac{-R_F}{N-1} \leq 0 !$$

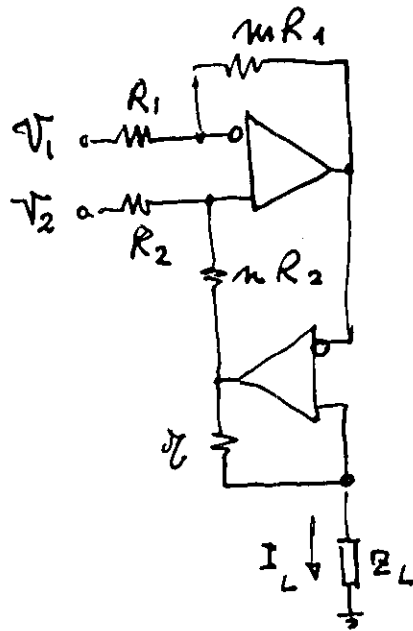WE CAN USE IT TO GENERATE INFINITE IMPEDANCES!



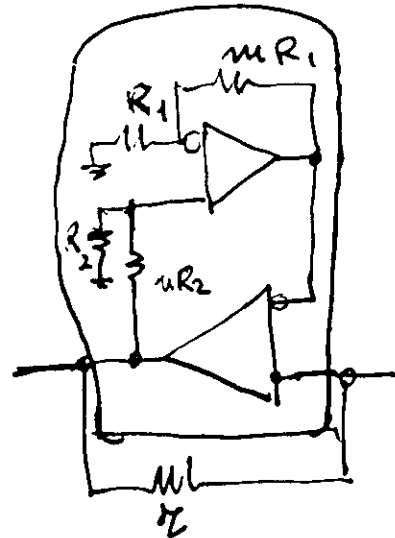WE WANT TO MAKE A VOLTAGE $(V_2 - V_1)$ CURRENT GENERATOR.
THE IMPEDANCE SEEN FROM LOAD Z_L MUST BE ∞ .



$$Z_{inf} = \frac{Z_{in} R_F}{R_F + Z_{in} (1 - A_{OL})}$$


$$R_F = R_L \quad Z_{in} = \infty$$

$$Z_{inf} = \frac{R_L}{1 - A_{OL}} \quad \text{TO HAVE } Z_{inf} = \infty$$

$$A_{OL} \text{ MUST BE } = 1$$

CONDITION TO
FROM Z_L . BUT WHICH IS

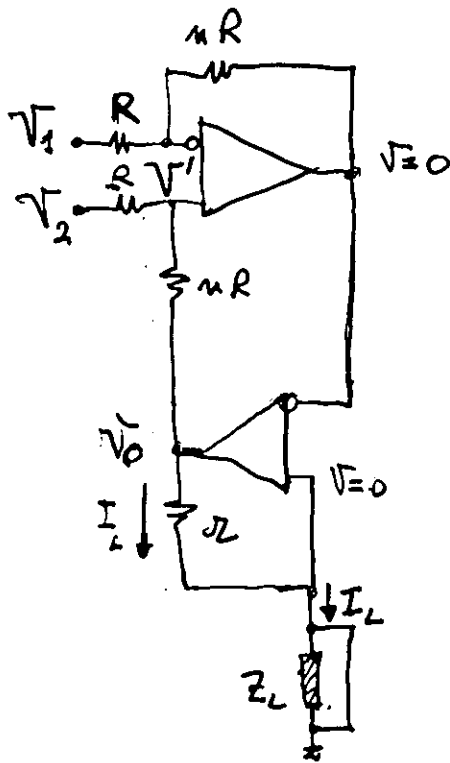THAT MEANS $M = M_L$
HAVE I_L INDEPENDENT
THE VALUE OF I_L ?




$$V_1' = \frac{V_1}{R + nR} \cdot nR = \frac{V_1 n}{1 + n}$$

$$V_2' = \frac{V_2 - V_0}{R + nR} \cdot nR + V_0 = \frac{V_2 - V_0}{1 + n} n + V_0$$

$$\begin{aligned} V_1' \frac{n}{1 + n} &= \frac{V_2 n}{1 + n} - V_0 \left[\frac{n}{1 + n} - 1 \right] \\ &= \frac{V_2 n}{1 + n} + V_0 \left[\frac{1}{1 + n} \right] \end{aligned}$$

$$V_0 = (V_1 - V_2) n$$

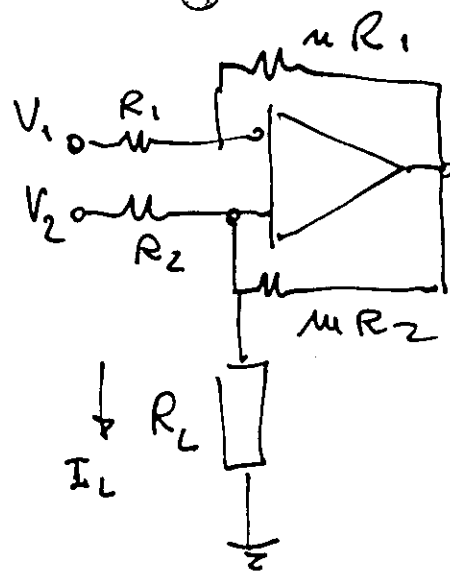
$$I_L = \frac{V_0}{Z_L} = \frac{V_1 - V_2}{Z_L} n$$




TRY TO FIND THE CONDITIONS
TO HAVE $I_L = f(V_1, V_2)$

OR

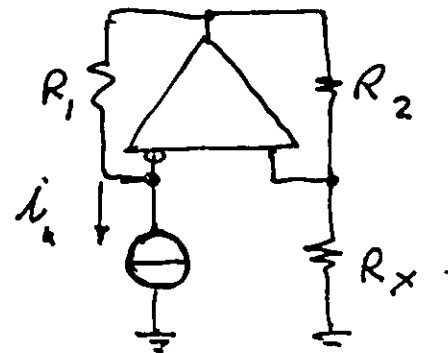④ CALCULATE I_L ON R_x AS A FUNCTION OF
 R_1 & R_2




Single pole system

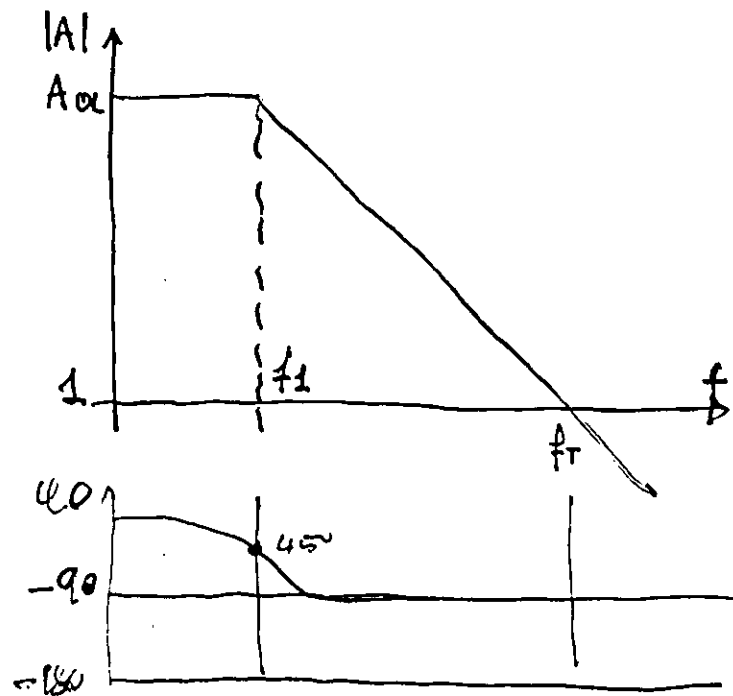


$$A = \frac{A_0}{1 + j f / f_1}$$

Two pole system

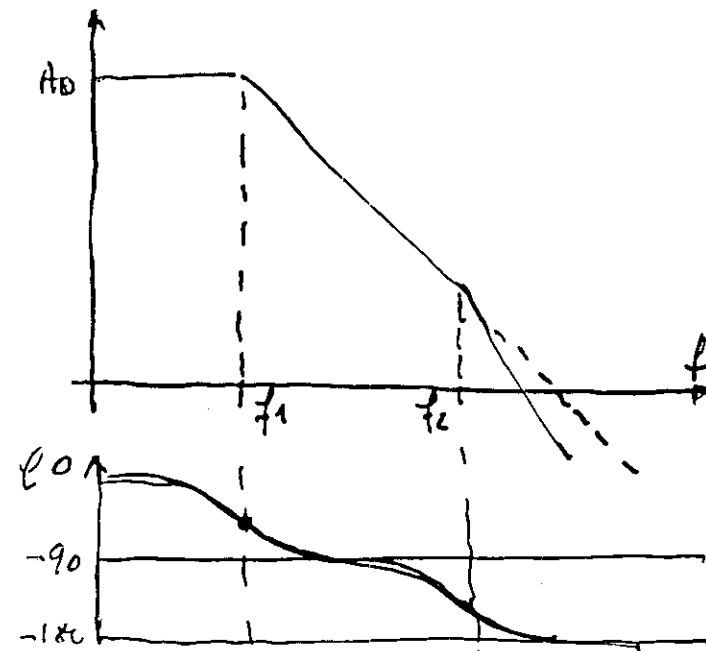

$$A = \frac{A_0}{(1 + j f / f_1)(1 + j f / f_2)}$$

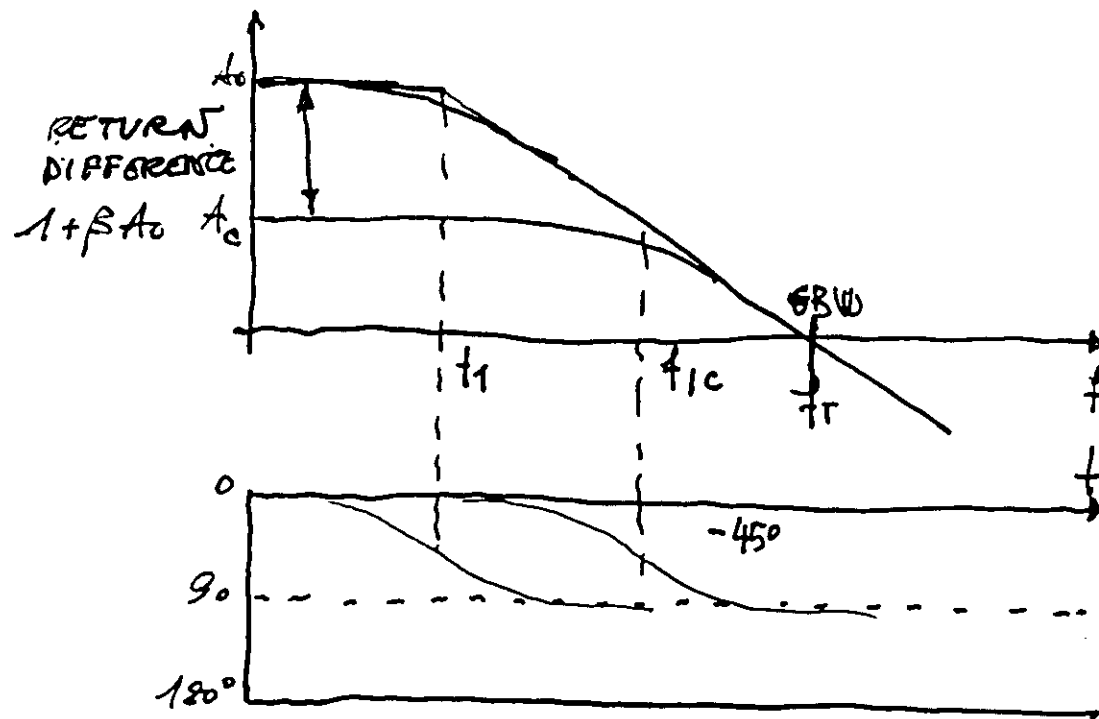CLOSED LOOP GAIN A_c IN A ONE-POLE SYSTEM




$$A_0 f_1 = 1 + \beta A_0 A_c$$

$$A_c f_{1c} = f_T$$

GBW

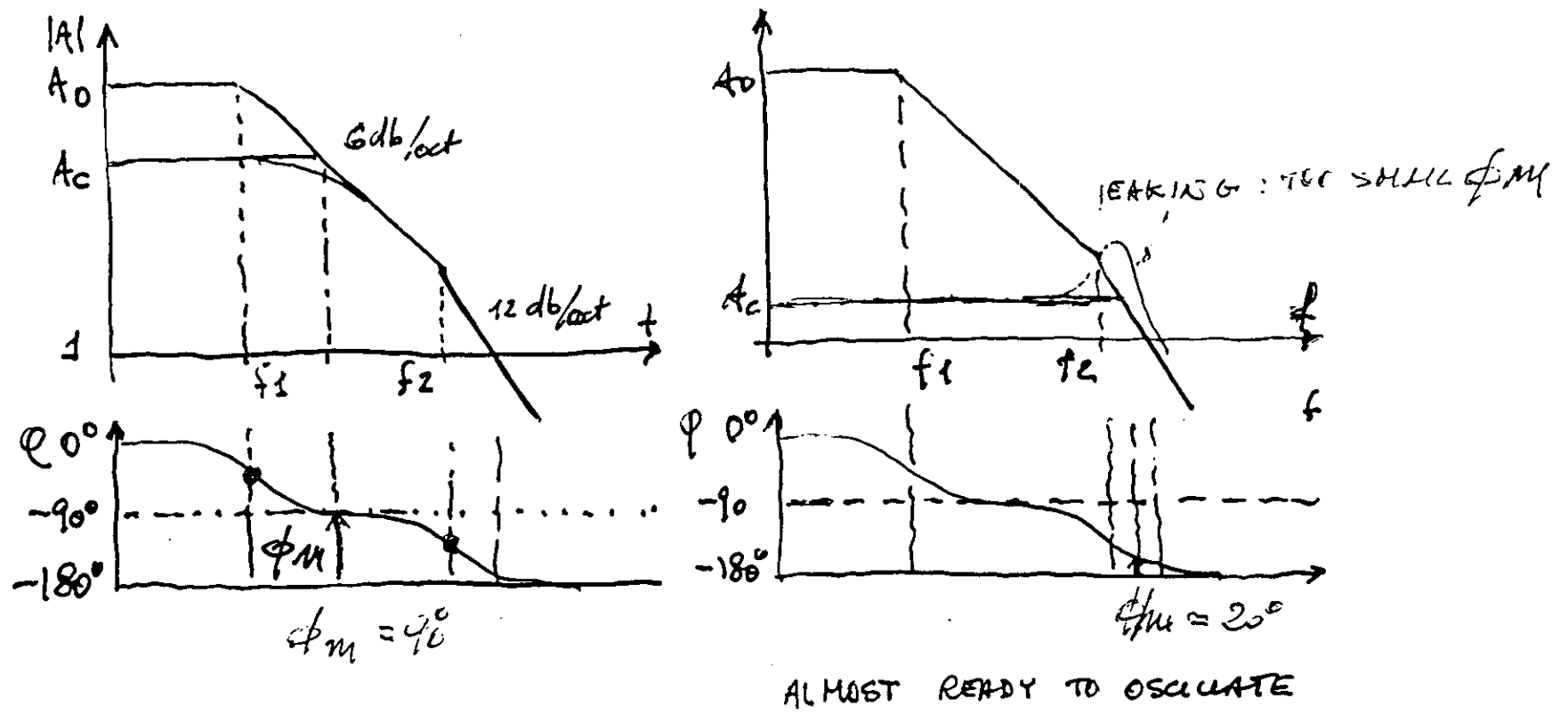TWO POLES SYSTEM WITH DIFFERENT CLOSED LOOP GAIN A_c



THE CRITERION FOR STABILITY AGAINST OSCILLATION A CLOSED LOOP IS:

THE OPEN LOOP PHASE SHIFT MUST BE LESS THAN 180°

AT THE FREQUENCY AT WHICH THE LOOP GAIN (IN THE FEEDBACK CONFIGURATION) IS UNITY.

$$\text{NB } A_c = \frac{A_o}{1 + \beta A_o}$$

$$\frac{1 + \beta A_o}{\beta A_o}$$

RETURN DIFFERENCE
LOOP GAIN

$$A_o \rightarrow \infty \approx \frac{1}{\beta}$$

THE HARDEST CONDITION IS WHEN THE AMPLIFIER CONNECTED AS FOLLOWER AS LOOP GAIN EQUALS THE OPEN LOOP GAIN AT THE f WHERE THE PHASE SHIFT IS 180° .

