


Outline

- Introduction – *“Is there a limit?”*
- Transistors – *“CMOS building blocks”*
- Parasitics I – *“The [un]desirables”*
- Parasitics II – *“Building a full MOS model”*
- The CMOS inverter – *“A masterpiece”*
- Technology scaling – *“Smaller, Faster and Cooler”*
- Technology – *“Building an inverter”*
- Gates I – *“Just like LEGO”*
- The pass gate – *“An useful complement”*
- Gates II – *“A portfolio”*
- Sequential circuits – *“Time also counts!”*
- DLLs and PLLs – *“A brief introduction”*
- Storage elements – *“A bit in memory”*


Sequential circuits

- Time in logic circuits
- “A bad memory”
- Latch 1
- Latch 2
- D flip-flop
- State machine timing
- Interconnects
- Clock distribution


“Time also counts”

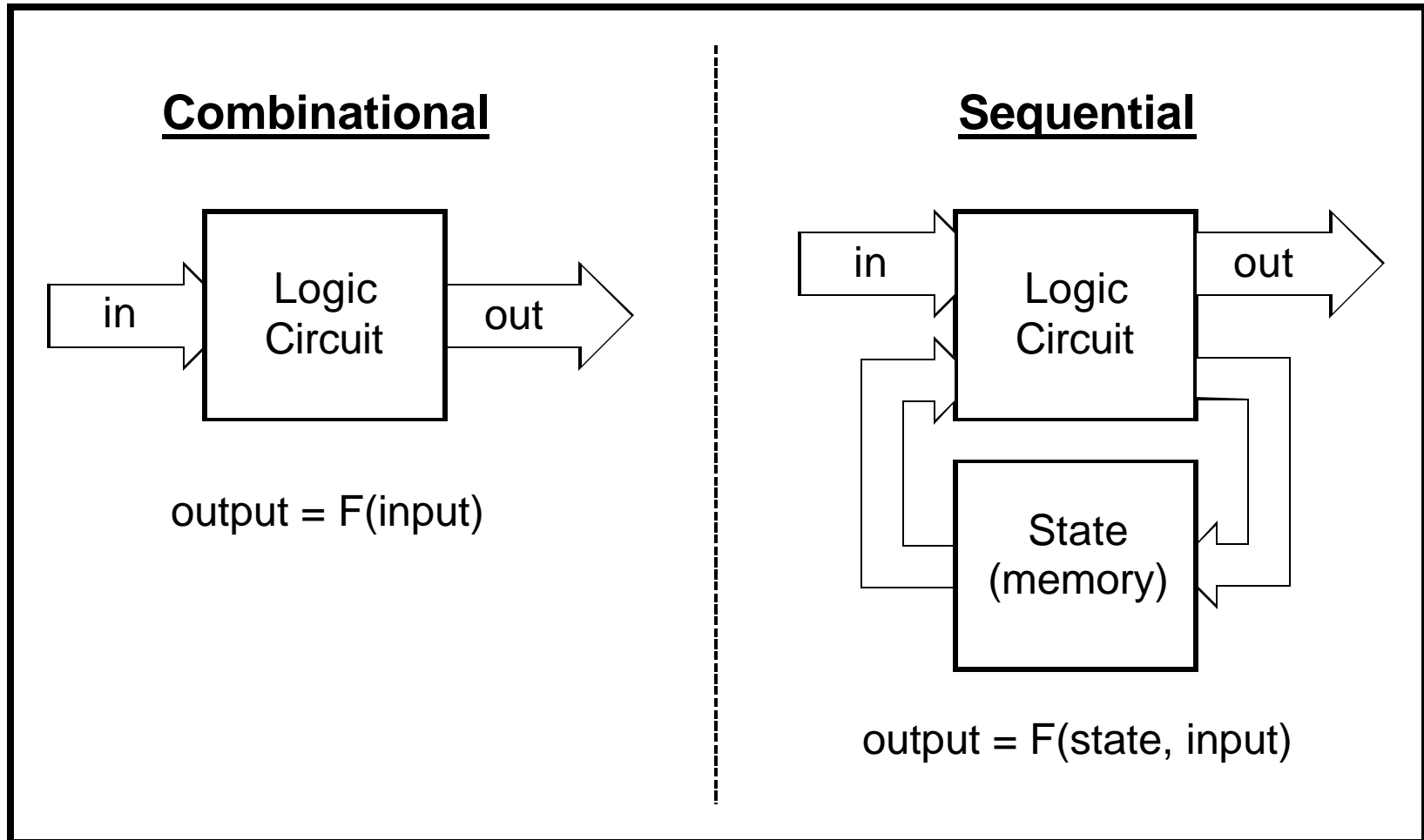


RS Latch – “A bad memory”

 


Latch

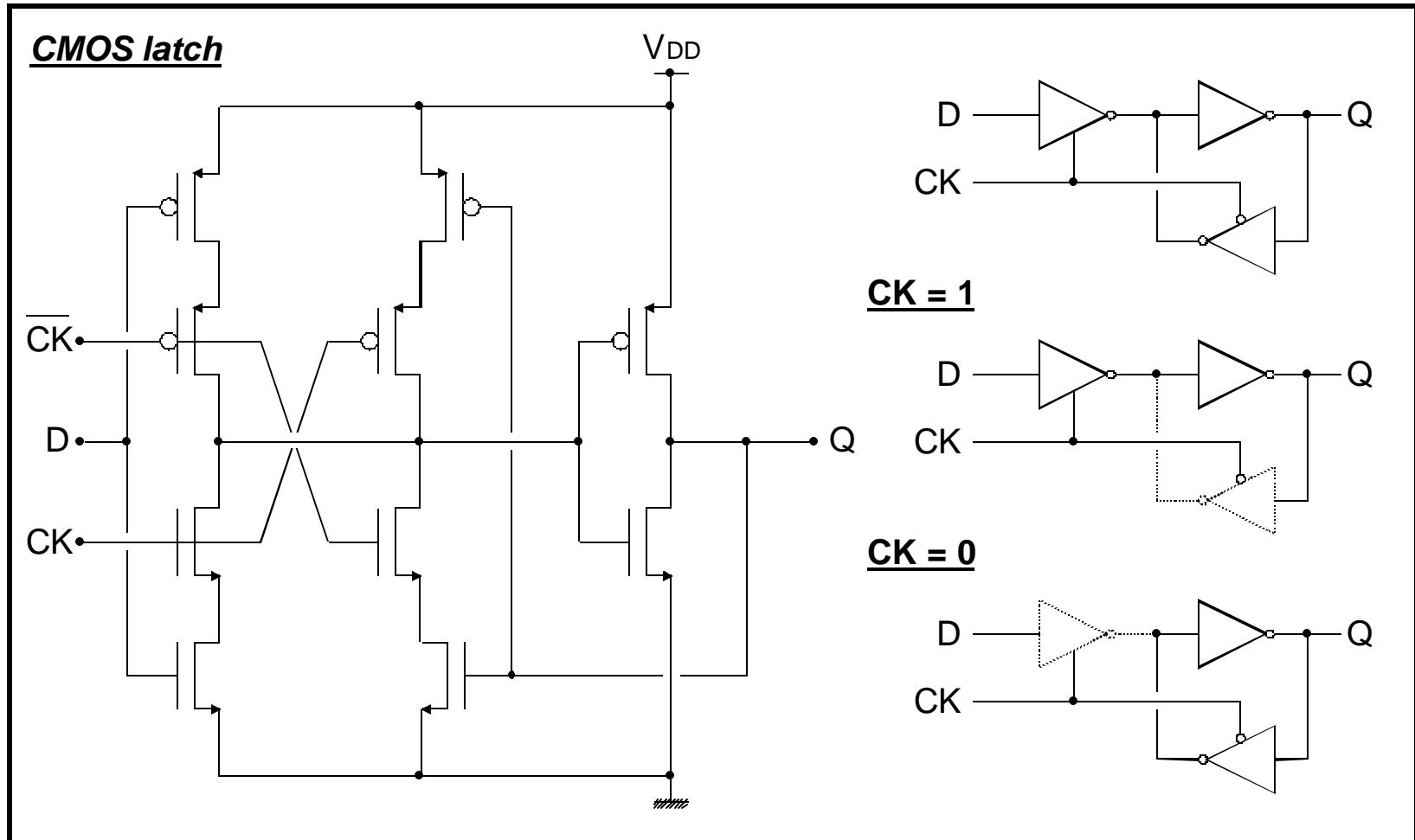


Latch

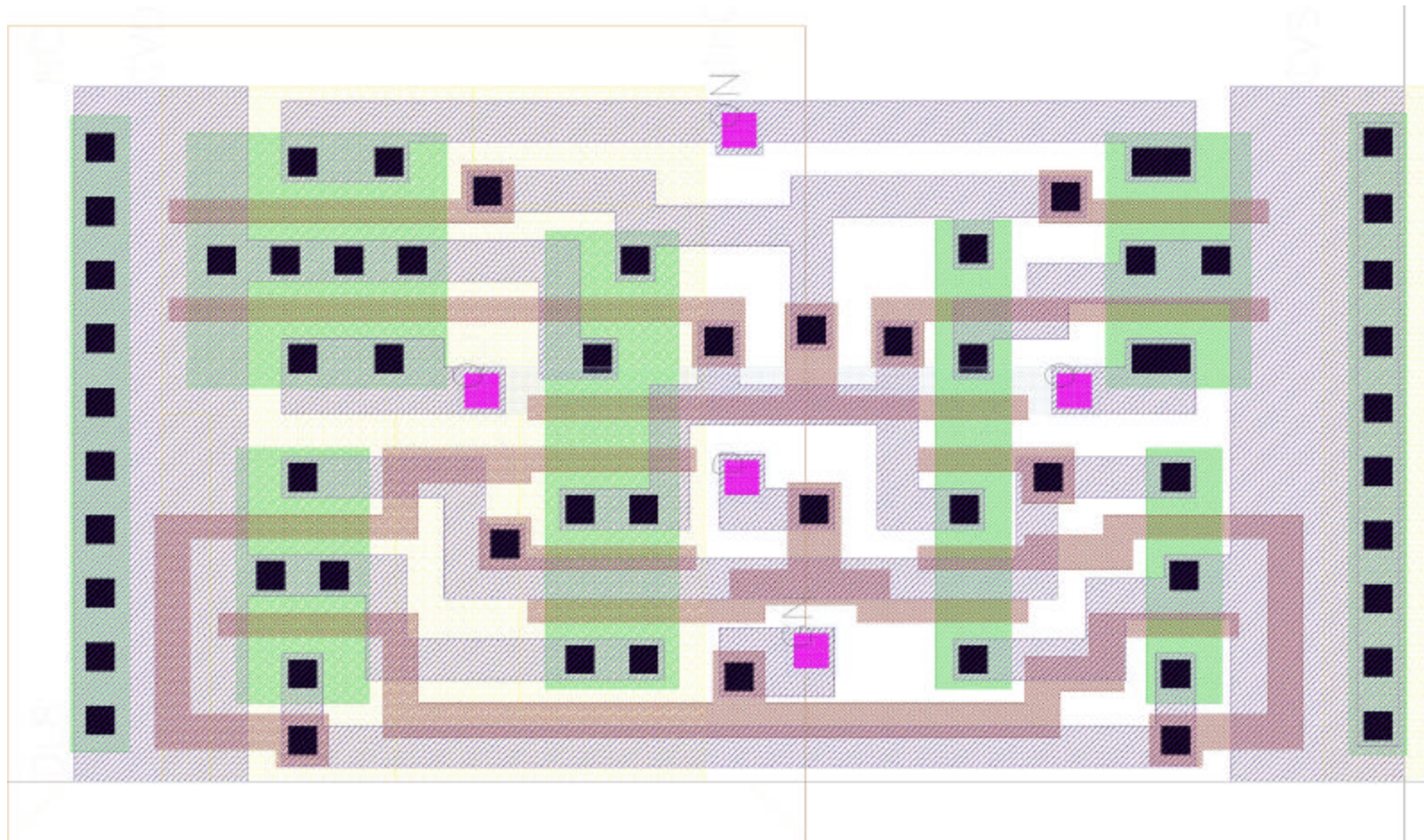


Latch

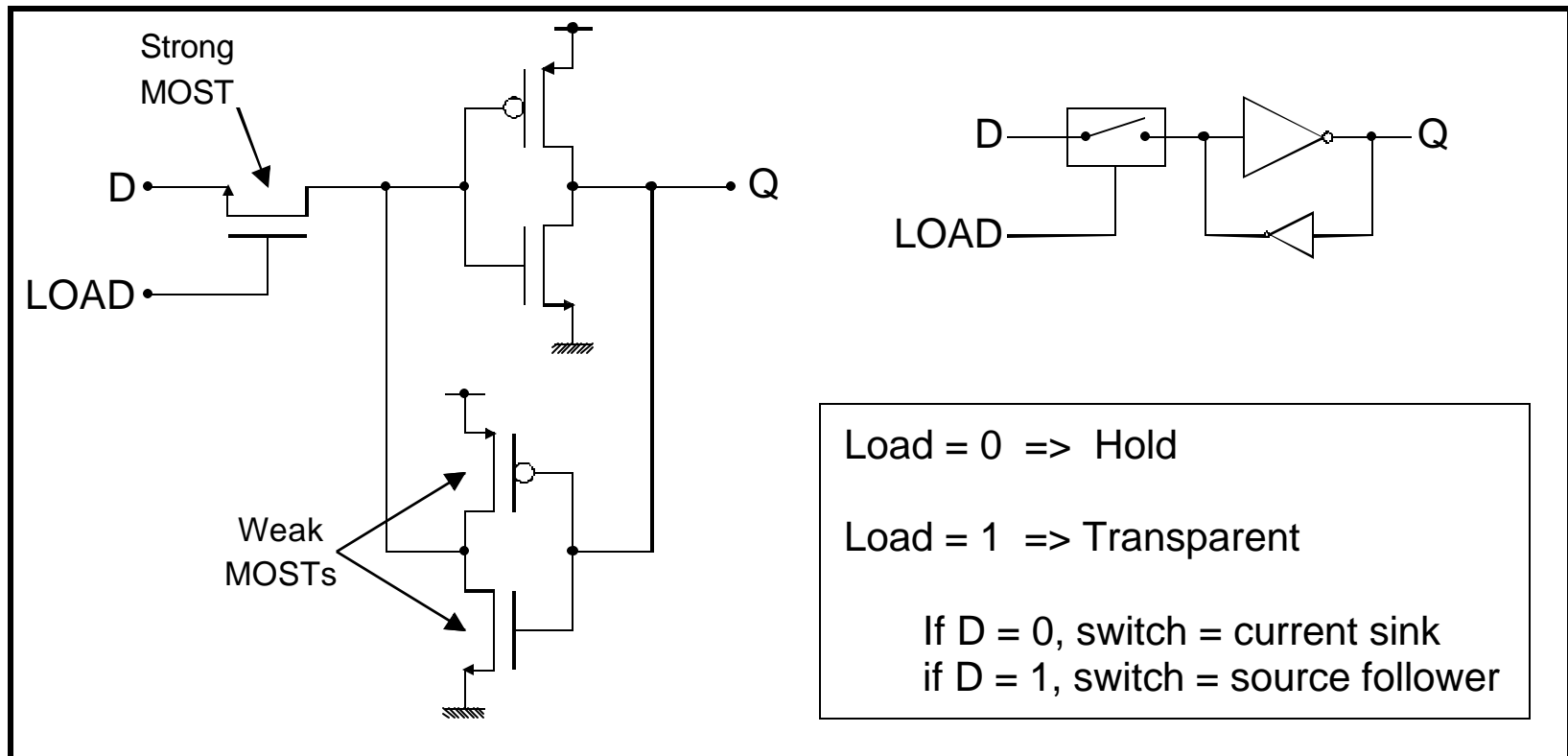


D Flip-Flop

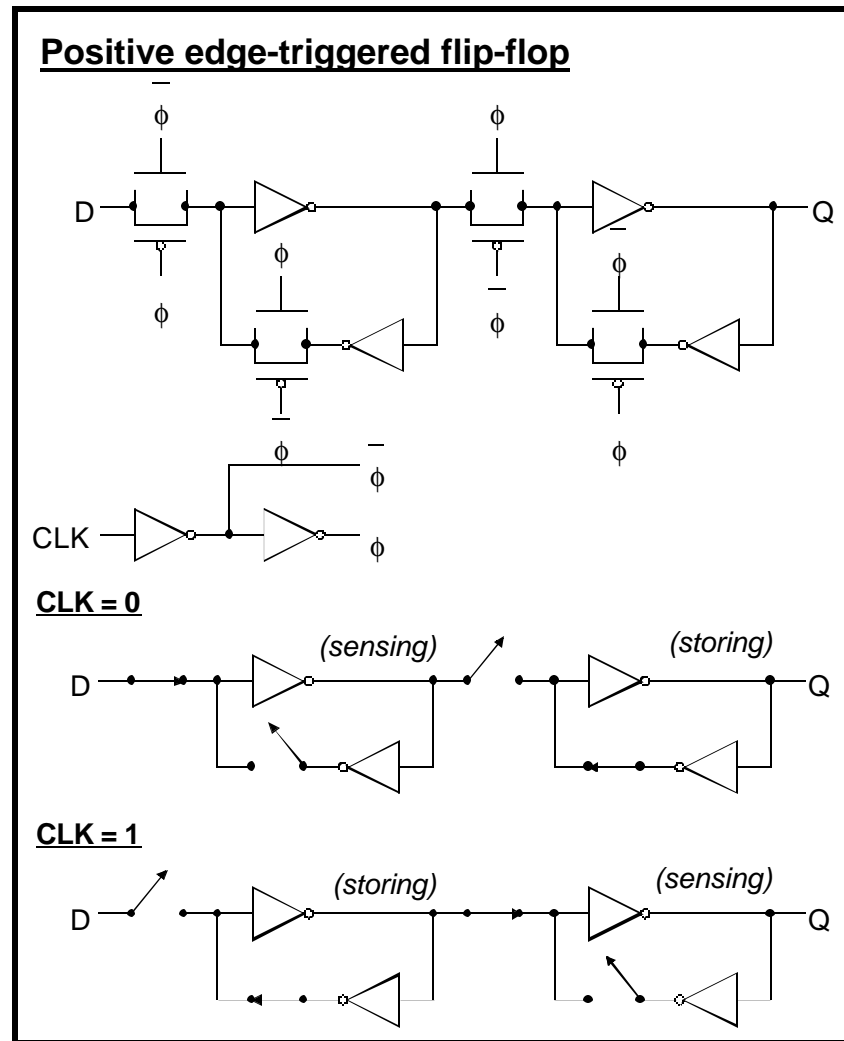


D Flip-Flop

 

State machine timing

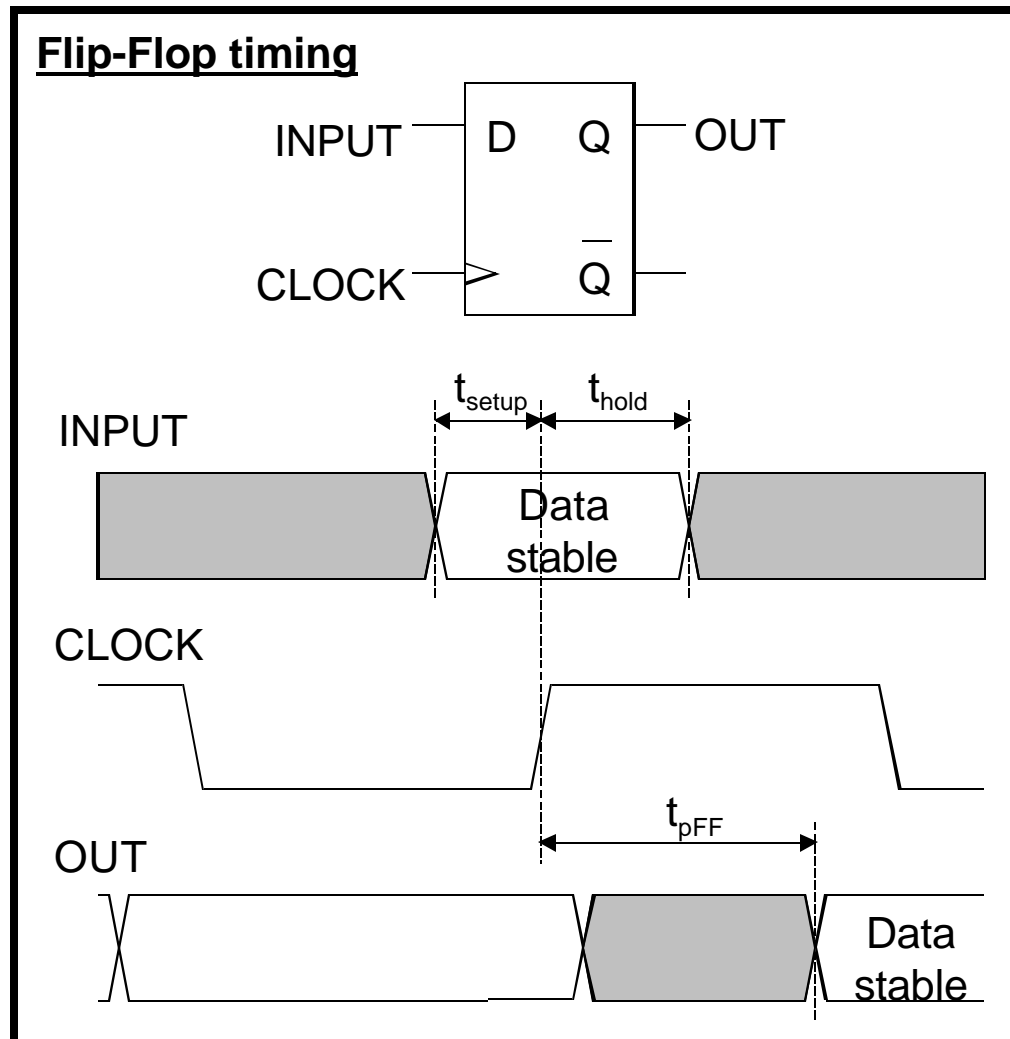



State machine timing

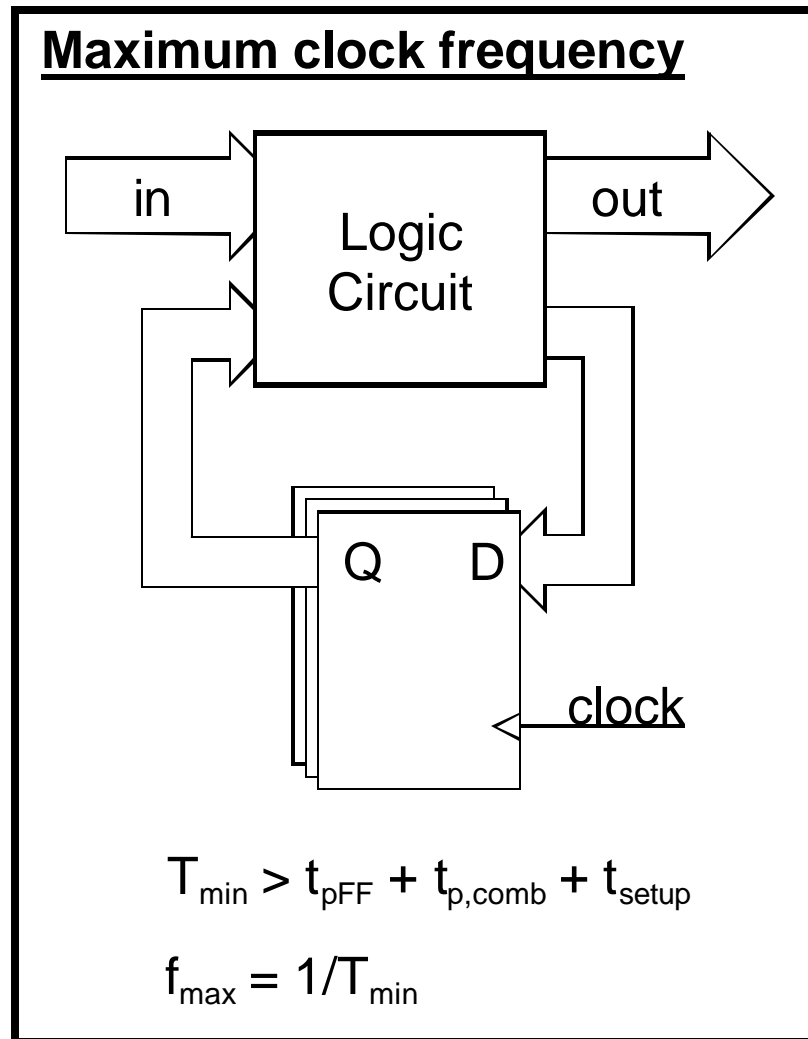

Interconnects

- The previous result assumes that signals can propagate instantaneously across interconnects
- In reality interconnects are metal or polysilicon structures with associated resistance and capacitance.
- That, introduces signal propagation delay that has to be taken into account for reliable operation of the circuit

Interconnects

 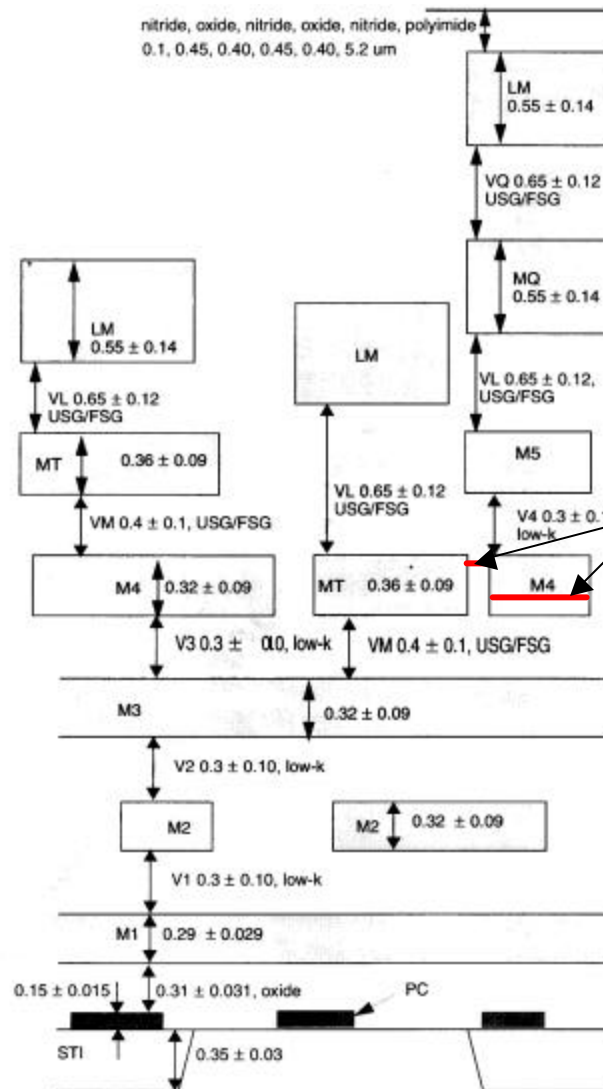

- § Capacitance to substrate becomes irrelevant
- § Capacitance to neighboring signal becomes dominating
- § Noise to neighboring signal also not negligible
- § Extraction for Timing simulation horribly complicated: tools absolutely mandatory

Interconnects


 
 


Figure 3.10: Interconnect capacitance including wire-to-wire capacitance [Schaper83]. (© 1983 IEEE)

Interconnects

Conductor

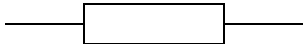


$$R = R_{\square} \frac{L}{W}$$
A circuit symbol for a resistor, consisting of a rectangle with horizontal lines extending from its left and right sides.

Film	Sheet resistance (Ω/square)
n-well	310
p+, n+ diffusion (salicided)	4
polysilicon (salicided)	4
Metal 1	0.12
Metal 2, 3 and 4	0.09
Metal 5	0.05

(Typical values for an advanced process)

Interconnects

 


- Via or contact resistance depends on:
 - The contacted materials
 - The contact area

Via/contact	Resistance (Ω)
M1 to n+ or p+	10
M1 to Polysilicon	10
V1, 2, 3 and 4	7



Interconnects

Routing capacitance

 


Interconnect layer	Parallel-plate (fF/ μm^2)	Fringing (fF/ μm)
Polysilicon to sub.	0.058	0.043
Metal 1 to sub.	0.031	0.044
Metal 2 to sub.	0.015	0.035
Metal 3 to sub.	0.010	0.033

Interconnects

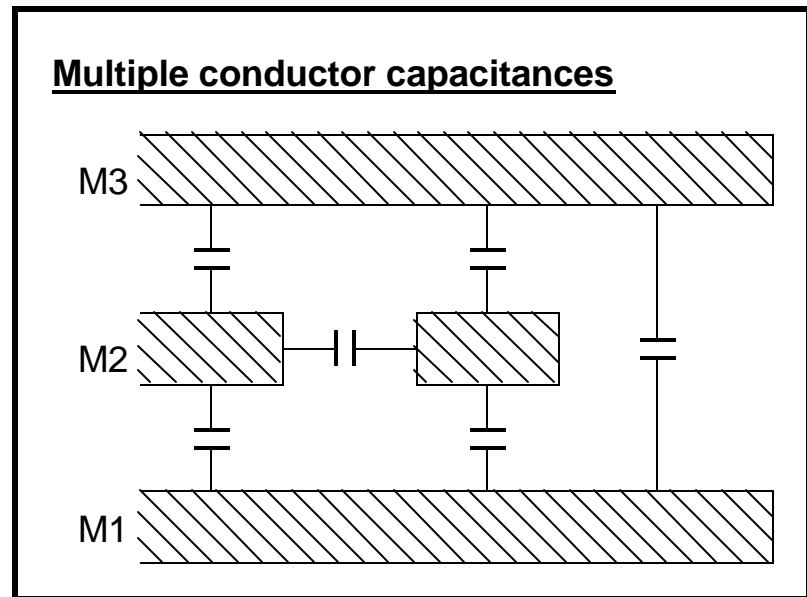 


- Three dimensional field simulators are required to accurately compute the capacitance of a multi-wire structure

Interconnects

 

- Delay depends on:
 - Impedance of the driving source
 - Distributed resistance/capacitance of the wire
 - Load impedance
- Distributed RC delay:
 - Can be dominant in long wires
 - Important in polysilicon wires (relatively high resistance)
 - Important in salicided wires
 - Important in heavily loaded wires


Interconnects

 

Clock distribution


- Clock signals are “special signals”
- Every data movement in a synchronous system is referenced to the clock signal
- Clock signals:
 - Are typically loaded with high fanout
 - Travel over the longest distances in the IC
 - Operate at the highest frequencies

Clock distribution

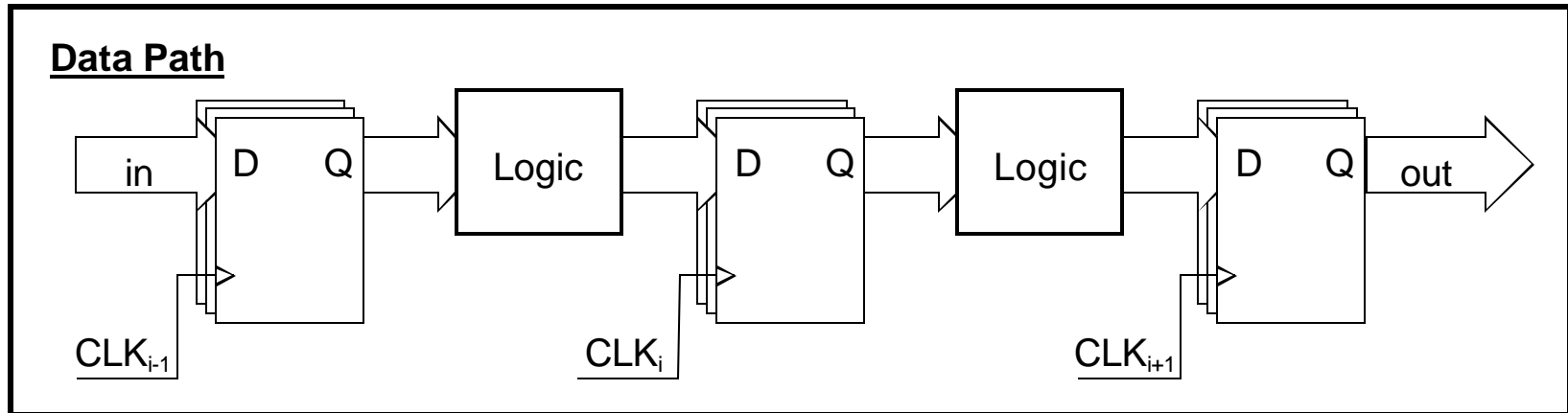

- “Equipotential” clocking:
 - In a synchronous system all clock signals are derived from a single clock source (“clock reference”)
 - Ideally: clocking events should occur at all registers simultaneously ... = $t(\text{clk}_{i-1}) = t(\text{clk}_i) = t(\text{clk}_{i+1}) = \dots$
 - In practice: clocking events will occur at slightly different instants among the different registers in the data path

Clock distribution

 

Clock distribution

- Skew: difference between the clocking instants of two “sequential” registers:

$$\text{Skew} = t(\text{CLK}_i) - t(\text{CLK}_{i+1})$$

- Maximum operation frequency:


$$T_{\min} = \frac{1}{f_{\max}} = t_{dFF} + t_{\text{int}} + t_{p,comb} + t'_{\text{int}} + t_{\text{setup}} + t_{\text{skew}}$$

- Skew > 0, decreases the operation frequency
- Skew < 0, can be used to compensate a critical data path BUT this results in more positive skew for the next data path!

Clock distribution

- Different clock paths can have different delays due to:
 - Differences in line lengths from clock source to the clocked registers
 - Differences in delays in the active buffers within the clock distribution network:
 - Differences in passive interconnect parameters (line resistance/capacitance, line dimensions, ...)
 - Differences in active device parameters (threshold voltages, channel mobility)
- In a well designed and balanced clock distribution network, the distributed clock buffers are the principal source of clock skew


Clock distribution

 

- Clock buffers:
 - Amplify the clock signal degraded by the interconnect impedance
 - Isolate the local clock lines from upstream load impedances

Clock distribution

Balanced clock tree

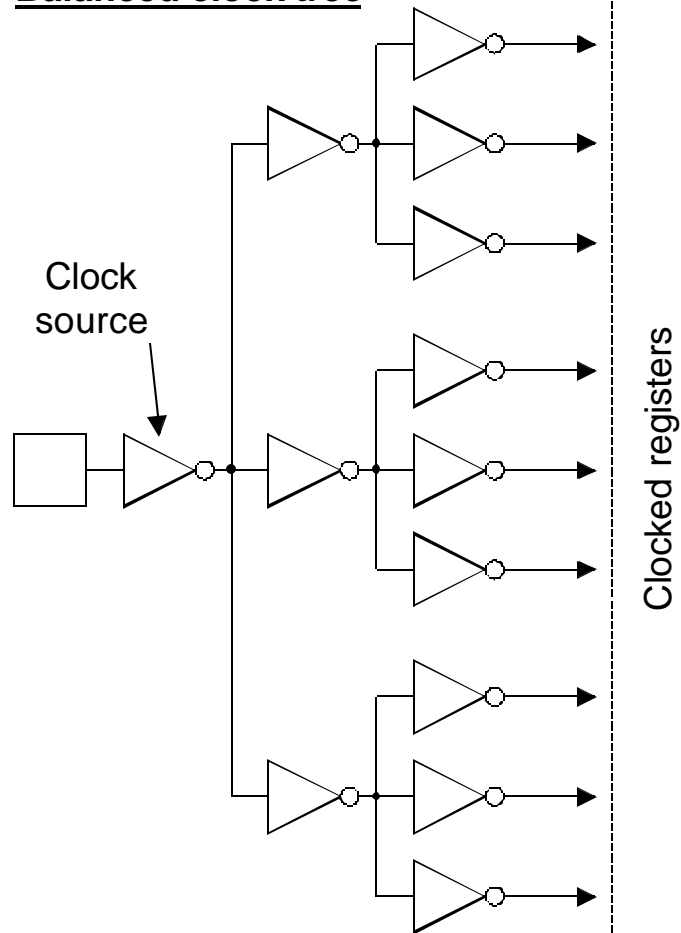

Clock buffer

