

OUTLINE

I - INTRODUCTION


II - DESIGN METHODOLOGY: AN OVERVIEW

III - ABSTRACTION LEVELS IN ALLIANCE

IV - VHDL: A HARDWARE DESCRIPTION LANGUAGE

V - VHDL: THE ALLIANCE SUBSET


VI - ALLIANCE: A COMPLETE DESIGN SYSTEM

 


Synthesis Levels

- ✗ Architectural
- ✓ Finite State Machine
 - ✓ Logic
 - ✓ Layout

Synthesis Architecture

 

Optimization and Synthesis Flow

 

Logic Synthesis


```
ENTITY dec2to4 is
PORT(A,B,enable:in BIT;
      vdd,vss,vdde,vsse:in BIT;
      Y:out bit_vector(0 to 3));
end dec2to4;
```

architecture dflow of dec2to4 is

```
signal a_bar,b_bar:bit;
signal a1,a2,a3,a4:bit;
```

```
begin
  a_bar <= not a;
  b_bar <= not b;
```

Combinational
Logic Synthesis

 

Gate Netlist =
Gate Level
Structural Description


```
ENTITY adder is
PORT(A,B,enable:in BIT;
      vdd,vss,vdde,vsse:in BIT;
      ck: in bit;
      Y:out bit_vector(0 to 3));
end dec2to4;
```

architecture dflow of adder is

```
signal regstr:reg_vector(0 to 3)
      register;
signal a1,a2,a3,a4:bit;
```

```
begin
```

Sequential
Logic Synthesis

 

Gate Netlist =
Gate Level
Structural Description


Optimization

Improve Description at Equivalent Level

$$\begin{cases} X = A + \bar{A}.C.D \\ Y = C.D \end{cases} \Rightarrow \begin{cases} X = A + Y \\ Y = C.D \end{cases}$$

Representation

Boolean Network

 

Binary Decision Diagram (BDD) (1)

Based on the Shannon Theorem

$$F(X_1, X_2, \dots, X_n) = \overline{X_1} \cdot F(0, X_2, \dots, X_n) + X_1 \cdot F(1, X_2, \dots, X_n)$$

✓ Canonical Representation of a Boolean Equation


Binary Decision Diagram (BDD) (2)

Example: $F(a, b) = a + b$

$$\begin{aligned} F &= \bar{a}.F(0, b) + a.F(1, b) \\ &= \bar{a}.(0 + b) + a.(1 + b) \\ &= \bar{a}.(b) + a.(1) \\ &= \bar{a}.(\bar{b}.(0) + b.(1)) + a.(\bar{b}.(1) + b.(1)) \end{aligned}$$



Binary Decision Diagram (BDD) (3)
 
$$F = \bar{a} \cdot (\bar{b} \cdot (0) + b \cdot (1)) + a \cdot (\bar{b} \cdot (1) + b \cdot (1))$$




Binary Decision Diagram (BDD) (3)

 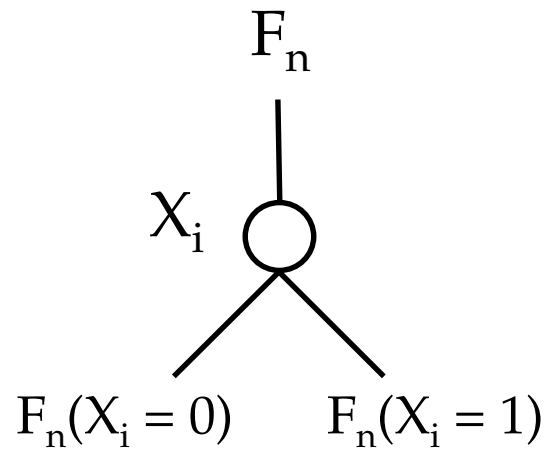Ex: $F = \bar{a}\bar{b} + \bar{a}b\bar{c} + a\bar{b}\bar{c}$




Logic Synthesizer


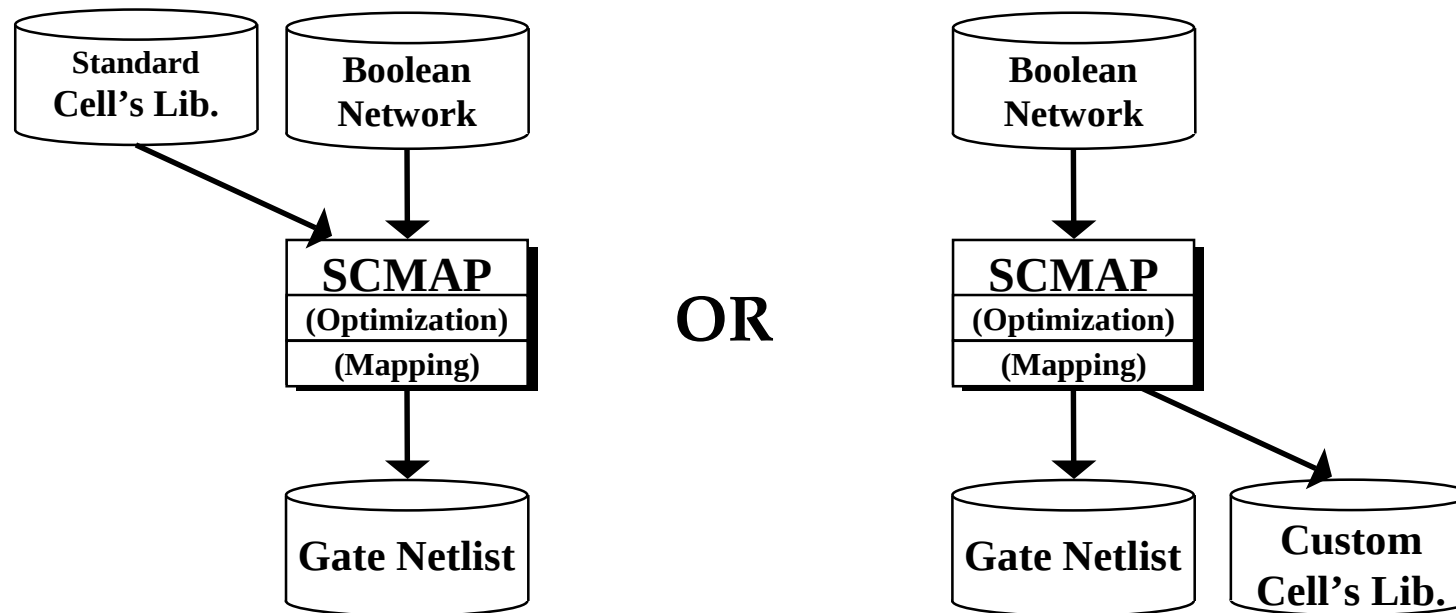


YAGLE: Functional Abtractor (1)

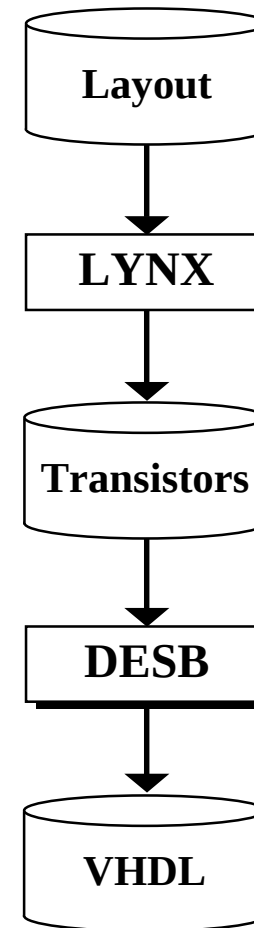
- ✓ Generates behavioral data flow VHDL
- ✓ Provides Functional Verifications
- ✓ Does not use any cell library
- ✓ Accepts standard transistor netlist format (VTI, SPICE)



YAGLE: Functional Abtractor (2)

  

THE GATE 'E'

 

$E \leq (\text{NOT } A \text{ AND } C) \text{ OR } (\text{NOT } B \text{ AND } D);$

$H \leq \text{NOT } F;$

$G \leq \text{NOT } E;$

$F \leq \text{NOT } B;$

FSM: Finite State Machine (1)


- ❑ Models Sequential Circuits
- ❑ Two Kinds of FSM
- ❑ Graph Representation
- ❑ Definition:

$$\text{State (t+1)} \quad \leq F(i_1, \dots, i_n, \text{State(t)})$$

$$\text{Output}_i \quad \leq F(i_1, \dots, i_n, \text{State(t)})$$

FSM: Finite State Machine (2)

Example: Four Consecutive Ones Counter

 

FSM: Finite State Machine (3)

The Description Language

- ❑ Standard
- ❑ VHDL Subset
- ❑ The States are Enumerated Types
- ❑ Two Special Signals
- ❑ Two Processes

FSM: The Four Consecutive Ones Counter (1)

--

Entity counter is port (ck, I, reset: in bit; O: out bit);

End counter;

Architecture automate of counter is

type STATE_TYPE is (E0, E1, E2, E3, E4);

signal CURRENT_STATE, NEXT_STATE: STATE_TYPE;

-- pragma CUR_STATE CURRENT_STATE;

-- pragma NEX_STATE NEXT_STATE;

-- pragma CLOCK ck;

begin

 Process(CURRENT_STATE, I, reset)

 begin

 if (reset = '1') then

 NEXT_STATE <= E0;

 O <= '0';

 else

FSM: The Four Consecutive Ones Counter (2)

```
case CURRENT_STATE is
    WHEN E0 =>
        if (I='1') then
            NEXT_STATE <= E1;
        else
            NEXT_STATE <= E0;
        end if;
        O <= '0';

    WHEN E1 =>
        if (I='1') then
            NEXT_STATE <= E2;
        else
            NEXT_STATE <= E0;
        end if;
        O <= '0';
```

FSM: The Four Consecutive Ones Counter (3)

```
WHEN E2 =>  
    if (I='1') then  
        NEXT_STATE <= E3;  
    else  
        NEXT_STATE <= E0;  
    end if;  
    O <= '0';
```

```
WHEN E3 =>  
    if (I='1') then  
        NEXT_STATE <= E4;  
    else  
        NEXT_STATE <= E0;  
    end if;  
    O <= '0';
```

FSM: The Four Consecutive Ones Counter (4)

```
        WHEN E4 =>
            if (I='1') then
                NEXT_STATE <= E4;
            else
                NEXT_STATE <= E0;
            end if;
            O <= '1';


        WHEN others =>
            assert ('1')
            report "Illegal State";

    end case;
end if;
end process;
```

FSM: The Four Consecutive Ones Counter (5)

```
Process (ck)
begin
    if (ck = '0' and not ck'stable) then
        CURRENT_STATE <= NEXT_STATE;
    end if;
end process;
end counter;
```

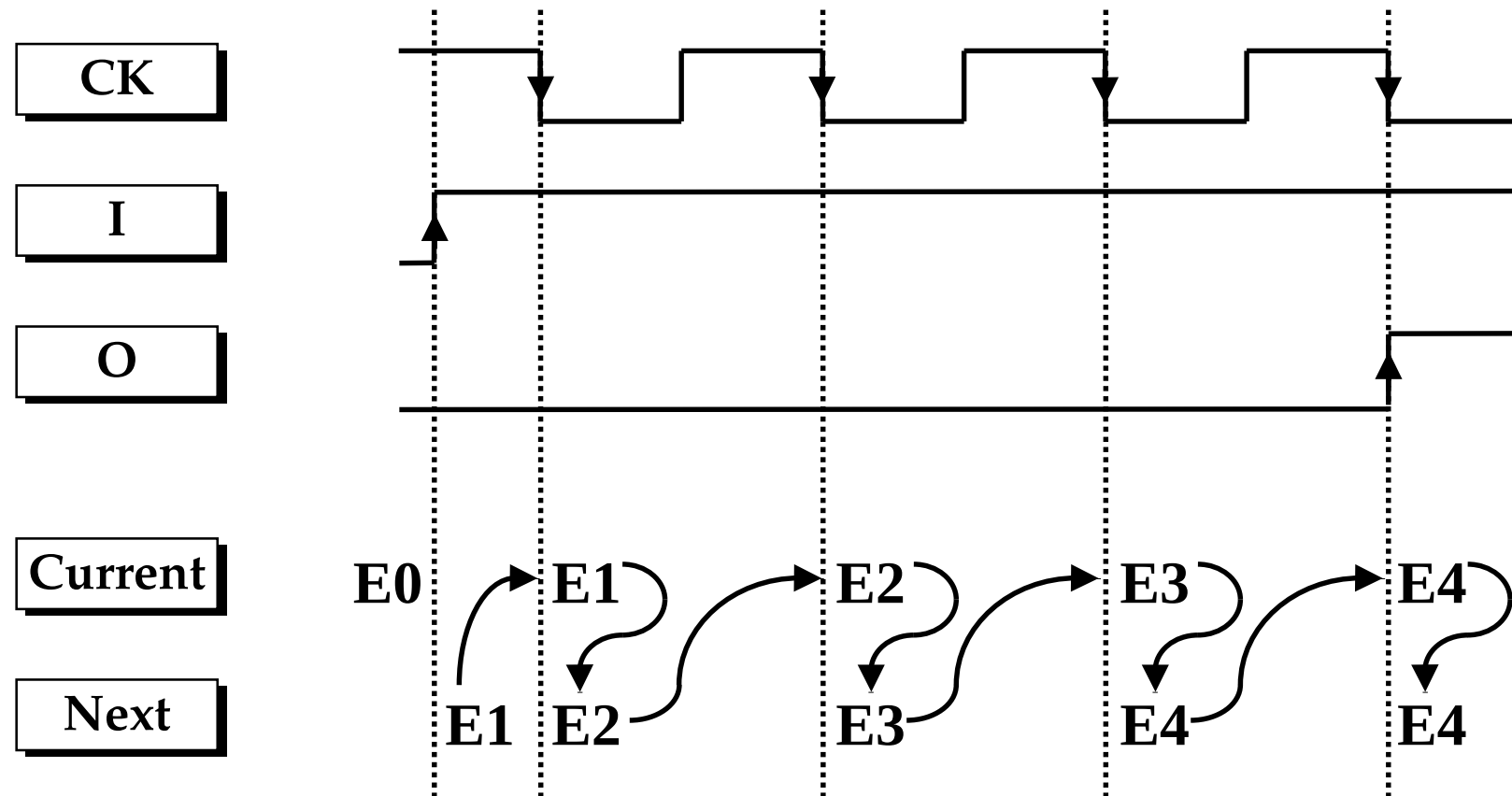FSM: The Four Consecutive Ones Counter (6)





FSM: Warning (1)

**All Signals which are Assigned to within a
Clocked Process Have Registers on their
Outputs**


FSM: Warning (2)

**Signal Assignments within a Process are
Effective only before the wait (implicit or
explicit) Statement**

FSM: Different Machine Types

  


FSM: The Counter with Mealey Machine

 


SYF: FSM Synthesizer

 
- ✓ Verification
- ✓ Encoding
- ✓ Optimization
- ✓ Driving Data Flow Description





DATA PATH (1)

 

DATA PATH (2)

 


DATA PATH (3)

  


Standard Cells Router
Versus
Data Path Router

DATA PATH (4)

 

DATA PATH (5)

 


Timing


- **Simulators**
 - Circuit-Level**
 - Timing**
 - Switch-Level**
 - Logic-Level**
- **Verifiers (Pattern Independent)**
 - Timing**

Simulation Design Flow

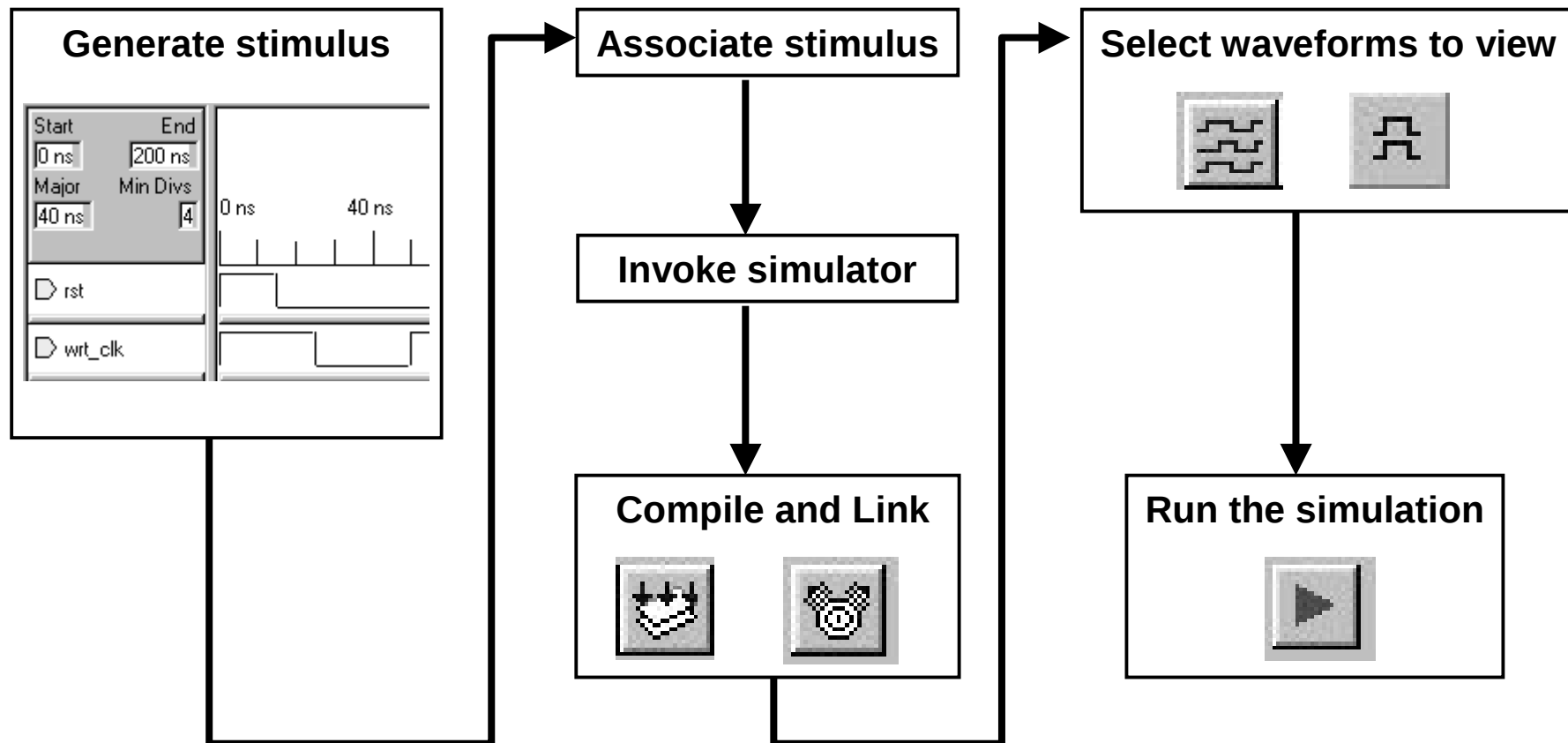For each block you want to simulate . . .




Timing

 


Timing

- Timing Driven Synthesis
- Timing Driven Combiner
- Timing Driven Floor-Planner
- Timing Driven Place & Route

Timing

 

Timing

 

----- Paths from Constraints on <GLOBAL_CLOCKS> -----

Actual	Needed	Slack (ID)	Source Pin(Net)	Sink Pin(Net)
17.1	15.0	-2.1 (WFM0)	FF1:CLK(N35)	FF1:D(N8)
17.1	15.0	-2.1 (WFM0)	FF1:CLK(N35)	FF2:D(N10)
17.1	15.0	-2.1 (WFM0)	FF2:CLK(N35)	FF1:D(N8)