

The Abdus Salam International Centre for Theoretical Physics



2023-11

Workshop on Topics in Quantum Turbulence

16 - 20 March 2009

Measurement Methods of Vibrating Mechanical Objects Used for Generation and Detection of Quantum Turbulence

> P. Skyba Slovak Academy of Sciences Inst. of Experimental Physics Kosica Slovak Republic

# Notes on measurement methods of vibrating objects in low temperature physics

# Peter Skyba

Talk outline:

Introduction

Voltage measurement (vibrating wires technique)

Current measurement (tuning forks, torsional oscillators, grids technique)

Conclusion





# **Vibrating objects**

Traditional resonators used: vibrating wires, spheres, grids, oscillating discs,...

- resonators are immersed in liquid and bring into forced oscillations,
- properties of the liquids inferred from the resonance characteristics



# **Mechanical resonators - basic properties**

**Equation of motion:** 

$$\left|\ddot{x} + \gamma \dot{x} + \omega_0^2 x = f_0 \exp(i\omega t)\right|$$



tuning fork



$$I(t) = \alpha \frac{dx(t)}{dt}$$

 $\alpha$  – is the constant

vibrating wire

$$V_i \approx Bl \frac{dx(t)}{dt}$$

Velocity of the object:

$$v(\omega) = v(\omega_0) \frac{\gamma_2^2 \omega^2 + i\omega(\omega_0^2 - \omega^2 - \gamma_1 \omega)}{(\omega_0^2 - \omega^2 - \gamma_1 \omega)^2 + \gamma_2^2 \omega^2}$$

# Voltage measurements of vibrating wires - theory

Phase sensitive detection technique (lock in) in frequency range up to few kHz).

## **Typical experimental arrangement**

 $V_i \approx Blv(\omega)$ 



For the total voltage  $V_{out}$  being measured one can get (simplified form):

$$V_{out} = V_i \left( 1 - \frac{i\omega L_w}{R'} \right) + V_g \left( \frac{R_w}{R} - \frac{i\omega L_w}{R} \right)$$

 $R' = \frac{R.R_i}{R+R_i}$ 

## **Transformers** !

# Voltage measurements of vibrating wires - experiment

Total measured voltage:

$$V_{out} = V_i \left( 1 - \frac{i \omega L_w}{R'} \right) + V_g \left( \frac{R_w}{R} - \frac{i \omega L_w}{R} \right)$$

If B = 0 T, then  $V_i$  = 0 Volts, and  $V_{out}$  is:



If  $R_w$ =0, then in phase component is zero



#### $R_w$ and $L_w$ of the wire can be measured.

## Quadrature component



Slope is  $L_{\mu}/R$ 

Comment on L<sub>w</sub>!

# Vibrating wire with transformer – theory

As  $T \rightarrow 0K$ , in superfluid 3He-B dominant scattering process is Andreev reflection. Therefore, the wire (and any other mechanical resonator) is driven at low velocities.

$$V_i \approx B l v$$

This induced voltage becomes comparable with noise voltage of preamplifier as it operates at room temperature. Low temperature transformers are used to improve the signal to noise ratio.

Typical experimental arrangement:



For transformer the "T" model has been used.

## Vibrating wire with transformer – theory

Typical experimental arrangement:



## Higher transformer gain leads to a nontrivial amplitude-frequency response.

#### Vibrating wire with transformer – experiment

Measurement performed on wire of diameter 4.5  $\mu$ m having f<sub>0</sub> = 700 Hz. Transformer with gain N=30 and B=0Tesla.



#### **Current measurements – tuning forks**



Superposition theorem:

$$V_0 = V_{bgrd}(V_g) + Z(\omega)I_F$$

#### **Current measurements – tuning forks**



#### **Current measurements – tuning forks - experiment**

Let discuss first influence of the background voltage

$$V_{bgrd} = -\frac{Z_2}{R_1 + Z_2} \frac{1}{1 + (\omega C_0 R_i)^2} \left[ \omega^2 R_F R_i C C_0 - \frac{R_1}{Z_2} + ik\omega R_F C \right] V_g$$

Proper I/V converter  $R^{}_i \rightarrow 0 \Omega$  and  $R^{}_1 \rightarrow 0 \Omega,$  then



#### **Current measurements – tuning forks - experiment**

Effect of non zero input resistance ( $R_i \neq 0\Omega$ ) of an I/V converter on measurements

$$V_{sig} = -\frac{1 - i\omega C_0 R_i}{1 + (\omega R_i C_0)^2} R_F I_F(\omega)$$

Amplitude and phase change due to non-zero R<sub>i</sub>



#### Nearly all commercial available lock-in amplifiers having I/V converters have Ri $\neq 0\Omega$

#### **Current measurements – grids and torsional oscillators**

Typical measurement setup



$$I_{i}(t) = V_{DC} \frac{dC_{i}}{dt} = -V_{DC} \frac{C_{i}}{d_{i}} v_{i} \qquad v_{i}(\omega) = v_{i}(\omega_{0}) \frac{\gamma_{2}^{2}\omega^{2} + i\omega(\omega_{0}^{2} - \omega^{2} - \gamma_{1}\omega)}{(\omega_{0}^{2} - \omega^{2} - \gamma_{1}\omega)^{2} + \gamma_{2}^{2}\omega^{2}}$$

Superposition theorem ( $I_1$  is not contributed to  $V_0$ ):

$$V_0 = V_{bgrd}(V_g) + Z(\omega)I_2$$

#### **Current measurements – grids and torsional oscillators**



#### **Current measurements – grids - experimental**

Measurements performed using a Lancaster grid at  $\rm f_{0}$  ~ 1kHz and Q ~ 10^{5}

Proper I/V converter having  $R_i \rightarrow 0\Omega$ , then  $V_{bgrd}$  can be expressed as:

$$V_{bgrd} = -\frac{Z_2}{R_1 + Z_2} \left[ -\frac{R_1}{Z_2} + i\omega R_F C_P \right] V_g$$



Allows ratio  $R_1/(R_1+Z_2)$  to be determined experimentally ~ 0.0015

Allows  $C_P$  to be measured  $C_P$  7.7 pF

## **Problem with ground!**

# Conclusion

Voltage measurements on vibrating wires:

- easy to measure and determine the background when B=0T;

- direct wire measurements – an agreement between the model and experiment;

- transformers improve signal to noise ratio, but they change the frequency dependence of background (can be measured) and reduce input impedance of the preamplifier ( $R_i/N^2$ );

- higher N results in nontrivial (resonance) response of the background voltage;

- Instead of using R to determine current – use proper V/I converter.

Current measurement tuning forks, grids and torsional oscillators:

- impossibility to measure pure background like for vw's;

 non-zero input impedance of the I/V converter affects precision of measurements;

 ground problems – resistive attenuators dividers followed by a voltage follower providing impedance insulation and proper voltage source;

## Acknowledgement

Acknowledgement to lads who shared their experience of using these devices with me:

D. Bradley, V. Efimov, V. Eltsov, S. Fisher, D. Garg, T. Guenault, R. Haley, M. Jackson, G. Pickett, L. Skrbek, V. Tsepelin and L. Wheatland.

Thank's for your attention.