



**The Abdus Salam
International Centre for Theoretical Physics**



2177-18

**ICTP Latin-American Basic Course on FPGA Design for Scientific
Instrumentation**

15 - 31 March 2010





**Digital arithmetic II
(basic arithmetic operations - Comparators)**

BAZARGAN SABET Pirouz
*LIP6, University Pierre et Marie Curie
Paris
France*

Outline

Digital CMOS design


Arithmetic operators

-  Adders
-  Comparators
-  Shifters
-  Multipliers

Comparators

Comparing a natural number to a constant : =

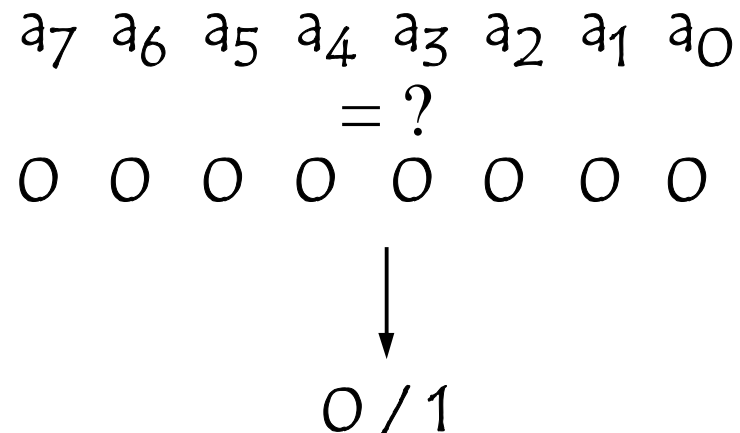Let consider a natural number a coded on 8 bits using Natural Binary Code



Comparators

Comparing a natural number to zero : =

Boolean function

Null = 1 if


$$\bar{a}_7 \cdot \bar{a}_6 \cdot \bar{a}_5 \cdot \bar{a}_4 \cdot \bar{a}_3 \cdot \bar{a}_2 \cdot \bar{a}_1 \cdot \bar{a}_0 = 1$$

$$\text{Null} = a_7 + a_6 + a_5 + a_4 + a_3 + a_2 + a_1 + a_0$$

Comparators

Comparing a natural number to zero : =


Implementation

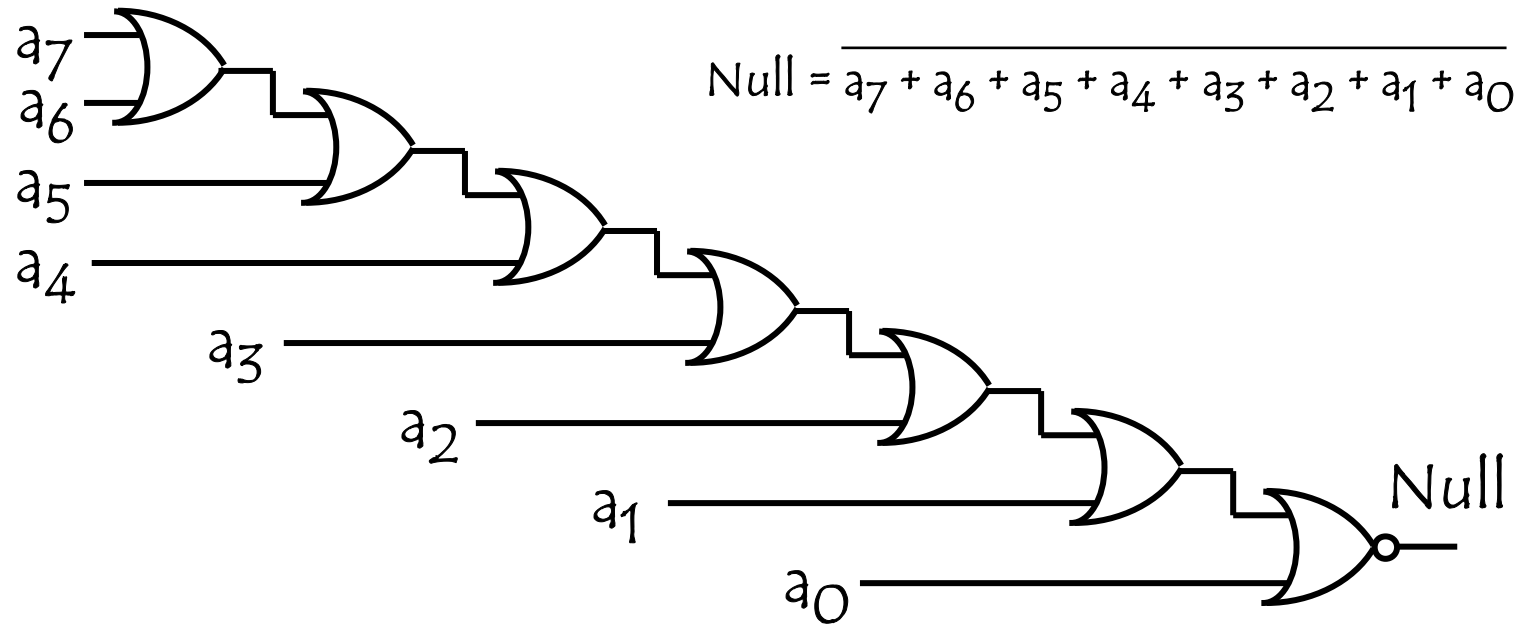

Comparators

Comparing a natural number to zero : =


Implementation

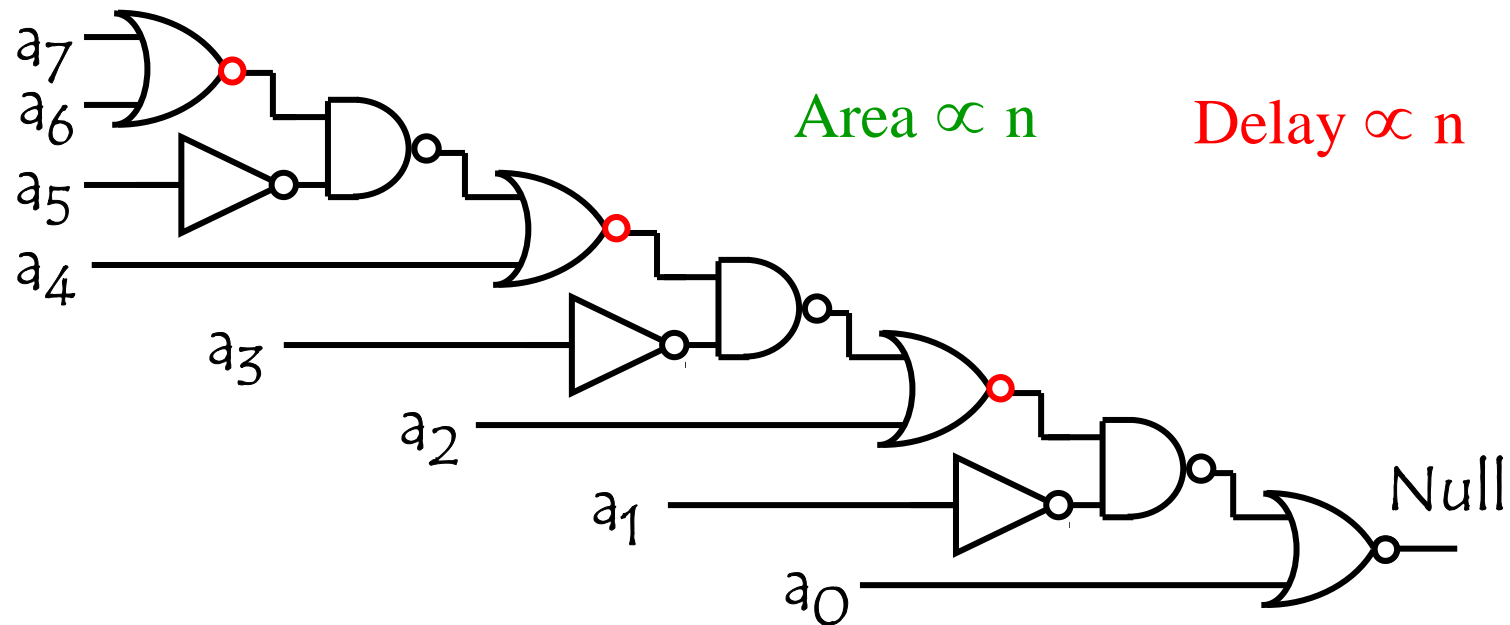

Comparators

Comparing a natural number to zero : =


Implementation improvement

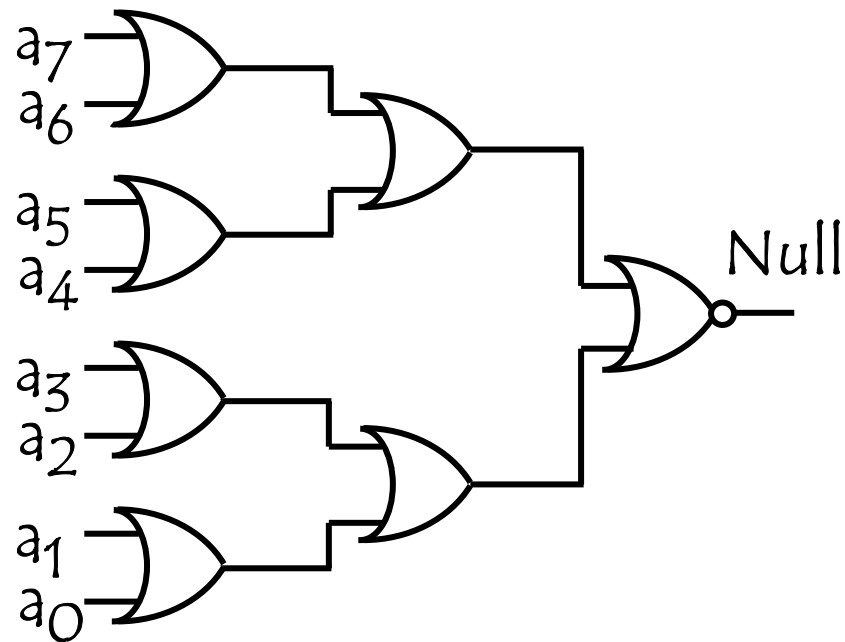

Comparators

Comparing a natural number to zero : =

Implementation improvement

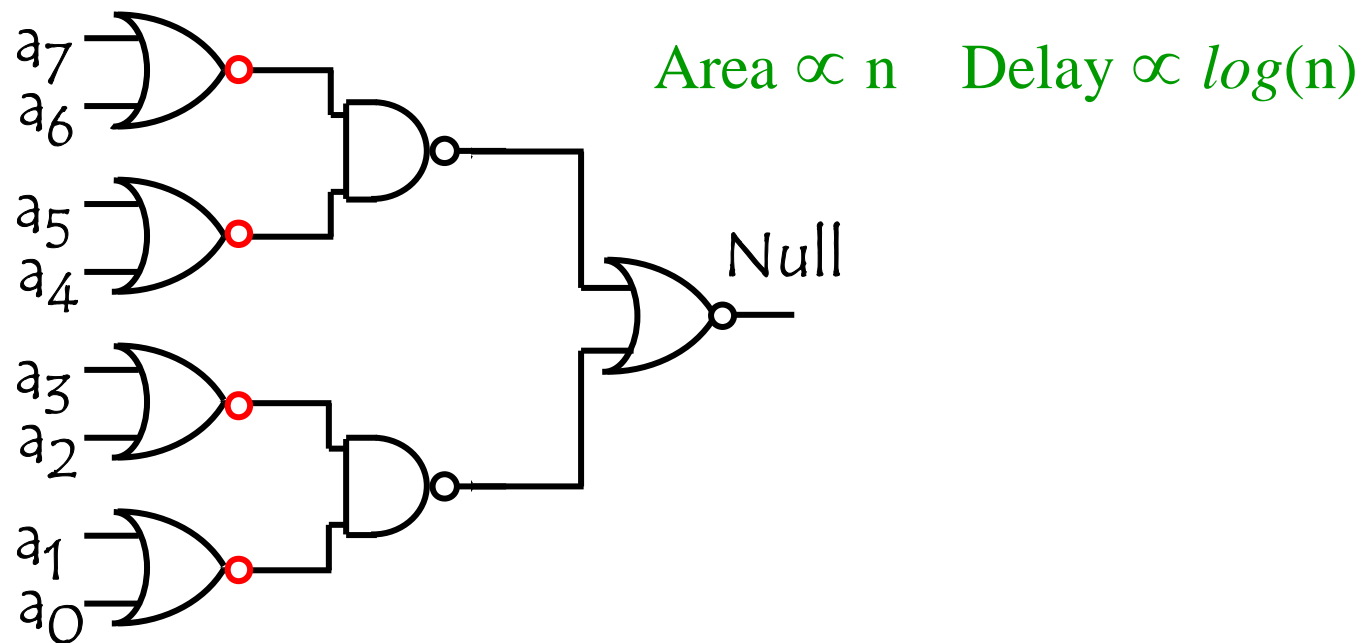

Comparators

Comparing two natural numbers : =

Let consider two natural numbers a and b
coded on 8 bits using Natural Binary Code

$$\begin{array}{cccccccc} a_7 & a_6 & a_5 & a_4 & a_3 & a_2 & a_1 & a_0 \\ & & & & = ? & & & \\ b_7 & b_6 & b_5 & b_4 & b_3 & b_2 & b_1 & b_0 \end{array}$$

↓

0 / 1

Comparators

Comparing two natural numbers : =

Boolean function

a Equal b if : $a_7=b_7$ and $a_6=b_6$ and ... and $a_0=b_0$

a Equal b if : $\overline{(a_7 \oplus b_7)} \cdot \dots \cdot \overline{(a_0 \oplus b_0)} = 1$

$$\text{Equal} = \overline{(a_7 \oplus b_7)} + \dots + \overline{(a_0 \oplus b_0)}$$


$$\text{Equal} = (\overline{e_7}) + \dots + (\overline{e_0})$$

Comparators

Comparing two natural numbers : =

Implementation


Area $\propto n$ Delay $\propto \log(n)$

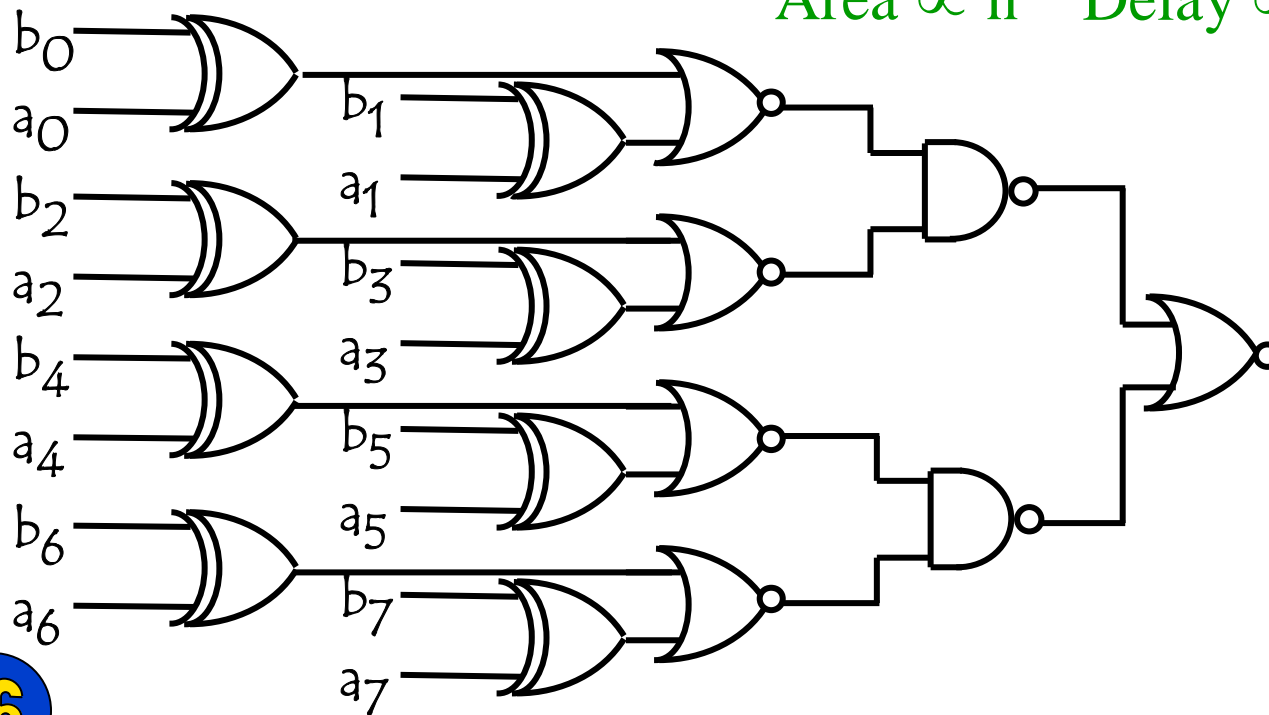

Comparators

Comparing two natural numbers : <

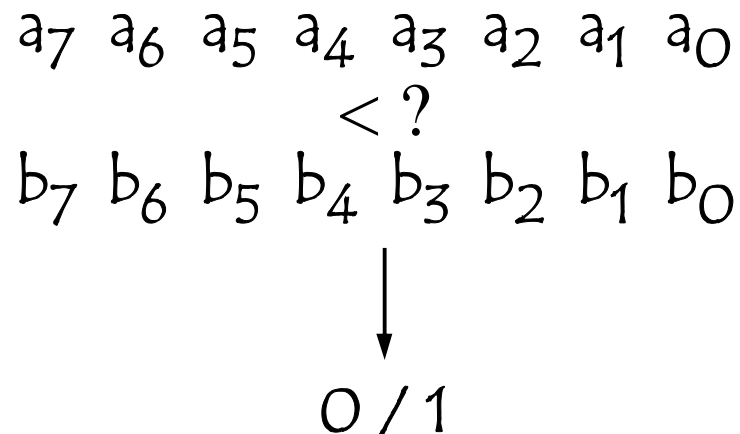Let consider two natural numbers a and b
coded on 8 bits using Natural Binary Code



Comparators

Comparing two natural numbers : <

Boolean function

$a < b$ if : $a_7 < b_7$ or $(a_7 = b_7 \text{ and } (a_6 < b_6 \text{ or } (a_6 = b_6 \text{ and } \dots)))$

a_7	a_6	a_5	a_4	a_3	a_2	a_1	a_0
				< ?			
b_7	b_6	b_5	b_4	b_3	b_2	b_1	b_0
				↓			
				0 / 1			

Comparators

Comparing two natural numbers : <


Boolean function

$a < b$ if : $a_7 < b_7$ or $(a_7 = b_7 \text{ and } (a_6 < b_6 \text{ or } (a_6 = b_6 \text{ and } \dots)))$

$a < b$ if : $\overline{a_7}b_7 + ((\overline{a_7 \oplus b_7}) \cdot (\overline{a_6}b_6 + ((\overline{a_6 \oplus b_6}) \cdot \dots)))$

Comparators

Comparing two natural numbers : <

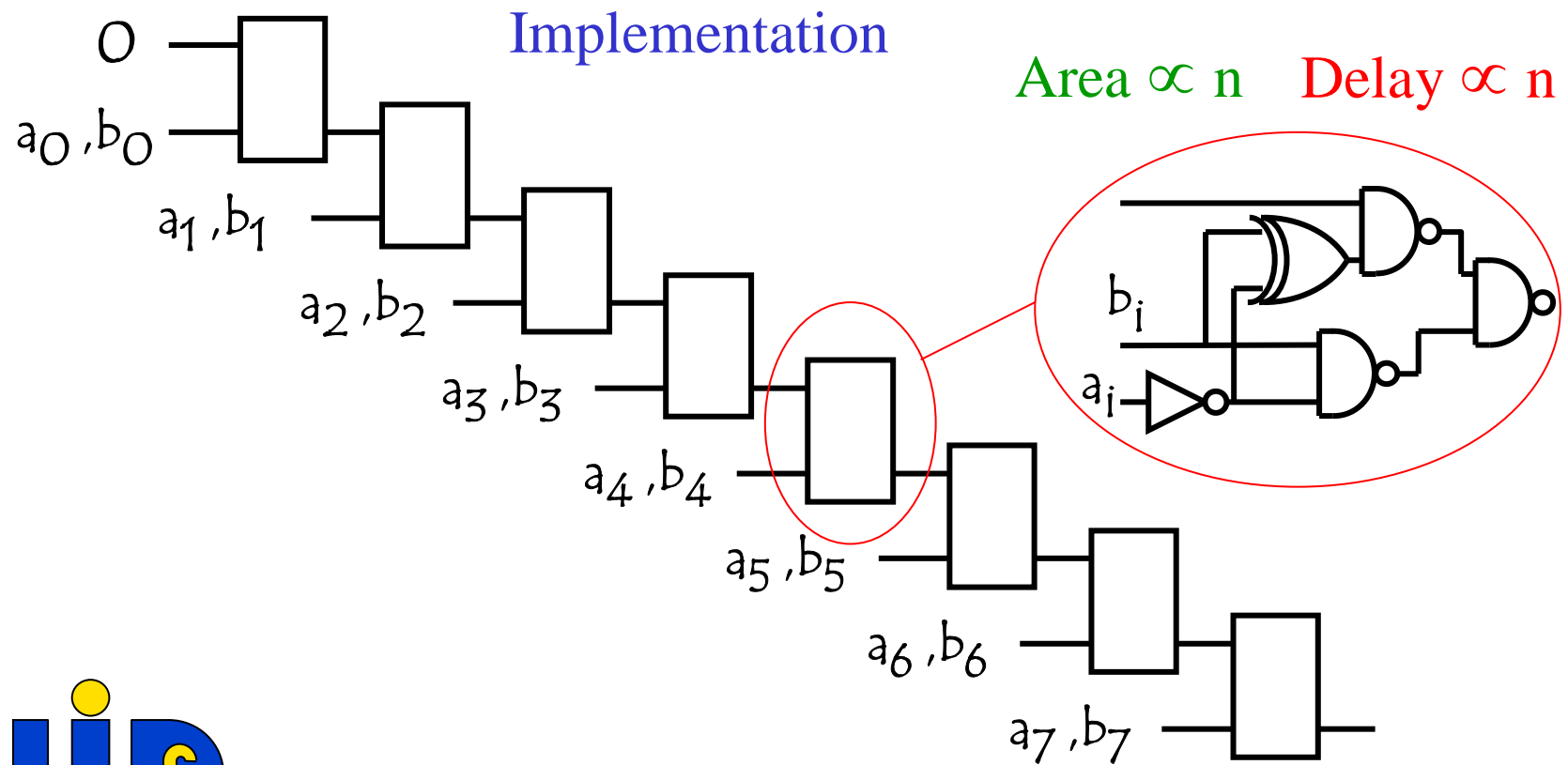

Comparators

Comparing two natural numbers : <

Implementation Improvement

$a < b$ if : $a_7 < b_7$ or ($a_7 = b_7$ and ($a_6 < b_6$ or ($a_6 = b_6$ and ...)))

$a < b$ if : $\overline{a_7}b_7 + ((\overline{a_7 \oplus b_7}) \cdot (\overline{a_6}b_6 + ((\overline{a_6 \oplus b_6}) \cdot \dots)))$


$\overline{a_i}b_i + (\overline{a_i \oplus b_i}) \cdot \text{previous}$

Propagation
Generation

Comparators


Comparing two natural numbers : <

Implementation Improvement

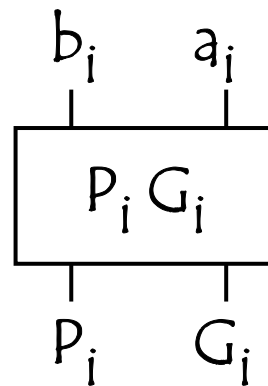

$$G_i = \overline{a_i} b_i$$


$$P_i = \overline{a_i} \oplus b_i$$

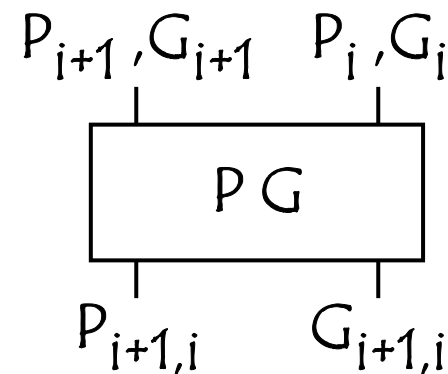

$$G_{i+1,i} = G_{i+1} + G_i \cdot P_{i+1}$$

$$P_{i+1,i} = P_i \cdot P_{i+1}$$

Comparators

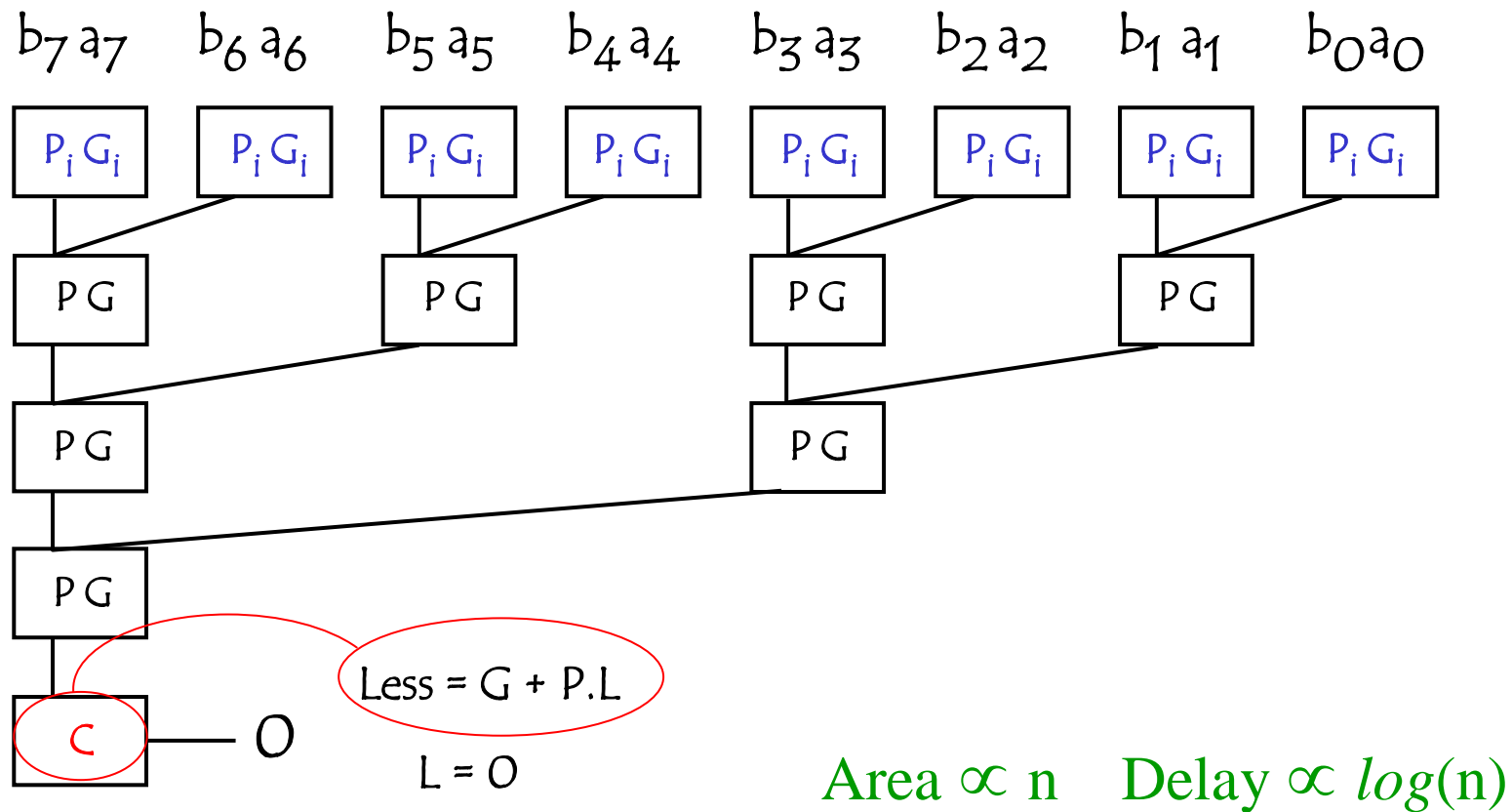

Comparators

