

Outline





- ❏ Digital CMOS design
- ❏ Arithmetic operators
- ❏ Sequential functions



Outline

Digital CMOS design


Arithmetic operators

-  Adders
-  Comparators
-  Shifters
-  Multipliers

Adders

Adding two natural numbers

 Let consider two natural numbers **a** and **b**
coded on 8 bits using Natural Binary Code



Adders

Adding two natural numbers

At each stage, I need to sum 3 single bit numbers a_i b_i c_i
The carry out of the stage i is the input carry of the next stage

$$\begin{array}{r} c_i + c_i \\ a_i \\ b_i \\ \hline s_i \end{array}$$

A red arrow points from the sum of the two c_i terms to the c_{i+1} label above it.

s_i and c_{i+1} are
Boolean functions of
 a_i b_i c_i

Adders

Adding two natural numbers

	00	01	11	10	a_i b_i
0	0	1	0	1	
1	1	0	1	0	

c_i

s_i

$$s_i = a_i \oplus b_i \oplus c_i$$

	00	01	11	10	a_i b_i
0	0	0	1	0	
1	0	1	1	1	

c_i

c_{i+1}

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$



Adders

Adding two natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$
  
$$c_{i+1} = a_i \cdot (b_i + c_i) + b_i \cdot c_i$$





Adders

Adding two natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$
  
$$c_{i+1} = a_i \cdot b_i + (a_i + b_i) \cdot c_i$$



Adders



Adding two natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$

$$c_{i+1} = a_i \cdot b_i + (a_i + b_i) \cdot c_i$$

  
$$c_{i+1} = a_i \cdot b_i + (a_i \oplus b_i) \cdot c_i$$



Adders


Adding two natural numbers

 The circuit generating s_i and c_{i+1} is called a Full Adder (FA)




Adders

Adding two natural numbers

 


Adders

Adding two natural numbers

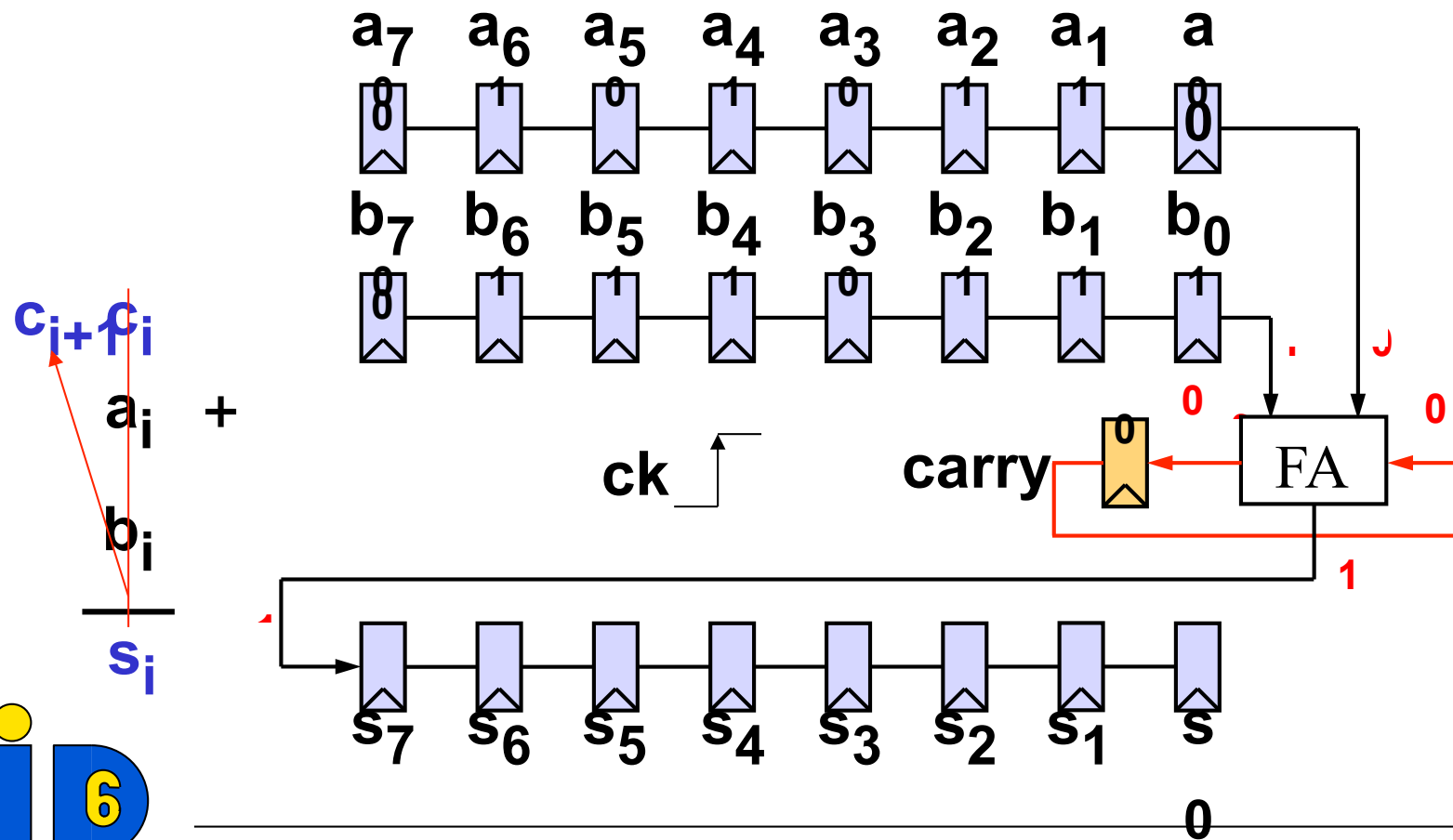

Adders

Adding two natural numbers

 

Adders

Adding two natural numbers

Sequential Adder

Area $\propto n$

Delay $\propto n$ cycles


Timing should be improved



Adders

Adding two natural numbers

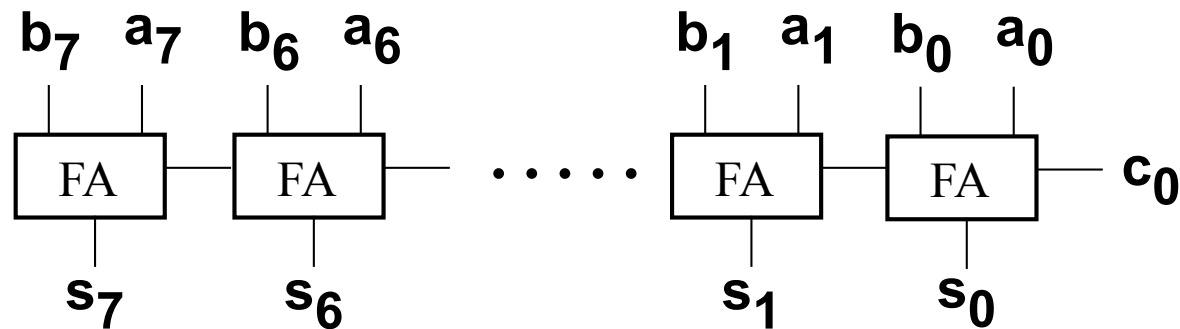At each stage, I need to sum 3 single bit numbers a_i b_i c_i
The carry out of the stage i is the input carry of the next stage



Ripple Carry Adder (RCA)


Adders

Adding two natural numbers

Ripple Carry Adder (RCA)

Area $\propto n$

Delay $\propto n$

 


Timing should be improved

Adders

Adding two natural numbers

Acceleration techniques

 


Adders

Adding two natural numbers Carry Select Adder (CSLA)

$$\text{Area} \propto n^{\log(3)} = n^{1.585}$$

$$\text{Delay} \propto \log(n)$$

 

Adders

Adding two natural numbers Acceleration techniques

	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$a_i b_i$

c_i

c_{i+1}

carry out depends
on carry in

carry out does not
depend on carry in

00	01	11	10
absorption	propagation	generation	propagation

$a_i b_i$

Adders

Adding two natural numbers
Acceleration techniques

	00	01	11	10
0	0	0	1	0
1	0	1	1	1

c_i

c_{i+1}

$a_i b_i$

$$G_i = a_i b_i$$

$$P_i = a_i \oplus b_i$$

$$c_{i+1} = G_i + P_i c_i$$


$$s_i = P_i \oplus c_i$$

00	01	11	10
absorption	propagation	generation	propagation

$a_i b_i$

Adders

 Adding two natural numbers
Acceleration techniques



$$G_i = a_i b_i$$

$$P_i = a_i \oplus b_i$$


$$c_{i+1} = G_i + P_i c_i$$

$$s_i = P_i \oplus c_i$$

00	01	11	10	$a_i \ b_i$
absorption	propagation	generation	propagation	


Adders

 Adding two natural numbers
Acceleration techniques



Adders

 Adding two natural numbers
Acceleration techniques




$$G_{i+1} = a_{i+1} b_{i+1} \quad G_i = a_i b_i$$

$$P_{i+1} = a_{i+1} \oplus b_{i+1} \quad P_i = a_i \oplus b_i$$


$$G_{i+1,i} = G_{i+1} + G_i \cdot P_{i+1}$$

$$P_{i+1,i} = P_i \cdot P_{i+1}$$

Adders

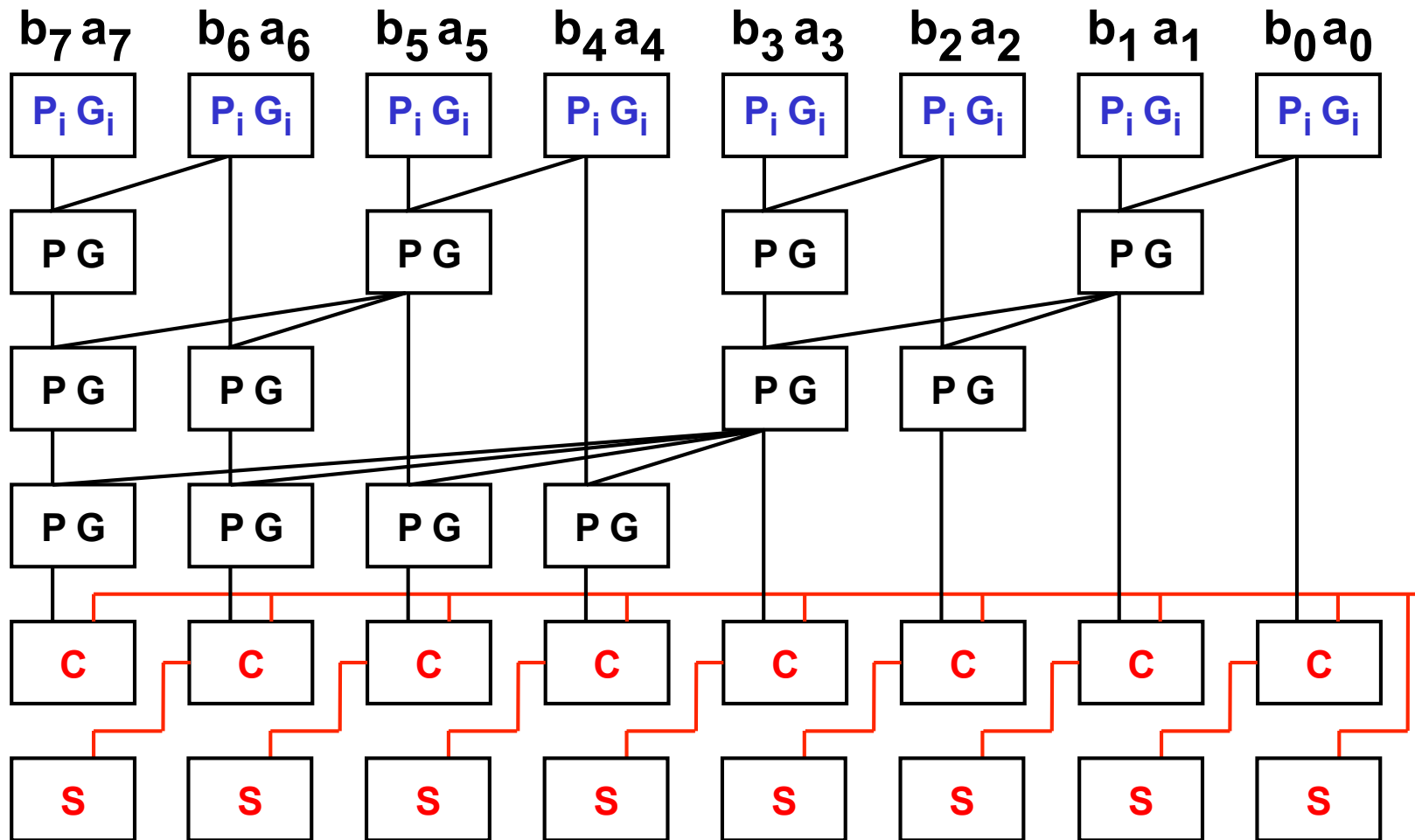


Adders

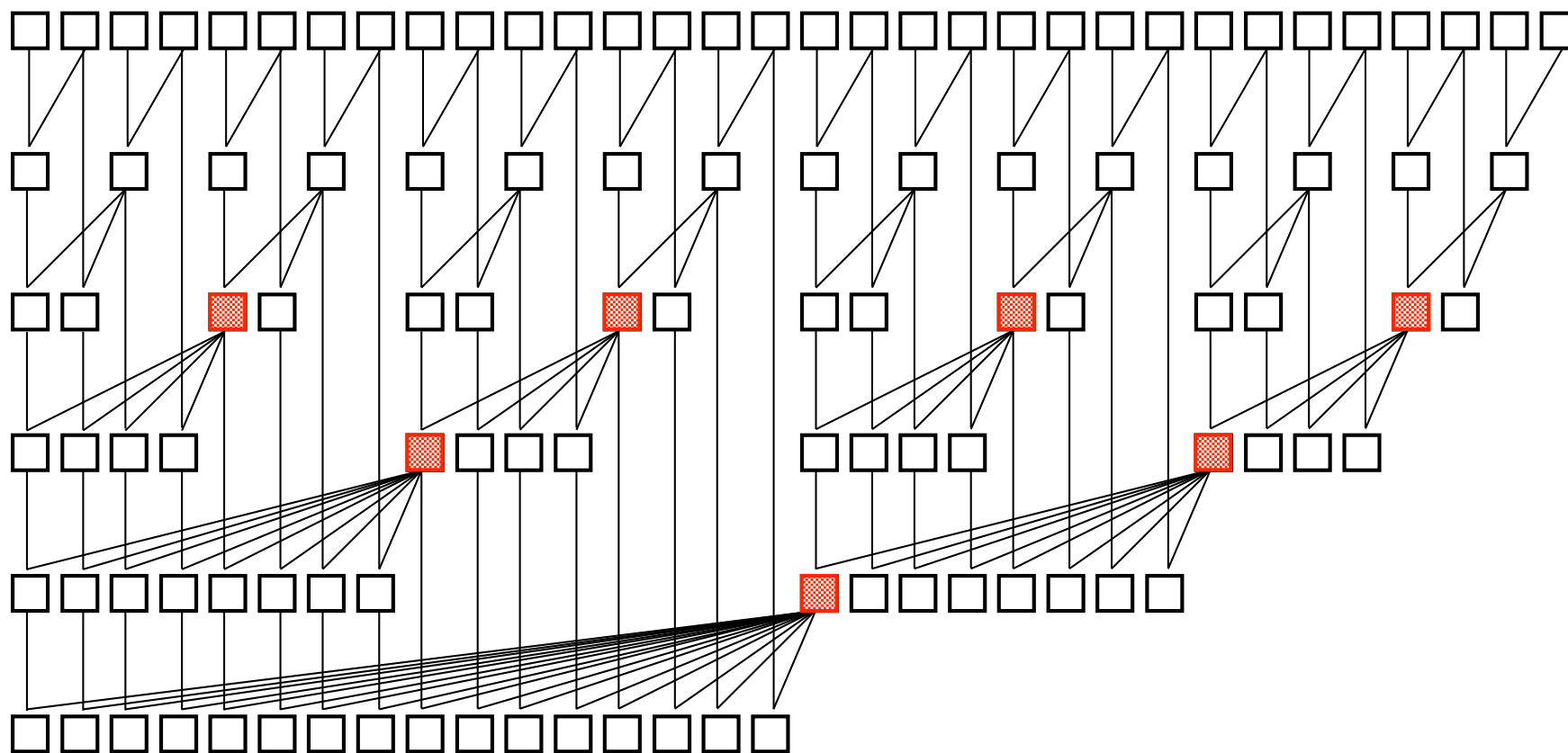

Slansky Adder

Adders

 

Kogge-Stone Adder

Adders


Adding two natural numbers (summary)

	Area	Delay
Ripple Carry (RCA)	n	n
Carry Select (CSLA)	$n \log(3)$	$\log(n)$
Carry Lookahead (CLA)	$n \log(n)$	$\log(n)$
Magic Adder	n	C_{ste}

Adders

Adding two natural numbers

Ripple Carry Adder (RCA)

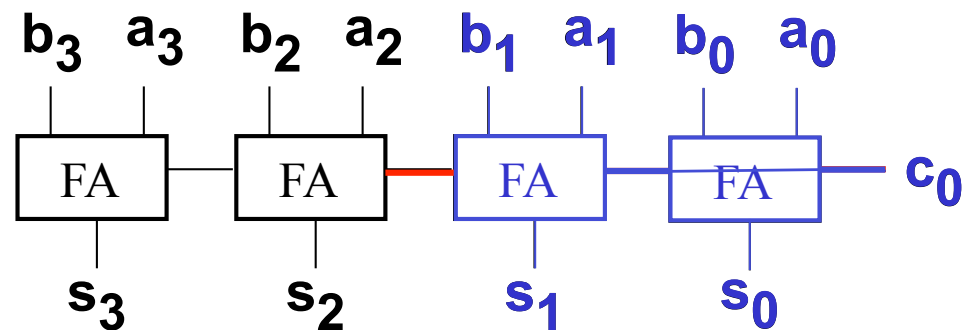


Adders

Adding two natural numbers

Ripple Carry Adder (RCA)

pipelining

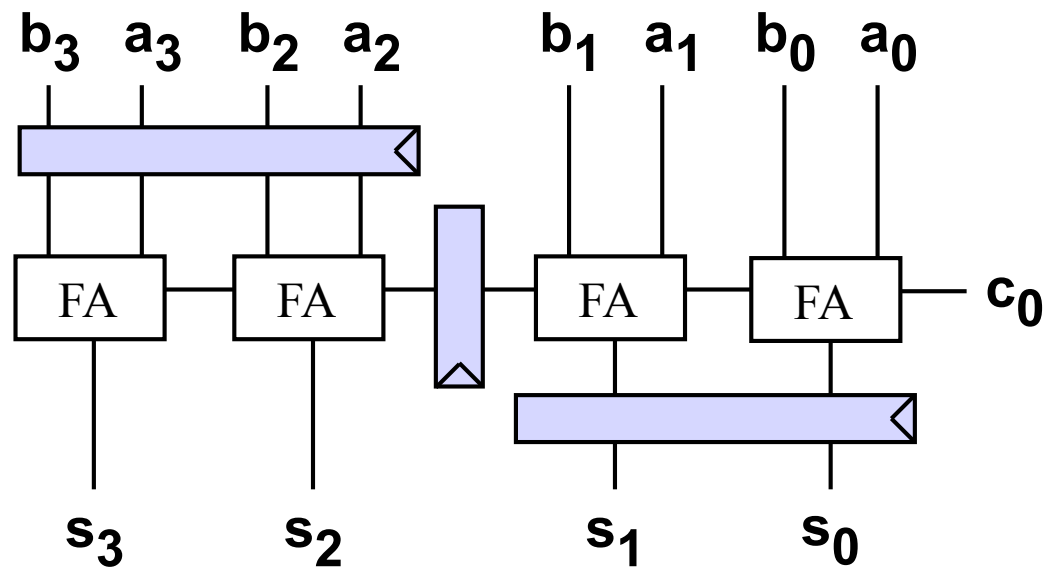


Adders

Adding two natural numbers


Ripple Carry Adder (RCA)

pipelining

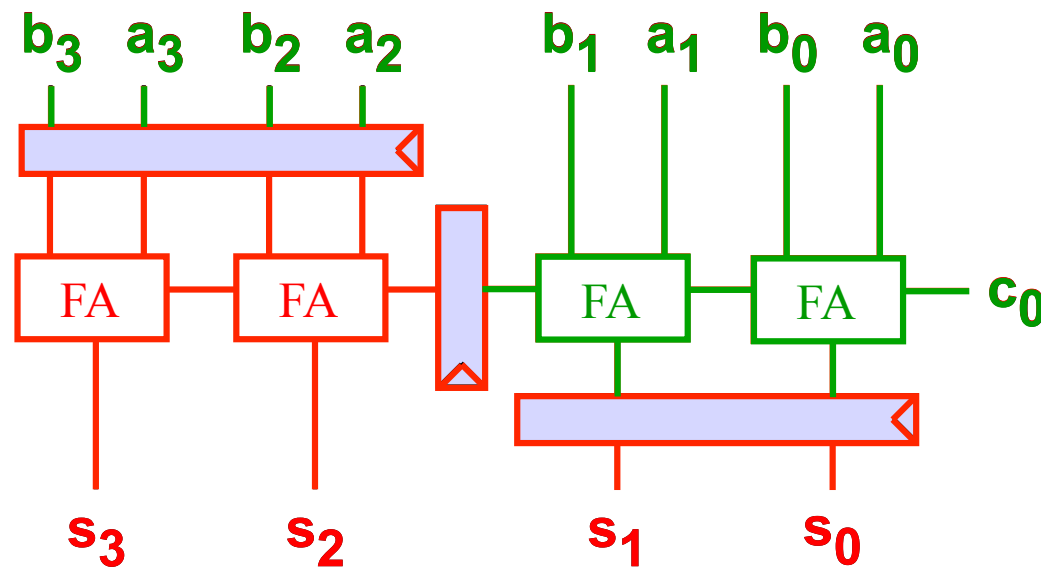

Adders

Adding two natural numbers

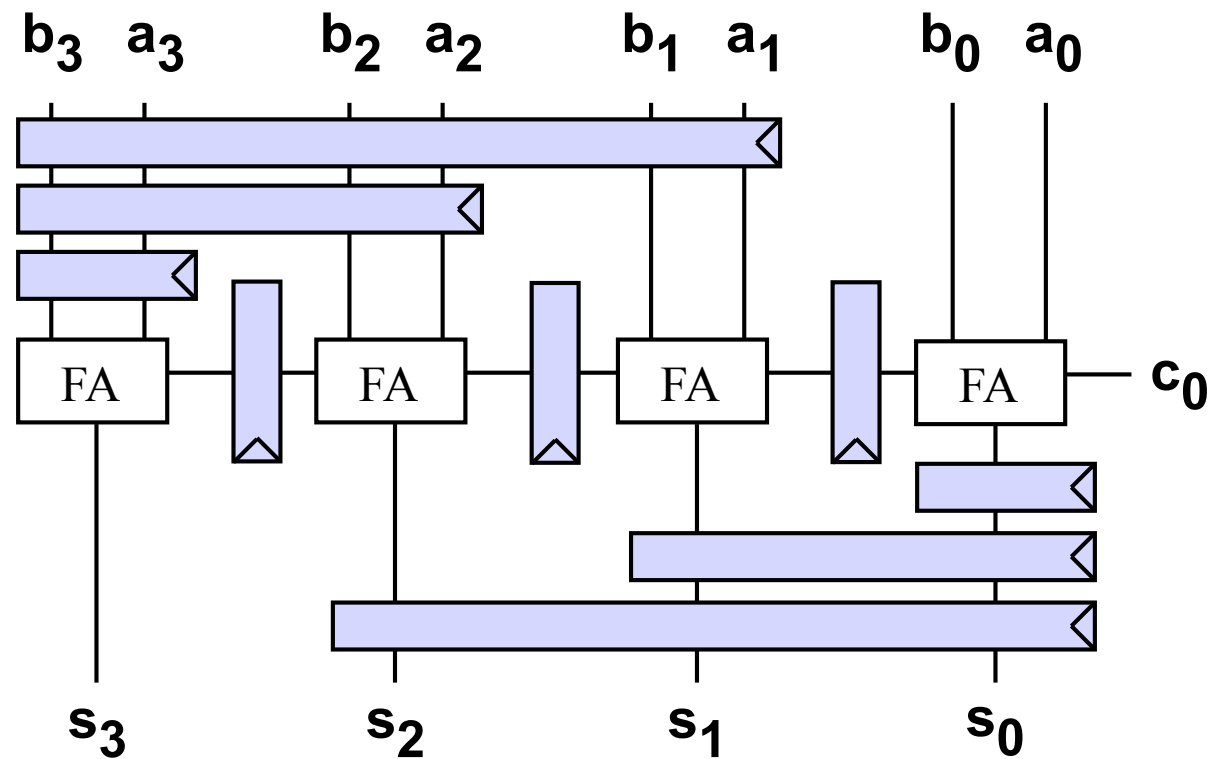

Adders

Adding two natural numbers (summary)


	Area	Delay
Ripple Carry (RCA)	n	n
Carry Select (CSLA)	$n \log(3)$	$\log(n)$
Carry Lookahead (CLA)	$n \log(n)$	$\log(n)$
Pipeline Adder	n^2	$C_{ste} (1 \text{ cycle})$
Magic Adder	n	C_{ste}



When there is no door to escape break the wall

Adders

Adding **three** natural numbers

 


Adders

Adding **three** natural numbers

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$$

 the expressions are symmetrical in regard of **a**, **b** and **c**




A full adder creates 2
numbers from 3

Adders


Adding **three** natural numbers

Carry Save Adder (CSA)

 

Adders

Adding **three** natural numbers

 

Delay = cste
Area $\propto n$

Adders

Adding two natural numbers

Change the representation of numbers

Given a natural number **a** : **a** is coded using **2n** bits

a = a0 + a1 **Redundant Binary Code**

Example : the number 5 can be coded on 4 bits as

0000 + 0101

0001 + 0100

0010 + 0011



Adders

Adding two natural numbers

Changing the representation of numbers

$$\mathbf{a} = \mathbf{a0} + \mathbf{a1}$$

$$\mathbf{b} = \mathbf{b0} + \mathbf{b1}$$

Adding **a** and **b** in Redundant Binary Code is finding **c**

$$\mathbf{c} = \mathbf{c0} + \mathbf{c1} \text{ such as}$$


$$\mathbf{c0} + \mathbf{c1} = \mathbf{a0} + \mathbf{a1} + \mathbf{b0} + \mathbf{b1}$$

Adding 4 numbers to generate 2



Adders

Adding two natural numbers

 

Delay = cste
Area $\propto n$