



The Abdus Salam  
**International Centre  
for Theoretical Physics**



smr2499

# **International Training Workshop on FPGA Design for Scientific Instrumentation and Computing**

**11 November – 22 November 2013**

**Trieste – Italy**

---

## **LABORATORY EXERCISES II**

### **COMBINATIONAL AND SEQUENTIAL LOGIC**


#### **DESCRIBED in VHDL**

#### **Logic Synthesis and FPGA Implementation**

**ICTP Multidisciplinary Laboratory  
MLAB**
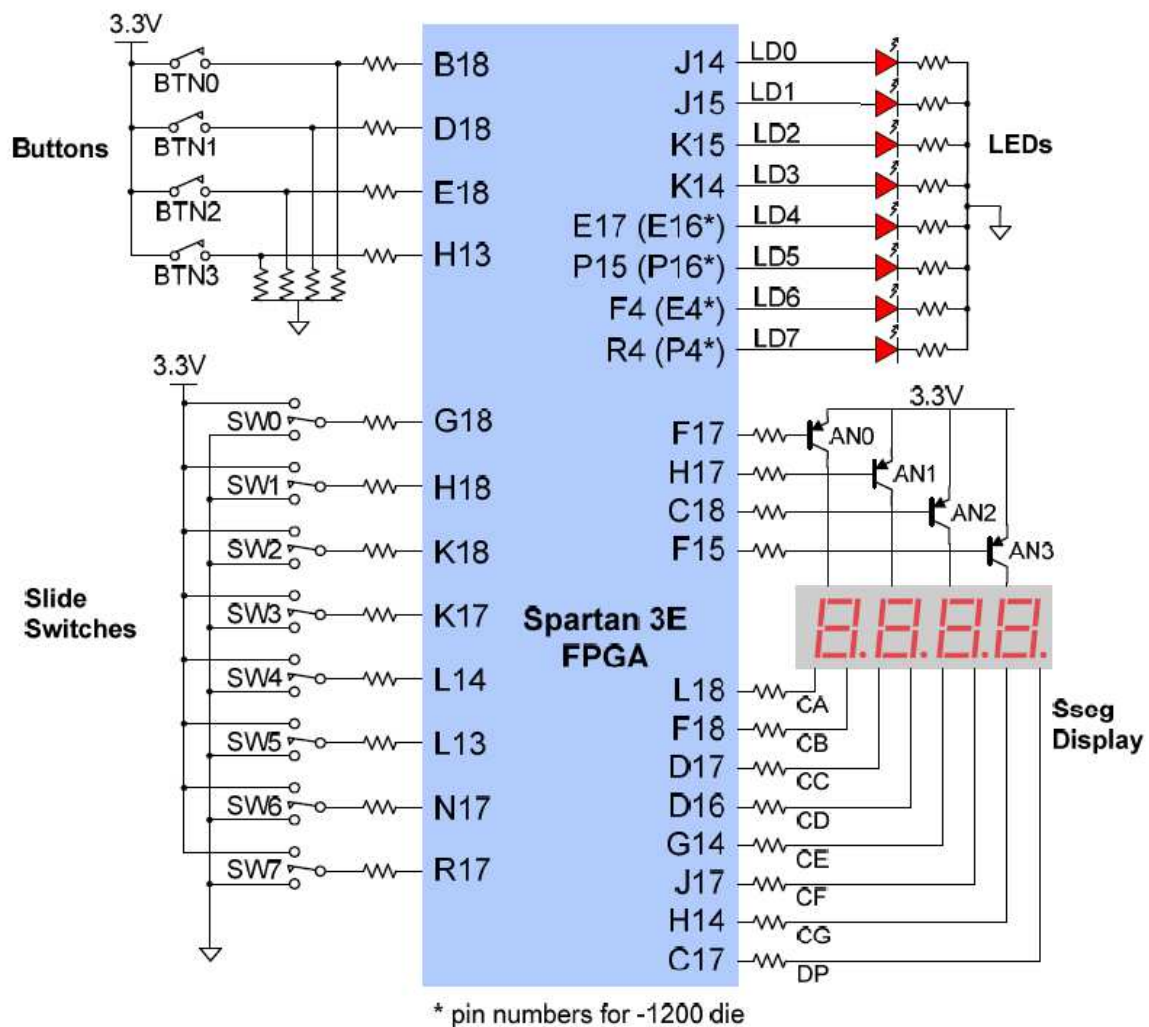
### Objective

- Implementation of your designs in the *FPGA Spartan 3E of the Nexys 2 board* (see I/O in figure below and user guide for more details).
- Writing and Utilization of *User Constraints Files (.ucf)*



### Exercise 8

- Design and Synthesize a Clock Divider that allows generating 1 Hz, 2 Hz, 5 Hz and 10 Hz clocks from the on-board 50 MHz clock. Use the on-board LEDs to show each one of the generated clocks.
- Write the corresponding user constraints file, configure the FPGA, and test your design.

### Exercise 9

- Implement on the FPGA the *hexadecimal to 7-segment decoder* designed in exercise 3. Use the on-board SW0-SW3 switches and the display controlled by pin F15.
- Write the corresponding user constraints file, configure the FPGA, and test your design.

### Exercise 10


- Implement on the FPGA the system designed in exercise 6. Use a common reset to initialize the counters, and the *switches* available in the board for the up/down input to define the counting mode of each counter. Use the available *buttons* for the *select* signal, and one of the *7-segment display* for visualization.
- Write the corresponding user constraints file, configure the FPGA, and test your design.

### Exercise 11

- Implement on the FPGA the system designed in exercise 7 (part a).
- Write the corresponding user constraints file, configure the FPGA, and test your design.
 
### Exercise 12

- Design a system for serial data transmission according to the RS-232 protocol. The format of the data to be transmitted is described in the figure below:



**RS-232 formato de transmisión**

- Set the reception/transmission frequency at 9600 baud.
- Transmit your first name that will be defined as a constant.

- 2) Write the corresponding user constraints file, configure the FPGA, and test your design (use the figure below as reference).

