

2499-11

**International Training Workshop on FPGA Design for Scientific
Instrumentation and Computing**

11 - 22 November 2013

**Digital CMOS Design
Basic digital CMOS gates**

Pirouz Bazargan-Sabet
*Department ASIM, LIP6, University Pierre & Marie Curie (VI), place
Jussieu, 75252 Paris Cedex 0
France*

Outline

- Digital CMOS design
 - Boolean algebra
 - Basic digital CMOS gates
 - Combinational and sequential circuits
 - Coding - Representation of numbers

Basic CMOS Gates



How to implement Boolean functions
in CMOS technology ?

Which functionalities are available





Basic CMOS Gates

○ N-MOS transistor

  

Basic CMOS Gates

○ P-MOS transistor

  

Basic CMOS Gates

The electrical behavior of a MOS transistor
is very complex


Design of a multi-million transistor circuit ?



Basic CMOS Gates


In a digital circuit a MOS transistor can be seen as a **Switch**

N-MOS

 

D = S when G = 1

P-MOS

 

D = S when G = 0

Basic CMOS Gates

When driving, a MOS transistor can be seen as a **Resistor**

$$\textit{Conductance} \propto \frac{W}{L}$$

For the same size, a P-MOS is twice more resistive than an N-MOS



Basic CMOS Gates

The N-MOS and P-MOS are not exactly symmetrical


A N-MOS is a good transmitter of 0

A P-MOS is a good transmitter of 1




Basic CMOS Gates

$$y = \text{Not } x$$


 


Dual CMOS gate

 


Basic CMOS Gates

$$y = \overline{x_1 \cdot x_2}$$

  

Basic CMOS Gates

Design of a dual gate

 

The P-network must be the dual of the N-network


Series \longrightarrow Parallel
Parallel \longrightarrow Series

Take care of the size of transistors

Basic CMOS Gates

- To set the output to **0** a path has to be created through the **N** network
- A series of N-transistor must be conducting

$$\prod x_i = 1$$

 

Only negative (inverting) functions can be created

Basic CMOS Gates

Implementing a Boolean function with a CMOS gate ?

- The function must be inverting in regard of all the variables
- Put the function in the form of $f = \bar{g}$
- Design the N-network of g

Basic CMOS Gates

Implementing a Boolean function with a CMOS gate ?

- In the expression of g each $'.'$ are two paths in series
- In the expression of g each $'+'$ are two paths in parallel
- The P-network is the dual network of the N-network
- **Avoid putting more than 3 transistors in series**



Basic CMOS Gates


Example :

$$f = \bar{a} + (\bar{b} \cdot \bar{c})$$

$$f = \bar{a} + \overline{(b+c)}$$

$$f = \overline{a \cdot (b+c)}$$

$$g = a \cdot (b+c)$$

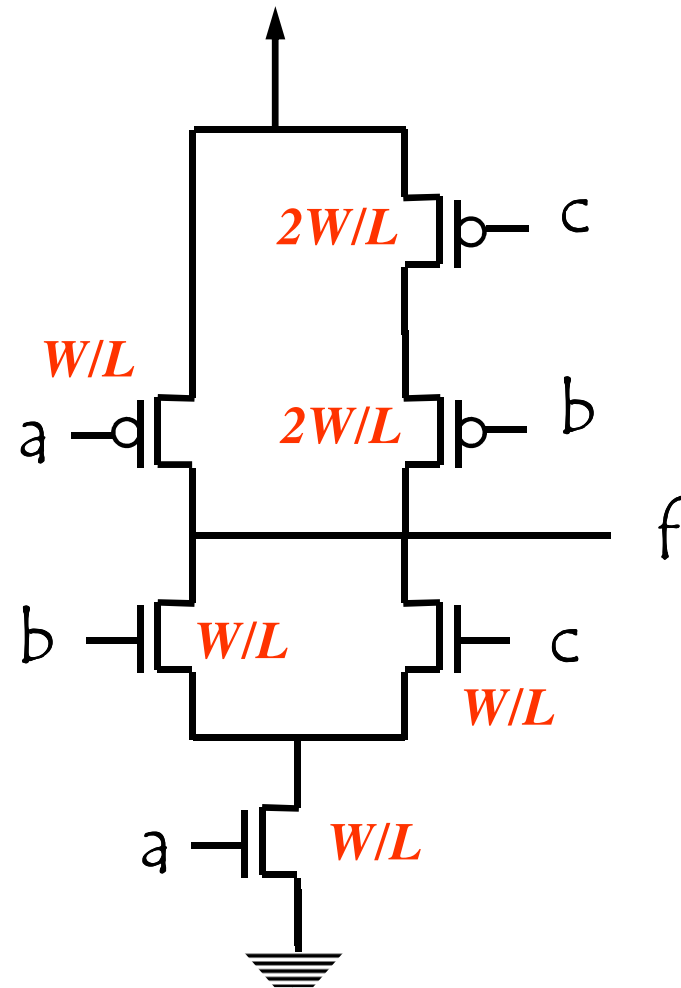



Basic CMOS Gates

Some gates :

Inverter : $f = \bar{a}$

Nand : $f = \overline{a.b}$

Nor : $f = \overline{a+b}$

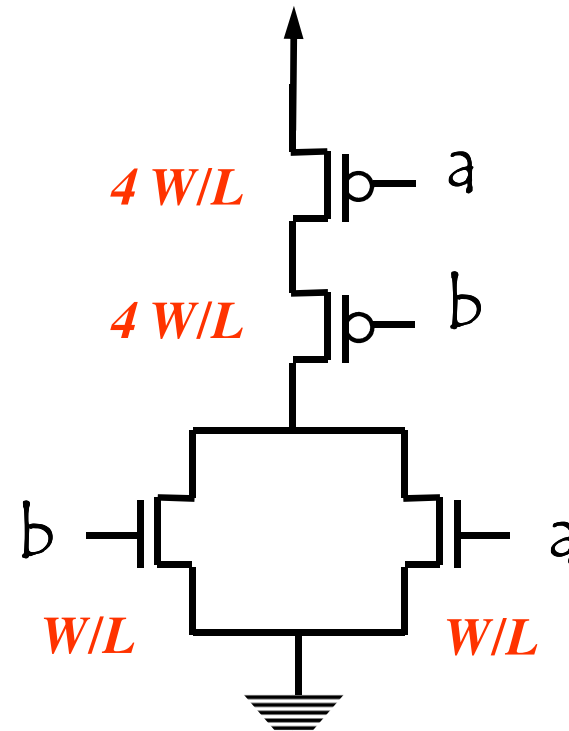
 


Basic CMOS Gates

Some gates :

Multiplexer :

  
$$f = \overline{a \cdot s} + b \cdot \overline{s}$$



Basic CMOS Gates

Some gates : Multiplexer :
 
$$f = a.s_1.s_2 + b.s_1.\bar{s}_2 + c.\bar{s}_1.s_2 + d.\bar{s}_1.\bar{s}_2$$




Basic CMOS Gates


Some gates :

Multiplexer :


$$f = \overline{a.s} + b.\overline{s}$$

 

Basic CMOS Gates

 


Basic CMOS Gates

 

If $s = 1$
 $f = \overline{a}$


If $s = 0$
 f is not defined

 

Tri-state driver


Basic CMOS Gates

Some gates : Multiplexer :

 


Basic CMOS Gates

Some gates : Multiplexer :

 

Basic CMOS Gates

Some gates :

 


If $b = 1$ If $b = 0$
 $f = a$ f is not defined

→ If $a = 0$ then $f = 0$
→ If $a = 1$ then $f = 1$

Pass-transistor

Basic CMOS Gates

Some gates :

 


If $b = 0$ If $b = 1$
 $f = a$ f is not defined

→ If $a = 1$ then $f = 1$
→ If $a = 0$ then $f = 0^+$

Pass-transistor

Basic CMOS Gates

Some gates :

 

If $b = 1$ If $b = 0$
 $f = a$ f is not defined

→ If $a = 0$ then $f = 0$
→ If $a = 1$ then $f = 1$


CMOS Switch

Basic CMOS Gates

Some gates :

Multiplexer :

$$f = a.s + b.\bar{s}$$

 


Basic CMOS Gates

Some gates :

Multiplexer :


$$f = \overline{a.s} + b.\overline{s}$$

 


Basic CMOS Gates

Some gates :
 
$$\text{Nxor} : f = \overline{\overline{a}.b + a.\overline{b}}$$



I need \overline{a} and \overline{b}

 

Basic CMOS Gates

Some gates :

Xor with Pass-transistors :

$$f = \overline{\overline{a} \cdot b} + a \cdot \overline{b}$$

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

